

3

$$i_{zn} = \frac{k_r i_x - v_i}{2}$$

$$2 = \frac{k_r i_x - v_i}{2}$$

$$k_r i_x - v_i = 4 \quad \textcircled{1}$$

$$i_x = \frac{8 - v_i}{3}$$

$$3i_x + v_i = 8 \quad \textcircled{2}$$

$$v_i : \frac{v_i - 8}{3} + \frac{v_i - k_r i_x}{2} + \frac{v_i - 0}{1} = 0$$

$$11v_i - 3k_r i_x = 16 \quad \textcircled{3}$$

put $i_x = \frac{8 - v_i}{3}$ in $\textcircled{1}$ & $\textcircled{3}$

$$k_r \left(\frac{8 - v_i}{3} \right) - v_i = 4$$

KHALID PHOTO STATE
U.E.T

$$8k_r - k_r v_i - 3v_i = 12 \quad \textcircled{4}$$

$$11v_i - 8k_r \left(\frac{8 - v_i}{3} \right) = 16$$

$$11v_i - 8k_r + k_r v_i = 16 \quad \textcircled{5}$$

from $\textcircled{4}$ put v_i

$$8k_r - v_i(k_r + 3) = 12$$

$$8k_r - 12 = v_i(k_r + 3)$$

$$v_i = \frac{4(2k_r - 3)}{k_r + 3} \text{ put in } \textcircled{5}$$

$$11 \left(\frac{8k_x - 12}{k_x + 3} \right) - 8k_x + k_x \left(\frac{8k_x - 12}{k_x + 3} \right) =$$


$$\frac{88k_x - 132}{k_x + 3} - 8k_x + \frac{8k_x^2 - 12k_x}{k_x + 3}$$

$$88k_x - 132 - 8k_x - 24k_x + \frac{8k_x^2 - 12k_x}{16k}$$

$$88k_x - 24k_x - 12k_x - 16k_x = 48 + 13 \\ 36k_x = 180$$

$$k_x = 5 \Omega$$

5.3

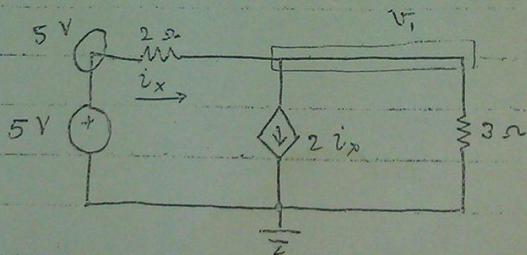

$$V_1: \frac{V_1 - 5}{2} + 2i_x + \frac{V_1 - 0}{3} = 0$$

$$3V_1 - 15 + 12i_x + 2V_1 = 0$$

$$5V_1 + 12i_x = 15 \quad \textcircled{1}$$

$$i_x = \frac{5 - V_1}{2}$$

$$V_1 + 2i_x = 5 \quad \textcircled{2}$$

Put $i_x = \frac{5-v_1}{2}$ in ①

$$5v_1 + \frac{1}{2} \left(\frac{5-v_1}{2} \right) = 15$$

$$5v_1 + 30 - \frac{1}{2}v_1 = 15$$

$$30 - 15 = v_1$$



$$15 = v_1$$

$$v_1 = 15 \text{ V}$$

$$i_x = -5 \text{ A}$$

Put in ②

Now,

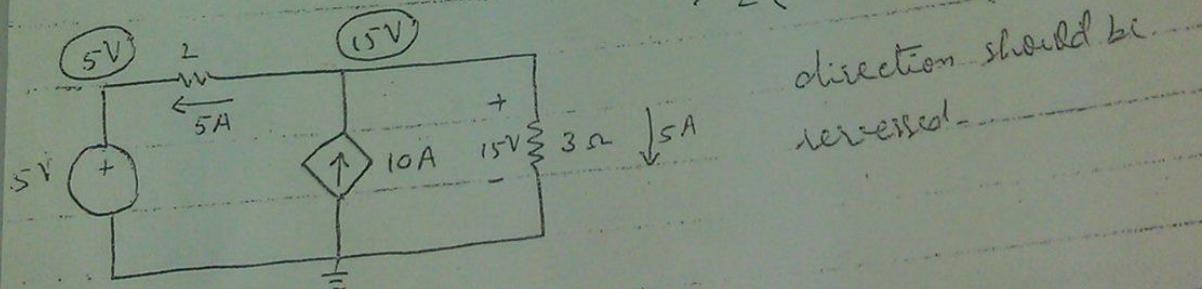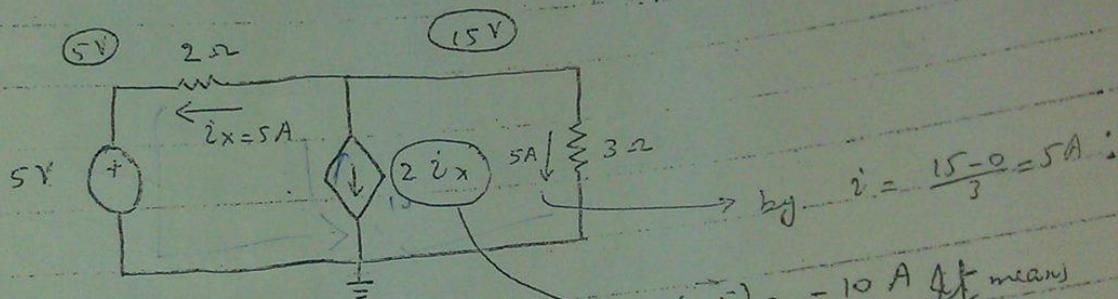

$$P_{5V} = 5 \times 5 = 25 \text{ W} \text{ (absorbed)}$$


$$P_{2\Omega} = (5)^2 \times 2 = 50 \text{ W} \text{ (absorbed)}$$

$$P_{3\Omega} = (5)^2 \times 3 = 75 \text{ W} \text{ (absorbed)}$$

$$P_{10A} = 15 \times 10 = 150 \text{ W} \text{ (released)}$$

5.4

6

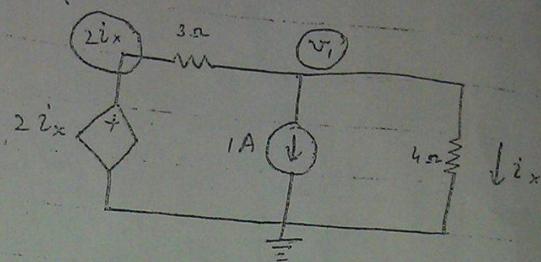 $v_{TA} = ?$  $Req =$

$$i_x = \frac{v_i - 0}{4} = \frac{v_i}{4}$$

$$i_x = \frac{v_i}{4} \quad \text{--- (1)}$$

 $v_i :$

$$\frac{v_i - 2i_x}{3} + 1 + \frac{v_i - 0}{4} = 0$$

$$4v_i - 8i_x + 12 + 3v_i = 0$$

$$7v_i - 8i_x = -12 \quad \text{--- (2)}$$


put $i_x = \frac{v_i}{4}$ in (2)

$$7v_i - 8\left(\frac{v_i}{4}\right) = -12$$


$$5v_i = -12$$

$$v_i = -\frac{12}{5} V$$

* Ans is corr
checked by power
conservation.

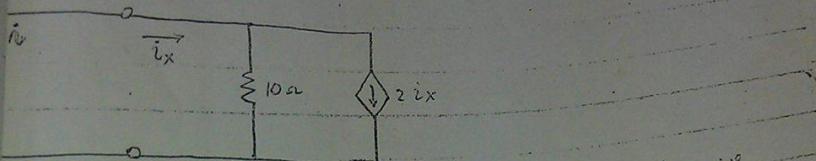$R_{eq} = ?$ 

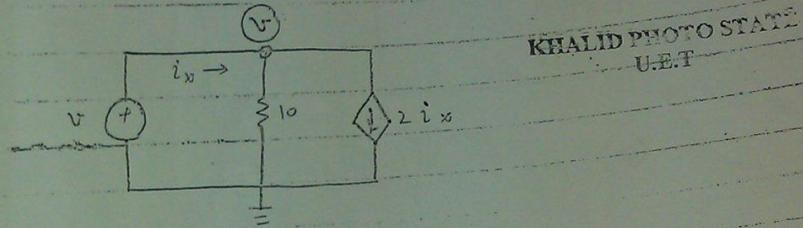as we can see that $i = ix$. So we have to find $R_{eq} = \frac{V}{i_x}$



V.E.


$$\frac{V-0}{10} + 2ix = ix$$

$$\frac{V}{10} = -ix$$


$$\frac{V}{ix} = -10$$

$$R_{eq} = -10\Omega$$

5.6

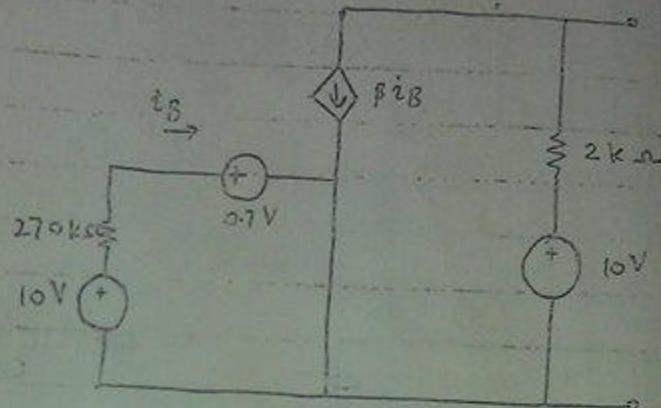

(a) $\beta = 85$ find $V_o = ?$

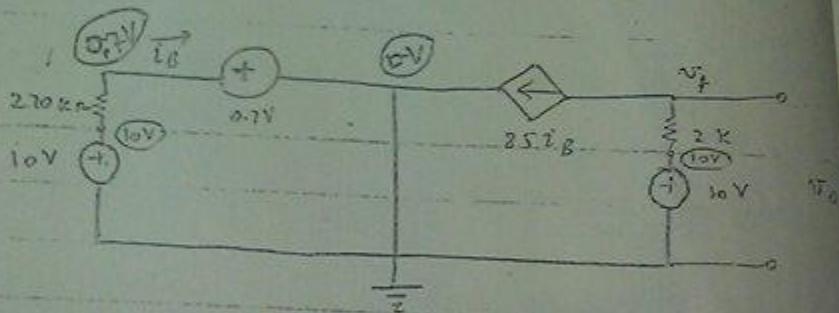

$$V_i: \frac{V_i - 10}{2} + 85 i_B = 0$$

$$V_i - 10 + 170 i_B = 0$$

$$V_i + 170 i_B = 10 \quad (1)$$

$$i_B = \frac{10 - 0.7}{270}$$

$$i_B = 0.034 \text{ mA}$$

$$i_c = 85 i_B = 2.929 \text{ mA}$$

5.6

but $i_B = 0.034 \text{ mA}$ in ①


$$V_i + 170(0.034) = 10$$

$$V_i = 4.22 \text{ V}$$

$$V_o = V_i - 0 = 4.22 - 0$$

$$V_o = 4.22 \text{ V } (+)$$

(b) $\beta = ?$ if $V_o = 1 \text{ V}$

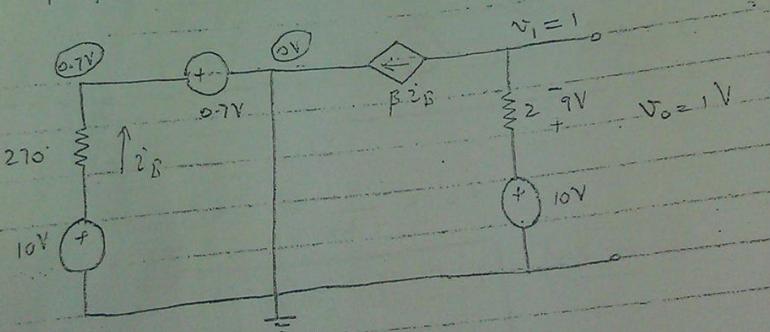


$$i_B = \frac{10 - 0.7}{270} = 0.034 \text{ mA}$$

$$i_B = 0.034 \text{ mA}$$

$$R_B = ?$$

$$R_C = ?$$

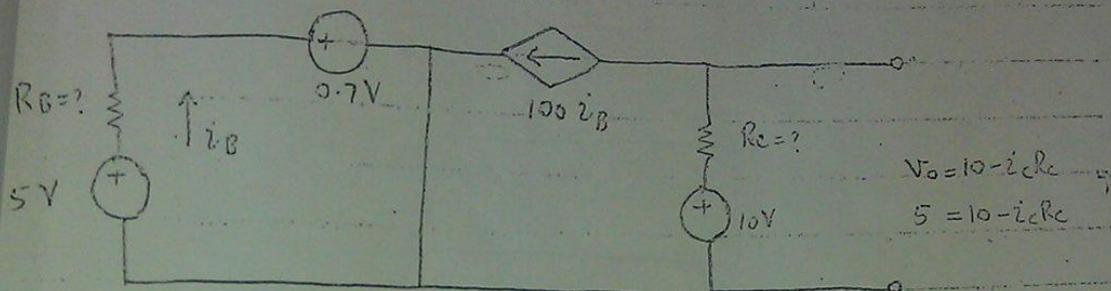Power dissipated in transistor = $i_C v_o$



$$\text{As } v_o = 10 - i_C R_C$$

$$5 = 10 - 100 i_B R_C$$

$$1 = 2 - 20 i_B R_C$$

$$20 i_B R_C = 2 - 1$$

$$i_B R_C = \frac{1}{20} \quad \text{--- (1)}$$

$$P_T = i_C v_o$$

$$\text{(given)} \quad 10 \text{ mW} = i_C (5)$$

$$2 \text{ mA} = i_C$$

$$100 i_B = 2 \text{ mA}$$

$$\boxed{i_B = 0.02 \text{ mA}} \quad \text{put in (1)}$$

$$R_C = \frac{1}{20 \times 0.02 \text{ mA}}$$

$$\boxed{R_C = 2.5 \text{ k}\Omega}$$



12

$$i_B = \frac{5 - 0.7}{R_B}$$

$$R_B = \frac{5 - 0.7}{i_B} = \frac{5 - 0.7}{0.02m} = 215k\Omega$$


R_B = 215 kΩ

5.8

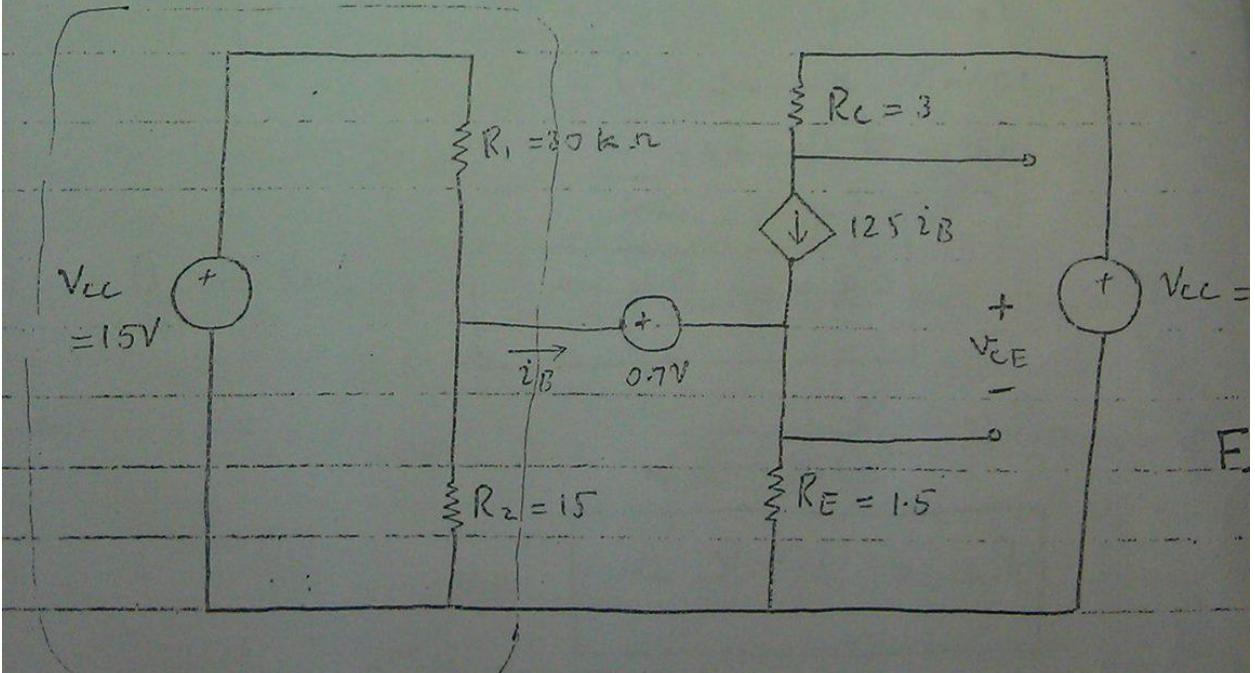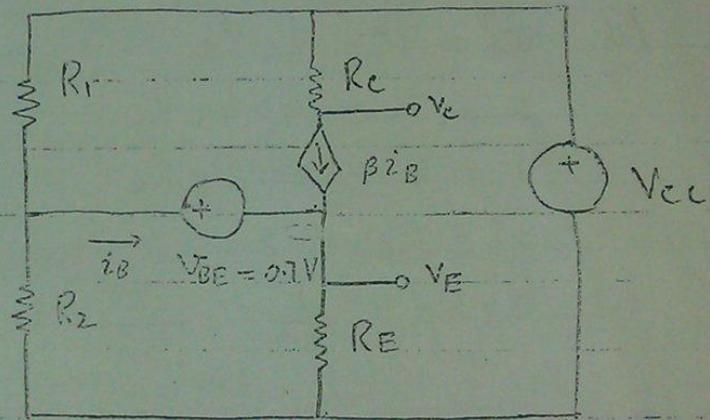

16

58

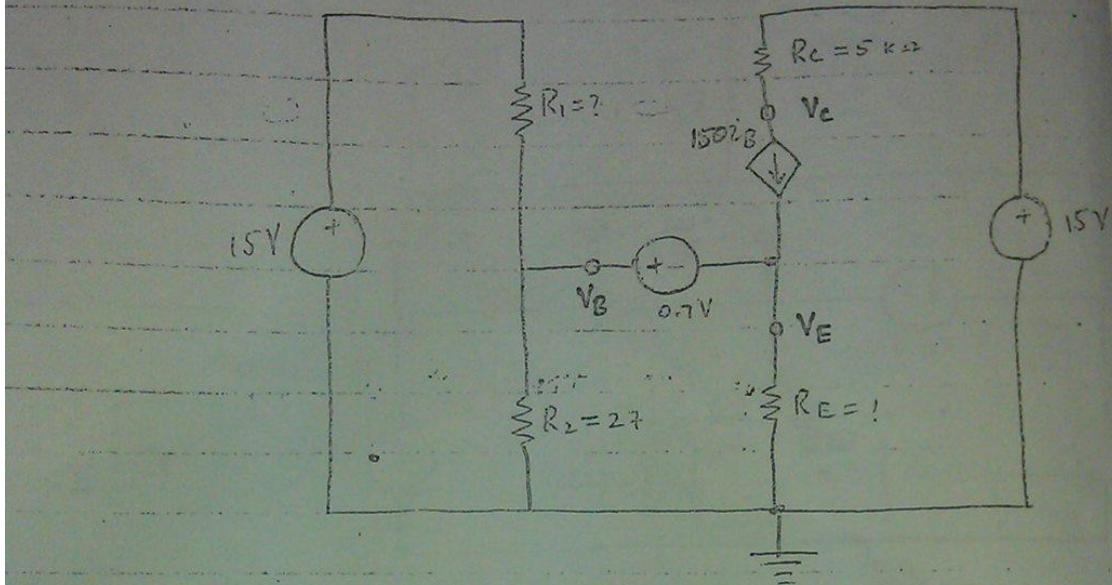

We can see that and we know of
the theory -

$$V_C = V_{CE} - i_C R_C \quad \text{--- (1)}$$

$$V_E = (\beta + 1) i_B R_E \quad \text{--- (2)}$$

$$V_B = V_E + V_{BE} = V_I - i_B R_B$$

For details visit
[www.w. Page #208 , Exh#5.
edu.ph](http://www.w. Page #208 , Exh#5.
edu.ph)

Given


$$V_C = 9V$$

$$V_B = 4.7V$$

To find

$$R_1 \& R_E$$

16

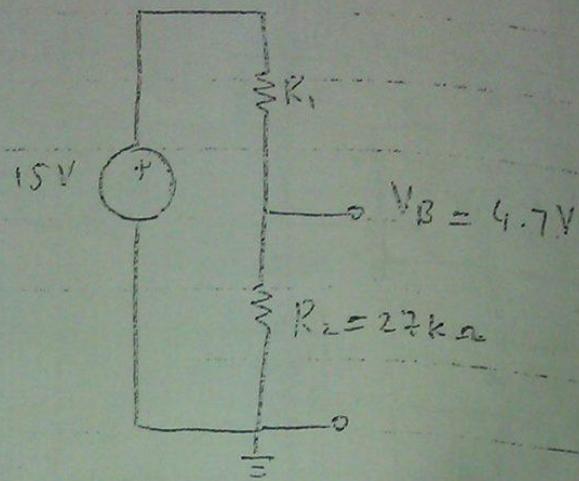Now for R_1 

$$V_B = \frac{R_2}{R_1 + R_2} \times 15$$

$$4.7 = \frac{27}{R_1 + 27} \times 15$$



$$4.7 R_1 + 126.9 = 40.5$$

$$4.7 R_1 = 278.1$$

$$R_1 = 59.2 k\Omega$$

$R_1 = 59.2 k\Omega$

so x

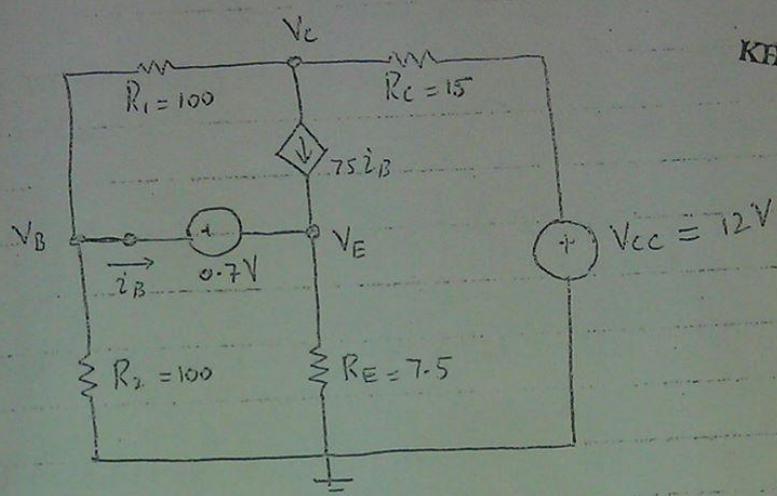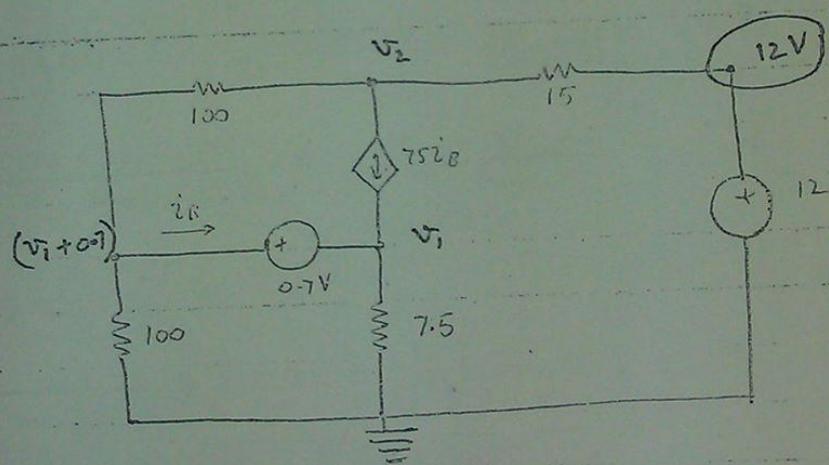KHALID PHOTO STATE
U.E.TKHALID PHOTO STATE
U.E.T

$$V_1 : 75i_B = \frac{V_1 - 0}{7.5} + \frac{(V_i + 0.7) - 0}{100} + \frac{(V_i + 0.7) - V_2}{100} = 0$$

$$750 \times (75i_B) = (100V_i) + (7.5V_1 + 5.25) + (7.5V_1 + 5.25 - 7.5V_2) = 0$$

$$56250i_B = 115V_1 - 7.5V_2 + 10.5 \quad (1)$$

18

$$56250 i_B = 115 v_1 - 7.5 v_2 + 10.5$$

 $v_2 =$

$$\frac{v_2 - (v_1 + 0.7)}{100} + 75 i_B + \frac{v_2 - 12}{15} = 0 \quad n = 115$$

$$15 v_2 - 15 v_1 - 10.5 + 112500 i_B + 100 v_2 = 225$$

$$115 v_2 - 15 v_1 = 1210.5 + 112500 i_B \quad 2265$$

$$15 v_1 - 115 v_2 + 1210.5 = 112500 i_B$$

$$i_B = \frac{0 - (v_1 + 0.7)}{100} + \frac{v_2 - (v_1 + 0.7)}{100} \quad 265$$

$$100 i_B = -v_1 - 0.7 + v_2 - v_1 - 0.7 \quad 9105$$

$$v_2 - 2 v_1 - 1.4 = 100 i_B \quad ③$$

from ③

$$i_B = \frac{v_2 - 2 v_1 - 1.4}{100} \quad \text{put in ①}$$

$$562.5(v_2 - 2 v_1 - 1.4) = 115 v_1 - 7.5 v_2 + 10.5$$

$$562.5 v_2 - 1125 v_1 - 787.5 = 115 v_1 - 7.5 v_2 +$$

$$(562.5 + 7.5) v_2 - (1125 + 115) v_1 - (787.5 + 10.5) = 0$$

$$570 v_2 - 1240 v_1 - 798 = 0$$

$$2.85 v_2 - 62.0 v_1 - 3.98 = 0$$

19.

from ③

$$i_B = \frac{v_2 - 2v_1 - 1.4}{100} \text{ put in } ②$$

$$-115v_2 + 1210.5 = 112500 \left(\frac{v_2 - 2v_1 - 1.4}{100} \right)$$

$$-115v_2 + 1210.5 = 1125v_2 - 2250v_1 - 157.5$$

$$2250v_1 - (115 + 1125)v_2 + (1210.5 + 157.5) = 0$$

$$265v_1 - 1240v_2 + 2785.5 = 0 \quad \text{--- } ⑤$$

from ④

$$v_2 = \frac{620v_1 + 399}{285} \text{ put in } ⑤$$

$$65v_1 - \frac{1240}{285} \left(\frac{620v_1 + 399}{285} \right) + 2785.5 = 0$$


$$105v_1 - 153760v_1 - 98952 + 158773.5 = 0$$

$$-24655v_1 + 59821.5 = 0$$

$$v_1 = \frac{59821.5}{24655}$$

$$v_1 = 2.426V \quad \text{put in } ④$$
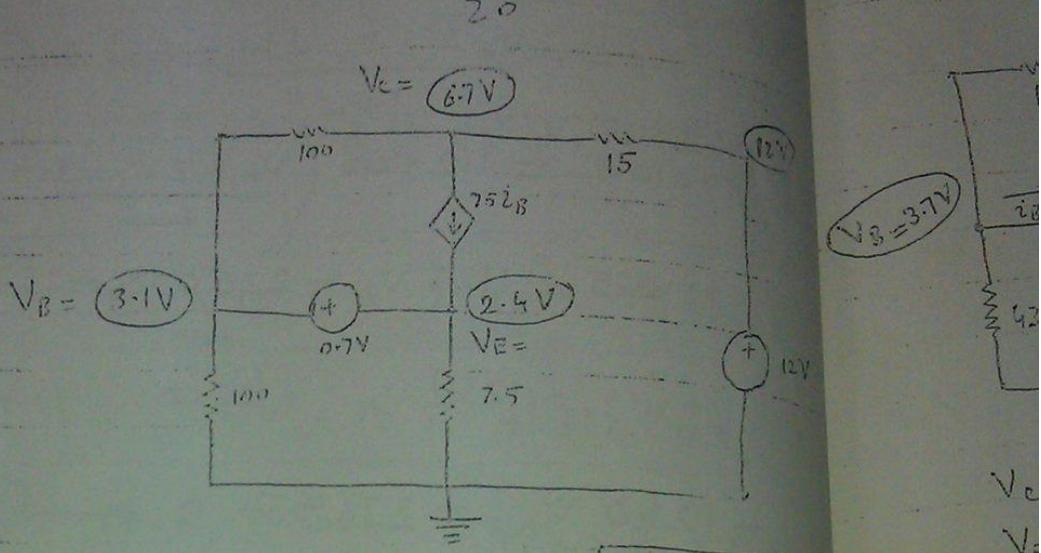
$$v_2 = 6.678V \Rightarrow v_1 = 2.4V \\ v_2 = 6.7V$$



Check:


$$i_C = \frac{V_C - V_E}{15k}$$

$$i_C = 0.35 \text{ mA}$$

$$i_B = \frac{i_C}{\beta} = \frac{0.35}{75}$$

$$i_B = 4.6 \mu\text{A}$$

21

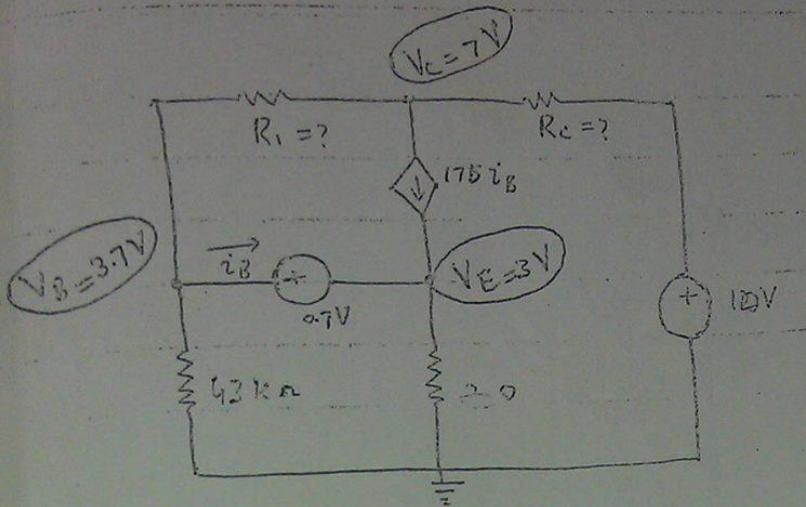

$$V_c = 7V$$

$$V_e = 3V \quad \text{given}$$

$$\therefore V_{CE} = 7 - 3 = 4V$$

$$\therefore V_B = V_E + V_{BE} = 3 + 0.7 = 3.7V$$

* As we know

$$V_E = (i_B + i_C) R_E$$

$$V_E = 176 i_B R_E$$

$$3 = 176 \times 2k \cdot i_B$$

$$i_B = \frac{3}{352k} = 8.5 \times 10^{-3} \text{ mA}$$

$$i_B = 8.5 \mu A$$

* As we know

$$V_c = 10 - i_C R_C$$


$$7 = 10 - i_C R_C$$

$$i_C R_C = 3$$

$$R_C = \frac{3}{175 i_B} = \frac{3}{175 \times 8.5 \mu} = 2.0 \times 10^3$$

22.

* For R_1 ,

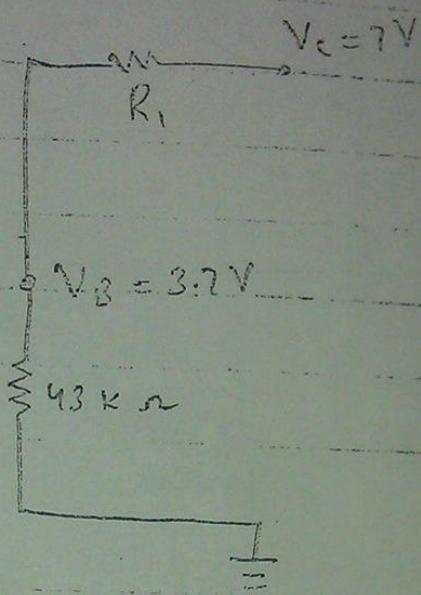

$$V_B = \frac{43}{R_1 + 43} \times 7$$

$$3.7(R_1 + 43) = 301$$


$$3.7R_1 + 159.1 = 301$$

$$R_1 = \frac{301 - 159.1}{3.7} = 38.35$$

$$R_1 = 38.4 \text{ k}\ \Omega$$

2 Circuit Analysis with Dependent Sources:-

2

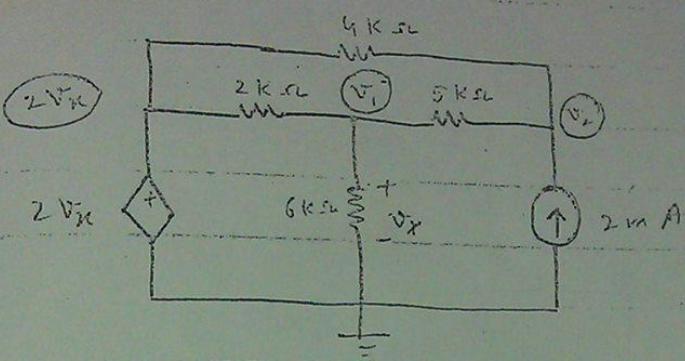 $P_{S-Kn} = ?$ [mA], [k Ω], [V]KHALID PHOTOSTATE
U.E.T

$$\frac{V_1 - 2V_x}{2} + \frac{V_1 - 0}{6} + \frac{V_1 - V_2}{5} = 0.$$

$$15V_1 - 30V_x + 5V_1 - 6V_1 - 6V_2 = 0$$

$$26V_1 - 6V_2 = 30V_x \quad \text{--- (1)}$$

$$\frac{V_2 - 2V_x}{4} + \frac{V_2 - V_1}{5} = 2$$

$$5V_2 - 10V_x + 4V_2 - 4V_1 = 40$$

$$9V_2 - 4V_1 = 40 + 10V_x \quad \text{--- (2)}$$

~~from~~
 $V_x =$

$$V_x = (V_1 - 0)$$

$$V_x = V_1 \quad \text{--- (3)} \quad \text{put in (1) & (2)}$$

$$26V_1 - 6V_2 = 30V_1$$

$$-6V_2 = 4V_1$$

24

$$9V_2 - 4V_1 = 40 + 10V_1$$

$$9V_2 - 14V_1 = 40$$

from (4) $V_1 = \frac{-3}{2}V_2$ (5)

$$9V_2 - 14 \left(\frac{-3}{2}V_2 \right) = 40$$


$$9V_2 + 21V_2 = 40$$

$$30V_2 = 40$$

$$\boxed{V_2 = \frac{4}{3}}$$
 put in (4)

$$V_1 = -\frac{3}{2} \left(\frac{4}{3} \right)$$
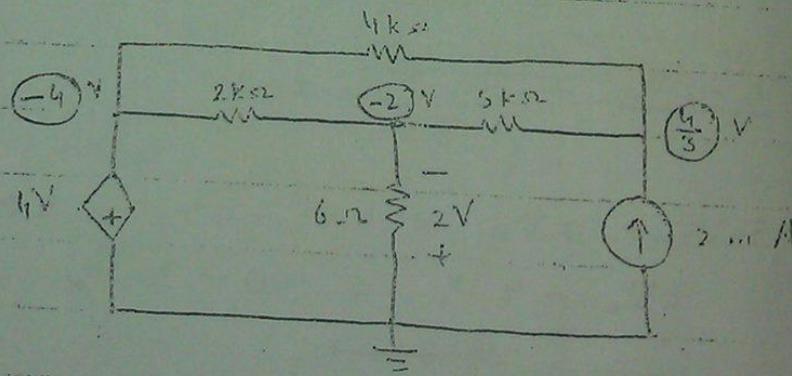
$$\boxed{V_1 = -2} \Rightarrow \boxed{V_K = -2}$$



$$V_{4k\Omega} = \frac{4}{3} - (-4) = \frac{4}{3} + 4 = \frac{16}{3}$$


$$P_{4k\Omega} = \frac{\left(\frac{16}{3}\right)^2}{4k} = \frac{64}{9}$$

$$Q] P_{6K2} = ?$$

[mA], [k₂], [V]

Wrong Method:- (For Concept)

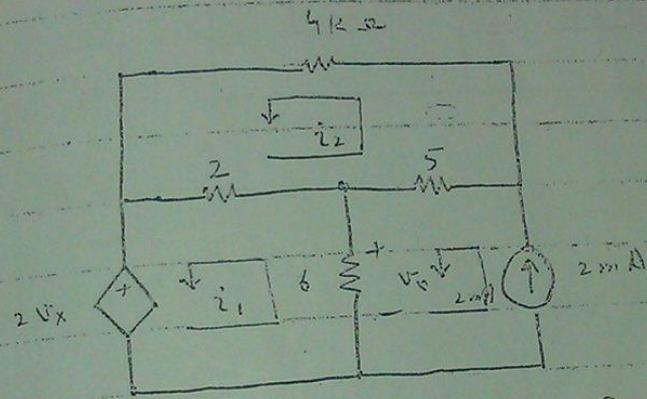We should have to solve this q₁ by taking the direction of i_2 as shown in the fig.



But in this way
6K2 is potential rising as we are assuming
 v_{x-} + and $(i_1 - i_2) \uparrow$ and 2Vx is potential
dropping -


The answer will be wrong in this way -
because we can never take a resistive component
as an active component -

So we will do this q₁ as :

Q5. 13

26

Right Method :-

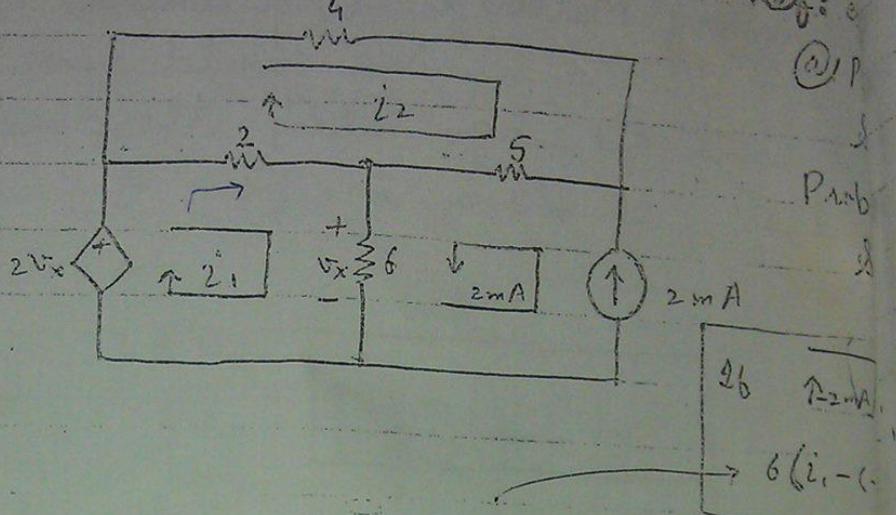

Ref:

Q1P

P1ab

\$\Delta\$

$$2V_x = 6(i_1 + 2) + 2(i_1 - i_2)$$

i_2

$$4i_2 + 5(i_2 + 2) + 2(i_2 - i_1) = 0$$

V_x :

$$V_x = 6(i_1 + 2)$$

On solving the above eqns by MS graphing calculator we get -

$$V_x = -2$$

$$i_1 = -\frac{7}{3}$$

$$i_2 = -\frac{4}{3}$$

STATE


$$i_{6ka} = i_1 + 2 = -\frac{7}{3} + 2 = -\frac{1}{3}$$

$$P_{6ka} = V_{2k} \cdot i_{6ka} = (-2) \left(-\frac{1}{3}\right) = \frac{2}{3}$$

HOSTA

D

27

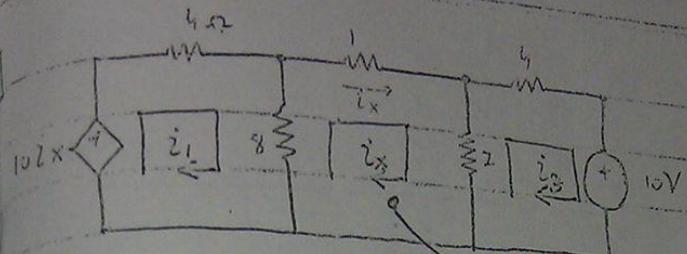

(a) P

P_{1ab}

S

P_{2...A}

$$(i_1 - i_x) + 10 = 4i_1 + 8(i_x - i_3)$$

$$i_x : 8(i_x - i_1) + i_x + 2(i_x - i_3) = 0$$

$$= 0 \quad i_x : 2(i_3 - i_x) + 4i_3 + 10 = 0$$

MS:


$i_x = 2$
$i_1 = 3$
$i_3 = -1$

$$V_{CCVS} = 10i_x = 20V \quad (+ at top)$$

$$V_{8\Omega} = 8(3-2) = 8V \quad (+ at top)$$

$$V_{2\Omega} = 2(2 - (-1)) = 2(2+1) = 2(3) = 6V \quad (+ at top)$$

28

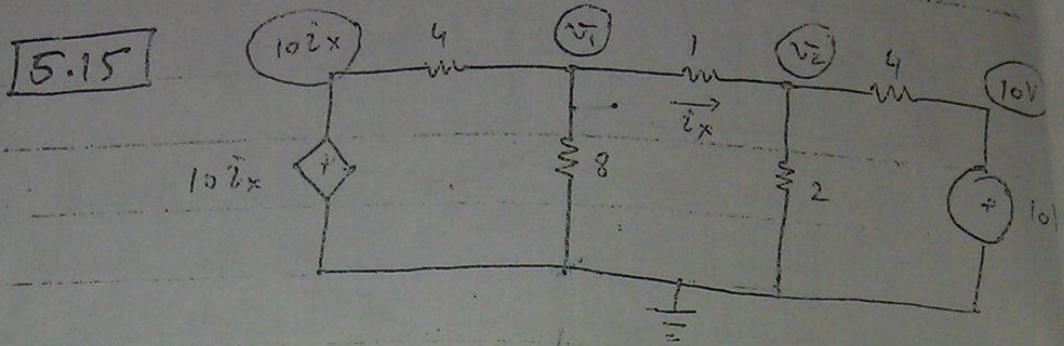

$$i_x = \frac{V_1 - V_2}{1} = V_1 - V_2$$

For V_1

$$\frac{V_1 - 10i_x}{4} + \frac{V_1 - 0}{8} + \frac{V_1 - V_2}{1} = 0$$

For V_2

$$\frac{V_2 - 10}{4} + \frac{V_2 - 0}{2} + \frac{V_2 - V_1}{1} = 0$$

$i_x = 2 \text{ A}$
$V_1 = 8 \text{ V}$
$V_2 = 6 \text{ V}$

$$V_{CEV} = 10i_x = 20 \text{ V}$$

$$V_{QD} = 8 \text{ V}$$


$$V_{SD} = 6 \text{ V}$$

all (+ at top)

30.

P_{B12}

[5.17]

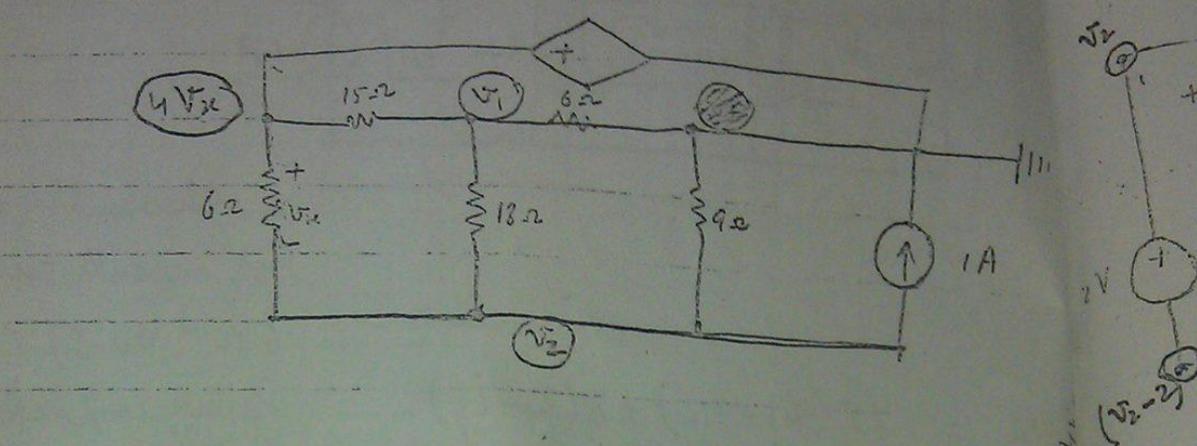

$$V_x = 4V_x - V_2$$

$$\frac{V_1 - 4V_x}{15} + \frac{V_1 - V_2}{18} + \frac{V_1 - 0}{6} = 0$$

$$\frac{V_2 - V_1}{18} + \frac{V_2 - 4V_x}{6} + 1 + \frac{V_2 - 0}{9} = 0$$

$$\boxed{\begin{aligned} V_x &= 12V \\ V_1 &= 18V \\ V_2 &= 36V \end{aligned}}$$

$$\boxed{\begin{aligned} V_x &= -4V \\ V_1 &= -6V \\ V_2 &= -12V \end{aligned}}$$

$$V_{TA} = V_1 - 0 = 36V = 36V (+)$$


$$V_{TA} = 0 - V_2$$

$$V_{TA} = 0 + 12V = 12V (+ \text{ at top})$$

31

$$P_{8\text{ k}\Omega} = ?$$

[mA], [kΩ], [V]:

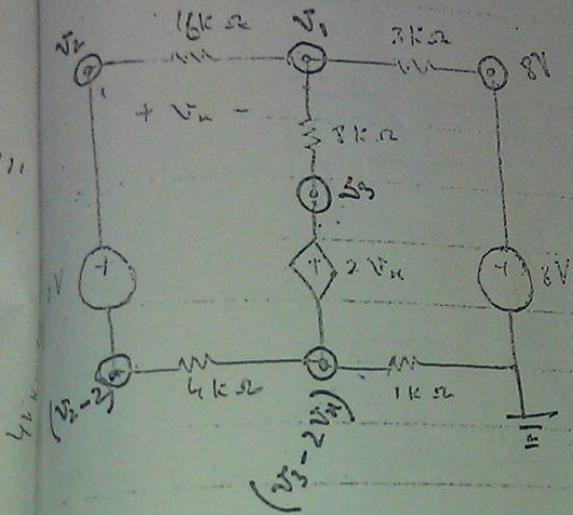

$$v_x = v_2 - v_1$$

$$\frac{v_1 - 3}{3} + \frac{v_1 - v_2}{16} + \frac{v_1 - v_3}{8} = 0$$

$$\frac{v_2 - v_1}{16} + \frac{(v_2 - 2) - (v_3 - 2v_x)}{4} = 0$$

$$\frac{v_3 - v_1}{8} + \frac{(v_3 - 2v_x) - (v_2 - 2)}{4} + \frac{(v_3 - 2v_x) - 0}{1} = 0$$

$$v_x = -\frac{2}{5} \text{ V}$$

$$v_1 = 5 \text{ V}$$


$$v_2 = 17/5 \text{ V}$$

$$v_3 = -11/5 \text{ V}$$

$$v_{8\text{k}\Omega} = V_1 - V_3 = 5 + \frac{11}{5} = \frac{36}{5} = 7.2 \text{ mV}$$

32

5.19

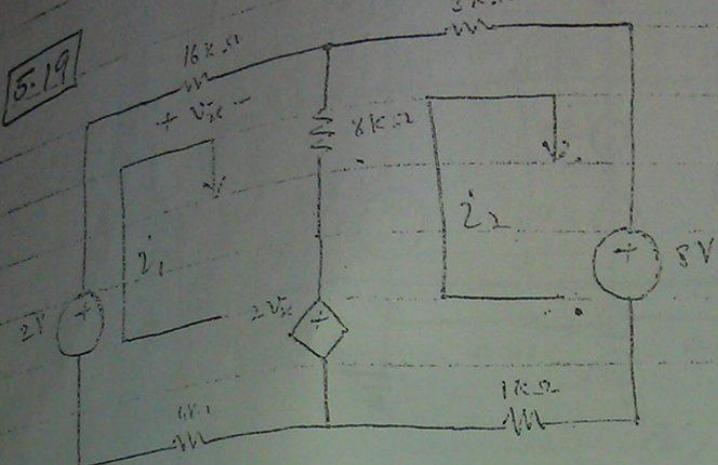

this some
base

potential -
polarities -

* I choose the

of currents to

$16\text{ k}\Omega$ desired

$$16i_1 + 8(i_1 - i_2) + 2V_K + 4i_1 = 2$$

$$3i_2 + 3(i_2 - i_1) + 8 + i_2 = 2V_K$$

$$V_K = 16i_1 \quad \text{--- (3)}$$

$$V_K = -\frac{8}{5} \text{ V}$$

$$i_1 = -1/10 \text{ m.A}$$

$$i_2 = -1 \text{ m.A}$$

5.20

5.21


$$V_{KVS} = 2V_K = 2\left(-\frac{8}{5}\right) = -\frac{16}{5} \text{ V}$$

$$i_{KVS} = i_1 = -1/10 \text{ mA} =$$

33

The answer given in the book is wrong.
 This source can never be releasing
 because they are

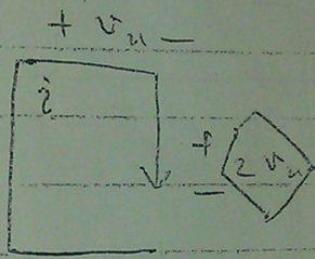$V_{\text{out}} = +V_u -$ this
 initial drift is $2V_u$ dependent source has same
 quantities -



third

to in 5.20

ratio 5.21

do yourself-

$$i = \frac{v - v_1}{15} \quad \textcircled{1}$$

At v_1

$$\frac{v_1 - v}{15} + 4v_x + \frac{v_1 - v_x}{10} = 0$$

$$5v_1 + 117v_x - 2v = 0 \quad \textcircled{2}$$

At v_x

$$\frac{v_x - v_1}{10} + \frac{v_x - v_2}{5} = 0$$

$$3v_x - v_1 = 0 \quad [5.22]$$

$$\textcircled{1}' \quad v_x = v_1 / 3$$

(2)

(2) \Rightarrow

$$5v_1 + 117\left(\frac{v_1}{3}\right) - 2v = 0 \quad \frac{v}{i} = 15.7\Omega$$


$$44v_1 - 2v = 0$$

$$v_1 = \frac{v}{22}$$

$$\textcircled{1} \Rightarrow 15i = v - \frac{v}{341}$$

$$15i = v - \frac{v}{22}$$

$$R_{eq} = ?$$

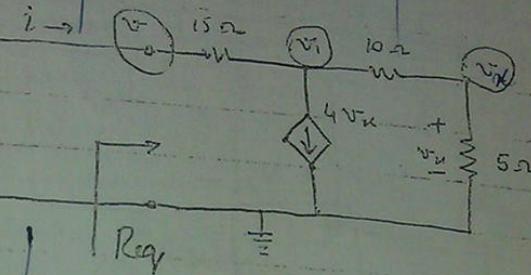

(3)

$$i = \frac{v - v_1}{15} + 4v_2 + \frac{v_1 - v_2}{10}$$

$$+ 30i = 5v_1 - 2v + 117v_x \quad \textcircled{1}$$

$$\frac{v_x - v_1}{5} + \frac{v_x - v_2}{10} = 0$$

$$3v_x - v_1 = 0$$

$$v_x = \frac{v_1}{3}$$

$$\textcircled{1}' \quad \text{put } \textcircled{1} \text{ into } \textcircled{1}$$

$$+ 30i = 5v_1 - 2v + 117\left(\frac{v_1}{3}\right)$$

$$+ 30i = 5v_1 - 2v + 39v_1$$

$$+ 30i = 44v_1 - 2v$$

$$\text{But } i = \frac{v - v_1}{15}$$

$$\textcircled{3} \quad \text{KHALED PHOTOSTA} \quad 15i = \frac{v - v_1}{15}$$

$$v_1 = \frac{v - v}{15}$$

$$\textcircled{1} \Rightarrow$$

$$+ 30i = 44(15i + v) - 2v$$

$$R_{eq} = \frac{v}{i}$$

$$\frac{v_1 - v}{15} + \frac{v_1 - v_2}{10} + 4v_u = 0$$

$$\frac{v_2 - v_1}{10} + \frac{v_2 - v}{5} = 0$$

$$v_u = \frac{v_2 - v}{5} = \frac{v_2}{5} \quad [5]$$

$$i = \frac{v - v_1}{15}$$

From $\textcircled{1}, \textcircled{2}$ & $\textcircled{3}$

$$v_1 = \frac{4 + 5\left(-\frac{1}{10}\right) + 3\left(\frac{1}{10} + \frac{1}{15}v + \frac{1}{15}(1-v)\right)}{15}$$

$$v_2 = \frac{3\left(4 + 5\left(-\frac{1}{10}\right) + 3\left(\frac{1}{10} + \frac{1}{15}v + \frac{1}{15}(1-v)\right)\right)}{5}$$

from ①

$$5V_1 - 3V_2 + 120V_u = 2V \quad \text{--- } ①'$$

from ②

$$V_2 = 3V_1/5 \quad \text{--- } ②'$$

from ③

$$V_u = \frac{V_2}{24} \quad \text{--- } ③'$$

yourself

from ② & ③ put in ①

$$5V_1 - 3\left(\frac{V_1}{5}\right) + 120\left(\frac{V_2}{24}\right) = 2V$$

$$5V_1 - \frac{3V_1}{5} + 5V_2 = 2V$$

from ③' $V_u = \frac{V_2}{24}$ put in ①'

$$5V_1 - 3V_2 + 120\left(\frac{V_1}{5}\right) = 2V$$

$$5V_1 - 3V_2 + 24V_1 = 2V$$

$$29V_1 - 3V_2 = 2V$$

from ② $V_2 = \frac{V_1}{3}$ put in ⑤

$$29V_1 - 3\left(\frac{V_1}{3}\right) = 2V$$

$$28V_1 = 2V$$

$$-2V_1 = 2V$$

$$-V_1 = V$$

$$\boxed{V_1 = -V}$$

put in ⑥

36


$$i = \frac{v_n - v}{15} \text{ A}, i = \frac{2v_n}{15}$$

$$\frac{15}{2} = \frac{v}{2}$$

$$R_{eq} = \frac{v}{i} = \frac{15}{2} \Omega$$

$$R_{eq} = 7.5 \Omega$$

5.23

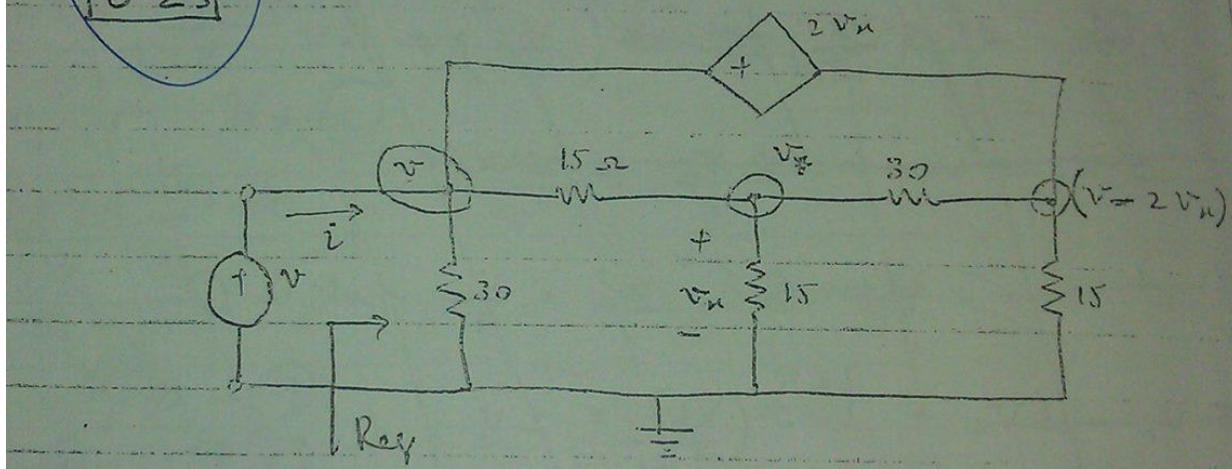

$$v_i = v_{n1} = 0$$

$$v_i = v_n \quad \text{--- (1)}$$

v_{n3}

$$i = \frac{v-0}{30} + \frac{v-v_i}{15} + \frac{(v-2v_n)-0}{15}$$

$$+ \frac{(v-2v_n)-v_i}{15}$$

$$30i = (v) + (2v - 2v_n) + (2v - 2v_n) + (v - 2v_n) - v_i$$

$$30i = 6v - 6v_n - 3v_i$$

From (1) $v_i = v_n$ but in above

37:

$$\frac{v_1 - v_o}{15} + \frac{v_1 - (v - 2v_n)}{30} + \frac{v_1 - v}{15} = 0$$

$$2v_1 - 2v + v_1 - v + 2v_n + 2v_1 = 0$$

$$5v_1 + 2v_n - 3v = 0$$

as from ① $v_1 = v_n$ put in above

$$5v_n + 2v_n - 3v = 0$$

$$7v_n = 3v$$

$$v_n = \frac{3v}{7} \quad \text{--- } ③$$

put in ②

[5.]

$$30i = 6v - 9\left(\frac{3v}{7}\right)$$

$$210i = 42v - 27v$$


$$210i = 15v$$

$$\frac{210}{15} \rightarrow \frac{v}{i}$$

$$\frac{v}{i} = 14$$

$$R_v = 14 \Omega$$

V

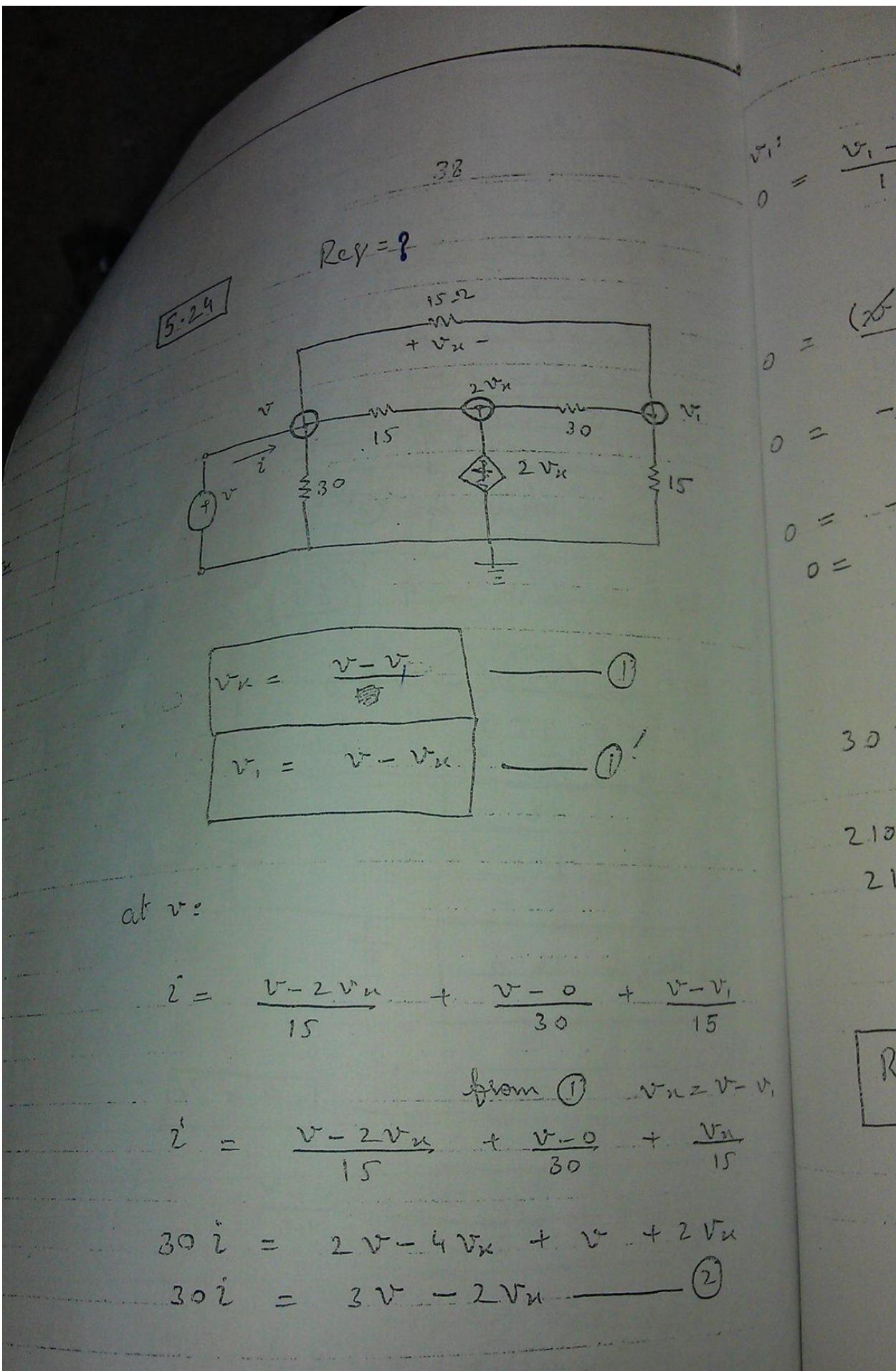

$$0 = \frac{v_i - v}{15} + \frac{v_i - 2v_n}{30} + \frac{v_i - 0}{15}$$

that $v_i = v - v_n$ in above

$$0 = \frac{(v - v_n) - v}{15} + \frac{v - v_n - 2v_n}{30} + \frac{v - v_n}{15}$$

$$0 = -\frac{v_n}{15} + -\frac{v - 3v_n}{30} + \frac{v - v_n}{15}$$

$$0 = -2v_n + v - 3v_n + 2v - 2v_n$$

$$0 = 3v - 7v_n$$

$$7v_n = 3v$$

$$\boxed{v_n = \frac{3v}{7}} \quad \text{③ put in ②}$$

$$30i = 3v - 2\left(\frac{3v}{7}\right)$$

$$210i = 21v - 6v$$

$$210i = 15v$$


$$14i = v$$

$$\frac{v}{i} = 14$$

$$\boxed{R_{eq} = 14 \Omega}$$

5.25

$$R_{eq} = ?$$

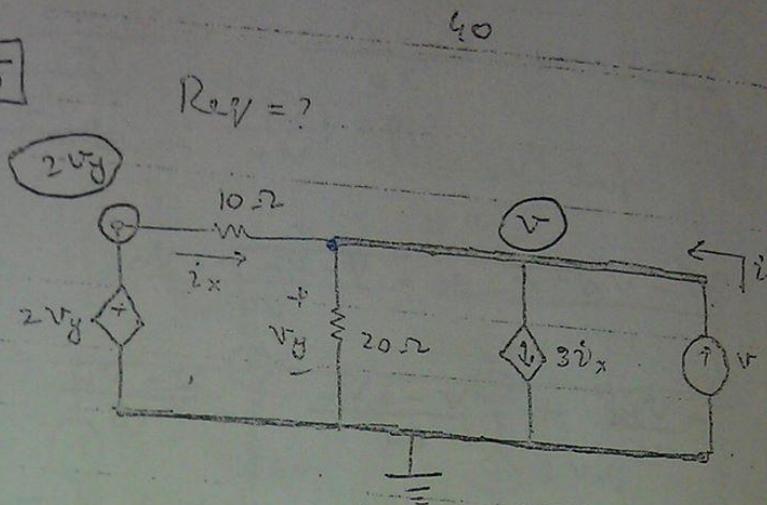

$$V_y = V - 0$$

$$V = V_y \quad \text{--- (1)}$$

$$i_x = \frac{2V_y - V}{10}$$

$$\text{from (1)} \quad V = V_y$$

$$i_x = \frac{2V_y - V_y}{10}$$

$$i_x = \frac{V_y}{10} \quad \text{--- (2)}$$

at V:

$$i = 3i_x + \frac{V - 0}{20} + \frac{V - 2V_y}{10}$$

$$i = 3i_x + \frac{V}{20} + \frac{V - 2V_y}{10}$$

$$20i = 60i_x + V + 2V - 4V_y$$

$$20i = 60i_x + 3V - 4V_y$$

$$\text{from (2)} \quad i_x = \frac{V_y}{10}$$

$$20i = 6 \left(\frac{v_y}{10} \right) + 3v - 4v_y$$

$$20i = 6v_y + 3v - 4v_y$$

from ① $v = v_y$ put in above

$$20i = 6v + 3v - 4v$$

$$420i = 8v$$


$$\frac{v}{i} = 4$$

$$R_g = 4 \Omega$$

26


[Ω], [mA], [V]

(a)

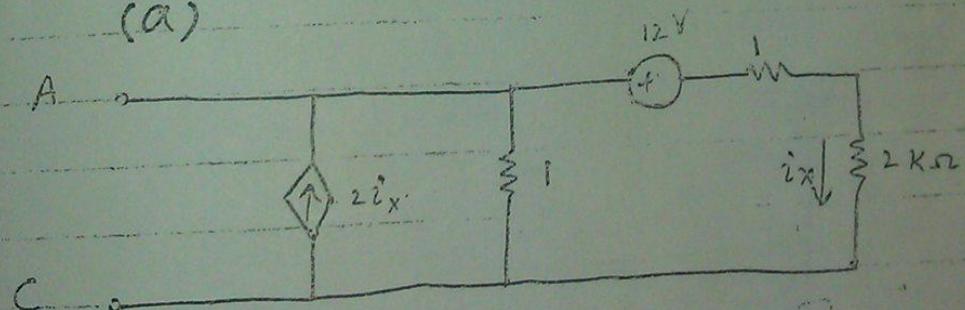

For this we have to find R_{eq} & V_{oc}

For V_{oc} by loop Method -

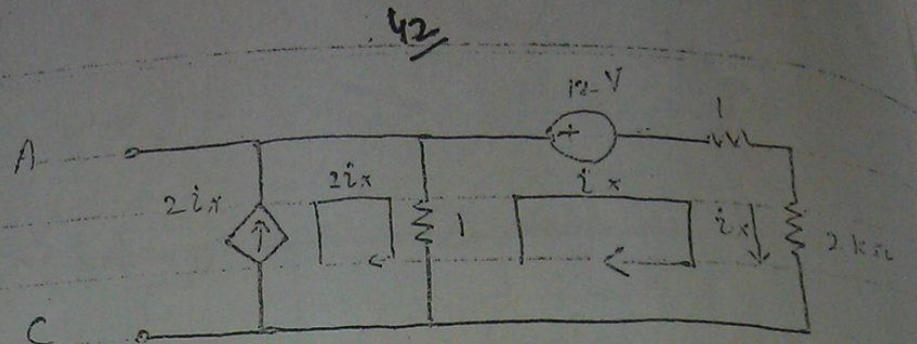

loop I:

$$12 + i_x + 2i_x + (i_x - 2i_x) = 0$$

$$12 + i_x + 2i_x + i_x - 2i_x = 0$$

$$12 + 2i_x = 0$$

$$2i_x = -12$$

$$\boxed{i_x = -6 \text{ A}}$$

$$v_{12} = 1(i_x - 2i_x)$$

$$= (-6 - 2(-6))$$


$$= -6 + 12$$

$$\boxed{v_{12} = 6 \text{ V } (+)} \quad \text{as } i_x \uparrow$$


as 1-2 resistance & 2ix source in parallel.

$$\boxed{V_{OC} = v_{12} = 6 \text{ V } (+)}$$


For Part (b) find i_x

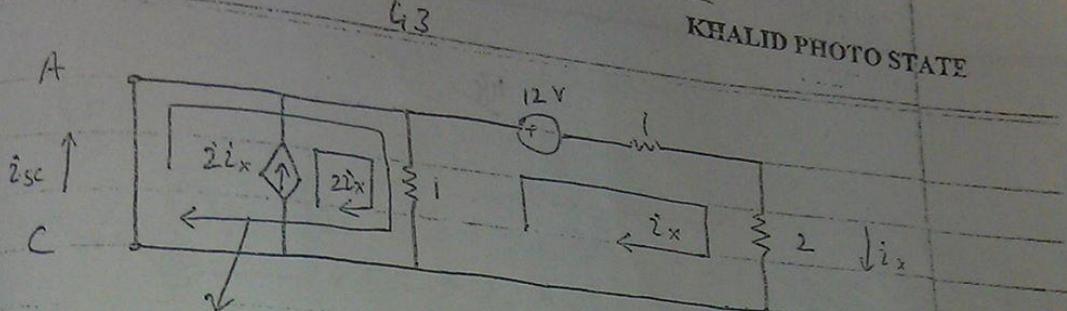

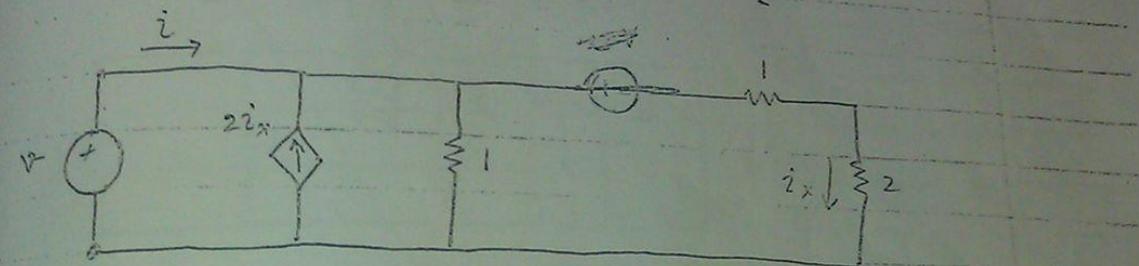we can assume this loop - So we
will find R_{eq} by 2nd Method



Now applying loop analysis

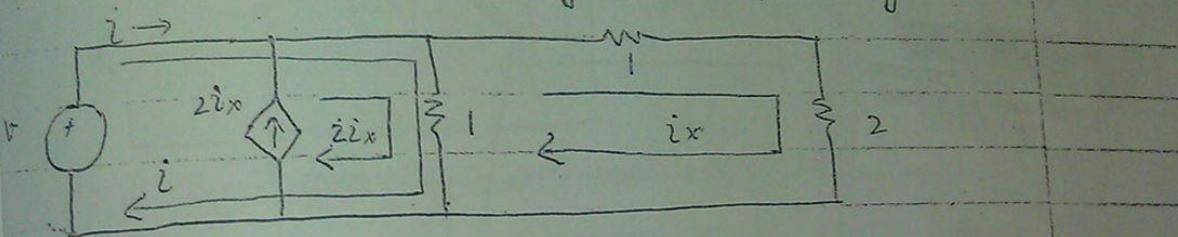

Loop I :

$$(i_x - 2i_x) + i_x + 2i_x = 0$$

$$2i_x + 2i_x + (i_x - (i + 2i_x)) = 0$$

$$3i_x + i_x - i - 2i_x = 0$$

$$2i_x - i = 0 \quad \text{--- (1)}$$

Loop II :

$$v = (i + 2i_x)$$

$$v = i + 2i_x \quad \text{--- (2)}$$

49

$$2ix - i = 0 \quad \text{--- (1)}$$

$$v = i + 2ix \quad \text{--- (2)}$$

from (1)

$$ix = \frac{i}{2} \quad \text{put in (2)}$$



$$v = i + 2\left(\frac{i}{2}\right)$$

$$v = 2i$$

$$\frac{v}{i} = 2$$





$R_{eq} = 2k\Omega$

Now Thervin's equivalent

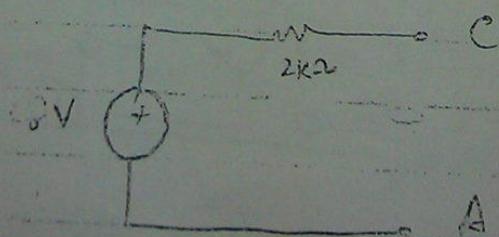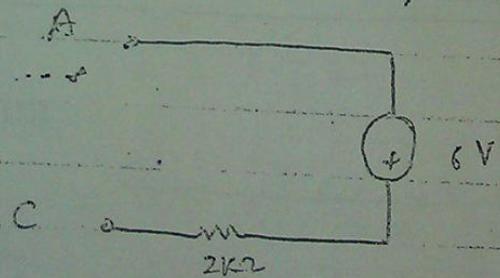

45

(b)

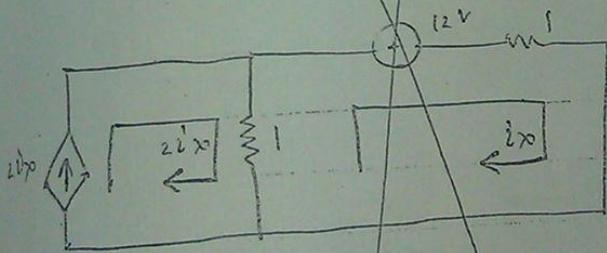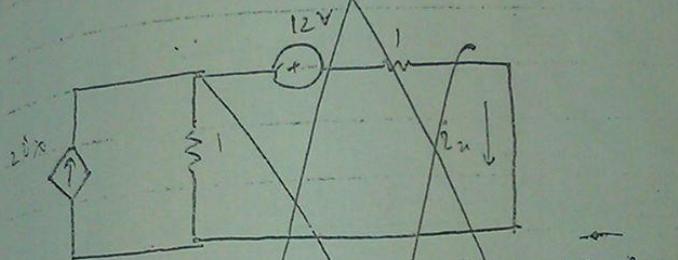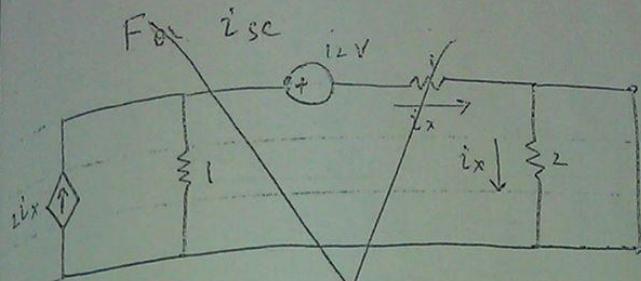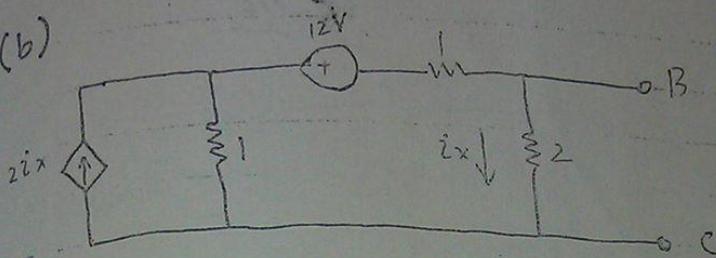loop I₂

$$12 + i_x - (i_x - 2i_x) = 0$$


$$12 + i_x + i_x - 2i_x = 0$$

$$12 \neq 0$$

KHALID PHOTO STATE
Composing And Photo Copy
Student Services Centre
J.E.T. LHR.

KHALID PHOTO STATE
Composing And Photo Copy
Student Services Centre
J.E.T. LHR.

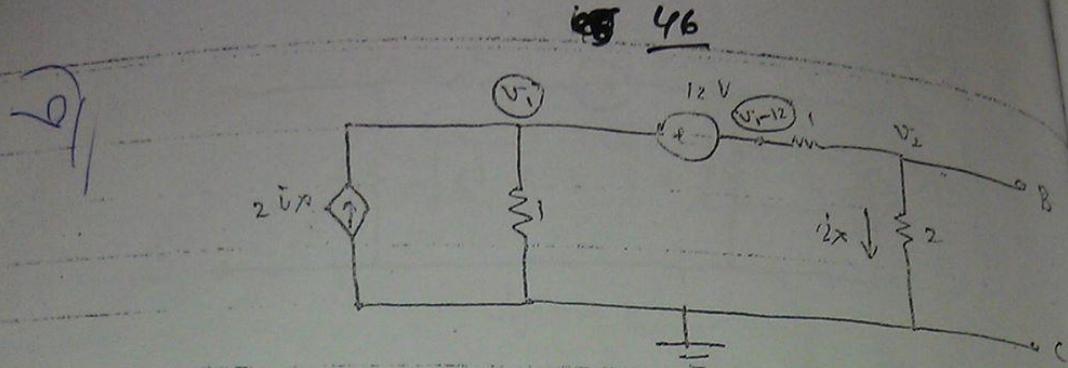KHALID PHOTO STATE
Composing And Photo Copy
Student Services Centre
J.E.T. LHR.



at V_1 :

$$2i_x = \frac{V_1 - 0}{1} + \frac{(V_1 - 12) - V_2}{1}$$

$$2i_x = V_1 + V_1 - 12 - V_2$$

$$2i_x = 2V_1 - V_2 - 12$$

$$2V_1 - V_2 = 2i_x + 12 \quad \textcircled{1}$$

at V_2 :

$$\frac{V_2 - 0}{2} + \frac{V_2 - (V_1 - 12)}{1} = 0$$

$$V_2 + 2V_2 - 2V_1 + 24 = 0$$

$$3V_2 - 2V_1 = -24 \quad \textcircled{2}$$

i_x :

$$i_x = \frac{V_1 - 0}{2} - \frac{V_2}{2}$$

$i_x = \frac{V_2}{2}$
\textcircled{3}

$V_1 = -6 \text{ V}$

$V_2 = -12 \text{ V}$

47

KHALID PHOTO STATE


$$V_{OC} = V_C - 0 \\ = -12 - 0$$

$$V_{OC} = -12 \text{ V}$$

B

$$V_{OC} = 12 \text{ V} \quad (-) \quad (+)$$

For Reg.

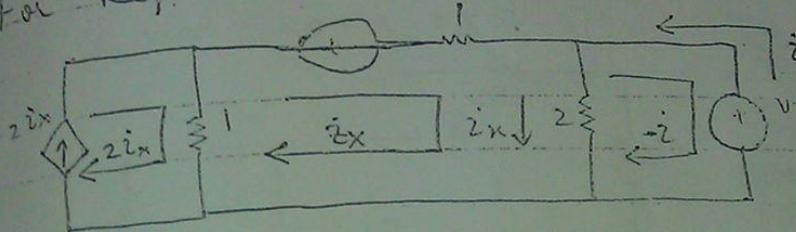

loop I:

$$i_x + (i_x - 2i_x) + 2(i_x - (-i)) = 0$$

$$i_x + i_x - 2i_x + 2i_x + 2i = 0$$

$$2i_x + 2i = 0$$

$$i_x + i = 0$$

loop II:

$$2(-i) + v = 0$$

$$-2i + v = 0$$


$$v = 2i$$

KHALID PHOTO STATE
U.E.T

$$\frac{v}{i} = 2$$


R_{reg} = 2 k Ω

KHALID PHOTO STATE
U.E.T

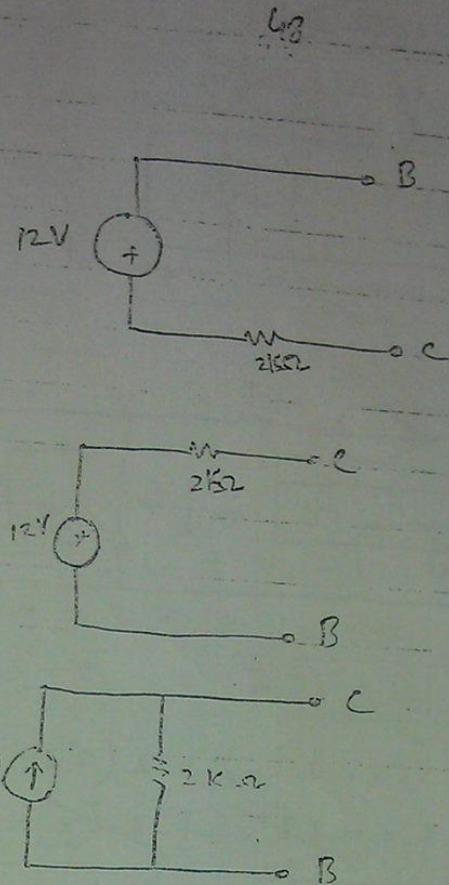

Alternate :-


Forise :-

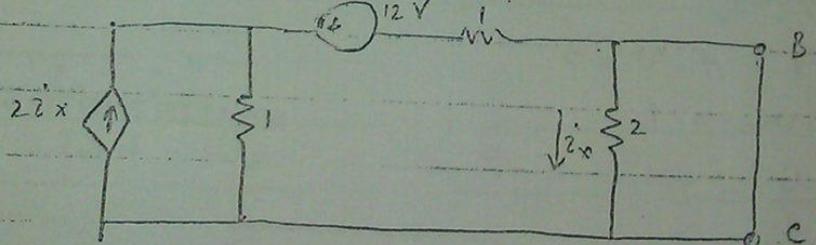

In this case, $i_x = 0$, then $i_{22x} = 0$
 is also 0 - when current is zero it means that
 circuit is open.

So our circuit will become.


KHALID PHOTO STATE
U.E.T

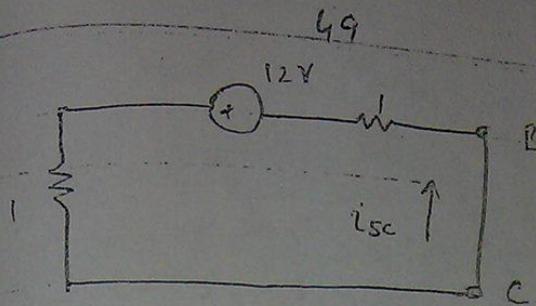


$$i_{sc} = 6 \text{ mA}$$

by 2nd law
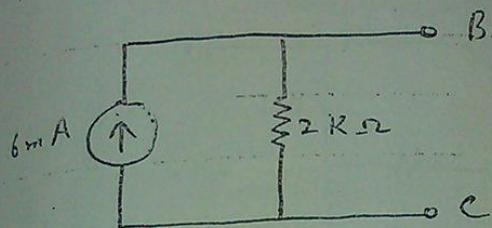
$$\text{and } R_{eq} = 2 \text{ k}\Omega$$



KHALID PHOTO STATE
U.E.T

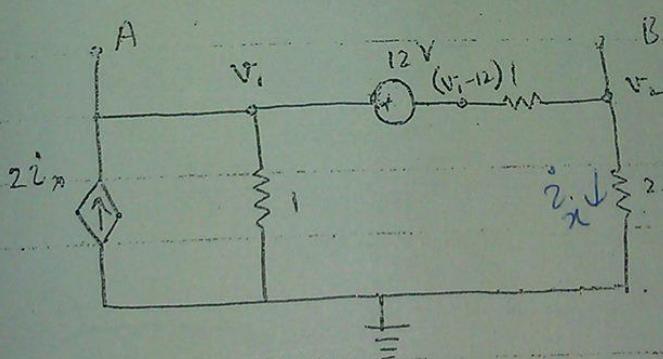

$$2i_x = \frac{V_1 - 0}{1} + \frac{(V_1 - 12) - V_2}{1} \quad (1)$$

$$\frac{V_1 - 0}{2} + \frac{V_2 - (V_1 - 12)}{1} = 0 \quad (2)$$

$$i_x = \frac{V_2 - 0}{2} = \frac{V_2}{2} \quad (3)$$

$$\begin{cases} V_1 = -6 \text{ V} \\ V_2 = -12 \text{ V} \end{cases}$$


50

$$V_{OC} = V_A - V_B$$

$$= -6 - (-12) = 6V$$

$$\boxed{V_{OC} = 6V}$$

For Reg

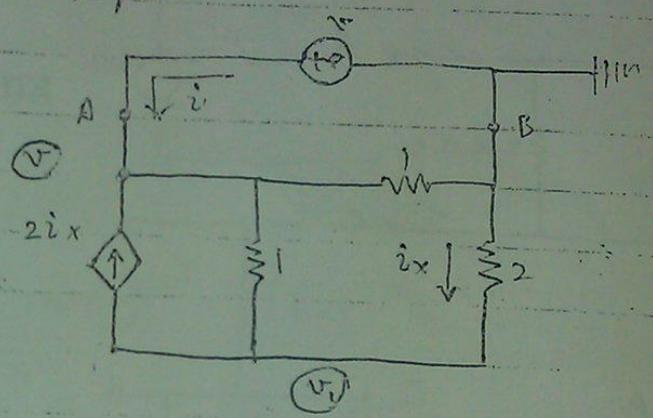

at V :

$$i + 2i_x = \frac{V_0}{R_1} + \frac{V - V_1}{R_1}$$

$$i + 2i_x = V + 11 - V,$$

$$i + 2i_x = 2V - V, \quad (1)$$

at V_1 :

$$2i_x + \frac{V_1 - V}{R_1} + \frac{V_1 - 0}{R_2} = 0$$

$$4i_x + 2V_1 - 2V + V_1 = 0$$

$$3V_1 - 2V = -4i_x \quad (2)$$

2_p:

$$2i_x = \frac{0 - V_1}{2}$$

5.1

put $v_1 = -2i_x$ in ①


$$i + 2i_x = 2v - (-2i_x)$$

$$i + 2i_x = 2v + 2i_x$$

$$i = 2v$$

$$\frac{v}{i} = \frac{1}{2}$$

$$R_{eq} = \frac{1}{2} \text{ k}\Omega$$

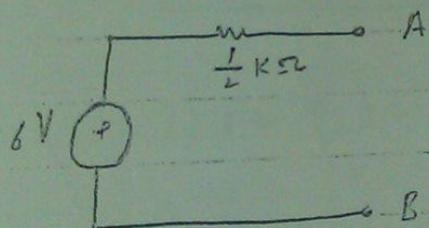


$$P_{max} = \frac{1}{4} \cdot \frac{v_s^2}{R_s} = \frac{1}{4} \cdot \frac{36}{1/2} = 18 \text{ mW}$$

$$P_{max} = 18 \text{ mW}$$

52

5.28 (a)

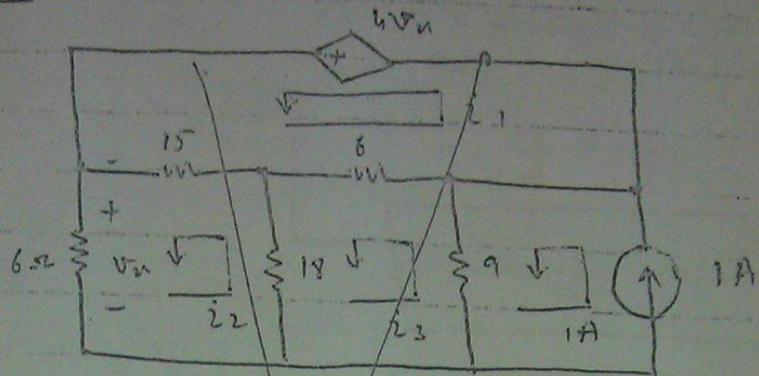 $i_{1,2}$

$$4v_n = 15(i_1 - i_2) + 6(i_1 - i_3)$$

 $i_{2,3}$

$$6i_2 + 15(i_2 - i_1) + 18(i_2 - i_3) = 0$$

 i_3

$$18(i_3 - i_2) + 6(i_3 - i_1) + 9(i_3 - i) = 0$$

 v_n


$$v_n = 6i_2$$

$i_n = -4V$
$i_1 = -\frac{4}{3}A$
$i_2 = -\frac{2}{3}A$
$i_3 = -\frac{1}{3}A$

$$v_{18\Omega} = 18(i_3 - i_2) =$$

By here $P_{6\Omega} = (i_3 - i_1)^2 \cdot \frac{1}{3} + \frac{4}{3} = \frac{2}{3} = 1W$

5.28

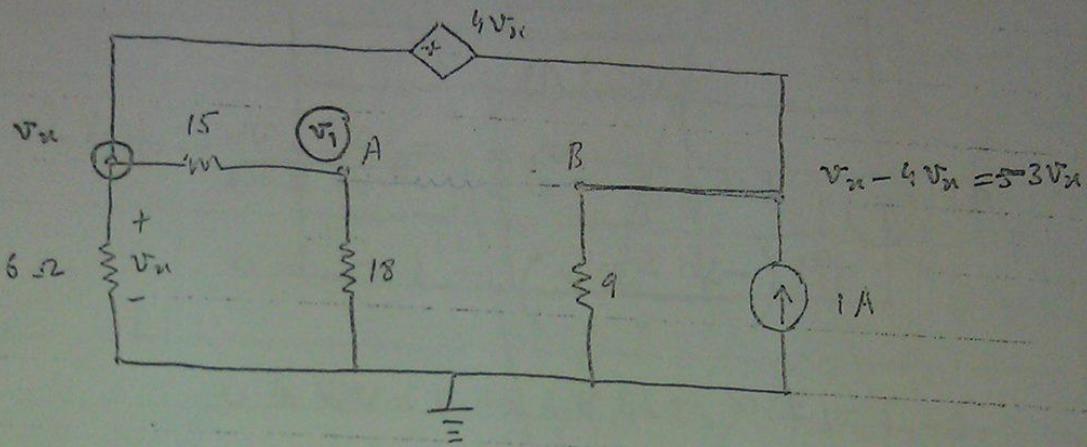at v_u :

$$I = \frac{v_u - 0}{6} + \frac{v_u - v_1}{15} + \frac{-3v_u - 0}{9}$$

$$90 = 15v_u + 6v_u - 6v_1 - 30v_u$$

$$90 = -9v_u - 6v_1$$

$$-30 = 3v_u + 2v_1$$

$$2v_1 + 3v_u = -30 \quad \textcircled{1}$$

at v_1 :

$$\frac{v_1 - v_u}{15} + \frac{v_1 - 0}{18} = 0$$

$$18v_1 - 18v_u + 15v_1 = 0$$

$$33v_1 - 18v_u = 0$$

$$11v_1 - 6v_u = 0 \quad \textcircled{2}$$

54

$$2v_1 + 3v_x = -30 \quad \text{--- (1)}$$

$$11v_1 - 6v_x = 0 \quad \text{--- (2)}$$

Solve (1)

$$v_1 = \frac{-30 - 3v_x}{2} \text{ put in (2)}$$

$$11 \left(\frac{-30 - 3v_x}{2} \right) - 6v_x = 0$$

$$-330 - 33v_x - 12v_x = 0$$

$$45v_x = -330$$

$$\boxed{v_x = -\frac{22}{3} V} \quad \text{put in (1)}$$

$$2v_1 + 3\left(-\frac{22}{3}\right) = -30$$

$$2v_1 - 22 = -30$$

$$2v_1 = -30 + 22$$

$$2v_1 = -8$$

$$\boxed{v_1 = -4 V}$$


$$v_{oc} = v_1 - (-3v_x)$$

$$= -4 + 3v_x = -4 + 3\left(-\frac{22}{3}\right)$$

$$= -4 - 22 = -26 V (+ -)$$

$$\boxed{v_{oc} = 26 V (-+)}$$

For Rep

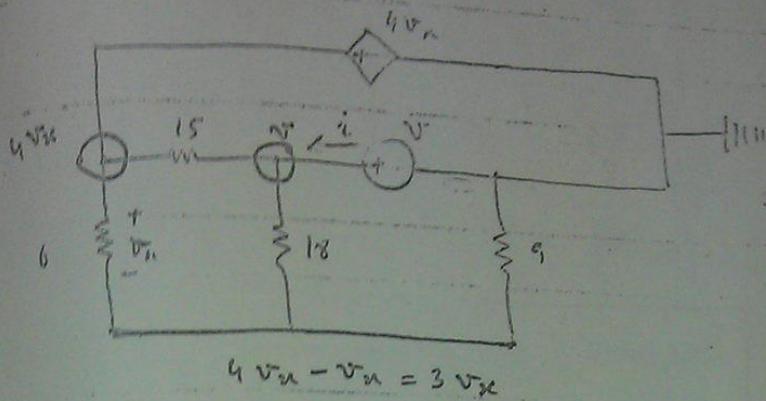at v :

$$i = \frac{v - 3v_n}{18} + \frac{v - 4v_n}{15}$$

$$270i = 15v - 45v_n + 18v - 72v_n$$

$$270i = 33v - 117v_n \quad \text{--- (1)}$$

at $(3v_n)$:

$$\frac{3v_n - 4v_n}{6} + \frac{3v_n - v}{18} + \frac{3v_n - 0}{9} = 0$$

$$(9v_n - 12v_n) + (3v_n - v) + 6v_n = 0$$

$$(-3v_n + 3v_n) - v + 6v_n = 0$$

$$\cancel{-v} + 6v_n - v = 0$$

$$6v_n - v = 0$$

$$v = 6v_n$$

$$v_n = \frac{v}{6}$$

put in (1)

$$270i = 33v - 117\left(\frac{v}{6}\right)$$

$$1620i = 198v - 117v = 81v$$


56

$$1620i = 81V$$


$$\frac{1620}{81} = \frac{V}{i}$$

$$20 = \frac{V}{i}$$

$R_{eq} = 20 \Omega$

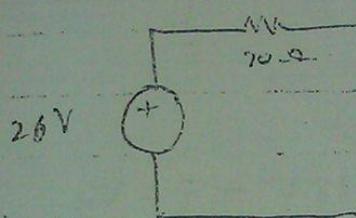

(a) $P_{6\Omega} = ?$

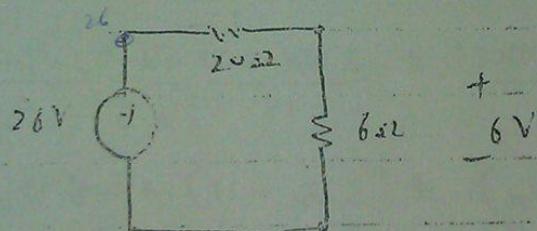

$$P_{6\Omega} = \frac{(6)^2}{6} = 6$$

$P_{6\Omega} = 6W$

(b) For max Power transfer

$$R_L = R_S$$

So 6Ω should be replaced by 20Ω

and the max power will be

57



$$P_{\max} = 8.45 \text{ W}$$

5:29

do yourself -

5:30

$$P_{\max} = ?$$

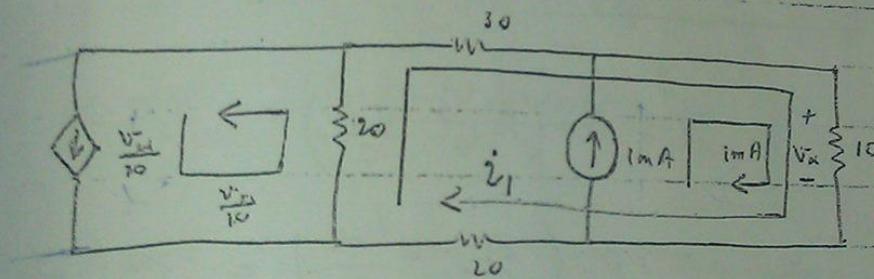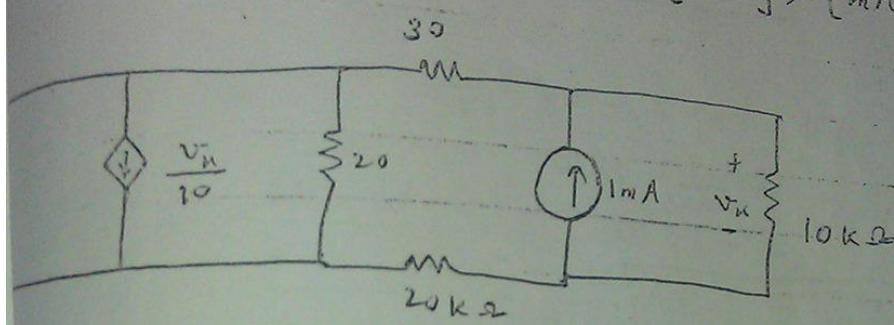 $[k_2], [mA], [V]$


loop I:

$$10(i_1 + i) + 20i_1 + 30i_1 + 20(i_1 + \frac{V_u}{10}) = 0$$

$$10i_1 + 10 + 50i_1 + 20i_1 + 2V_u = 0$$

$$80i_1 + 2V_u + 10 = 0$$

$$40i_1 + V_u + 5 = 0 \quad \text{--- (1)}$$

V_K:

$$V_K = 10(i_1 + i)$$

$$V_K = 10i_1 + 10 \quad \text{--- (2)}$$

put in (1)

$$40i_1 + 10i_1 + 10 + 5 = 0$$

53

$$i_1 = -\frac{15}{50} = -\frac{3}{10}$$

$$\boxed{i_1 = -\frac{3}{10} \text{ mA}}$$

$$v_u = 10 i_1 + 10$$

$$= 10 \left(-\frac{3}{10} \right) + 10$$

$$= -3 + 10$$


$$\boxed{v_u = 7 \text{ V}}$$


$$v_{oc} = v_{o.c} = 20 \left(i_1 + \frac{v_u}{10} \right)$$

$$= 20 \left(-\frac{3}{10} + \frac{7}{10} \right) = 20 \left(\frac{4}{10} \right)$$

$$\boxed{v_{oc} = 8 \text{ V}}$$

For Regs -

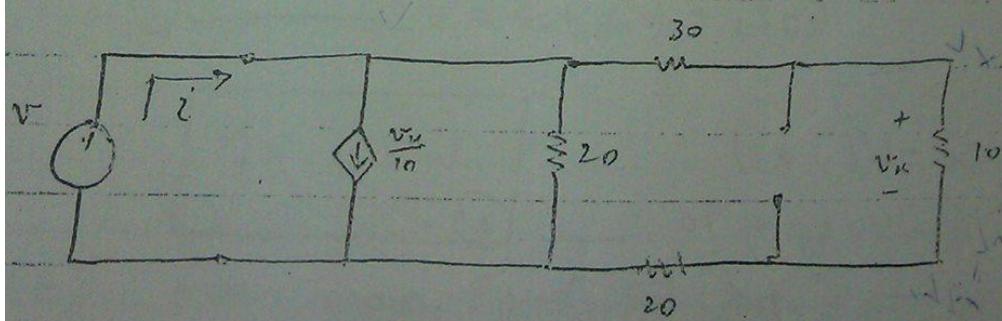

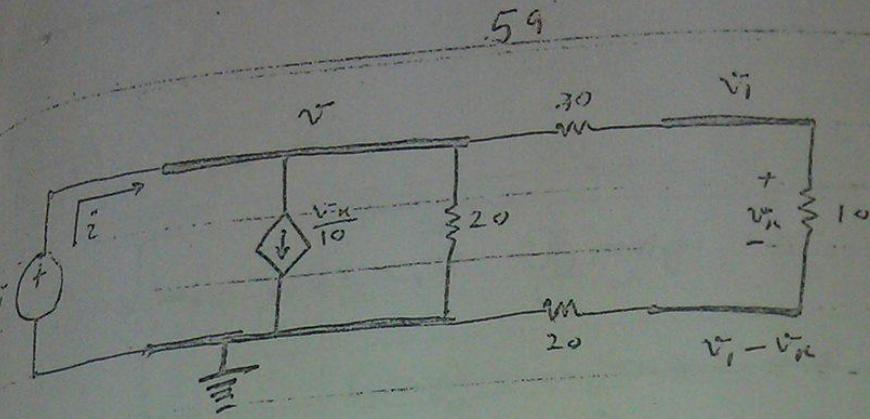

for v:

$$i = \frac{v_n}{10} + \frac{v - 0}{20} + \frac{v - v_1}{30}$$

$$60i = 6v_n + 3v + 2v - 2v_1$$

$$60i = 5v + 6v_n - 2v_1 \quad \text{--- (1)}$$

for v1:

$$\frac{v_1 - v}{30} + \frac{(v_1 - (v_1 - v_n))}{10} = 0$$

KHALID PHOTO STAT
U.E.T

$$v_1 - v + 3v_n = 0$$

$$v_1 - v + 3v_n = 0 \quad \text{--- (2)}$$

for $(v_1 - v_n)$:

$$\frac{(v_1 - v_n) - 0}{20} + \frac{(v_1 - v_n) - v_1}{10} = 0$$

$$\frac{v_1 - v_n}{20} + \frac{-v_1}{10} = 0$$

KHALID PHOTO ST.
U.E.T

$$v_1 - v_n - 2v_n = 0$$

$$v_1 - 3v_n = 0$$

(3)

60

from ③ $v_1 = 3v_n$ from ①


$$60i = 5v + 6v_n - 2(3v_n)$$

$$60i = 5v + 6v_n - 6v_n$$

$$60i = 5v$$

$$\frac{v}{i} = \frac{60}{5} = 12$$

Reg = $12\text{ k}\Omega$

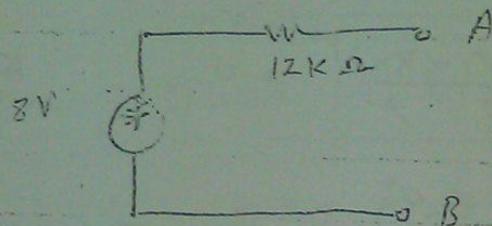

$$P_{max} = \frac{1}{4} \frac{V_s^2}{R_S} = \frac{(8)^2}{12} \times \frac{1}{4} = \frac{64}{12} \times \frac{1}{4}$$


$P_{max} = \frac{3}{2} \text{ mW}$

61


5.31

For this -

①

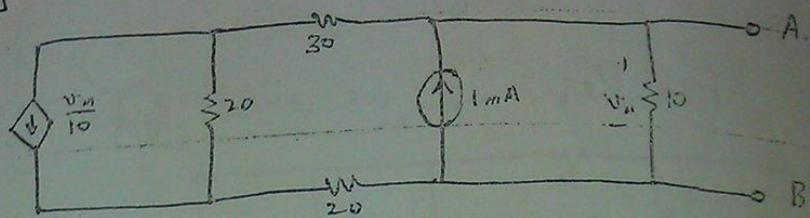For V_{OC}

By loop Method

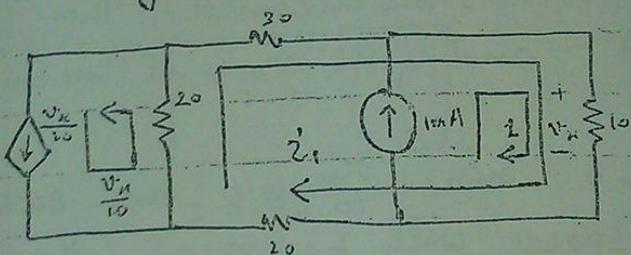By loop I & by V_u from 5.30 @ 1 Pst


$$i_1 = \frac{-3}{10} \text{ mA}$$

$$V_u = 7 \text{ V}$$

$$V_{OC} = V_u = 7 \text{ V}$$



$$V_{OC} = 7 \text{ V}$$

62

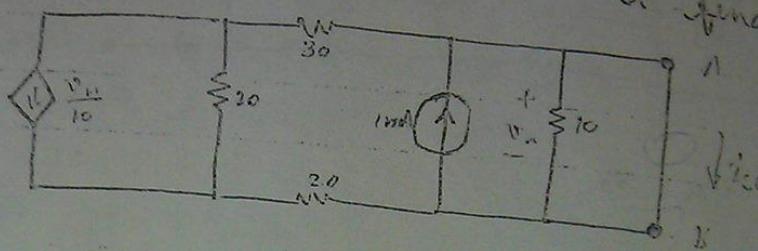For R_{eq} we will find i_{sc} 

when A B is short circuited then
 $i_{short} = 0 \text{ mA}$ and no v_x it means
 $v_x = 0$.

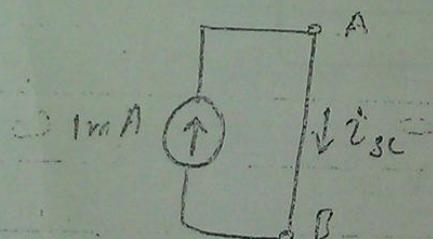
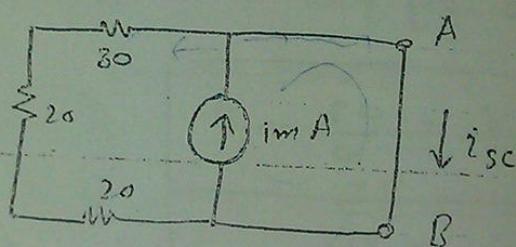
If $v_x = 0$ then $\frac{v_x}{10} = 0$ and current of dependent source will be zero. Then circuit will be




$$i_{sc} = 1 \text{ mA}$$

$$R_{eq} = \frac{v_{oc}}{i_{sc}} = \frac{7V}{1 \text{ mA}} = 7 \text{ k}\Omega$$

63

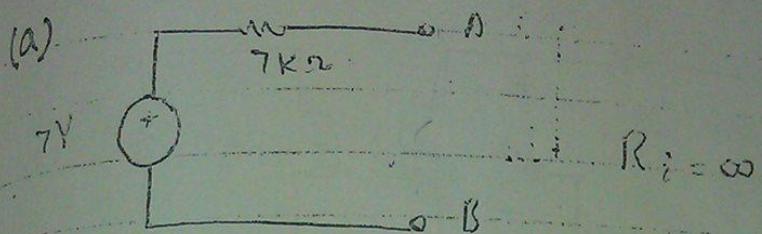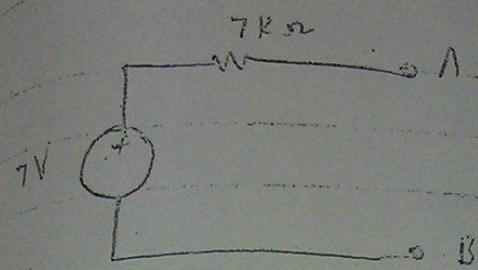

$$v_i = 7 \text{ V}$$

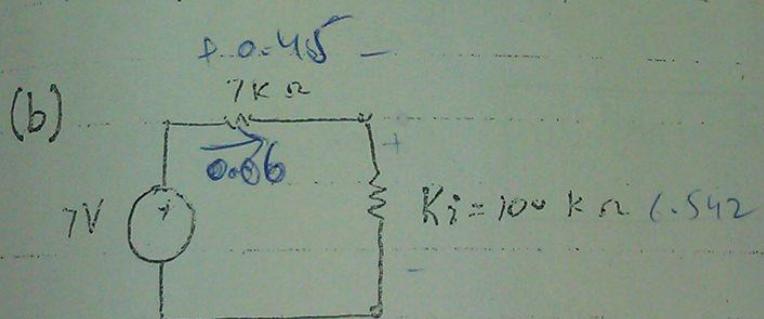


$$v_i = \frac{100}{107} \times 7 = 6.542$$

$$v_i = 6.542 \text{ V}$$

64

5.3 The Ideal Transformer :-

[5.32]

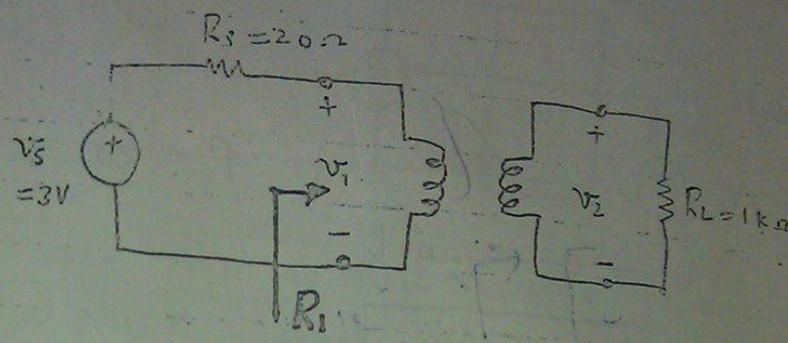

$$\begin{aligned}v_2 &= n v_1 \\i_2 &= i_1 / n \\R_2 &= n^2 R_1\end{aligned}$$

(a)

$$P = 100 \text{ mW}$$

given

$$R_1 = \frac{R_L}{n^2} = \frac{1k}{n^2}$$

$$R_{eq} = R_1 + R_s \quad (2)$$

$$\frac{P}{v} = \frac{(v_s)^2}{R_{eq}}$$

$$\frac{100 \text{ mW}}{(3V)^2} = \frac{1}{R_{eq}}$$

$$R_{eq} = \frac{9}{100m}$$

$$R_1 + R_s = \frac{9}{100m}$$

$$R_1 = \frac{9}{100m} - R_s$$

$$\frac{1k}{n^2} = \frac{9}{100m} - 20$$

65

KHALID PHOTO STATE

$$n^2 = 1K \times \left(\frac{100 \text{ m}}{9 - 2000 \text{ m}} \right)$$

$$= \frac{100}{9 - (2K) \text{ m}} = \frac{100}{9 - 2}$$

5.3

5.

$$n^2 = \frac{100}{7}$$

$$n = 3.779$$

KHALID PHOTO STATE
U.E.T

$$n = 3.8$$

(b) For more Power

For this $R_s = R_i$

$$R_s = \frac{R_i}{n^2}$$

$$20 \approx \frac{1K}{n^2}$$

$$n^2 = \frac{1000}{20} = \frac{100}{2}$$

KHALID PHOTO STATE
U.E.T

$$n = 7.07$$

$$n = 7$$

$$\begin{aligned} P &= 100 \text{ mW} \\ V_s &= 2 \\ P &= \frac{V_s^2}{R_{eq}} \\ P &= \frac{V_s^2}{R_1 + R_s} \end{aligned}$$



15.3 \uparrow [5.33]

$$\begin{aligned} R_1 &= \frac{R_L}{n^2} \\ R_1 &= 2.5 \Omega \\ V_s^2 &= P(R_1 + R_s) \\ V_s^2 &= 100 \times 10^{-3} (2.5 + 15) \\ V_s &= 15.8 \text{ V} \\ \text{do yourself...} \end{aligned}$$

$$\begin{aligned} \eta &= \frac{P_1}{R_s + R_1} \\ \eta &= \frac{2.5 \times 10^{-3}}{2.5 \times 10^{-3} + 15} \\ \eta &= 99.4\% \end{aligned}$$

Hint: Find R_1 as in [5.32] then
for (b) consult chapter 4 and use the formula
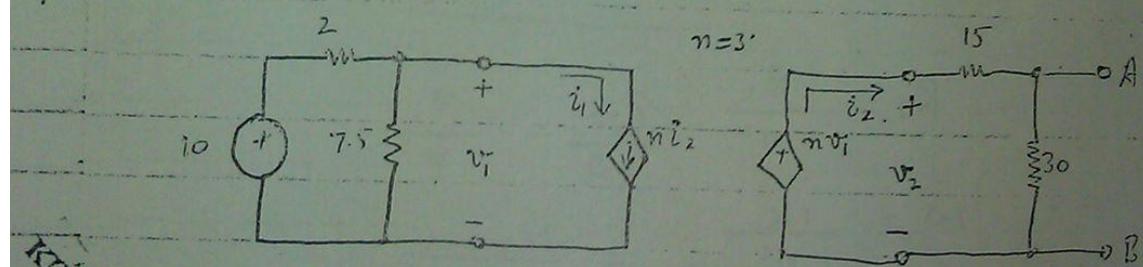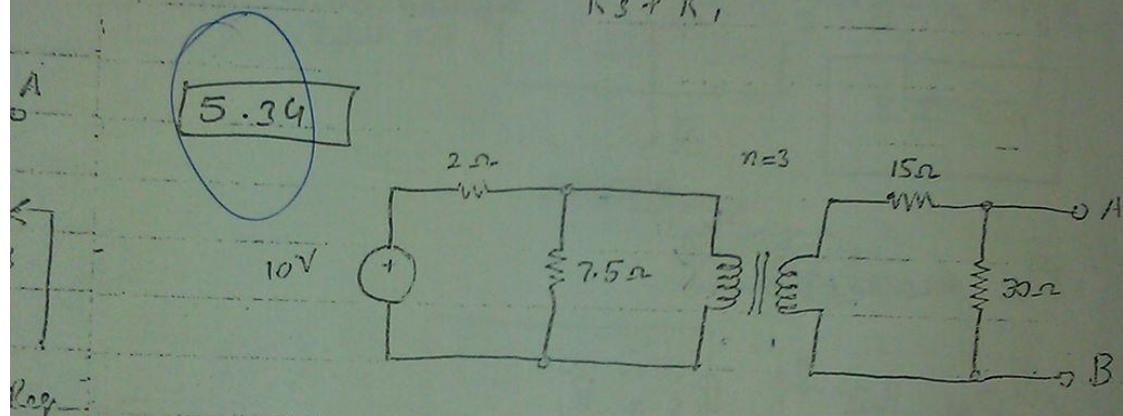
$$\eta = \frac{R_1}{R_s + R_1} \quad (\text{for voltage source})$$



$$V_1 = V_{7.5\Omega} = \frac{7.5}{2+7.5} \times 10 = 7.89$$

$V_1 = 7.9 \text{ V}$

$$V_2 = n V_1 = 3 (7.9) = 23.7 \text{ V}$$

REARED VECTOR STATE
U.E.T



6.7

$$V_{OC} = V_{AB} = V_{30\Omega} = \frac{30}{15+30} (23.7) = 15.8$$

5.

$$V_{OC} = 15.8 \text{ V}$$


For Req

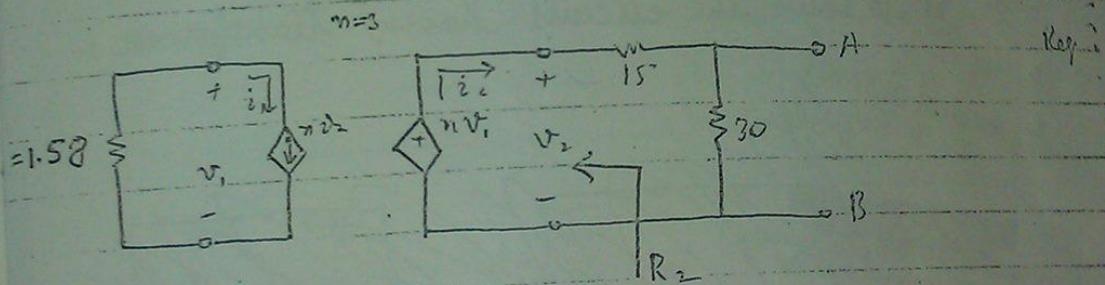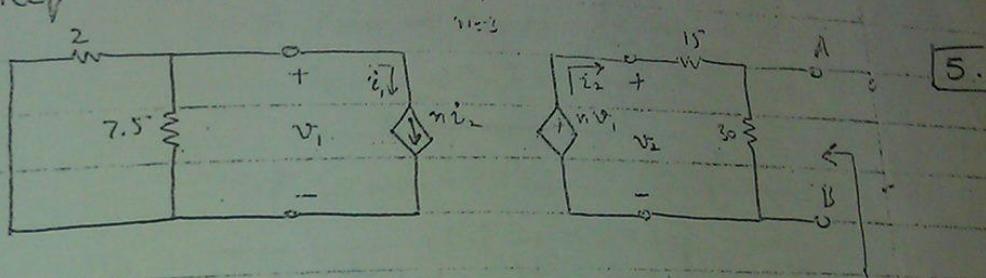


$$R_2 = n^2 R_1$$

$$= 9 (1.58) = 14.22$$

$$R_2 = 14.22 \Omega$$

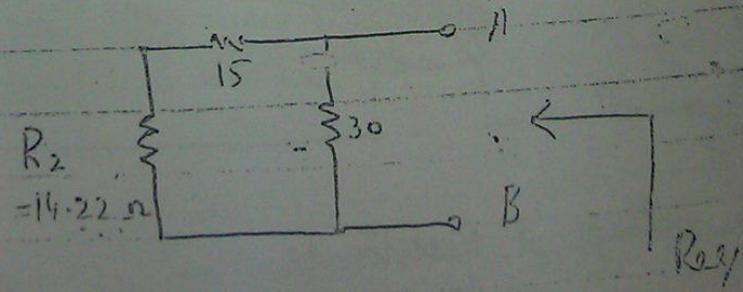


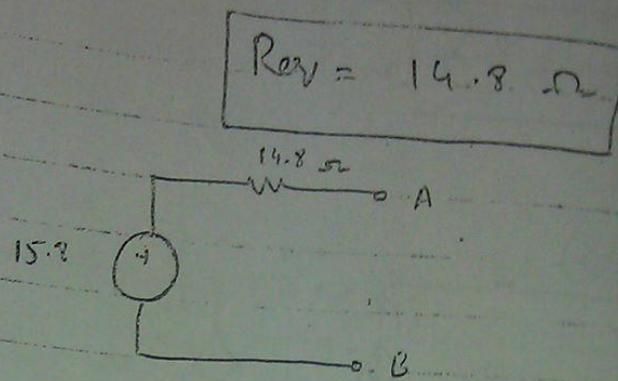


II:

Tips to solve the circuits having transformer:-

Consider,

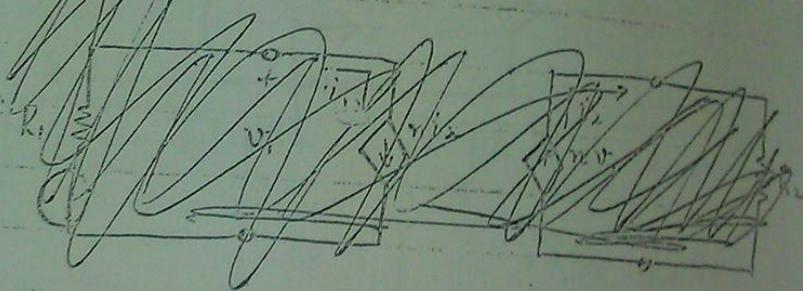

Consider,

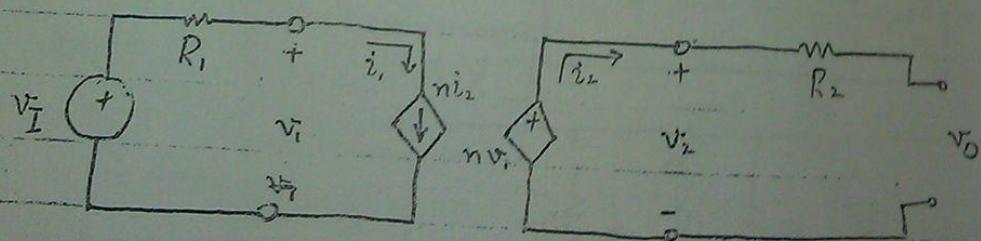

I: * For voltage & Resistance

* Prim. \rightarrow Second. \propto by n^{m^n}

69

* Second. \rightarrow Prim. \otimes by $n \omega^2$

$$\text{e.g. } V_1 = \frac{V_2}{n}$$

$$R_1 = \frac{R_2}{n^2}$$

II: * For current :

It is reversed $i_1 - i_2$

* Prim. \rightarrow Second. \otimes by n

$$\text{e.g. } i_2 = \frac{i_1}{n}$$

* Second. \rightarrow Prim. \otimes by n

$$\text{e.g. } i_1 = n i_2$$

KHALID PHOTO STATE
U.E.T

Composing And Photo Copy
Student Services Centre
U.E.T. LHR.


KHALID PHOTO STATE

Composing And Photo Copy
Student Services Centre
U.E.T. LHR.

KHALID PHOTO STA

70

5.35

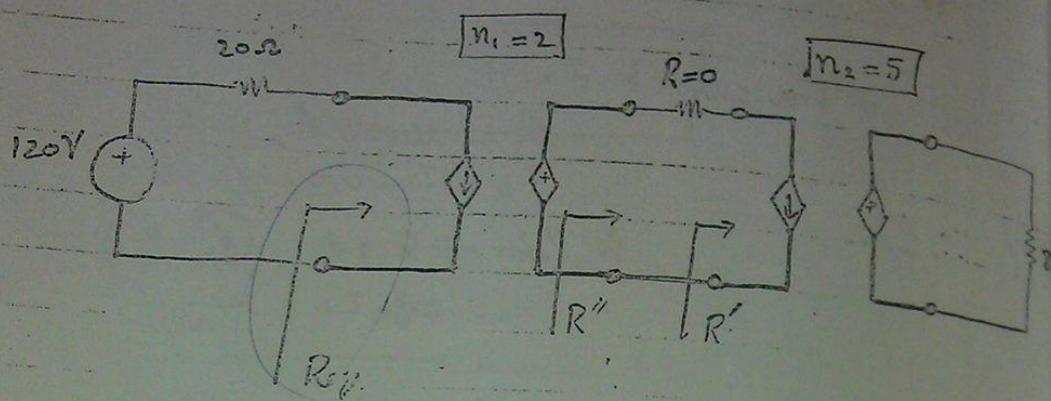

Find $R_{eq} = ?$

$$R' = \frac{8\text{ K}}{(n_2)^2} = \frac{8\text{ K}}{25} = 320$$


$R' = 320 \Omega$

$$R'' = R' + R = 320 + 0 = 320$$


$R'' = 320 \Omega$

$$R_{eq} = \frac{R''}{(n_1)^2} = \frac{320}{4} = 80$$

$R_{eq} = 80 \Omega$

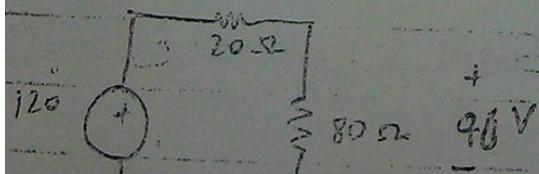

5.36

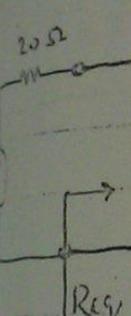

71

$$V_{80\text{ m}} = 96 \text{ V}$$

$$P_{80\text{ m}} = P_{80\text{ m}} = \frac{(96)^2}{80} = 115.2 \text{ mW} \quad \therefore R = 0$$


$$P_{80\text{ m}} = 115.2 \text{ mW}$$

\therefore No power is dissipated across $R=0\Omega$.
 If $R \neq 0\Omega$ then we will go reverse to find $V_{80\text{ m}}$ then we will find $P_{80\text{ m}}$.

5.36

 $n_1 = 2$

[912-5]

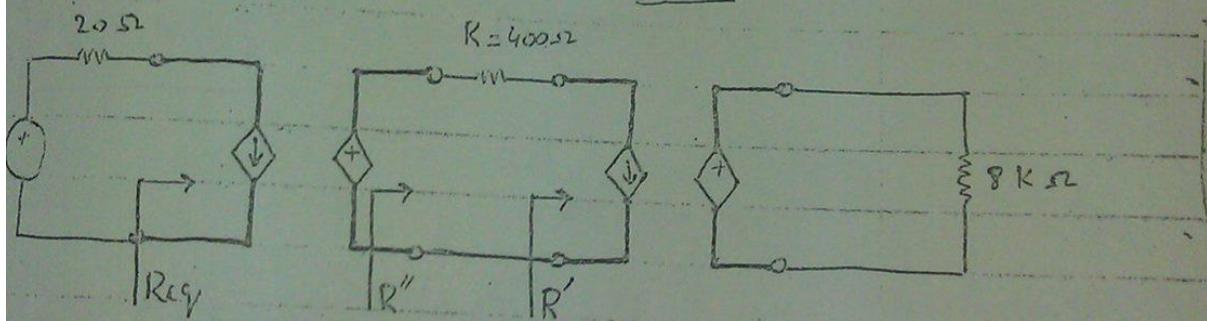

$$R' = \frac{8K}{(n_1)^2} = \frac{8000}{2^2} = 320 \Omega$$

$$R' = 320 \Omega$$

$$R'' = R' + R = 320 + 400 = 720 \Omega$$

$$R'' = 720 \Omega$$

$$R_{\text{Rev}} = \frac{R''}{(n_1)^2} = \frac{720}{4} = 180 \Omega$$


$$R_{\text{Rev}} = 180 \Omega$$

$$V_{\text{Rev}} = \frac{180}{20+180} \times 120 = 108 \text{ V}$$

$$V_{\text{Rev}} = 108 \text{ V}$$

For R_{eff} big (a)

min. 35%

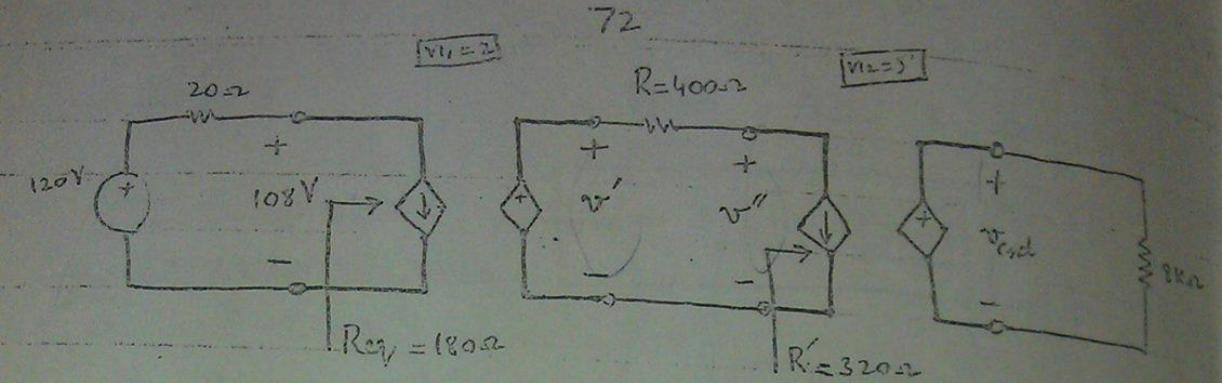

$$v' = (n_1)(108) = 2(108) = 216\text{V}$$

$$v'' = \frac{R'}{R+R'} v' = \frac{320}{400+320} \times 216 = 96\text{V}$$

$$v_{end} = (n_2)(v'') = 5(96) = 480\text{V}$$

$v' = 216\text{V}$
$v'' = 96\text{V}$
$v_{end} = 480\text{V}$

$$v_{8\text{k}\Omega} = v_{end} = 480\text{V}$$

$$P_{8\text{k}\Omega} = \frac{(v_{8\text{k}\Omega})^2}{R_{8\text{k}\Omega}} = \frac{(480)^2}{8\text{k}\Omega} = 28.8\text{mW}$$

$P_{8\text{k}\Omega} = 28.8\text{mW}$

~~74~~


74

$$n_1 = 5$$

$$R'_L = \frac{120}{(n_1)^2} = \frac{120}{25} = 4.8 \Omega$$

$$R''_L = R_L + R' = 180 + 4.8 = 184.8 \Omega$$

(b)

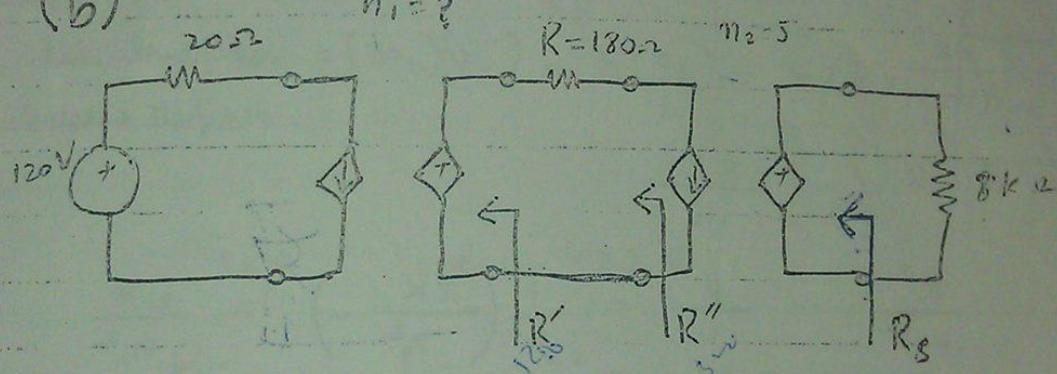

For max power transfer

$$R_S = R_L$$

$$R_S = 8\text{k}\Omega \quad \text{--- (1)}$$

$$R' = (n_1)^2 20$$

$$R'' = R_L + R' = 180 + 20n_1^2$$


$$R_S = (n_2)^2 R'' = (25)(180 + 20n_1^2)$$

Note:-


The answer of part(b) is wrong in the book as some power is also dissipated by $R = 180 \Omega$. but we want to transfer maximum p. to $8k\Omega$.


For this first find thevenin equivalent at $8k\Omega$ then find max power transfer to 8Ω .

5.38 (a)

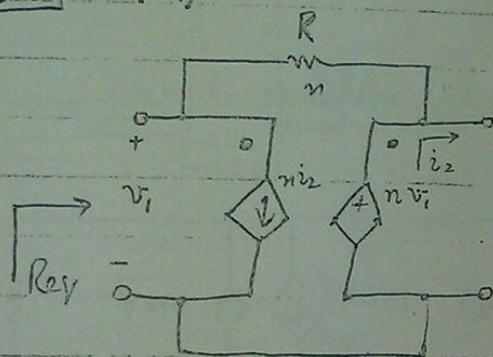

By 2nd Method

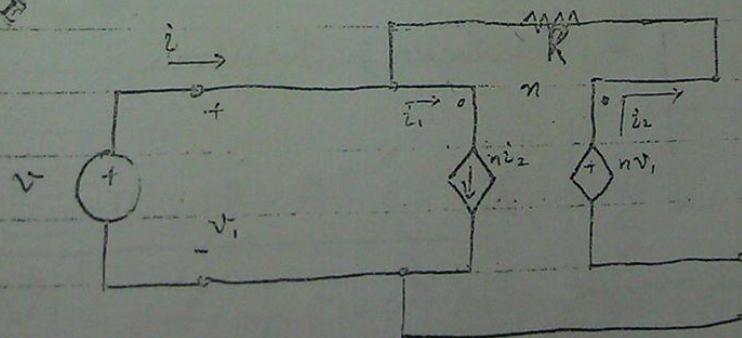

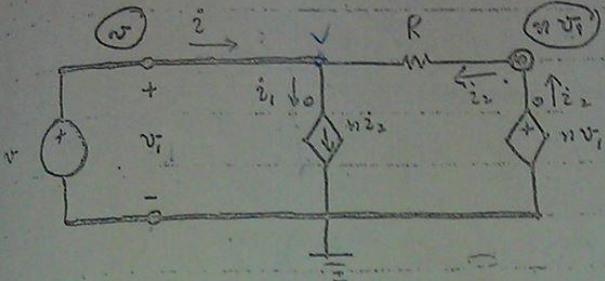

$$nv_1 - 0 = nv_1$$

Fig (a)

at v.s

$$i = i_1 + \frac{v - nv_1}{R}$$

$$i = ni_2 + \frac{v - nv_1}{R} \quad (1)$$

v1:

$$v_1 = v \quad \text{put in } (1)$$

$$i = ni_2 + \frac{v - nv}{R}$$

$$i = ni_2 + \frac{1-n}{R} v \quad (3)$$

i2:

$$i_2 = \frac{nv_1 - v}{R}$$

from (2)

$$i_2 = \frac{nv - v}{R} = \frac{n-1}{R} v$$

$$i_2 = \frac{n-1}{R} v$$

$$\boxed{i_2 = \frac{n-1}{R} v} \quad (4) \quad \text{put in } (3)$$

TANVIR
Composing And Photo C
Student Services Cent

$$i = n \left(\frac{n-1}{R} v \right) + \left(\frac{1-n}{R} v \right)$$

$$= \frac{v}{R} [n(n-1) + (1-n)]$$

$$= \frac{v}{R} (n^2 - n + 1 - n)$$


$$i = \frac{v}{R} (n^2 - 2n + 1)$$

$$\frac{v}{i} = \frac{R}{(n^2 - 2n + 1)}$$

$$R_{eq} = \frac{R}{(n-1)^2}$$

(b)

from fig (a)

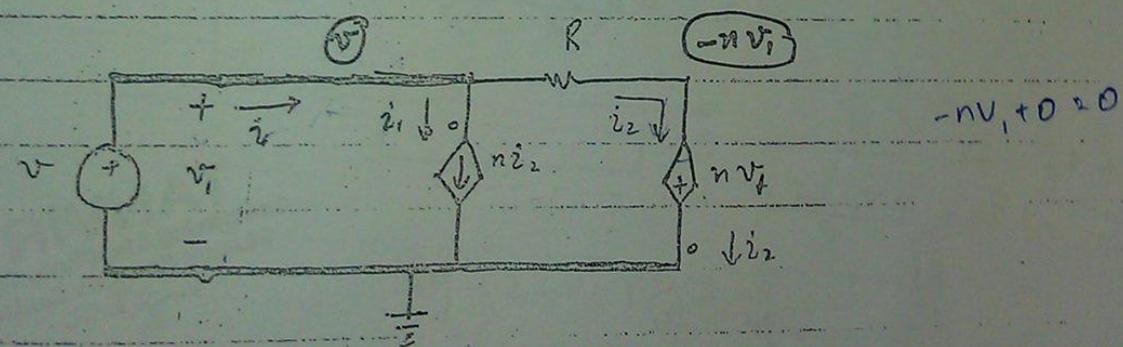

$$v_1 = v \quad \text{--- (1)}$$

at v :

$$i = n i_2 + \frac{v - (-nV_1)}{R}$$

beam (1)

79

$$i = n i_2 + \left(\frac{1+n}{R}\right) v \quad \textcircled{1}$$

i₂:

$$i_2 = \frac{v - (-n v_1)}{R}$$

$$i_2 = \frac{v + nv}{R}$$

\textcircled{2} from \textcircled{1} $v_1 = v$

~~at v~~

$$i = \frac{v + nv}{R}$$

~~at v~~

from \textcircled{3} put in \textcircled{2}

$$i = n \left(\frac{v + nv}{R} \right) + \left(\frac{(1+n)v}{R} \right)$$

$$= \frac{v}{R} (n(1+n) + (1+n))$$


$$i = \frac{v}{R} (n^2 + 2n + 1)$$

$$\frac{v}{i} = \frac{R}{(n+1)^2}$$

80

[5.39]

$$P_{loss} = ?$$

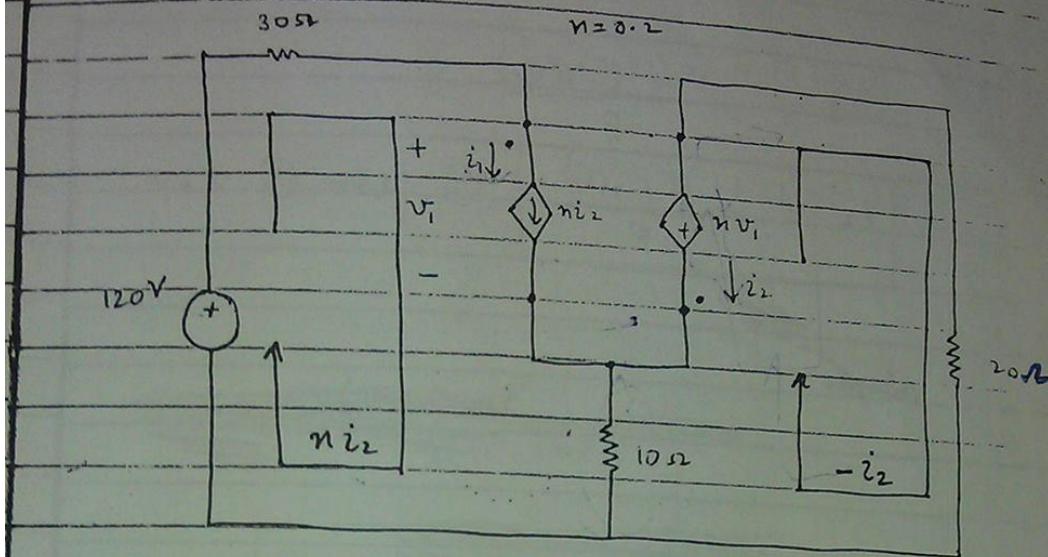

loop I:

$$120 = 30n i_2 + v_1 + 10(n i_2 + i_2) \quad \cancel{\text{---}}$$

$$120 = 30n i_2 + v_1 + 10(n+1)i_2$$

put $n = 0.2$ (given)

$$120 = 6i_2 + v_1 + 12i_2$$

$$120 = 18i_2 + v_1$$

$$v_1 + 18i_2 = 120 \quad \text{--- (1)}$$

loop II:

$$n v_1 + 20(-i_2) + 10(-i_2 - n i_2) = 0$$

$$n v_1 - 20i_2 - 10i_2(1+n) = 0$$


put $n = 0.2$

$$0.2v_1 - 20i_2 - 12i_2 = 0$$

82

15.4

$n = 0.2$

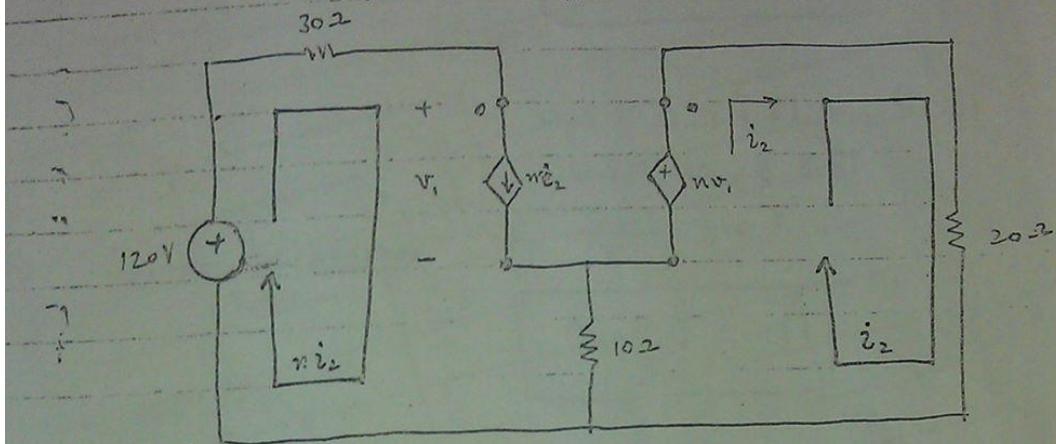

loop I:

$$120 = 30ni_2 + v_1 + 10(ni_2 - i_2) \rightarrow$$

$$120 = 6i_2 + v_1 - 8i_2$$

$$120 = v_1 - 2i_2$$

$$v_1 - 2i_2 = 120 \quad \text{--- (1)}$$

loop II:

$$nv_1 = 20i_2 + 10(i_2 - ni_2)$$


$$0.2v_1 = 20i_2 + 8i_2$$

$$0.2v_1 = 28i_2$$

$$v_1 = \frac{28i_2}{0.2}$$

$$v_1 = 140i_2 \quad \text{--- (2)}$$

5.41

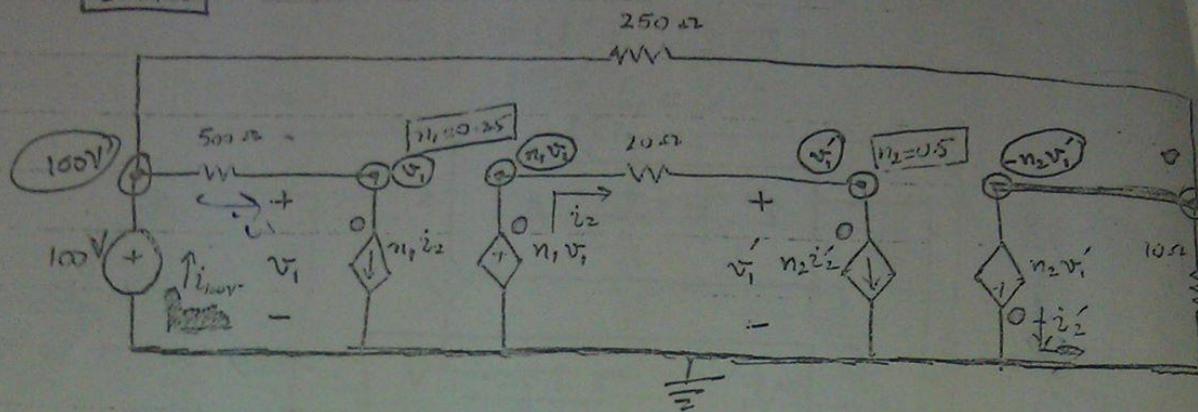at v_i :

$$\frac{v_i - 100}{500} + n_1 i_2 = 0$$

$$v_i - 100 + (500)(0.25) i_2 = 0$$

$$v_i + 125 i_2 = 100 \quad \textcircled{1}$$

at v'_i :

$$\frac{v'_i - n_1 v_i}{20} + n_2 i'_2 = 0$$

$$v'_i - n_1 v_i + 20 n_2 i'_2 = 0$$

$$v'_i - 0.25 v_i + 10 i'_2 = 0 \quad \textcircled{2}$$

~~at v_i~~ $v = (2v_i)$ at $n_1 v_i$:

$$i_2 = \frac{n_1 v_i - v'_i}{20}$$

$$20 i_2 = n_1 v_i - v'_i$$

$$20 i_2 = 0.25 v_i - v'_i \quad \textcircled{3}$$

KHALID PHOTO STATE
U.E.T

85

$$at \Rightarrow n_2 v_i' =$$

$$0 = i_2' + \frac{-n_2 v_i' - 100}{250} + \frac{-n_2 v_i' - 0}{10}$$

5

$$0 = 250 i_2' - n_2 v_i' - 100 - 25 n_2 v_i'$$

$$0 = 250 i_2' - 0.5 v_i' - 100 - 12.5 v_i'$$

$$250 i_2' - 13 v_i' = 100$$

100V

100V

$$v_i = \frac{50800}{933} V$$

$$v_i' = \frac{5900}{933} V$$

$$i_2 = \frac{340}{933} A$$

$$i_2' = \frac{680}{933} A$$

$$i_2' = \frac{n_2 v_i'}{10} + \frac{n_2 v_i - 100}{250}$$

$$250 i_2' = 25 n_2 v_i + n_2 v_i' - 100$$

$$250 i_2' = 12.5 v_i' + 0.5 v_i - 100$$

$$n_2 i_2 = \frac{85}{933} A$$

$$n_2 i_2' = \frac{340}{933} A$$

$$n_2 v_i = \frac{12700}{933} V$$

$$n_2 v_i' = \frac{2950}{933} V$$

KHALID PHOTO STATE
U.E.T

$$v_{250,22} = (100 + n_2 v_i') = \frac{96250}{933} V \quad P_{250,22} = \frac{(100 - (-n_2 v_i'))}{Power} = 42.57 W$$

$$v_{500,22} = (100 - v_i) = \frac{42500}{933} V \quad P_{500,22} = 4.15 W$$

$$v_{20,22} = (n_2 v_i - v_i') = \frac{6800}{933} V \quad P_{20,22} = 2.66 W$$

$$v_{10,22} = 0 - (-n_2 v_i') = \frac{2950}{933} V \quad P_{10,22} = 1 W$$

~~we want to find power supplied by Port~~

KHALED PHOTOSTATE
U.E.T.

~~$$\begin{aligned}
 & P_{100V} = (5.25) \frac{5.25}{933} = 0.285 \text{ W} \\
 & P_{100V} = (100) \frac{85}{933} = 8.11 \text{ W}
 \end{aligned}$$~~

For P_{100V} find $i_{100V} = ?$

~~$$i_{100V} = i_2 + i_{100V} = n_1 i_2 + n_2 i'_2 + i'_2$$~~

$$\begin{aligned}
 i_{100V} &= n_1 i_2 + n_2 i'_2 + i'_2 - i_2 - i_{100V} \\
 &= \frac{85}{933} + \frac{340}{933} + \frac{680}{933} - \frac{340}{933} - \frac{295}{933} \\
 &= \frac{85 + 340 + 680 - 340 - 295}{933}
 \end{aligned}$$

$$= \frac{85 + 340 + 680 - 340 - 295}{933}$$

$$i_{100V} = \frac{470}{933} \text{ A}$$


$$P_{100V} = 100 \times \frac{470}{933} = 50.375 \text{ W}$$

$$P_{100V} = 50.375 \text{ W}$$

* Power is conserved


5.4 Amplifiers

5.42

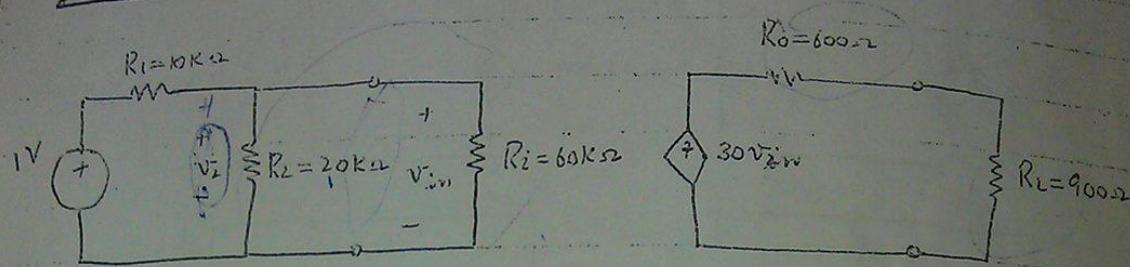

$$V_2 = \frac{R_2}{R_i + R_2} \times (1) = \frac{20}{10+20} \times (1) = \frac{2}{3} \text{V}$$

$$V_2 = \frac{2}{3} \text{V}$$

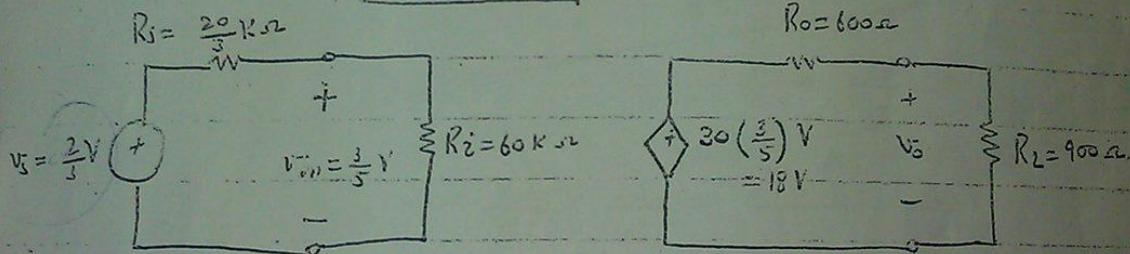


$$V_o = V_L = \frac{900}{600+900} \times 18 \text{V} = 10.8 \text{V}$$

$$V_L = 10.8 \text{V}$$


It can be verified
by gain formula also

88

[5.43]

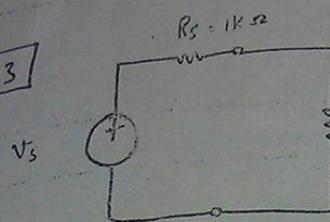
 i_{in}

$R_{in} = 200 \Omega$

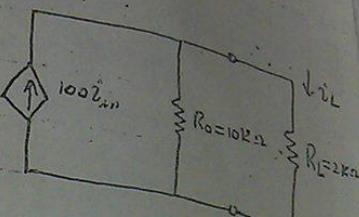


[5.44]

$i_s = \frac{V_s}{1k}$

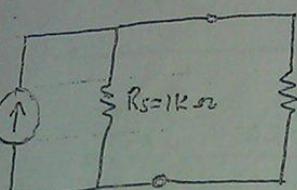

$R_{in} = 200 \Omega$

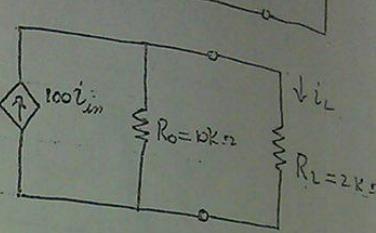

(a)

we want to find

$\frac{v_L}{v_s} = ?$

$\frac{v_L}{v_s} = \frac{i_L R_L}{i_s R_s} = \frac{i_L}{i_s} \times \frac{2k}{1k}$

$$\boxed{\frac{v_L}{v_s} = 2 \frac{i_L}{i_s}} \quad \text{--- (1)}$$

Now apply the formula for current amplifier -


$$\frac{i_L}{i_s} = \frac{R_s}{R_{in} + R_s} A_{sc} \frac{R_o}{R_o + R_L}$$

$$= \frac{1k}{200 + 1k} (100) \frac{10k}{10k + 2k}$$

$$\frac{i_L}{i_s} = \frac{62.5}{9} \quad \text{put in (1)}$$


$$\boxed{\frac{v_L}{v_s} = \frac{1250}{9}}$$

44

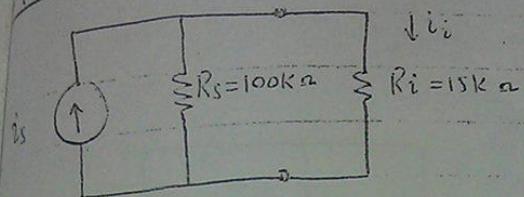

i_s

$R_i = 15k\Omega$

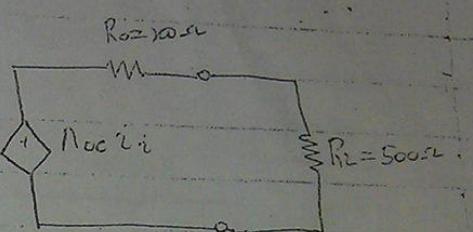

5

i_s

$R_s = 2k\Omega$

$$\frac{V_L}{i_s} = \frac{R_s}{R_s + R_i} A_{oc} \frac{R_L}{R_L + R_o}$$

$$(a) \quad \frac{V_L}{i_s} = \frac{100K}{100K + 15K} (1000) \frac{500}{500 + 100}$$

$$= \frac{100}{115} (1000) \frac{500}{600}$$

$$\boxed{\frac{V_L}{i_s} = \frac{500000}{69} \frac{V}{A}}$$

(b)


$$\frac{V_L}{i_s} = 1000 \frac{V}{A} \quad \text{but in (1)} \quad A_{oc} = ?$$

$$1000 = \frac{100K}{100K + 15K} A_{oc} \frac{500}{500 + 100}$$

$$1000 \times \frac{115}{100} \times \frac{600}{500} = A_{oc}$$

$$1380 = A_{oc}$$

$$\boxed{A_{oc} = 1380 \frac{V}{A}}$$

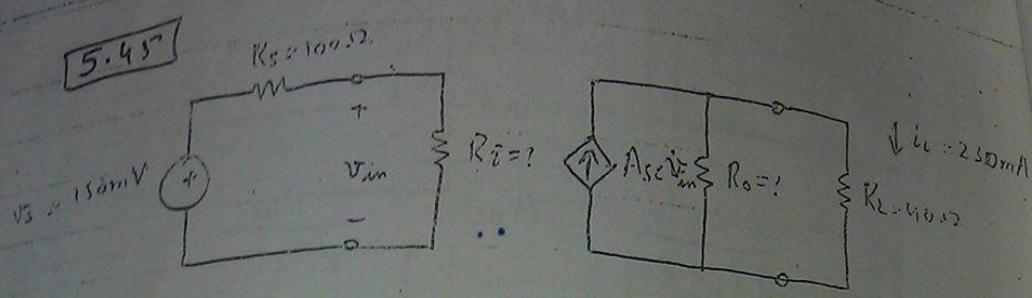

$$\therefore \text{If } R_L = 60\text{ }\Omega, i_L = 2.20\text{ mA}$$

Find R_i, A_{sc}, R_o

We know that

base

$$\frac{i_L}{V_s} = \frac{R_i}{R_i + R_s} A_{sc} \frac{R_o}{R_o + R_L} \quad \text{--- (1)}$$

Case I: $V_s = 150\text{mV}, i_L = 230\text{mA}$
 $R_L = 60\text{ }\Omega, R_s = 100\text{ }\Omega$

$$\frac{230\text{mA}}{150\text{mV}} = \frac{R_i}{R_i + 100} A_{sc} \frac{R_o}{R_o + 60}$$

$$23(R_i + 100)(R_o + 60) = 15 R_i R_o A_{sc} \quad \text{--- (2)}$$

Case II:

$$V_s = 150\text{mV}, i_L = 220\text{mA}$$

$$R_L = 60\text{ }\Omega, R_s = 100\text{ }\Omega$$

$$\frac{220\text{mA}}{150\text{mV}} = \frac{R_i}{R_i + 100} A_{sc} \frac{R_o}{R_o + 60}$$

$$22(R_i + 100)(R_o + 60) = R_i R_o A_{sc} 15 \quad \text{--- (3)}$$

KHALID PHOTO STATE
U.E.T


91

$$\text{eqn III: } V_{in} = \frac{R_o}{R_i + R_s} 150 \text{ mV}$$

$$V_{in} = \frac{R_i}{R_i + 100} 150 \text{ mV}$$

[5]

v₃ = 11

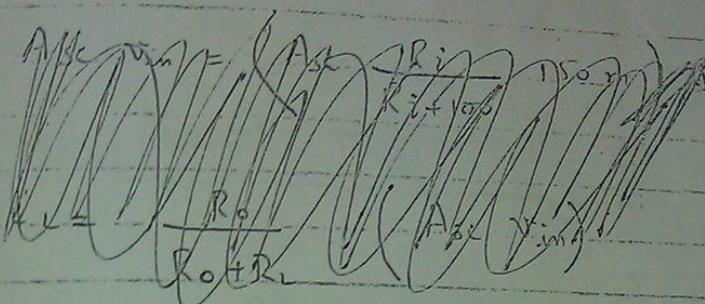

$$V_{in} = 125 \text{ mV} \quad (\text{given}) \quad \text{put in above}$$

$$+2FADV = \frac{R_i}{R_i + 100} 150 \text{ mV}$$

$$5(R_i + 100) = 6R_i$$

$$5R_i + 500 = 6R_i$$

$$500 = R_i$$

$$R_i = 500 \Omega \quad (4)$$

KHALID PHOTO STATE
U.E.T

Solving (2), (3) & (4)

Put $R_i = 500 \Omega$ in (4)

$$23(600)(R_o + 40) = 7500 R_o \text{ Ase}$$

$$13800 R_o + 552000 = 7500 R_o \text{ Ase}$$

$$138 R_o + 5520 = 75 \text{ Ase } R_o \quad (5)$$

$$22(600)(R_o + 60) = 7500 R_o \text{ Ase}$$

92


Solving ⑤ & ⑥

$$R_o = 400 \Omega$$

$$R_i = 500 \Omega$$

$$A_{sc} = \frac{253}{125} \frac{A}{V}$$

[5.46]

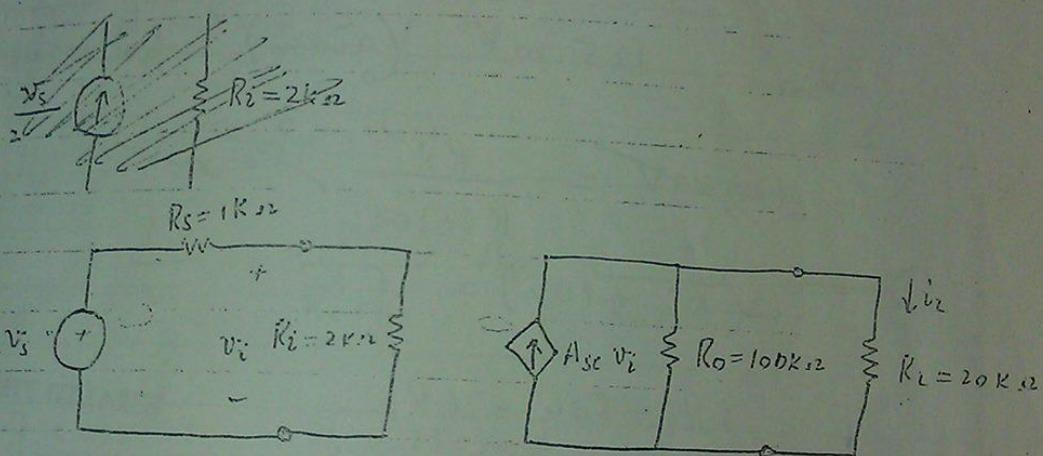

$$A_{sc} = 9 m \frac{A}{V}$$

We wanna find $\frac{V_L}{V_s} = ?$

$$\frac{V_L}{V_s} = \frac{i_L R_L}{V_s} = R_L \frac{i_L}{V_s} \quad \text{--- (1)}$$

Now apply the formula

$$\frac{i_L}{V_s} = \frac{R_o}{R_i + R_s} \cdot A_{sc} \frac{R_o}{R_o + R_i}$$

93

putting the values.

$$\frac{i_L}{v_s} = \frac{2K}{(2+1)K} = \frac{2}{3}$$


$$= \frac{2}{3} \cdot 9m = \frac{18}{6} = 3m$$

$$\frac{i_L}{v_s} = 5m \quad \text{put in } ①$$

$$\frac{v_L}{v_s} = (20\text{ k}\Omega) (5m)$$

$\frac{v_L}{v_s} = 100 \frac{V}{V}$

5.47

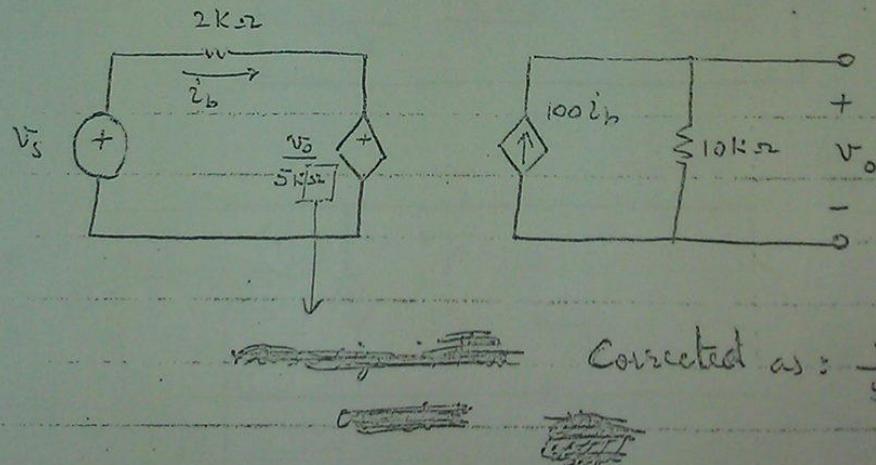In part 1 consider the loop containing i_b - $\boxed{\square}$

$$v_s = 2K \cdot i_b + \frac{v_o}{5K} \quad \text{--- } ①$$

In part 2:

$$v_o = (100i_b) (10\text{ k}\Omega) = 1000K i_b \quad \text{--- } ②$$

94

from ②

$$i_b = \frac{V_o}{1000 \text{ K} \Omega} \quad \text{put in } ①$$


$$v_s = \cancel{K} \cancel{\chi} \frac{V_o}{\cancel{1000} \cancel{K} \cancel{\chi}} + \frac{V_o}{5 \text{ K}}$$

$$= V_o \left(\frac{1}{500} + \frac{1}{5000} \right)$$

$$v_s = V_o \left(\frac{11}{5000} \right)$$

$$\boxed{\frac{V_o}{v_s} = \frac{5000}{11} \frac{V}{V}}$$

5.48

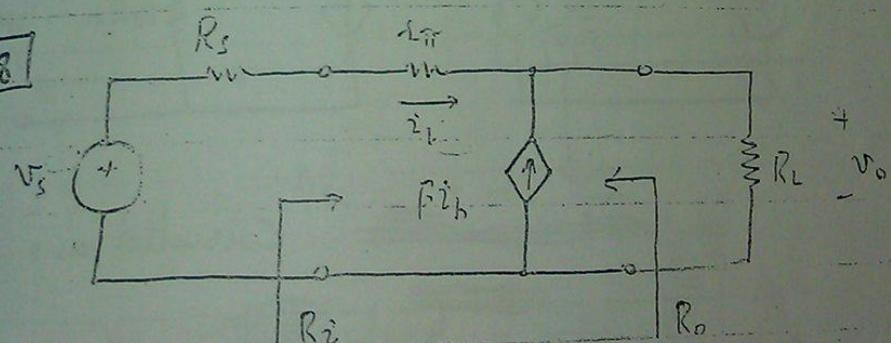

For $\frac{V_o}{v_s} = ?$

By Loop Method

$$i_L \boxed{\beta i_b}$$

$$v_o = R_L (i_b + \beta i_b)$$

$$i_{b,1} = \frac{V_o}{R_L (\beta + 1)} \quad \text{--- } ①$$

95


$$V_s = i_b R_s + i_b R_{\pi} + V_o$$

$$\approx \frac{V_o}{K_L(\beta+1)} R_s + \frac{V_o}{R_L(\beta+1)} R_{\pi} + V_o$$

$$\approx V_o \left[\frac{R_s}{R_L(\beta+1)} + \frac{R_{\pi}}{R_L(\beta+1)} + 1 \right]$$

$$V_s = V_o \left[\frac{R_s + R_{\pi} + R_L + \beta R_L}{R_L(\beta+1)} \right]$$
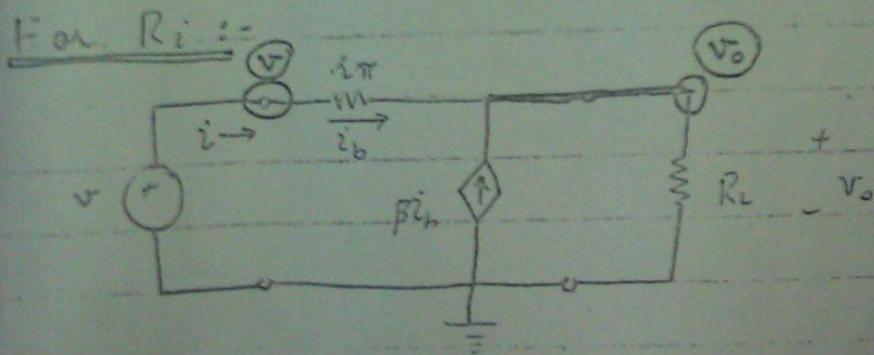
$$\frac{V_o}{V_s} = \frac{R_L(\beta+1)}{R_s + K_L + R_{\pi} + K_L \beta}$$



∴ as we can see $i = i_b$ — (a)
so

at v :

$$i = i_b = \frac{v - V_o}{R_{\pi}}$$

$$i_b = v - V_o$$

96

at v_o :

$$i_b + \beta i_b = \frac{v_o - o}{R_L}$$

$$\boxed{v_o = R_L (i_b + \beta i_b)} \quad \text{--- (2)}$$

from (2) put in (1)

$$i_b = \frac{v - R_L (i_b + \beta i_b)}{r_{\pi}}$$

$$i_b = \frac{v}{r_{\pi}} - \frac{R_L i_b (1 + \beta)}{r_{\pi}}$$

$$\frac{v}{r_{\pi}} = i_b + r_L \left(\frac{R_L (1 + \beta)}{r_{\pi}} \right)$$

$$\approx i_b \left(1 + \frac{R_L (1 + \beta)}{r_{\pi}} \right)$$

$$\frac{v}{r_{\pi}} = i_b \frac{r_{\pi} + R_L (1 + \beta)}{r_{\pi}}$$

$$\frac{v}{i_b} = r_{\pi} + R_L (1 + \beta)$$

$$\therefore i_b = i$$

$$R_i = \frac{v}{i} = r_{\pi} + R_L (1 + \beta)$$