

n. 1: Capacitance:

7.1)

$$C = ?$$

$$d = 0.1 \times 10^{-3} \text{ m}$$

$$S = 1 \text{ in} \times 1 \text{ in}$$

$$S = (2.54 \times 10^{-2} \times 2.54 \times 10^{-2}) \text{ m}^2$$

$$S = 6.45 \times 10^{-4} \text{ m}^2$$

$$\epsilon_r = 1$$

$$\epsilon_r = \epsilon / \epsilon_0$$

$$\epsilon = \epsilon_r \epsilon_0$$

$$= 1 \cdot \frac{1}{36\pi}$$

$$\epsilon = 8.8 \times 10^{-12}$$

Now,

$$C = \frac{\epsilon S}{d}$$

$$C = 8.8 \times 10^{-12} \cdot \frac{6.45 \times 10^{-4}}{0.1 \times 10^{-3}}$$

$$C = 5.67 \times 10^{-12} \text{ F}$$

$$C = 56.7 \text{ PF}$$

7.2) $C = ?$

$$S = 2 \text{ mm} \times 2 \text{ in}$$

$$S = 2 \times 10^{-3} \times 2 \times 2.54 \times 10^{-2}$$

$$S = 1.016 \times 10^{-4} \text{ m}^2$$

$$\epsilon_r = 5$$

$$\epsilon = \epsilon_r \epsilon_0$$

$$\epsilon = 5 \times \frac{10^{-9}}{36\pi}$$

$$\epsilon = 4.4 \times 10^{-11}$$

$$C = \epsilon \frac{s}{d}$$

$$C = 4.4 \times 10^{-11} \times \frac{1.016 \times 10^{-4}}{1 \times 10^{-3}}$$

$$C = 4.4 \text{ PF}$$

$$\underline{\text{Q7.3})^a} \quad S = ?$$

$$C = 1 \times 10^{-6} \text{ F}$$

$$d = 1 \times 10^{-3} \text{ m}$$

$$\epsilon_r = 7500$$

$$\begin{aligned} \epsilon &= \epsilon_r \times \epsilon_0 \\ &= 7500 \times \frac{10^{-9}}{36\pi} \end{aligned}$$

$$\epsilon = 6.6 \times 10^{-8}$$

$$\text{As } S = l \times l = l^2$$

so,

$$C = \epsilon \frac{s}{d}$$

$$C = \epsilon \frac{l^2}{d}$$

$$l^2 = 0.015 \text{ m}^2$$

$$l = 0.123 \text{ m}$$

$$l = 4.84 \text{ inch}$$

b)

$$C = 1F$$

$$l^2 = \frac{cd}{\epsilon}$$

$$l^2 = \frac{1 \times 1 \times 10^{-3}}{6.6 \times 10^{-8}}$$

$$l^2 = 1.51 \times 10^4$$

$$l = 12.3 \text{ m}$$

Q7.4)

a) parallel combination

$$C_1 = 0.2 \mu F$$

$$C_2 = 0.6 \mu F$$

$$C_{eq} = C_1 + C_2$$

$$C_{eq} = 0.8 \mu F$$

$$V = 10V$$

$$q = ?$$

$$w = ?$$

$$q = CV$$

$$\text{Energy} = \frac{1}{2} CV^2 \text{ or } \frac{q^2}{2C}$$

$$W = \frac{q^2}{2C}$$

$$W = \frac{(8 \times 10^{-6})^2}{2 \times 0.8 \times 10^{-6}}$$

$$W = 4 \times 10^{-5} \text{ J}$$

Series Combination

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$= \frac{0.2 \times 10^{-6} \times 0.6 \times 10^{-6}}{0.2 \times 10^{-6} + 0.6 \times 10^{-6}}$$

$$C_{eq} = 1.5 \times 10^{-7}$$

$$V = C_{eq} V$$

$$V = 1.5 \times 10^{-7} \times 10$$

$$V = 1.5 \mu\text{C}$$

$$W = \frac{V^2}{2C}$$

$$W = \frac{(1.5 \times 10^{-6})^2}{2 \times 1.5 \times 10^{-7}}$$

$$W = 7.5 \times 10^{-6} \text{ J}$$

5) a)

$$C_{eq} = C_1 + \frac{CC_1}{C+C_1}$$

$$C_{eq} = \frac{(C+C_1)C_1 + CC_1}{C+C_1}$$

$$C(C+C_1) = CC_1 + C_1^2 + CC_1$$


$$C^2 + CC_1 = C_1^2 + 2CC_1$$

$$C^2 - CC_1 - C_1^2 = 0$$

$$C = \frac{C_1 \pm \sqrt{C_1^2 + 4C_1^2}}{2}$$

$$C = \frac{C_1 \pm C_1\sqrt{5}}{2}$$

$$C = \frac{C_1(1 \pm \sqrt{5})}{2}$$

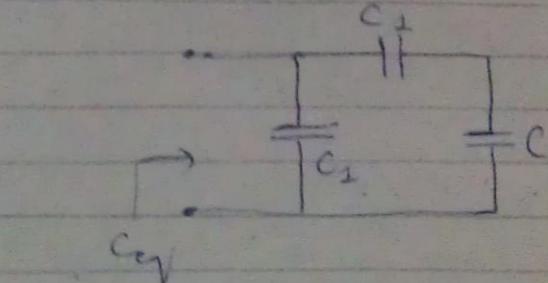

$$\therefore C_{eq} = C$$

$$C = \frac{C_1(1 + \sqrt{5})}{2}$$

ignoring -ve value


b)

$$C_{eq} = \frac{(C_1 + C) \cdot C_1}{C_1 + C + C_1}$$

$$C = \frac{CC_1 + C_1^2}{C + 2C_1}$$

$$C(C + 2C_1) = CC_1 + C_1^2$$

$$C^2 + 2CC_1 = CC_1 + C_1^2$$

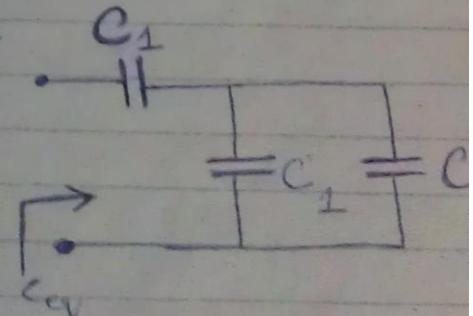

$$C^2 + CC_2 - C_2^2 = 0$$

$$C = \frac{-C_2 \pm \sqrt{C_2^2 + 4C_2^2}}{2}$$


$$C = C_2 \left(-\frac{1}{2} \pm \frac{\sqrt{5}}{2} \right)$$

$$C = \frac{C_2(\sqrt{5}-1)}{2}$$


Q6)

2nF, 3nF, 6nF


$$C_{eq} = 1.6 \text{ nF}$$

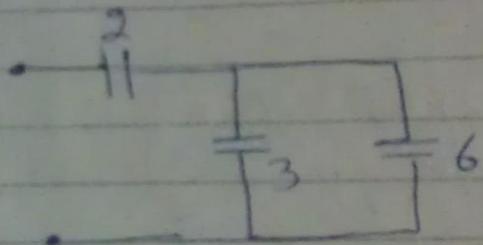


$$C_{eq} = 2.1 \text{ nF}$$

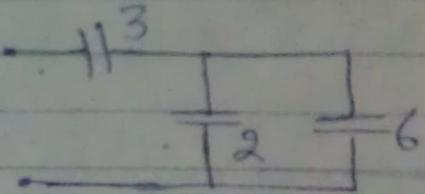


$$C_{eq} = 2.7 \text{ nF}$$

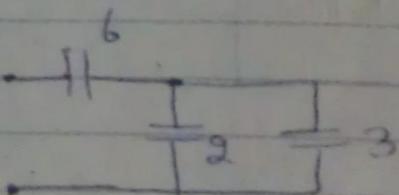


$$C_{eq} = 1 \text{ nF}$$

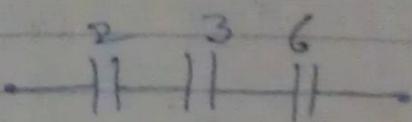


$$C_{eq} = 11 \text{ nF}$$

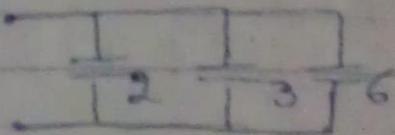


$$C_{eq} = 4 \text{ nF}$$

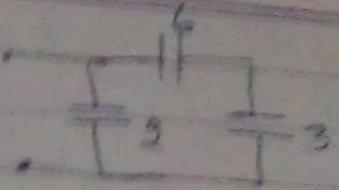

$$C_{eq} = 7.2 \text{ nF}$$

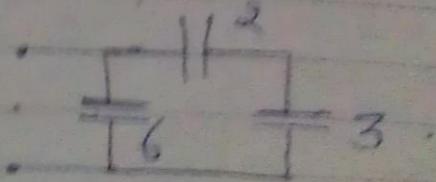


$$C_{eq} = 4.5 \text{ nF}$$

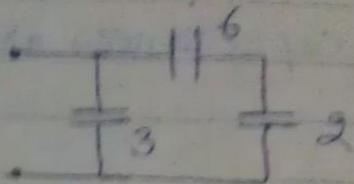

Q7.7(a)


$$10 \parallel 2$$

$$10 + 2 = 12$$

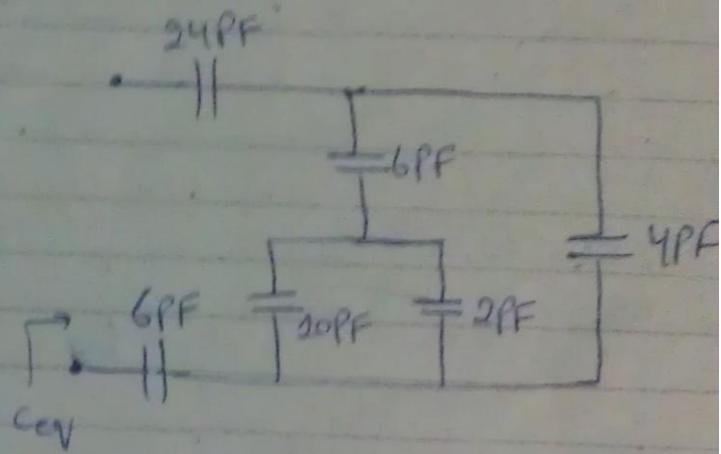


6 Series 12

$$= \frac{6 \times 12}{6+12} = 4$$

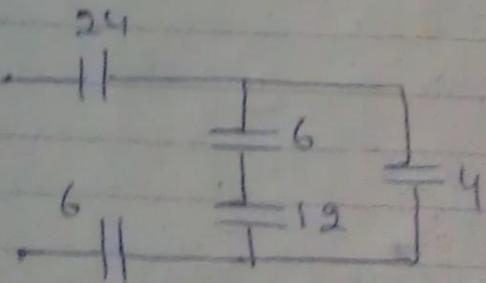

$$4 \parallel 4$$

$$4 + 4 = 8$$

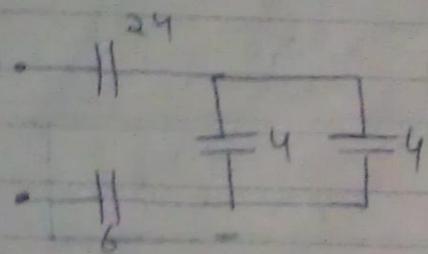


24 Series 8 series 6

$$\frac{24 \times 8}{24+8} = 6$$

$$\frac{6 \times 6}{6+6} = 3$$

So,


$$C_{eq} = 3 \text{ pF}$$

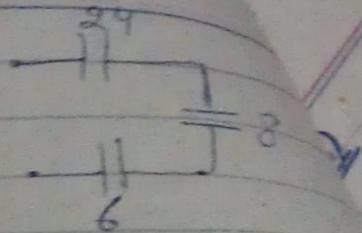

24 Series
6+8
6

b) All capacitances are 10 pF

$$10 \parallel 10 = 20$$

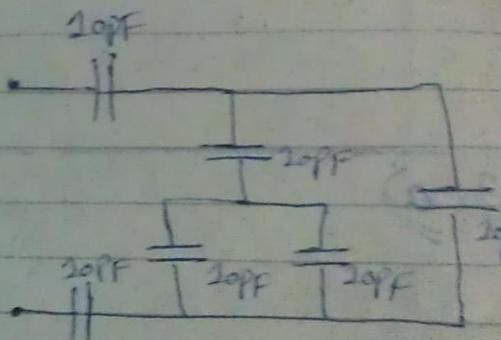


10 Series 20

$$\frac{10 \times 20}{10+20} = 6.66$$


$$6.66 \parallel 10$$

$$6.66 + 10 = 16.66$$

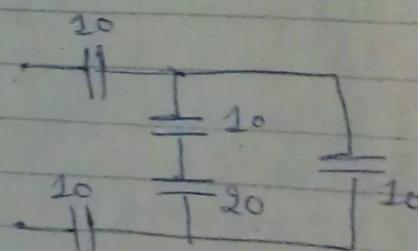

$$\frac{10 \times 10}{20+10} = 5$$
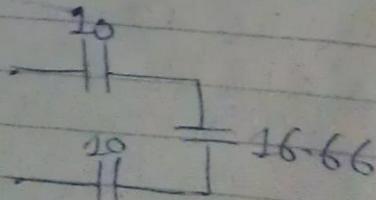
$$\frac{5 \times 16.66}{5+16.66} = 3.84$$



$$C_{eq} = 3.84 \text{ pF}$$


a)

6 Series 8

$$\frac{6 \times 8}{6+8} = 3.42$$

12 Series 18


$$\frac{12 \times 18}{12+18} = 7.2$$

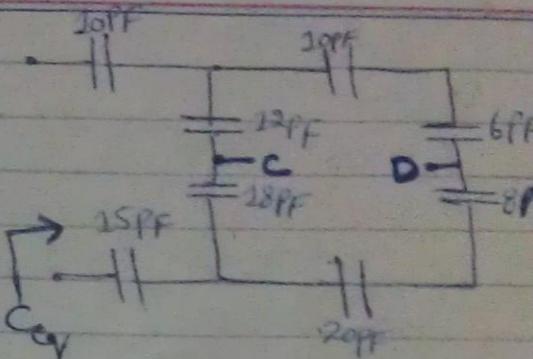

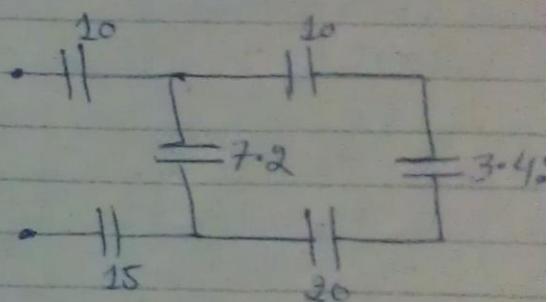3.42 Series 10 Series 20

$$\frac{20 \times 10}{20+10} = 6.66$$

$$\frac{3.42 \times 6.66}{3.42 + 6.66} = 2.25$$




2.25 || 7.2

$$\Leftrightarrow 2.25 + 7.2 = 9.45$$

9.45 Series 10 Series 15

$$\frac{10 \times 15}{10+15} = 6$$

$$\frac{6 \times 9.45}{6+9.45} = 3.66$$

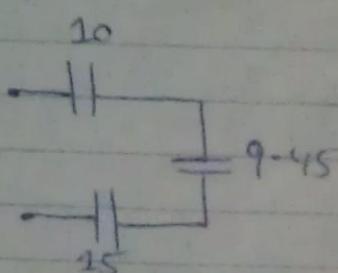

So,

$$C_{eq} = 3.66 \text{ pF}$$

b) C & D are shorted together

6 Series 10

$$\frac{6 \times 10}{6+10} = 3.75$$

20 Series 8

$$\frac{20 \times 8}{20+8} = 5.71$$

$$3.75 \parallel 19$$

$$3.75 + 19 = 15.75$$

$$5.71 \parallel 18$$


$$5.71 + 18 = 23.7$$

15.75 Series 23.7 Series 10 series 25

$$\frac{15.75 \times 23.7}{15.75 + 23.7} = 9.46$$

$$15.75 + 23.7$$

$$\frac{10 \times 15}{10 + 15} = 6$$

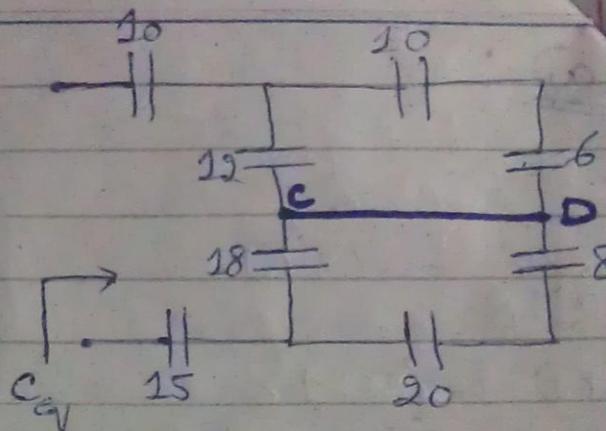


$$\frac{6 \times 9.46}{6 + 9.46} = 3.66$$

$$C_{eq} = 3.66 \text{ PF}$$

4.9(a)

$$W_1 = \frac{1}{2} C_1 V_1^2$$

$$= \frac{1}{2} (3) (2)^2$$

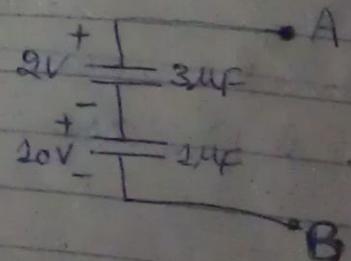

$$w_2 = \frac{1}{2} C_2 V_2^2$$

$$= \frac{1}{2} (1) (10)^2$$

$$W_2 = 50 \mu J$$

$$W = W_1 + W_2$$

$$= 50 + 6$$

$$W = 56 \mu J$$

Now,

$$W' = ?$$


$$C_{eq} = \frac{3 \times 1}{3+1} = 0.75 \mu F$$

$$V_{AB} = V_A + V_B$$

$$V_{AB} = 10 + 2$$

$$V_{AB} = 12 V$$

connecting A & B

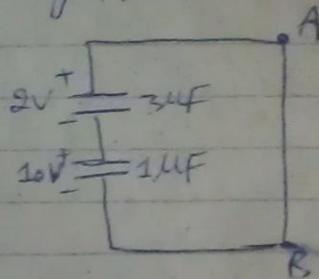

$$W' = \frac{1}{2} C V_{AB}^2$$

$$= \frac{1}{2} (0.75)(12)^2$$

$$W' = 54 \mu J$$


$$\text{Fraction} = \frac{54}{56} \times 100$$

$$\text{Fraction} = 96.42\%$$

b)

$$W = 56 \mu J$$

$$C_{eq} = 0.75 \mu F$$

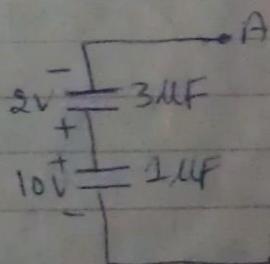

$$V_{AB} = V_B - V_A \\ = 10 - 2$$

$$V_{AB} = 8V$$

$$w' = \frac{1}{2} C_{eq} V_{AB}^2$$

$$w' = \frac{1}{2} (0.75)(8)^2$$

$$w' = 24 \mu J$$

$$\text{Fraction} = \frac{24}{56} \times 100$$

$$\text{Fraction} = 42.85\%$$

Q7.10)

$$C_1 = 2 \mu F, V_1 = 5V$$

$$C_2 = 3 \mu F, V_2 = 6V$$

$$C_3 = 6 \mu F, V_3 = 3V$$

$$W_1 = \frac{1}{2} C_1 V_1^2$$

$$= \frac{1}{2} \cdot (2) \cdot (5)^2$$

$$W_1 = 25 \mu J$$

$$W_2 = \frac{1}{2} C_2 V_2^2$$

$$= \frac{1}{2} \cdot (3) \cdot (6)^2$$

$$w_3 = \frac{1}{2}(6)(3)^2$$

$$w_3 = 27 \mu J$$

Now,

$$C_{eq} = 1 \mu F$$


For w_{max}

$$V_{max} = 5 + 6 + 3 \\ = 14 V$$

$$W_{max} = \frac{1}{2} C V_{max}^2$$

$$W_{max} = \frac{1}{2} (1) (14)^2$$

$$W_{max} = 98 \mu J$$

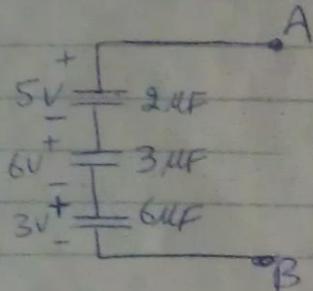

For w_{min}


$$V_{min} = -5 + 3 + 6 = 6 - 5 + 3$$


$$V_{min} = 4 V$$

$$W_{min} = \frac{1}{2} C V_{min}^2$$

$$= \frac{1}{2} (1) (4)^2$$

$$W_{min} = 8 \mu J$$

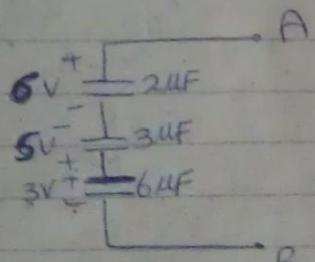

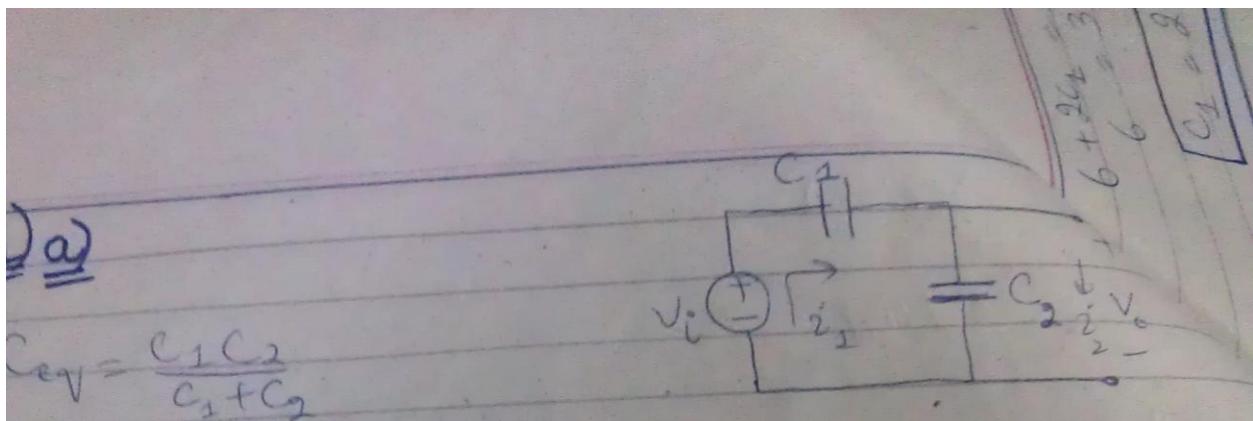

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$= \frac{C_1 C_2}{C_1 + C_2} \cdot \frac{dV_i}{dt}$$

$$= C_2 \frac{dV_o}{dt}$$

$$i_1 = i_2$$

$$\frac{C_1 C_2}{C_1 + C_2} \frac{dV_i}{dt} = C_2 \frac{dV_o}{dt}$$

$$V_o = \frac{C_1}{C_1 + C_2} V_i$$

OR

By voltage divider rule for capacitor

$$V_o = \frac{C_1}{C_1 + C_2} V_i$$

$$C_2 = 3 \text{nF}$$

$$V_i = 5V$$

$$V_o = 2V$$

$$C_1 = ?$$

$$V_o = \frac{C_1}{C_1 + C_2} V_i$$

$$2 = \frac{C_1}{C_1 + 3} \times 5$$

$$6 + 2C_1 = 5C_1$$

$$6 = 3C_1$$

$$C_1 = 2 \text{nF}$$

Q7.12) a)

$$\text{As } V_N = V_P = 0$$

$$i_1 = C_1 \frac{dV_i}{dt}$$

$$i_2 = C_2 \frac{dV_o}{dt}$$

$$i_1 + i_2 = 0$$

$$C_1 \frac{dV_i}{dt} + C_2 \frac{dV_o}{dt} = 0$$

$$V_o = -\frac{C_1}{C_2} V_i$$

b)

$$C_1 = 40 \text{pF}$$


$$C_2 = 10 \text{pF}$$

$$V_o = 8 \text{V}$$

$$V_i = ?$$


$$V_o = -\frac{C_1}{C_2} V_i$$

$$8 = -\frac{40}{10} V_i$$

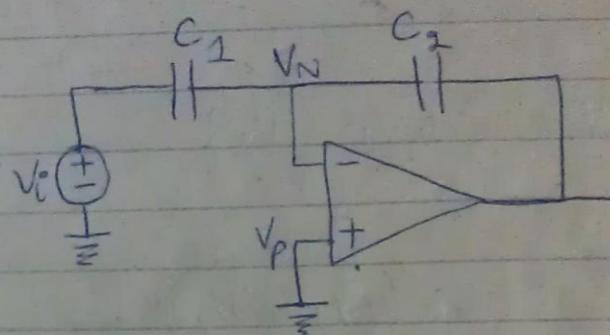


Q7.13) a)

$$V = CV_1$$

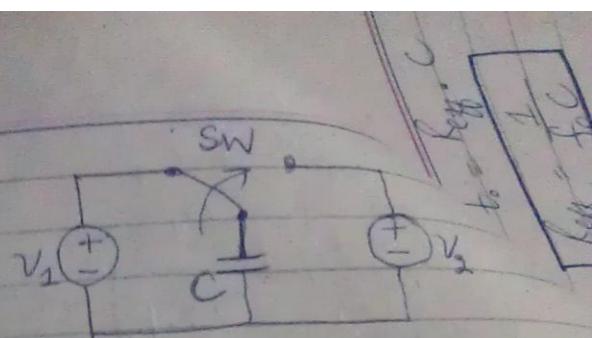

$$V = C(V_1 - V_2)$$

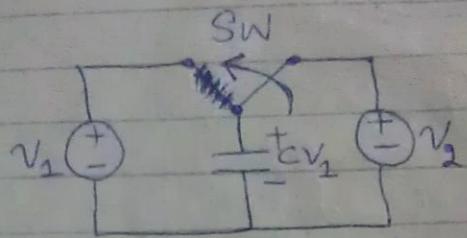

$$\frac{V}{t_0} = \frac{C}{t_0}(V_1 - V_2)$$

$$\therefore C = \frac{V}{V}$$

$$\frac{V}{t_0} = \frac{V}{Vt_0}(V_1 - V_2) \Rightarrow Vf_0 = \frac{C}{t_0}(V_1 - V_2)$$

$$\therefore i = \frac{V}{V}(V_1 - V_2)$$

$$\therefore i = \frac{(V_1 - V_2)}{V_i}$$

$$i = \frac{V_1 - V_2}{R_{eff}}$$

$$\therefore R_{eff} = \frac{1}{f_0 C}$$

$$i = \frac{V_1 - V_2}{\frac{t}{C}}$$

$$\therefore R_{eff} = \frac{t}{C}$$

$$i \neq V_1 - V_2 \cdot \frac{t}{C}$$

$$i = V_1 - V_2 \cdot \frac{C}{t_0}$$

$$t_0 = \frac{V_1 - V_2 \cdot C}{i}$$

$$t_0 = R_{eff} \cdot C$$

$$R_{eff} = \frac{1}{f_0 \cdot C}$$

$$R_{eff} = ?$$

$$C = 10 \text{ pF}$$

$$f_0 = 1 \text{ kHz}$$

$$R_{eff} = \frac{1}{f_0 \cdot C}$$

$$R_{eff} = \frac{1}{1 \times 10^3 \times 10 \times 10^{-12}}$$

$$R_{eff} = 1 \times 10^{18} \Omega$$

$$R_{eff} = 100 \text{ M}\Omega$$

$$\text{iii) } f = 1 \text{ MHz}$$

$$R_{eff} = \frac{1}{1 \times 10^6 \times 10 \times 10^{-12}}$$

$$R_{eff} = 1 \times 10^5 \Omega$$

$$R_{eff} = 100 \text{ k}\Omega$$

$$\text{Q7.14) } i = ?$$

$$C = 50 \text{ nF}$$

$$\text{a) } V = 5(1 - 10^4 t) \text{ V}$$

$$i = C \frac{dv}{dt}$$

$$i = 50 \times 10^{-9} \cdot \frac{d}{dt} (5 - 5 \times 10^4 t)$$

$$i = 50 \times 10^{-9} (-5 \times 10^4)$$

$$i = -2.5 \times 10^{-3} A$$

b) $V = 10(1 - e^{-10^4 t})$

$$i = 50 \times 10^{-9} \frac{d}{dt} 10 - 10 e^{-10^4 t}$$

$$i = 50 \times 10^{-9} (-10) e^{-10^4 t} \cdot (-10^4)$$

$$i = 5 \times 10^{-3} e^{10^4 t} A$$

c) $V = 4 \sin 10^4 t$

$$i = 50 \times 10^{-9} \frac{d}{dt} 4 \sin 10^4 t$$

$$i = 50 \times 10^{-9} \times 4 \cos 10^4 t \cdot 10^4$$

$$i = 2 \times 10^{-3} \cos 10^4 t A$$

d) $V = 15V$

$$i = 50 \times 10^{-9} \frac{d}{dt} 15$$

$$i = 0 A$$

Q7-15) $V = ?$

$$V(0) = 5V$$

$$C = 1 \mu F$$

$$V = \frac{1}{C} \int i dt + V(0)$$

$$V = \frac{1}{1 \times 10^{-6}} \int 10^5 t + 5$$

$$= 1 \times 10^6 \times 10^5 \cdot \frac{t^2}{2} + 5$$

$$= 5t^2 + 5$$

$$\boxed{V = 5(t^2 + 1)V}$$

$$\text{b) } i = 2e^{-10^5 t} A$$

$$V = \frac{1}{1 \times 10^{-6}} \int 2e^{-10^5 t} dt + 5$$

$$= 1 \times 10^6 \times 2 \cdot \frac{e^{-10^5 t}}{-10^5} + 5$$

$$= -20e^{-10^5 t} + 5$$

$$\boxed{V = 5(1 - 4e^{-10^5 t})V}$$

$$\text{c) } i = 0.5 \cos 10^5 t A$$

$$i = \frac{1}{1 \times 10^{-6}} \int 0.5 \cos 10^5 t dt + 5$$

$$= 1 \times 10^6 \times 0.5 \cdot \frac{-\sin 10^5 t}{10^5} + 5$$

$$= -5 \sin 10^5 t + 5$$

$$\boxed{i = 5(1 - \sin 10^5 t)}$$

$$V = \frac{1}{2 \times 10^{-6}} \int 5 \times 10^6 dt$$





$$\boxed{V = 5t \text{ V}}$$

e) $i = 0A$

$$V = \frac{1}{2 \times 10^{-6}} \int 0 dt$$

$$\boxed{V = 0 \text{ V}}$$

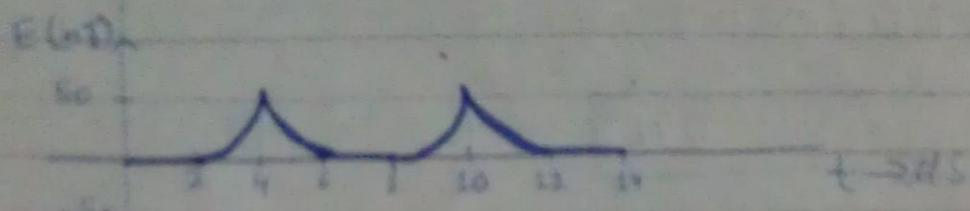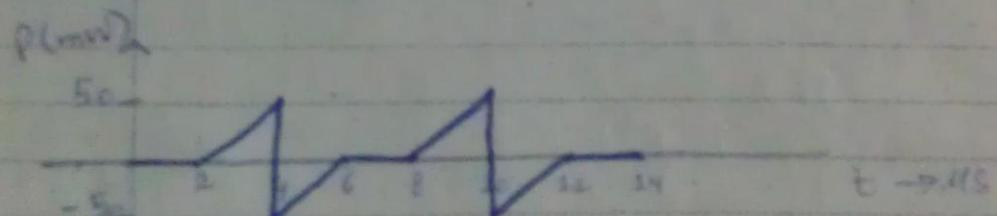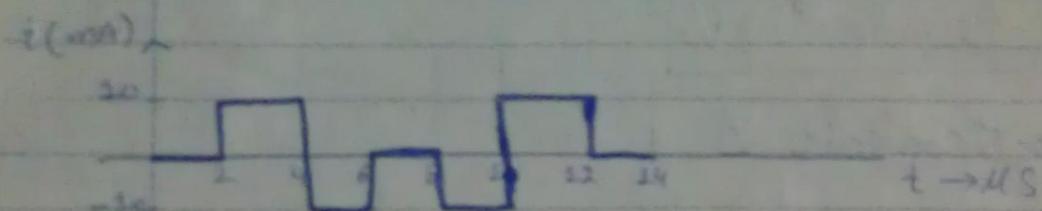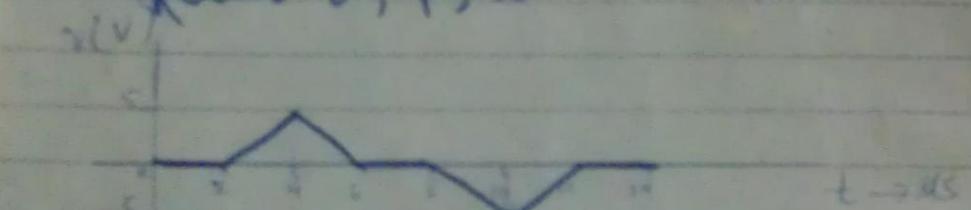Q7.16 $C = 4 \mu\text{F}$
Sketch i , P , w



$0 \rightarrow 2 \text{ } \mu\text{s}$

$$V = 0$$

$$I = 0$$

$$P = 0$$

$2 \rightarrow 4 \text{ } \mu\text{s}$

$$V = \frac{-5}{2 \times 10^6} t - 5$$

$$V = 2.5 \times 10^6 t - 5$$

$$\begin{aligned} P &= (2.5 \times 10^6 t - 5) 10 \times 10^{-3} \\ &= 2.5 \times 10^4 t - 0.05 \\ \text{put } t &= 4 \text{ } \mu\text{s} \end{aligned}$$

$$i = C \frac{dv}{dt}$$

$$P = 50 \text{ mW}$$

$$i = 4 \times 10^{-9} \frac{d}{dt} (2.5 \times 10^6 t - 5)$$

$$i = 10 \text{ mA}$$

$4 \rightarrow 6 \text{ } \mu\text{s}$

$$V = \frac{-5}{2 \times 10^6} t + 15$$

$$V = -2.5 \times 10^6 t + 15$$

$$i = 4 \times 10^{-9} \frac{d}{dt} (-2.5 \times 10^6 t + 15)$$

$$i = -10 \text{ mA}$$

$$\begin{aligned} P &= (-2.5 \times 10^6 t + 15) (-10 \times 10^{-3}) \\ &= 2.5 \times 10^4 t - 0.15 \end{aligned}$$

$$\text{put } t = 6 \text{ } \mu\text{s}$$

$$P = 0$$

$6 \rightarrow 8 \text{ } \mu\text{s}$

$$i = 0$$

$$P = 0$$

$8 \rightarrow 10 \text{ } \mu\text{s}$

-ve slope

$$V = \left(-0.5t + 20 \right) \times 10^6$$

$$V = 2.5 \times 10^6 t + 20$$

$$i = 4 \times 10^{-9} \frac{d}{dt} (2.5 \times 10^6 t + 20)$$

$$i = -10 \text{ mA}$$

$$t = 10 \rightarrow 12 \mu\text{s}$$

$$V = 2.5 \times 10^6 t - 30$$

$$i = 4 \times 10^{-9} \frac{d}{dt} (2.5 \times 10^6 t - 30)$$

$$i = 10 \text{ mA}$$

$$t = 12 \rightarrow 14 \mu\text{s}$$

$$i = 0$$

$$P = 25 \times 10^6 t - 200$$

$$\text{At } t = 10 \mu\text{s}$$

$$P = 50 \text{ mW}$$

$$P = 25 \times 10^6 t - 300$$

$$\text{At } t = 12 \mu\text{s}$$

$$P = 0$$

$$P = 0$$

Energy

$$2 \rightarrow 4 \mu\text{s}$$

$$W = \frac{1}{2} C V^2$$

$$= \frac{1}{2} 4 \times 10^{-9} (2.5 \times 10^6 t - 5)^2$$

$$= 2 \times 10^{-9} (6.25 \times 10^{12} t^2 + 25 - 2.5 \times 10^7 t)$$

$$= 12500 t^2 + 5 \times 10^{-8} - 0.05 t$$

$$\text{For } t = 4 \mu\text{s}$$

$$W = 2 \times 10^{-7} + 5 \times 10^{-8} - 2 \times 10^{-7}$$

$$= 50 \times 10^{-9} \text{ J}$$

For $4 \rightarrow 6 \mu\text{s}$

$$W = \frac{1}{2} 4 \times 10^{-9} (-2.5 \times 10^6 t + 15)^2$$

$$\begin{aligned} &= 2 \times 10^{-9} (6.25 \times 10^{12} t^2 + 225 - 7.5 \times 10^7 t) \\ &= 12500 t^2 + 4.5 \times 10^{-7} - 0.15 t \end{aligned}$$

For $t = 6 \mu\text{s}$

$$W = 4.5 \times 10^{-7} + 4.5 \times 10^{-7} - 9 \times 10^{-7}$$

$$W = 0$$

For $6 \rightarrow 8 \mu\text{s}$

$$W = 0$$

For $8 \rightarrow 10 \mu\text{s}$

$$W = \frac{1}{2} 4 \times 10^{-9} (-2.5 \times 10^6 t + 20)$$

$$\begin{aligned} &= 2 \times 10^{-9} (6.25 \times 10^{12} t^2 + 400 - 1 \times 10^8 t) \\ &= 12500 t^2 + 8 \times 10^{-7} - 0.2t \end{aligned}$$

At $t = 10 \mu\text{s}$

$$W = 1.25 \times 10^{-6} + 8 \times 10^{-7} - 2 \times 10^{-6}$$

$$W = 50 \times 10^{-9} \text{ J}$$

For $10 \rightarrow 12 \mu\text{s}$

$$W = \frac{1}{2} 4 \times 10^{-9} (2.5 \times 10^6 t - 30)$$

$$\begin{aligned} &= 2 \times 10^{-9} (6.25 \times 10^{12} t^2 + 900 - 1.5 \times 10^8 t) \\ &= 12500 t^2 + 1.8 \times 10^{-6} - 0.3t \end{aligned}$$

At $t = 12 \mu\text{s}$

$$W = 1.8 \times 10^{-6} + 1.8 \times 10^{-6} - 3.6 \times 10^{-6}$$




$$W = 0$$

For $12 \rightarrow 14 \mu\text{s}$

$$W = 0$$

Q17) $C = 2\text{nF}$

Sketch current

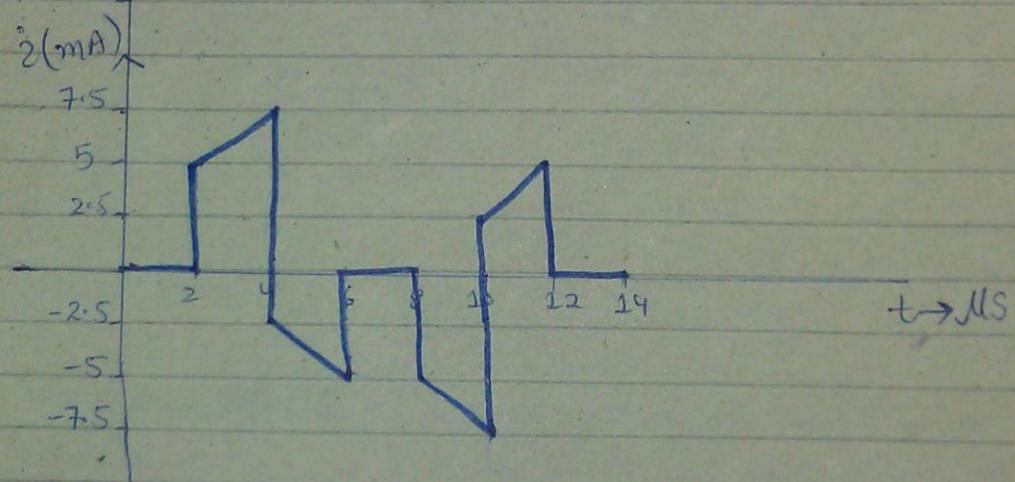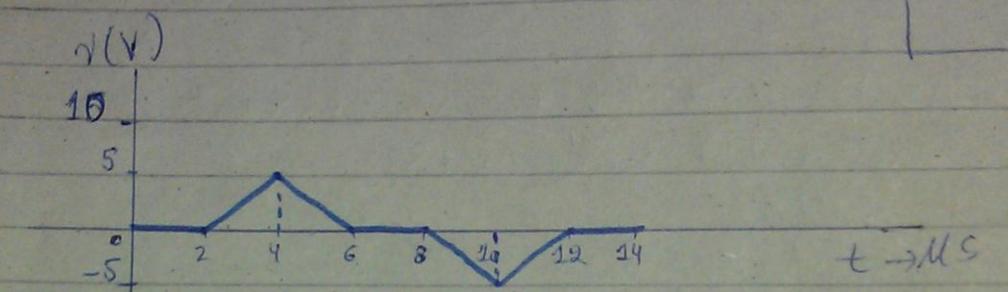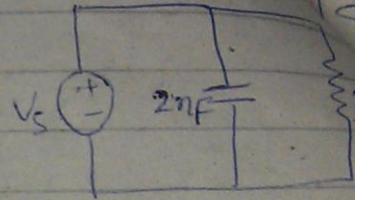

$$C = 2\text{nF}$$

$$i = \frac{V}{R} + C \cdot \frac{dV}{dt}$$

$0 \rightarrow 2\text{ }\mu\text{s}$

$$V = 0$$

$$i = 0$$

$2 \rightarrow 4\text{ }\mu\text{s}$

$$V = 2.5 \times 10^6 t - 5$$

$$i = \frac{2.5 \times 10^6 t - 5 + 2 \times 10^{-9} \frac{d}{dt} (2.5 \times 10^6 t - 5)}{2 \times 10^3}$$

At $t = 2 \mu s$

$$i = 7.5 \text{ mA}$$

At $t = 4 \mu s$

$$i = 5 \text{ mA}$$

$4 \rightarrow 6 \mu s$

$$V = -2.5 \times 10^6 t + 15$$

$$i = \frac{-2.5 \times 10^6 t + 15}{2 \times 10^3} + 2 \times 10^{-9} \frac{d}{dt} (-2.5 \times 10^6 t + 15)$$

At $t = 4 \mu s$

$$i = -2.5 \text{ mA}$$

At $t = 6 \mu s$

$$i = -5 \text{ mA}$$

$6 \rightarrow 8 \mu s$

$$i = 0$$

$8 \rightarrow 10 \mu s$

$$V = -2.5 \times 10^6 t + 20$$

$$i = \frac{-2.5 \times 10^6 t + 20}{2 \times 10^3} + 2 \times 10^{-9} \frac{d}{dt} (-2.5 \times 10^6 t + 20)$$

At $t = 8 \mu s$

$$i = -5 \text{ mA}$$

At $t = 10 \mu s$

$$i = -7.5 \text{ mA}$$

$10 \rightarrow 12 \mu s$

$$V = 2.5 \times 10^6 t - 30$$

$$i = \frac{2.5 \times 10^6 t - 30}{2 \times 10^3} + 2 \times 10^{-9} \frac{d}{dt} (2.5 \times 10^6 t - 30)$$

At $t = 10 \mu s$

$$i = 2.5 \text{ mA}$$



At $t = 12 \mu s$

$$i = 5 \text{ mA}$$

$12 \rightarrow 14 \mu\text{s}$

$$i = 0$$

Q7.18) $C = 5 \text{nF}$

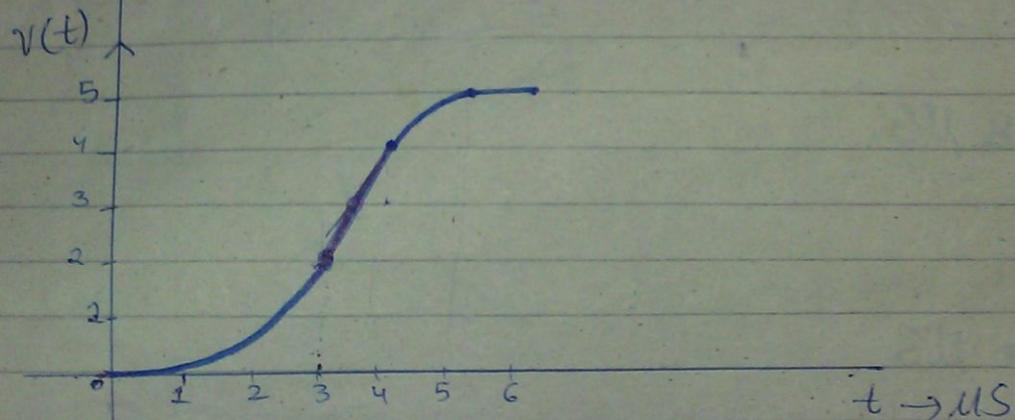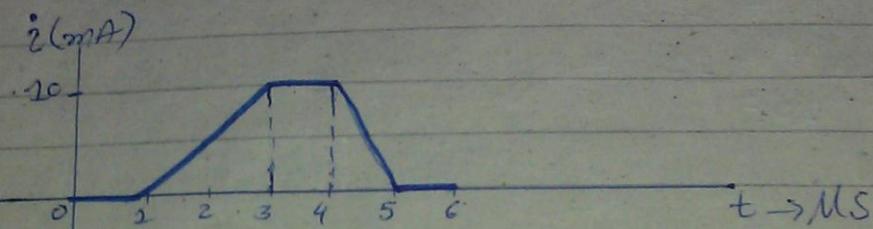

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\xi) d\xi - v(0) = \frac{1}{C} \int_0^t i(\xi) d\xi$$

$$v(t) = \frac{1}{C} \int_0^t i(\xi) d\xi + v(0)$$

$1 \rightarrow 3 \mu\text{sec}$

$$i(t) = \frac{10 \times 10^3}{2 \times 10^6} t - 5 \times 10^{-3}$$

$$i(t) = 5 \times 10^3 t - 5 \times 10^{-3}$$

$$\begin{aligned}
 V(t) &= V(0) + \frac{1}{C} \int_0^t i(\xi) d\xi \\
 &= 0 + \frac{1}{5 \times 10^{-9}} \int_{1 \times 10^{-6}}^{3 \times 10^{-6}} (5 \times 10^3 t - 5 \times 10^3) dt \\
 &= \frac{1}{5 \times 10^{-9}} \left[\frac{5 \times 10^3 t^2}{2} \right]_{1 \times 10^{-6}}^{3 \times 10^{-6}} - \left[5 \times 10^3 t \right]_{1 \times 10^{-6}}^{3 \times 10^{-6}} \\
 &= \frac{1}{5 \times 10^{-9}} \left[5 \times 10^3 \left\{ \frac{(3 \times 10^{-6})^2 - (1 \times 10^{-6})^2}{2} \right\} \right] \\
 &\quad - 5 \times 10^3 \left[3 \times 10^{-6} - 1 \times 10^{-6} \right] \\
 &= \frac{1}{5 \times 10^{-9}} \left[5 \times 10^3 (4 \cdot 5 \times 10^{-2} - 5 \times 10^{-3}) - 5 \times 10^3 (2 \times 10^{-6}) \right] \\
 &= \frac{1}{5 \times 10^{-9}} (200 - 1 \times 10^{-8}) \\
 &= \frac{200}{5 \times 10^{-9}}
 \end{aligned}$$

$$V(t) = 2V$$

For in-between shape

$$\begin{aligned}
 V(t) &= V(0) + \frac{1}{C} \int_0^t i(\xi) d\xi \\
 &= 0 + \frac{1}{5 \times 10^{-9}} \int_{1 \times 10^{-6}}^t (5 \times 10^3 \xi - 5 \times 10^{-3}) d\xi \\
 &= \frac{1}{5 \times 10^{-9}} \left[\frac{(5 \times 10^3 \xi)^2}{2} - 5 \times 10^{-3} \xi \right]_{1 \times 10^{-6}}^t \\
 &= \frac{1}{5 \times 10^{-9}} \left[\frac{5 \times 10^3 t^2}{2} - 5 \times 10^{-3} t - \frac{5 \times 10^3 (1 \times 10^{-6})^2}{2} \right. \\
 &\quad \left. + (5 \times 10^{-3}) (1 \times 10^{-6}) \right]
 \end{aligned}$$

$$V(t) = \frac{1}{5 \times 10^{-9}} \left[\frac{5 \times 10^3 t^2}{2} - 5 \times 10^3 t - \frac{5 \times 10^{-2}}{2} + 5 \times 10^{-3} \right]$$

$$V(t) = \frac{1}{2} \times 10^{12} t^2 - 10^6 t + \frac{1}{2} \rightarrow \text{Eq. of parabola}$$

Put $t = 3 \text{ ms}$

$$V(t) = 2V$$

$3 \rightarrow 4 \text{ ms}$

$$i(t) = 10 \text{ mA}$$

$$\begin{aligned} V(t) &= V(3 \times 10^{-6}) + \frac{1}{5 \times 10^{-9}} \int_{3 \times 10^{-6}}^t 10 \times 10^3 d\xi \\ &= 2 + \frac{1}{5 \times 10^{-9}} \left[10 \times 10^3 \xi \right]_{3 \times 10^{-6}}^t \\ &= 2 + \frac{1}{5 \times 10^{-9}} \left[10 \times 10^3 t - 30 \times 10^{-9} \right] \\ &= 2 + (2 \times 10^6 t - 6) \end{aligned}$$

$$V(t) = 2 \times 10^6 t - 4$$

put $t = 4 \text{ ms}$

$$V(t) = 4V$$

Now, initial condition is 4.

$4 \rightarrow 5 \text{ ms}$

$$i(t) = -10 \times 10^3 t + 50 \times 10^{-3}$$

$$V(t) = 4 + \frac{1}{C} \int_{4 \times 10^{-6}}^t i(\xi) d\xi$$

$$\begin{aligned}
 v(t) &= 4 + \frac{1}{5 \times 10^9} \int_{4 \times 10^{-6}}^t -10 \times 10^3 \xi + 50 \times 10^3 d\xi \\
 &= 4 + \frac{1}{5 \times 10^9} \left[-10 \times 10^3 \frac{\xi^2}{2} + 50 \times 10^3 \xi \right]_{4 \times 10^{-6}}^t \\
 &= 4 + \left[-10 \times 10^3 \frac{t^2}{2} + 10 \times 10^3 \frac{(4 \times 10^{-6})^2}{2} \right] + \left[\frac{50 \times 10^3 t}{(50 \times 10^3) \times 4 \times 10^{-6}} \right] \\
 &\vdots -10^3 t^2 + 10 \times 10^6 t - 90 \text{ parabola}
 \end{aligned}$$

At $t = 5 \mu\text{sec}$

$$v(t) = 5 \text{ V}$$

Q7.19) $C = 0.5 \mu\text{F}$
 $v = 5 \times \sin 10^3 t \text{ V}$
 $i, P, \omega = ?$ $0 \leq 10^3 t \leq 2\pi$

$$\text{take } 10^3 t = \theta$$

$$V_c = 5 \sin \theta$$

$$i_c = C \frac{dV_c}{dt}$$

$$= 0.5 \times 10^{-6} \times 5 \times 10^3 \cos 10^3 t$$

$$= 2.5 \times 10^{-3} \cos 10^3 t$$

$$i_c = 2.5 \cos 10^3 t \text{ mA}$$

$$i_c = 2.5 \cos \theta \text{ mA}$$

$$\begin{aligned}
 P &= V_c i_c \\
 &= 12.5 \sin 10^3 t \cos 10^3 t \text{ mW} \\
 &= 6.25 \sin 2 \times 10^3 t \text{ mW}
 \end{aligned}$$

$$P = 6.25 \sin 2\theta \text{ mW}$$

$$\omega = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times (0.5 \times 10^{-6}) \times 25 \sin^2 10^3 t$$

$$= \frac{6.25 \times 10^{-6}}{2} [1 - \cos 2 \times 10^3 t]$$

$$= 3.125 [1 - \cos 2 \times 10^3 t] \mu\text{J}$$

$$\boxed{\omega = 3.125 (1 - \cos 2\theta) \mu\text{J}}$$

At $\theta = 0$

V (volts)	i (mA)	P (mW)	ω (μJ)
$V = 0$	$i = 2.5$	$P = 0$	$\omega = 0$

At $\theta = \pi/2$

$V = 5$	$i = 0$	$P = 0$	$\omega = 6.25$
---------	---------	---------	-----------------

At $\theta = \pi$


$V = 0$	$i = -2.5$	$P = 0$	$\omega = 0$
---------	------------	---------	--------------

At $\theta = 3\pi/2$

$V = -5$	$i = 0$	$P = 0$	$\omega = 6.25$
----------	---------	---------	-----------------

At $\theta = 2\pi$

$V = 0$	$i = 2.5$	$P = 0$	$\omega = 0$
---------	-----------	---------	--------------

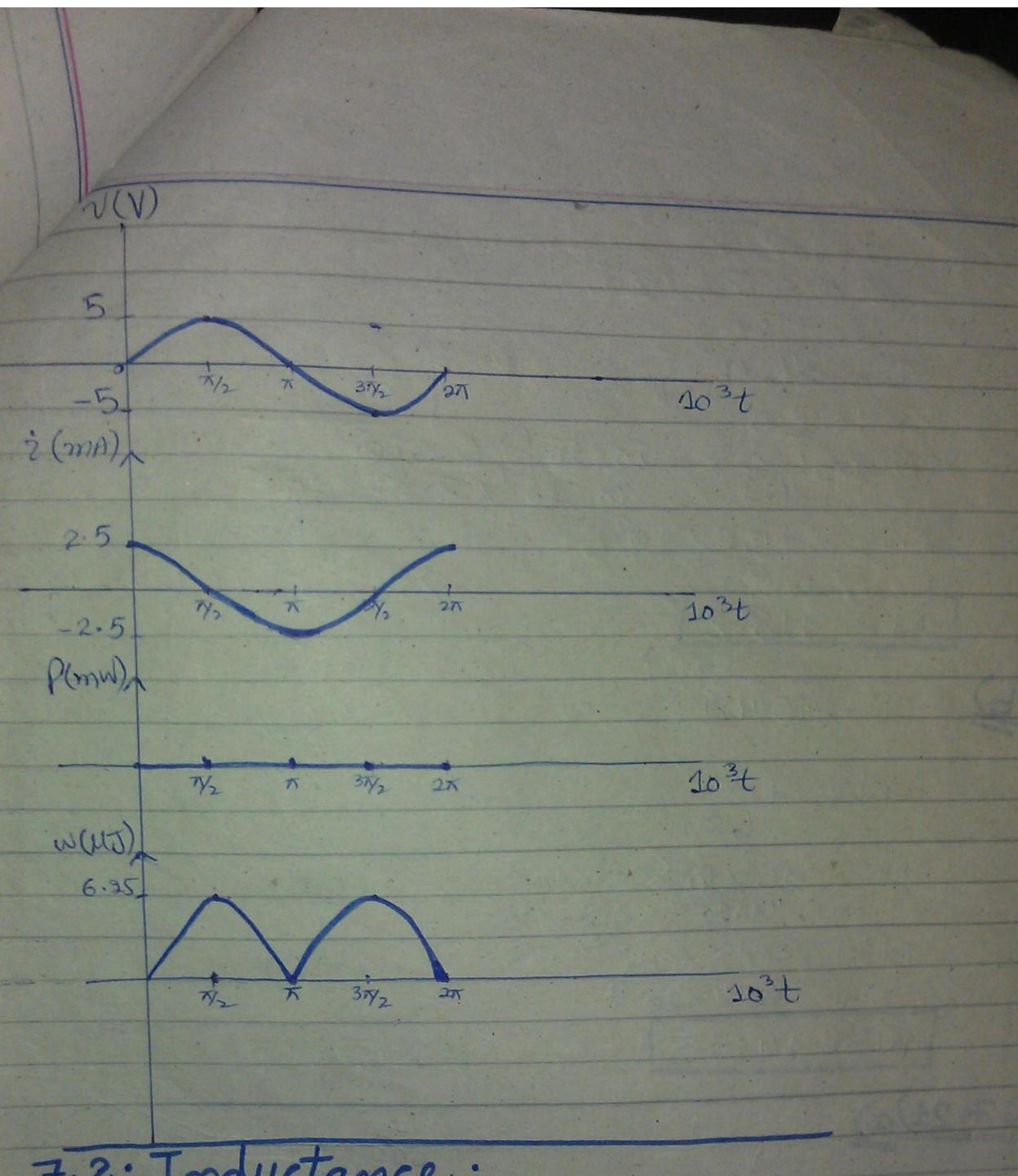

7.2: Inductance:

(Q7.20)(a) $N = ?$

$$d = 6 \text{ mm} = 6 \times 10^{-3} \text{ m}$$

$$l = 5 \text{ cm} = 5 \times 10^{-2} \text{ m}$$

$$L = 10 \text{ mH}$$

$$\mu_0 = 4\pi \times 10^{-7}$$

$$x = \frac{d}{2} = 3 \times 10^{-3} \text{ m}$$

$$S = \pi r^2$$

$$S = 2 \cdot 82 \times 10^{-5}$$

$$L = \mu_0 N^2 \frac{S}{l}$$

$$N^2 = \frac{Ll}{\mu_0 S} = \frac{10 \times 10^{-6} \times 5 \times 10^{-2}}{4\pi \times 10^{-7} \times 2.82 \times 10^{-5}}$$

$$N^2 = 1.412 \times 10^4$$

$$N = 118.8$$

b)

$$L = 15 \mu H$$

$$N^2 = \frac{Ll}{\mu_0 S}$$

$$N^2 = \frac{15 \times 10^{-6} \times 5 \times 10^{-2}}{4\pi \times 10^{-7} \times 2.82 \times 10^{-5}}$$

$$N^2 = \frac{7.5 \times 10^{-7}}{3.54 \times 10^{-11}}$$

$$N = 145.5$$

Q7.21(a)

$$L_{eq} = L$$


$$L_{eq} = \frac{L_1 L}{L_1 + L} + L_1$$

$$L = \frac{L_1 L + L_1^2 + LL_1}{L_1 + L}$$

$$LL_1 + L^2 = 2LL_1 + L_1^2$$

$$L^2 - LL_1 - L_1^2 = 0$$
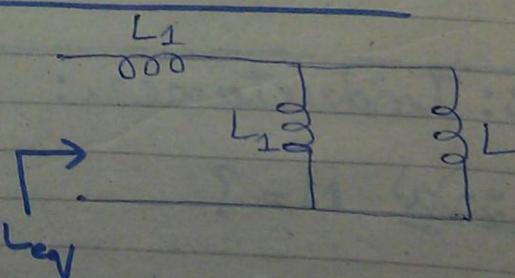
$$L = L_1 \pm \sqrt{\frac{L_1^2 + 4L^2}{2}}$$



$$L = \frac{L_1 + L_1\sqrt{5}}{2}$$

$$L = \frac{L_1(1+\sqrt{5})}{2}$$

b)

$$L_{eq} = \frac{(L+L_1)L_1}{L+L_1+L_1}$$

$$L = \frac{LL_1 + L_1^2}{L + 2L_1}$$


$$L^2 + 2LL_1 - L_1^2 = LL_1 + L_1^2$$

$$L^2 + LL_1 - L_1^2 = 0$$

$$L = \frac{-L_1 \pm \sqrt{L_1^2 + 4L_1}}{2}$$


$$L = \frac{-L_1 \pm L_1\sqrt{5}}{2}$$

$$L = \frac{L_1(\sqrt{5}-1)}{2}$$

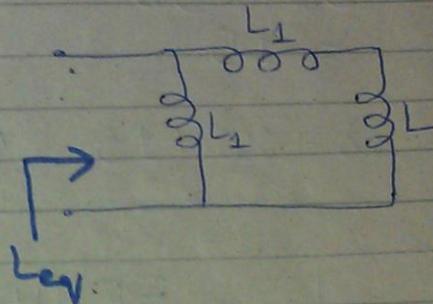

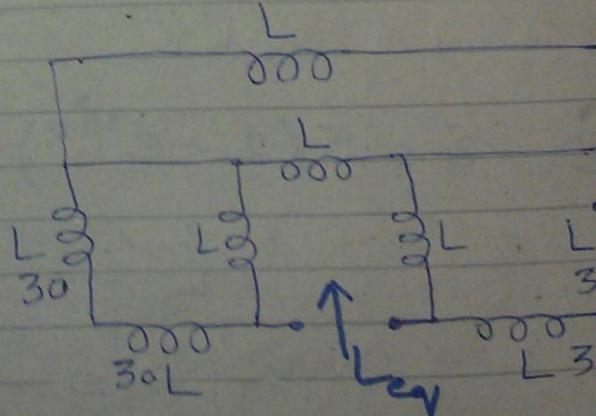Q7.22) $L_{eq} = ?$
 $L = 30 \mu H$

$$\begin{aligned} 30 \text{ series } 30 \\ = 60 \end{aligned}$$





$$= \frac{60 \times 30}{60 + 30} = 20$$

$$= 15$$

$$20 + 20 + 15 = 55$$

So,

$$L_{eq} = 55 \mu H$$

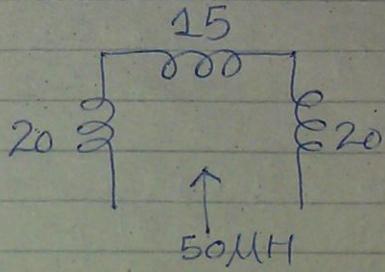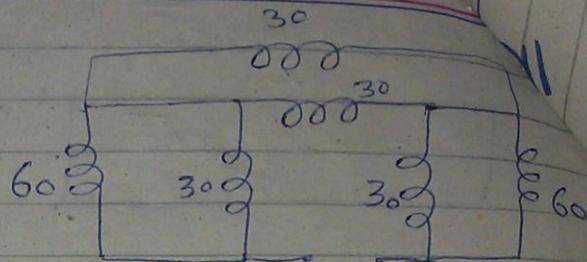

$$\text{Q7.23) a)} \quad L = 25 \text{ mH}$$

$$V_L = ?$$

$$a) \quad i = 10(1 - e^{-10^2 t}) A$$

$$V = L \frac{di}{dt}$$

$$= 25 \times 10^{-3} \frac{d}{dt} (10 - 10 \times 10^2 t)$$

$$= 25 \times 10^{-3} (-10 \times 10^2)$$

$$V = -25 V$$

$$b) \quad i = 5(1 - e^{-10^2 t}) A$$

$$V = 25 \times 10^{-3} \frac{d}{dt} (5 - 5 e^{-10^2 t})$$

$$V = 25 \times 10^{-3} (-5) e^{-10^2 t} \cdot (-10^2)$$

$$V = 12.5 e^{-10^2 t} V$$

$$i = 10 \text{ mA}$$

$$V = 25 \times 10^{-3} \frac{d}{dt} 10 \times 10^{-3}$$

$$V = 0 \text{ V}$$

d) $i = 2 \sin 10^2 t \text{ A}$

$$V = 25 \times 10^{-3} \frac{d}{dt} (2 \sin 10^2 t)$$

$$V = 25 \times 10^{-3} \times 2 \cos 10^2 t \times 10^2$$

$$V = 5 \cos 10^2 t \text{ V}$$

Q7.24) $L = 1 \text{ mH}$

$$i(0) = 10 \text{ mA}$$

a) $V = 10^{-5} t$

$$i = \frac{1}{L} \int V dt + i(0)$$

$$= \frac{1}{1 \times 10^{-3}} \int 10^{-5} t dt + 10 \times 10^{-3}$$

$$= 1 \times 10^3 \times 10^{-5} \frac{t^2}{2} + 10 \times 10^{-3}$$

$$= 5 \times 10^{-3} t^2 + 10 \times 10^{-3}$$

$$i = 5 \times 10^{-3} (5 \times 10^{-3} + t^2) \text{ A}$$

b) $V = 2 \bar{e}^{10^5 t}$

$$i = \frac{1}{1 \times 10^{-3}} \int 2 \bar{e}^{10^5 t} dt + 10 \times 10^{-3}$$

$$= 1 \times 10^3 \cdot \frac{2 \bar{e}^{10^5 t}}{-10^5} + 10 \times 10^{-3}$$

3.25) $L = 5$
 $V, R = 1$

$$i = -0.02 e^{-10^5 t} + 10 \times 10^{-3}$$
$$= 20 \times 10^{-3} e^{-10^5 t} + 10 \times 10^{-3}$$

$$i = 10 \times 10^{-3} (1 - 10 \times 10^{-3} e^{-10^5 t}) A$$

c) $v = 0.5 \cos 10^5 t$

$$i = \frac{1}{1 \times 10^{-3}} \int 0.5 \cos 10^5 t dt + 10 \times 10^{-3}$$

$$= 1 \times 10^3 (0.5) \frac{(-\sin 10^5 t)}{10^5} + 10 \times 10^{-3}$$

$$= -5 \times 10^{-3} \sin 10^5 t + 10 \times 10^{-3}$$

$$i = 5 \times 10^{-3} (5 \times 10^{-3} - \sin 10^5 t) A$$

d) $v = 15V$

$$i = \frac{1}{1 \times 10^{-3}} \int 15 dt + 10 \times 10^{-3}$$

$$= 1 \times 10^3 \times 15 t + 10 \times 10^{-3}$$

$$i = 15 \times 10^3 t + 10 \times 10^{-3} A$$

e) $v = 0V$

$$i = \frac{1}{1 \times 10^{-3}} \int 0 dt + 10 \times 10^{-3}$$

$$i = 10 \times 10^{-3} A$$

$$i = 10 mA$$

Q.25) $L = 500 \mu H$

$V, P = ?$

$i (mA)$

20

-10

0

5

-5

0

50

-50

0

1

2

3

4

5

6

$t \rightarrow \mu s$

$t \rightarrow \mu s$

$t \rightarrow \mu s$

$P (mW)$

50

-50

0

50

-50

0

1

2

3

4

5

6

$$\gamma = L \frac{di}{dt}$$

$0 \rightarrow 1 \mu s$

$i = 0$

$V = 0$

$1 \rightarrow 2 \mu s$

$$i = \frac{10 \times 10^{-3}}{1 \times 10^{-6}} t - 10 \times 10^{-3}$$

$$i = 1 \times 10^4 t - 10 \times 10^{-3}$$

$P = 0$

$P = Vi$

$P = (1 \times 10^4 t - 10 \times 10^{-3})$

put $t = 2 \mu s$

$P = 50 mW$

16
5

$$V = 500 \times 10^{-6} \frac{d}{dt} (1 \times 10^4 t - 10 \times 10^{-3})$$

$$V = 5V$$

$2 \rightarrow 3 \mu s$

$$i = -\frac{10 \times 10^{-3}}{1 \times 10^{-6}} t + 30 \times 10^{-3}$$

$$= -1 \times 10^4 t + 30 \times 10^{-3}$$

$$V = 500 \times 10^{-6} \frac{d}{dt} (-1 \times 10^4 t + 30 \times 10^{-3})$$

$$V = -5V$$

$$P = (-1 \times 10^4 t + 30 \times 10^{-3})(-5)$$

$$\text{At } t = 2 \mu s$$

$$P = -50 \text{ mW}$$

$$\text{At } t = 3 \mu s$$

$$P = 0$$

$3 \rightarrow 4 \mu s$

$$i = -\frac{10 \times 10^{-3}}{1 \times 10^{-6}} t + 30 \times 10^{-6}$$

$$i = -1 \times 10^4 t + 30 \times 10^{-3}$$

$$V = 500 \times 10^{-6} \frac{d}{dt} (-1 \times 10^4 t + 30)$$

$$V = -5V$$

$$P = (-1 \times 10^4 t + 30 \times 10^{-3})(-5)$$

$$\text{At } t = 3 \mu s$$

$$P = 0$$

$$\text{At } t = 4 \mu s$$

$$P = 50 \text{ mW}$$

$4 \rightarrow 5 \mu s$

$$i = \frac{10 \times 10^{-3} t}{1 \times 10^{-6}} - 50 \times 10^{-3}$$

$$i = 1 \times 10^4 t - 50 \times 10^{-3}$$

$$V = 500 \times 10^{-6} \frac{d}{dt} (1 \times 10^4 t - 50 \times 10^{-3})$$

$$V = 5V$$

$$P = (1 \times 10^4 t - 50 \times 10^{-3})(5)$$

$$\text{At } t = 4 \mu s$$

$$P = -50 \text{ mW}$$

$$\text{At } t = 5 \mu s$$

$$P = 0$$

$5 \rightarrow 6 \mu s$

$$\dot{i} = 0$$

$$V = 0$$

$$P = 0$$



Q7.26)

$$L = 250 \mu H$$


$$R = 300 \Omega$$

$$V = ?$$

$$i (\text{mA})$$

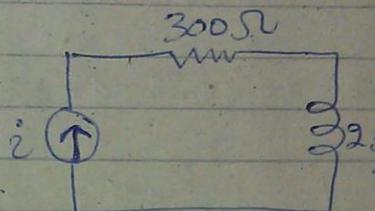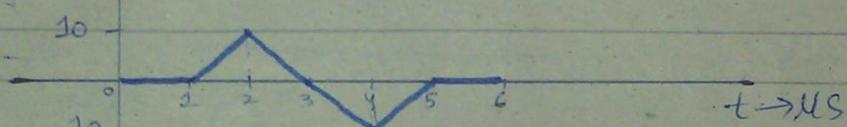

$$v (V)$$

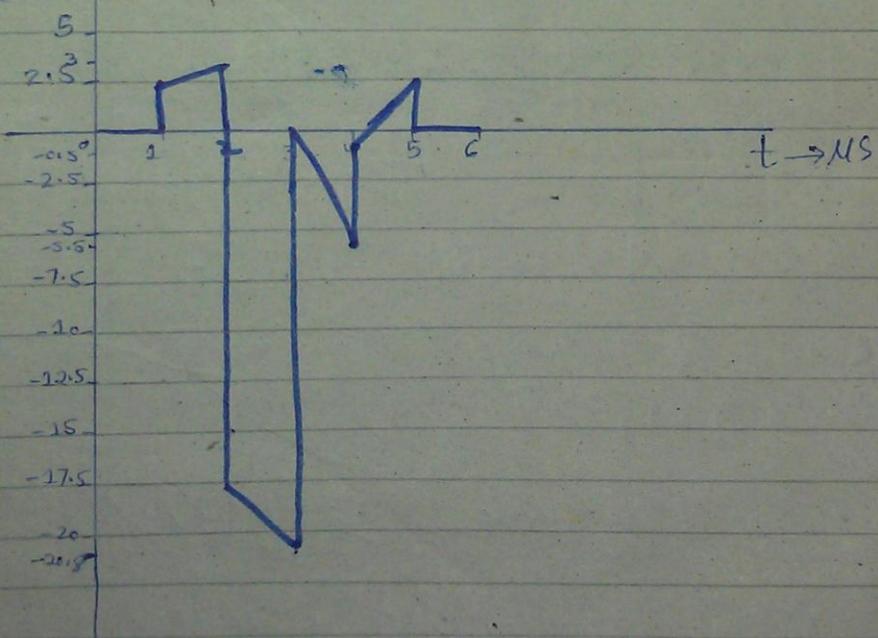

$$v = iR + L \frac{di}{dt}$$

$$4 \rightarrow 5$$

$$i = 1 \times 10^4 t$$

$$V = (1 \times 10^4 t)$$

$0 \rightarrow 1 \mu s$

$$i = 0$$

$$V = 0$$

$1 \rightarrow 2 \mu s$

$$i = 1 \times 10^4 t - 10 \times 10^{-3}$$

$$V = (1 \times 10^4 t - 10 \times 10^{-3})(300) + 250 \times 10^{-6} \frac{d}{dt} (1 \times 10^4 t - 10 \times 10^{-3})$$

$$\text{At } t = 1 \mu s$$

$$V = 2.5 V$$

$$\text{At } t = 2 \mu s$$

$$V = 3 V$$

$2 \rightarrow 3 \mu s$

$$i = -1 \times 10^4 t - 30 \times 10^{-3}$$

$$V = (-1 \times 10^4 t - 30 \times 10^{-3})(300) + 250 \times 10^{-6} \frac{d}{dt} (-1 \times 10^4 t - 30 \times 10^{-3})$$

$$\text{At } t = 2 \mu s$$

$$V = -17.5 V$$

$$\text{At } t = 3 \mu s$$

$$V = -20.5 V$$

$3 \rightarrow 4 \mu s$

$$i = -1 \times 10^4 t + 30 \times 10^{-3}$$

$$V = (-1 \times 10^4 t + 30 \times 10^{-3})(300) + 250 \times 10^{-6} \frac{d}{dt} (-1 \times 10^4 t + 30 \times 10^{-3})$$

$$\text{At } t = 3 \mu s$$

$$V = 0 V$$

$$\text{At } t = 4 \mu s$$

$$V = -5.5 V$$

4 → 5 μs

$$i = 1 \times 10^4 t - 50 \times 10^{-3}$$

$$v = (1 \times 10^4 t - 50 \times 10^{-3})(300) + 250 \times 10^{-6} \frac{d}{dt} (1 \times 10^4 t - 50 \times 10^{-3})$$

At $t = 4 \mu s$

$$v = -0.5 V$$

At $t = 5 \mu s$


$$v = 2.5 V$$

5 → 6 μs

$$i = 0$$

$$v = 0$$

Q7.23) $L = 2 mH$
 $i(0) = 0$

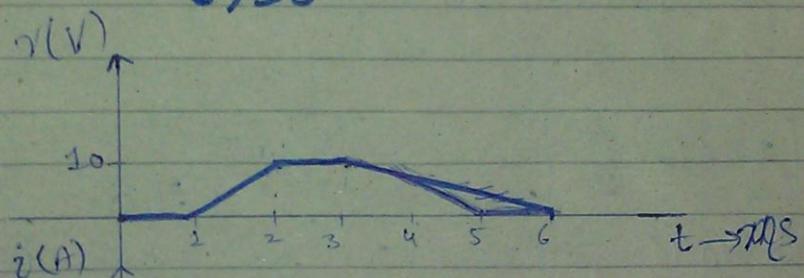

$$i(t) = \frac{1}{L} \int_0^t v(\xi) d\xi + i(0)$$

$$\frac{1}{2} = \frac{2 \times 10}{2}$$

$0 \rightarrow 1 \text{ msec}$

$$v = 0$$

$$i = 0$$

$1 \rightarrow 2 \text{ msec}$

$$v = \frac{10}{2 \times 10^{-3}} t - 10$$

$$v = 10 \times 10^3 t - 10$$

$$i = \frac{1}{2 \times 10^{-3}} \int_{2 \times 10^{-3}}^t 10 \times 10^3 \xi - 10 d\xi + 0$$

$$= 2 \times 10^3 \left[10 \times 10^3 \frac{\xi^2}{2} \right]_{2 \times 10^{-3}}^t - \left[10 \xi \right]_{2 \times 10^{-3}}^t$$

$$= 2 \times 10^3 \left\{ \left[10 \times 10^3 \frac{t^2}{2} - 5 \times 10^{-3} \right] - [10t - 0.01] \right\}$$

$$= 1 \times 10^7 t^2 - 2 \times 10^9 t + 10$$

put $t = 2 \text{ msec}$

$$i = 10 \text{ A}$$

$2 \rightarrow 3 \text{ msec}$

$$v = 10 \text{ V}$$

$$i = \frac{1}{2 \times 10^{-3}} \int_{2 \times 10^{-3}}^t 10 d\xi + 10$$

$$= 2 \times 10^3 \left[10 \xi \right]_{2 \times 10^{-3}}^t + 10$$

$$= 2 \times 10^3 [50t - 0.02] + 10$$

$$i = 2 \times 10^4 t - 30$$

put, $t = 3 \text{ msec}$

$$i = 30A$$

$3 \rightarrow 5 \text{ msec}$

$$V = \frac{-10}{2 \times 10^{-3}} t + 50$$

$$V = -5 \times 10^3 t + 50$$

$$i = \frac{1}{2 \times 10^{-3}} \int_{3 \times 10^{-3}}^t -5 \times 10^3 \xi + 50 d\xi + 30$$

$$= 2 \times 10^3 \left[-5 \times 10^3 \frac{\xi^2}{2} \Big|_{3 \times 10^{-3}}^t + [50 \xi] \Big|_{3 \times 10^{-3}}^t + 30 \right]$$

$$= 2 \times 10^3 \left\{ \left[-5 \times 10^3 \frac{t^2}{2} + 22.5 \times 10^3 \right] + [50t - 0.15] \right\} + 30$$

$$i = -8 \times 10^6 t^2 + 1 \times 10^5 t - 225$$

put $t = 5 \text{ msec}$

$$i = 150A$$

$5 \rightarrow 6 \text{ msec}$

$$V = 0$$

$$i = 0$$

$$Q7.28) L = 1.5 \text{ mH}$$

$$i = 2 \times \sin 10^6 t \text{ mA}$$

$$\text{Take } 10^6 t = \theta$$

$$i = 2 \sin \theta \text{ mA}$$

$$0 \leq \theta \leq 2\pi$$

$$V = ?$$

$$V = L \frac{di}{dt}$$

$$= 1.5 \times 10^{-3} \frac{d}{dt} (2 \times \sin 10^6 t) \text{ m}$$

$$= 2 \times 1.5 \times 10^{-3} (\cos 10^6 t) \times 10^6 \text{ m}$$

$$V = 3 \cos \theta \text{ V}$$

$$P = vi$$

$$= (3 \cos \theta) (2 \sin \theta)$$

$$= 3 \cdot 2 \sin \theta \cos \theta$$

$$P = 3 \sin 2\theta \text{ mW}$$

$$W = \frac{1}{2} LI^2$$

$$W = \frac{1}{2} (1.5 \times 10^{-3}) (2 \sin \theta \text{ m})^2$$

$$W = 3 (1 - \cos 2\theta) \text{ nJ}$$

$$\text{Put } \theta = 0$$

V (V)	i (mA)	P (mW)	W (nJ)
V = 3	i = 0	P = 0	W = 0

$$\theta = \pi/2$$

V (V)	i (mA)	P (mW)	W (nJ)
V = 0	i = 2	P = 0	W = 6

$$\theta = \pi$$


$$V = -3 \quad | \quad i = 0 \quad | \quad P = 0 \quad | \quad W = 0$$

$$\theta = 3\pi/2$$

$$V = 0 \quad | \quad i = -2 \quad | \quad P = 0 \quad | \quad W = 6$$

$$\theta = 2\pi$$

$$V = 3 \quad | \quad i = 0 \quad | \quad P = 0 \quad | \quad W = 0$$

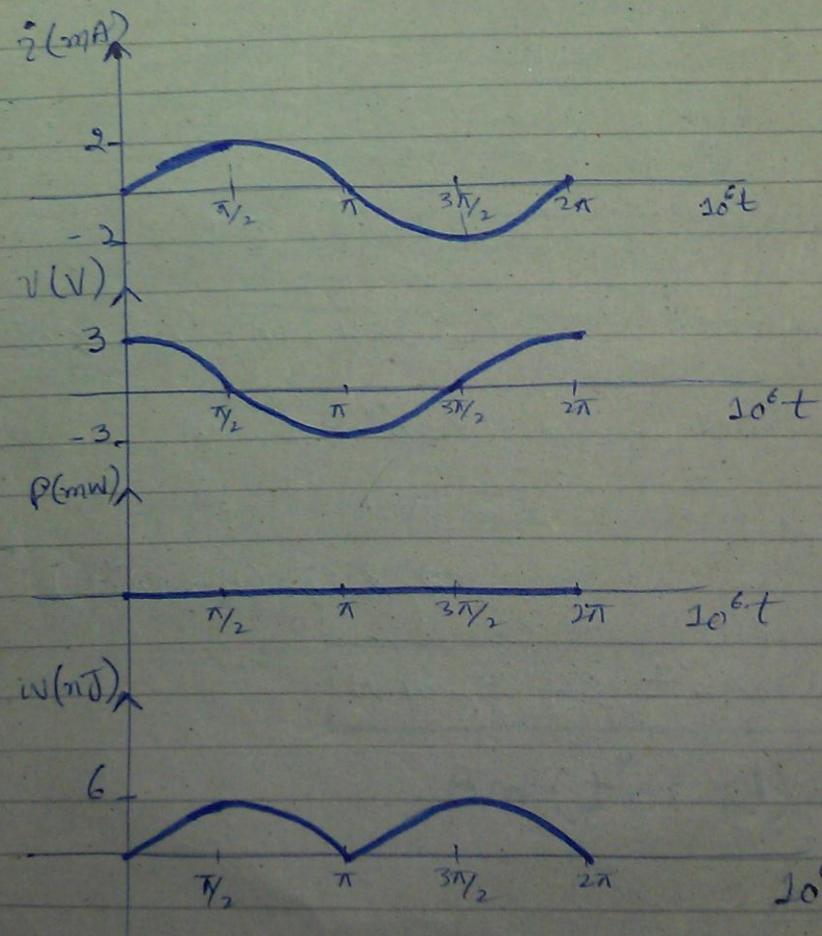


Q7.29)

$$\text{Given } i_L = 20 \sin(4 \times 10^4 t) \text{ mA}$$

$$i_S = ?$$

$$i_S = i_C + i_L$$

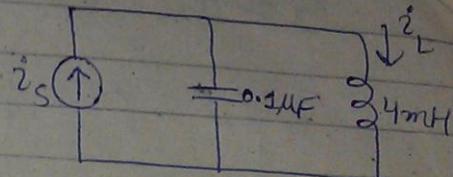

$$V_L = L \frac{di_L}{dt}$$

$$= 4 \times 10^{-3} \frac{d}{dt} 20 \sin(4 \times 10^4 t) \text{ mA}$$

$$= 4 \times 10^{-3} \times 20 \cos(4 \times 10^4 t) \cdot 4 \times 10^4$$

$$V_L = 3.2 \cos(4 \times 10^4 t) \text{ V}$$

$$V_L = V_C = V_S$$

$$i_C = C \frac{dV_C}{dt}$$

$$= 0.1 \times 10^{-6} \cdot \frac{d}{dt} (3.2 \cos 4 \times 10^4 t)$$

$$= 0.1 \times 10^{-6} \times 3.2 (-\sin 4 \times 10^4 t) \times 4 \times 10^4$$

$$i_C = 12.8 (-\sin 4 \times 10^4 t) \text{ mA}$$

$$i_S = i_L + i_C$$

$$i_S = 20 \sin(4 \times 10^4 t) - 12.8 \sin(4 \times 10^4 t)$$

$$i_S = \sin 4 \times 10^4 t \times 7.2 \text{ mA}$$

$$\text{Given } i_L = 20 \sin(6 \times 10^4 t) \text{ mA}$$

$$V_L = L \frac{di_L}{dt}$$

$$V_L = 4 \times 10^{-3} \frac{d}{dt} 20 \sin(6 \times 10^4 t)$$

$$= 4 \times 10^{-3} \times 20 \cos(6 \times 10^4 t) \times 6 \times 10^4$$

$$= 4800 \cos(6 \times 10^4 t) \text{ mV}$$

$$V_L = 4.8 \cos(6 \times 10^4 t) \text{ V}$$

$$i_C = C \frac{dV_C}{dt}$$

$$= 0.1 \times 10^{-6} \frac{d}{dt} (4.8 \cos(6 \times 10^4 t)) \text{ V}$$

$$= 0.1 \times 10^{-6} \times 4.8 (-\sin 6 \times 10^4 t) \times 6 \times 10^4$$

$$i_C = -2.8 \sin(6 \times 10^4 t) \text{ mA}$$


$$i_S = 20 \sin(6 \times 10^4 t) - 2.8 \sin(6 \times 10^4 t)$$

$$\boxed{i_S = 17.2 \sin 6 \times 10^4 t \text{ mA}}$$

Q7.30

a) $V_S = ?$

$$V_C = 10 \sin 10^4 t \text{ V}$$

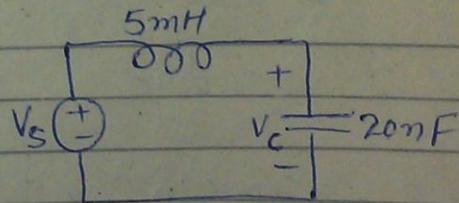

$$i_C = C \frac{dV_C}{dt}$$

$$= 20 \times 10^{-9} \frac{d}{dt} 10 \sin 10^4 t$$

$$i_C = 20 \times 10^{-9} \times 10 \cos(10^4 t) \times 10^4$$

$$i_C = 2 \cos(10^4 t) \text{ mA}$$

$$\text{As, } i_C = i_L = i_S$$

$$V_L = L \frac{di_L}{dt}$$

$$= 5 \times 10^{-3} \frac{d}{dt} (2 \cos 10^4 t) \times 10^{-3}$$

$$V_L = 5 \times 10^{-3} \times 2 \times 10^{-3} (-\sin 10^4 t) \times 10^4$$

$$V_L = -0.1 \sin(10^4 t) V$$

$$V_S = V_C + V_L$$

$$V_S = 10 \sin 10^4 t - 0.1 \sin 10^4 t$$

$$\boxed{V_S = \sin 10^4 t (9.9) V}$$

b)

$$V_C = 10 \sin 10^5 t V$$

$$i_C = C \frac{dV_C}{dt}$$

$$= 20 \times 10^{-9} \times \frac{d}{dt} 10 \sin 10^5 t$$

$$i_C = 20 \times 10^{-9} \times 10 \cos(10^5 t) \times 10^5$$

$$i_C = 0.02 \cos 10^5 t A$$

$$V_L = L \frac{di_L}{dt}$$

$$V_L = 5 \times 10^{-3} \frac{d}{dt} (0.02 \cos 10^5 t)$$

$$V_L = 10(-\sin 10^5 t) V$$

$$\begin{aligned} V_S &= V_C + V_L \\ &= 10 \sin 10^5 t - 10 \sin 10^5 t \end{aligned}$$

$$\boxed{V_S = 0 V}$$

7.3: Natural Response of RC & RL Circuits:

Q 7.31

$$\tau = ?$$

$$5 \times 10^{-3} \frac{dy(t)}{dt} + 2y(t) = 10^{-3} \frac{dx(t)}{dt} - x(t) \quad \textcircled{1}$$

$$\tau \frac{dy(t)}{dt} + y(t) = x(t)$$

◆ $\div \textcircled{1}$ by 2

$$\frac{5 \times 10^{-3}}{2} \frac{dy(t)}{dt} + y(t) = \frac{10^{-3}}{2} \frac{dx(t)}{dt} - \frac{1}{2} x(t)$$

$$\tau = \frac{5 \times 10^{-3}}{2} = 2.5 \times 10^{-3} \text{ s}$$

$$\beta = -\frac{1}{\tau} = -\frac{1}{2.5 \times 10^{-3}}$$

$$\boxed{\beta = -400 \text{ NP/sec}}$$

Q7.39)

$$V(t) = V(0) e^{-\frac{t}{\tau}}$$

$$V(1\mu s) = 12.28 V$$

$$V(7\mu s) = 3.7 V$$

a) $V(0) = ?$
 $\tau = ?$

$$12.28 = V(0) e^{-\frac{1 \times 10^{-6}}{\tau}} \quad \textcircled{1}$$

$$3.7 = V(0) e^{-\frac{7 \times 10^{-6}}{\tau}} \quad \textcircled{2}$$

$$\textcircled{1} \div \textcircled{2}$$

$$\frac{12.28}{3.7} = \frac{V(0)}{V(0)} \frac{e^{-\frac{1 \times 10^{-6}}{\tau}}}{e^{-\frac{7 \times 10^{-6}}{\tau}}}$$

$$3.3 = e^{\frac{6 \times 10^{-6}}{\tau}}$$

$$\ln 3.3 = \ln e^{\frac{6 \times 10^{-6}}{\tau}}$$

$$1.193 = \frac{6 \times 10^{-6}}{\tau}$$

$$\boxed{\tau = 5.02 \times 10^{-6} \text{ s}}$$

Put in $\textcircled{1}$ $-1 \times 10^{-6} / 5.02 \times 10^{-6}$

$$12.28 = V(0) e^{-\frac{1 \times 10^{-6}}{\tau}}$$

$$V(0) = 12.28 e^{0.2}$$

$$\boxed{V(0) = 15 V}$$

$$V(10\mu s) = ?$$

$$V(10 \text{ us}) = V(0) e^{-t/\tau}$$

$$\approx 10 \times 10^{-6} / 5 \times 10^{-6}$$

$$= 15 \text{ e}$$

$$= 15e^{-2} = 15/e^2$$

$$V(10 \text{ us}) = 2V$$

Q7.33)

$$i(t) = i(0) e^{-t/\tau}$$

$$t = ? \quad (6 \rightarrow 4 \text{ mA})$$

$$8 \rightarrow 2 \text{ mA}$$

$$t_e = 5.515 \text{ msec}$$

$$t_e = -\tau \ln \epsilon$$

$$t_p = -5.48 \ln(2-8)$$

$$= -5.48$$

$$5.45 = -\tau \ln(2-8)$$

$$5.45 = -\tau \ln \frac{2}{8}$$

$$\tau = 3.95$$

$$6 \rightarrow 4 \text{ mA}$$

$$t = -3.95 \ln(4-6)$$

$$t = -3.95 \ln \frac{4}{6}$$

$$t = 1.601 \text{ msec}$$

$$9 \rightarrow 1 \text{ mA}$$

$$E = \frac{1}{9}$$

$$t = -3.95 \ln\left(\frac{1}{9}\right)$$

$$t = 8.67 \text{ msec}$$

Q7.34) Solution = ?

$$2 \frac{dy(t)}{dt} + y(t) = 5e^{-t}$$

$$y(0) = 10$$

÷ by 2

$$\frac{dy(t)}{dt} + \frac{1}{2}y(t) = \frac{5}{2}e^{-t} \quad (1)$$

For Integrating Factor

$$e^{\int \frac{1}{2} dt} = e^{\frac{t}{2}} = c^{t/2}$$

$$\begin{aligned} (1) \Rightarrow & \int_{t_1}^{t_2} \frac{dy(t)}{dt} + \frac{1}{2} e^{t/2} y(t) = \frac{5}{2} e^{-t/2} \cdot e^{-t} \\ \text{product rule} \quad & \frac{d}{dt} (e^{t/2} \cdot y(t)) = \frac{5}{2} e^{-t/2} \end{aligned}$$

Integrating both sides

$$y(t)e^{t/2} = \frac{5}{2} e^{-t/2} + C$$

$$y(t) e^{t/2} = -5e^{-t/2} + c \quad (2)$$

using initial condition
 $y(0) = 10$
put $t=0$

$$\begin{aligned} (2) \Rightarrow y(0)e^0 &= -5e^0 + c \\ 10 &= -5 + c \\ c &= 15 \end{aligned}$$

put in (2)

$$y(t) e^{t/2} = -5e^{-t/2} + 15$$

$$y(t) = -5 \frac{e^{t/2}}{e^{-t/2}} + \frac{15}{e^{-t/2}}$$

$$= -5e^{-t} + 15e^{-t/2}$$

$$= 5(e^{-t} + 3e^{-t/2})$$

$$y(t) = 5(3e^{-t/2} - e^{-t})$$

(Q7.35)

$$2 \frac{d}{dt} y(t) + 3y(t) = x(t) \quad (1)$$

$$x(t) = 2te^{-t}, \quad y(0) = 5$$

put $x(t)$ in (1)

$$2 \frac{d}{dt} y(t) + 3y(t) = 2te^{-t}$$

÷ by 2

$$\frac{d}{dt} y(t) + \frac{3}{2} y(t) = t e^{-t} \quad (2)$$

$$e^{\int s dt} = e^{\int \frac{3}{2} dt} = e^{\frac{3}{2} t}$$

$$\times \quad (2) \text{ by } e^{\frac{3}{2} t}$$

$$e^{\frac{3}{2} t} \frac{d}{dt} y(t) + \frac{3}{2} y(t) e^{\frac{3}{2} t} = t e^{-t} \cdot e^{\frac{3}{2} t}$$

$$\frac{d}{dt} (y(t) \cdot e^{\frac{3}{2} t}) = t e^{t/2}$$

Integrating both sides

$$y(t) e^{\frac{3}{2} t} = t \cdot \frac{e^{t/2}}{\frac{1}{2}} - \int \frac{e^{t/2}}{\frac{1}{2}} dt$$

$$= 2t e^{t/2} - 2 \int e^{t/2} dt$$

$$y(t) e^{\frac{3}{2} t} = 2t e^{t/2} - 4 e^{t/2} + C \quad (3)$$

$$\text{put } y(0)=5 \text{ & } t=0$$

$$5 e^0 = -4 e^0 + C$$

$$C = 9$$

put in (3)

$$y(t)e^{3/2t} = 2te^{t/2} - 4e^{t/2} + 9$$

$$y(t) = 2t \frac{e^{t/2}}{e^{3/2t}} - 4 \frac{e^{t/2}}{e^{3/2t}} + \frac{9}{e^{3/2t}}$$


$$\boxed{y(t) = 2e^{-t}(t-2) + 9e^{-3/2t}}$$

Q7.36)

$$w(0) = 450 \mu J$$

$$v(2ms) = 0$$

$$V_s = V(\infty) = ?$$

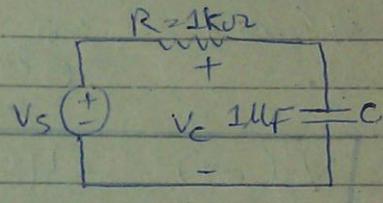

$$V(t) = [y(0) - y(\infty)] e^{-t/\tau} + y(\infty)$$

$$\tau = R \times C = 1 \times 10^{-6} \times 1 \times 10^3$$

$$\tau = 1 \times 10^{-3}$$

$$w = \frac{1}{2} (V^2(0))$$

$$450 \times 10^{-6} = \frac{1}{2} (1 \times 10^{-6}) V^2(0)$$

$$V(0) = 30V$$

$$V(t) = [30 - y(\infty)] e^{-t/1 \times 10^{-3}} + y(\infty)$$

$$V(2ms) = 0$$

$$0 = [30 - y(\infty)] e^{-2 \times 10^{-3} / 1 \times 10^{-3}} + y(\infty)$$

$$D = \frac{30}{e^2} - \frac{V(\infty)}{e^2} + V(\infty)$$

$$V(\infty) = V(\infty)$$

$$V(\infty) + V(\infty) = \frac{30}{e^2}$$

$$V(\infty) \left[1 + \frac{1}{e^2} \right] = \frac{30}{e^2}$$

$$V(\infty) = \frac{30}{e^2} \times \frac{e^2}{-e^2 + 1}$$

$$\boxed{V(\infty) = -4.7V}$$


Q7.37)

$$i(0) = ?$$

$$w = ?$$

$$i(\infty) = i = 25mA$$

$$i(40\mu s) = 0$$

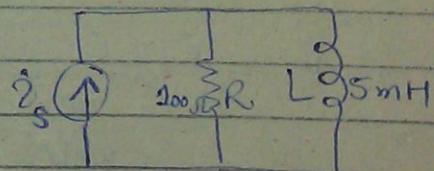

$$T = \frac{L}{R} = 5 \times 10^{-5}$$

$$i(t) = [i(0) - i(\infty)] e^{-t/T} + i(\infty)$$

$$i(40\mu s) = 0$$

$$0 = [i(0) - 25 \times 10^{-3}] e^{-40 \times 10^{-6} / 5 \times 10^{-5}} + 25 \times 10^{-3}$$

$$0 = 0.449 i(0) - 0.0112 + 25 \times 10^{-3}$$

$$0.449 i(0) = -0.0137$$

$$i(0) = -0.0306A$$

$$i(0) = -30.6 \text{ mA}$$

$$w = \frac{1}{2} L I^2$$

$$= \frac{1}{2} (5 \times 10^{-3}) (-30.6 \times 10^{-3})^2$$

$$w = 2.34 \mu \text{J}$$

Q7.38) a)

$$v = 5 (1 + e^{-t/\tau}) \text{ V}$$

$$v = 5 e^{-t/\tau} + 5$$

$$\begin{aligned} \text{Transient} &= [y(0) - y(\infty)] e^{-t/\tau} \\ &= 5 e^{-t/\tau} \end{aligned}$$

$$\text{Steady state} = y(\infty) = 5$$

$$y(\infty) = 5$$

$$\begin{aligned} y(0) - y(\infty) &= 5 \\ y(0) - 5 &= 5 \end{aligned}$$

$$y(0) = 10$$

$$\begin{aligned} y_{\text{natural}} &= y(0) e^{-t/\tau} \\ &= 10 e^{-t/\tau} \end{aligned}$$

$$y_{\text{forced}} = y(\infty) (1 - e^{-t/\tau})$$
$$= 5(1 - e^{-t/\tau})$$

$$y_{\text{forced}} = 5 - 5e^{-t/\tau}$$

b)

$$v = 5(2 - e^{-t/\tau})v$$

$$v = -5e^{-t/\tau} + 10$$

$$v_{\text{transient}} = -5e^{-t/\tau}$$

$$v_{\text{steady state}} = 10$$

$$y(\infty) = 10$$

$$y(0) - y(\infty) = -5$$

$$y(0) - 10 = -5$$

$$y(0) = 5$$

$$y_{\text{natural}} = y(0)e^{-t/\tau}$$

$$y_{\text{natural}} = 5e^{-t/\tau}$$

$$y_{\text{forced}} = y(\infty)[1 - e^{-t/\tau}]$$

$$y_{\text{forced}} = 10[1 - e^{-t/\tau}]$$
$$y_{\text{forced}} = 10 - 10e^{-t/\tau}$$

$$v = 5(3e^{-t/\tau} + 2) V$$

$$v = 15e^{-t/\tau} + 10$$

$$y(\infty) = 10$$

$$y(0) - y(\infty) = 15$$

$$y(0) - 10 = 15$$

$$y(0) = 25$$

$$y_{\text{transient}} = 15e^{-t/\tau}$$

$$y_{\text{s.s.}} = 10$$

$$y_{\text{natural}} = 25e^{-t/\tau}$$

$$y_{\text{forced}} = 10(1 - e^{-t/\tau})$$

$$\underline{\underline{Q7.39(a)}} \quad i = 5(2 - 3e^{-t/\tau}) A$$

$$i = -15e^{-t/\tau} + 10$$

$$i_{\text{transient}} = -15e^{-t/\tau}$$

$$i_{\text{s.s.}} = 10$$

$$y(\infty) = 10$$

$$y(0) - y(\infty) = -15$$

$$y(0) = -5$$

$$y_{\text{natural}} = y(0) e^{-t/\tau}$$

$$i_{\text{natural}} = -5 e^{-t/\tau}$$

$$\begin{aligned} i_{\text{forced}} &= y(\infty) (1 - e^{-t/\tau}) \\ &= 10 (1 - e^{-t/\tau}) \end{aligned}$$

b) $i = 5 e^{-t/\tau}$

$$i_{\text{transient}} = 5 e^{-t/\tau}$$

$$i_{\text{S.S.}} = 0$$

$$y(\infty) = 0$$

$$y(0) - y(\infty) = 5$$

$$y(0) = 5$$

$$i_{\text{natural}} = 5 e^{-t/\tau}$$

c) $i_{\text{forced}} = i(\infty) [1 - e^{-t/\tau}]$

$$i_{\text{forced}} = 0$$

