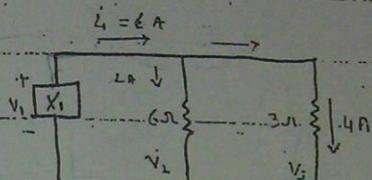


Chapter no. 2.

Resistive Circuits

2.1

Resistance



2.1

Solution:

α).

$$V_s = 3 \times 4 = 12 \text{ V}$$

$$R_{\text{eq}} = \frac{1}{6} + \frac{1}{3} = \frac{3+6}{3+6} = \frac{9}{9} = 1$$

As 3.n and 6.n are in parallel, so

$$V_3 = V_2 = V_1 = 12 \text{ V}$$

50

$$V_1 = 12 \text{ V}$$

$$-V_1 = -i R_{\text{env}}$$

$$I = \frac{V_i}{R_{eq}} = \frac{12}{2} = 6A$$

$$i_1 = 6.0$$

PHOTO STATE
U.S.T.

Вч

KCL


$$i_2 = 2A \downarrow$$

3

$$\text{Power released} = 12 \times 6 = 72 \text{ watt}$$

$$\text{Power absorbed} = 12 \times 4 + 12 \times 2 = 48 + 24 = 72 \text{ Watt}$$

Hence law of power conservation proved.

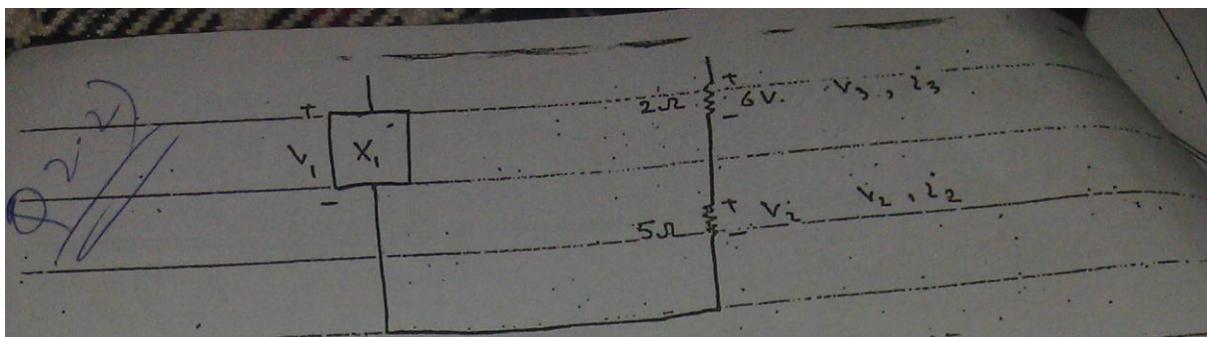

$$V_3 = 6V$$

$$R_3 = 2\Omega$$

$$i_3 = \frac{V_3}{R_3} = \frac{6}{2} = 3A$$

As in series

$$i_1 = i_2 = i_3$$

$$i_2 = 3A$$

$$i_1 = 3A$$

$$R_{eq} = 2 + 5 = 7\Omega$$

$$V_1 = i_1 R_{eq} = 3 \times 7 = 21V$$

By KVL

$$V_1 - V_2 - V_3 = 0$$

$$21 - V_2 - 6 = 0$$

$$V_2 = 15V$$

$$\text{Power released} = 21 \times 3 = 63W$$

$$\text{Power absorbed} = 6 \times 3 + 15 \times 3 = 63W$$

$$\Rightarrow \text{Power released} = \text{Power absorbed}$$

Khaleel Chahid
B0-06-CF-11

2-3

a)

Given:

$$P_1 = 10 \text{ W}, P_2 = 1 \text{ W}, P_3 = 1/3 \text{ W}$$

$$R = 1 \times 10^3 \Omega$$

Solution:

We know

$$P = Vi = i^2 R = \frac{V^2}{R}$$

So,

$$P_1 = i_1^2 R$$

$$P_1 = \frac{V^2}{R}$$

$$\Rightarrow i_1^2 = \frac{P_1}{R}$$

$$i_1 = \sqrt{\frac{P_1}{R}}$$

$$P_1 R = V^2$$

$$V = \sqrt{P_1 R} = \sqrt{10 \times 10^3}$$

$$i_1 = \sqrt{\frac{10}{100 \times 10^3}} = \sqrt{\frac{1}{10^5}}$$

$$V = \sqrt{10000}$$

$$i_1 = \frac{1}{\sqrt{10}} \text{ Amp} = 0.1 \text{ Amp}$$

$$V_1 = 100 \text{ V}$$

Similarly

$$P_2 = i_2^2 R$$

$$P_2 = \frac{V^2}{R}$$

$$i_2 = \sqrt{\frac{P_2}{R}}$$

$$V_2 = \sqrt{P_2 R}$$

$$i_2 = \frac{1}{\sqrt{1000}} \text{ Amp} = 31.6 \text{ mA}$$

$$V_2 = \sqrt{1 \times 10^3}$$

$$V_2 = \sqrt{1000} \text{ V} = 31.6$$

Also

$$P_3 = i_3^2 R$$

$$P_3 = \frac{V^2}{R}$$

$$i_3 = \frac{P_3}{R}$$

$$V_3 = \sqrt{P_3 R}$$

$$i_3 = \frac{1/8 \times 10^{-3}}{10} \text{ Amp} = 11.2 \text{ mA}$$

$$V_3 = \sqrt{1/8 \times 10^3} \text{ V} = 11.2 \text{ V}$$

$$b) R = 10 \Omega$$

$$As \quad i = \frac{P}{R}$$

$$V = \sqrt{PR}$$

$$i_1 = \sqrt{\frac{10}{10}} = 1$$

$$i_1 = 1 \text{ Amp}$$

$$V_1 = \sqrt{10 \times 10} = 10 \text{ V}$$

$$V_1 = 10 \text{ V}$$

$$i_2 = \sqrt{\frac{1}{10}}$$

$$i_2 = \frac{1}{\sqrt{10}} \text{ Amp} = 0.316 \text{ A}$$

$$V_2 = \sqrt{1 \times 10} = \sqrt{10} = 3.16 \text{ V}$$

$$V_2 = \sqrt{10} \text{ V} = 3.16 \text{ V}$$

$$i_3 = \frac{1/8}{10}$$

$$i_3 = \frac{1/8 \times 10^{-3}}{10} \text{ Amp} = 11.2 \text{ mA}$$

$$V_3 = \sqrt{1/8 \times 10}$$

$$V_3 = \sqrt{1/8 \times 10} \text{ V} = 1.12 \text{ V}$$

4) Given:

$$P = 1 \text{ W} \quad V = 12 \text{ V}$$

As

$$P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = \frac{144}{1}$$

$$R = 144 \Omega$$

$$P = 1 \text{ W} \quad V = 220 \text{ V}$$

$$R = \frac{V^2}{P} = \frac{(220)^2}{1} = 48400$$

$$R = 48400 \Omega$$

$$c) R = 2 \times 10^3 \Omega, I = 10 \times 10^3 A$$

$$P = ? \quad V = ?$$

$$P = I^2 R V$$

$$P = 100 \times 10^{-6} \times 2 \times 10^3$$

$$P = 200 \times 10^{-3}$$

By Haileb Shabot
36-CE-11

$$P = 200 \text{ mW}$$

$$P = \frac{V^2}{R} \Rightarrow V = \sqrt{PR}$$

$$V = \sqrt{200 \times 10^{-3} \times 2 \times 10^3}$$

$$V = \sqrt{400}$$

$$V = 20 V$$

2.5

$$a) l = 1 \text{ m}, d = 1 \times 10^3 \text{ m}, \delta = 0.5 \times 10^3 \text{ m}$$

$$\rho = 2.8 \times 10^6 \text{ ohm-cm}$$

$$\rho = 2.8 \times 10^8 \text{ m}$$

Solution:

$$R = \rho \frac{l}{A}$$

$$R = \frac{2.8 \times 10^8 \times 1}{3.14 \times 25 \times 10^8}$$

$$R = 35 \times 10^3 \Omega \quad 2275 \Omega$$

$$R = 35 \text{ m}\Omega$$

$$\beta = \frac{10 \times 5 \times 10^{-12}}{1 \times 10^{-3}}$$

$$\beta = 50 \times 10^{-9} \text{ N m}$$

$$C = 50 \times 10^{-7} \text{ N cm}$$

By Hooke's law
Hooke's law
Hooke's law

$$l = 15 \text{ mm} = 1 \text{ cm} \quad (\text{of cylinder})$$

$$d = 1 \text{ mm} = 0.1 \text{ cm} \quad (\text{of cylinder})$$

$$r = 0.05 \text{ cm}$$

$$l = 3 \times 10^{-3} \text{ m} \quad (\text{of material to be coated})$$


$$R = 100 \text{ N} \quad (\text{required resistance})$$

* Film thickness = ?

volume of cylinder =

surface area of cylinder = $2\pi rl$
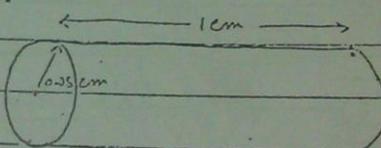
$$S = 0.31415 \text{ cm}^2 \quad \text{cylinder}$$



→ We know that

$$R = \frac{C \cdot l}{A} \quad (\text{of applied material})$$

$$100 = \frac{3 \times 10^{-3}}{A} \times 1 \quad A = 0.03 \times 10^{-3} \text{ cm}^2$$

$$A = 0.03 \times 10^{-3} \text{ cm}^2$$

∴ This is the cross-sectional area of the material wire

which is to be coated

on the given cylinder

* volume of applied material $V = A \times l$

$$V = 0.03 \times 10^{-3} \times 1 = 0.03 \times 10^{-3} \text{ cm}^3$$

Now we want to apply this volume V (of applied material)

b) on the surface of the cylinder. So from this that we can find the thickness of the film.

For this

$$\rightarrow \text{thickness of film} = \frac{\text{Volume of applied material}}{\text{surface area of cylinder}}$$

KHALID PHOTO STATE

U.E.T

~~COMPOSER~~
Composing And Photo Copy
Student Services Centre
U.E.T. LHR.

$$V = 0.03 \times 10^{-3} \text{ cm}^3$$

$$S = 0.31415 \text{ cm}^2$$

$$= 0.09549 \times 10^{-3} \text{ cm}$$

$$= 0.0955 \times 10^{-5} \text{ m}$$

$$= 0.955 \times 10^{-6} \text{ m}$$

$$\boxed{\text{Thickness of film} = 0.955 \mu\text{m}}$$

2.8

$$2 \quad (a) R_1 = 5 \Omega, R_2 = ?, R_3 = 20 \Omega, \text{ when } R_{eq} = 3 \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

①

$$R_{eq} = \frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2} = \frac{5 \times 20 \times R_2}{20 R_2 + 100 + 5 R_2}$$

$$3 = \frac{100 R_2}{100 + 25 R_2} \Rightarrow 300 + 75 R_2 = 100 R_2$$

$$R_2 = \frac{300}{25} = 12 \Omega$$

$$\boxed{R_2 = 12 \Omega}$$

$$(b) \text{ when } R_{eq} = 2 \Omega \text{ put in ① we get}$$

$$2 = \frac{5 \times 20 \times R_2}{20 R_2 + 100 + 5 R_2}$$

$$100 R_2 + 50 R_2 = 200$$

$$R_2 = \frac{200}{50} = 4 \Omega$$

$$\boxed{R_2 = 4 \Omega}$$

21

2.9

$$R_1 = 5 \text{ kN} \pm 5\%$$

a)

$$R_2 = 20 \text{ kN} \pm 10\%$$

$$R_{LT} = 5\% = \frac{5 \times 5}{100} = 0.25 \text{ kN} \quad (\because R_{LT} = R_1 \text{ tolerance})$$

$$R_{LT} = 10\% = \frac{20 \times 10}{100} = 2 \text{ kN}$$

In series

$$R_s = R_1 + R_2 = 5 + 20 = 25 \text{ kN}$$

$$\chi = R_{LT} + R_{LT} = 0.25 + 2 = 2.25 \text{ kN}$$

$$\chi\% = \frac{2.25}{25} \times 100 = 9\%$$

$$\chi\% = 9\%$$

Hence

$$R_{eq} = R_s + \chi\%$$

$$R_{eq} = 25 \text{ kN} \pm 9\%$$

b) In parallel:

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_p} = \frac{R_1 + R_2}{R_1 R_2} = \frac{25}{100} = \frac{25}{100}$$

$$2250$$

$$= 222.2 \text{ A} \quad R_p = \frac{100}{25} = 4 \text{ kN}$$

and

$$\chi = \frac{R_{LT} R_{LT}}{R_{LT} + R_{LT}} = \frac{0.25 \times 2}{2.25} = 0.222$$

$$\chi\% = \frac{0.222}{4} \times 100 = 5.5\%$$

$$R_{eq} = R_p \pm \chi\% = 4 \text{ kN} \pm 5.5\%$$

$$R_{eq} = 4 \text{ kN} \pm 5.5\%$$

2.10

a) $R_1 = mR$, $R_2 = \frac{R_1}{m-1}$ $m > 1$

By connecting them in parallel

~~$R_1 \parallel R_2$~~

$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} \quad (\because R_1 = mR)$$


$$= \frac{mR \cdot \frac{mR}{m-1}}{mR + \frac{Rm}{m-1}} = \frac{mR^2}{m^2R - mR + mR} \\ = \frac{mR^2}{m^2R - mR} = \frac{mR^2}{(m-1)mR}$$

$$R_1 \parallel R_2 = R$$

Hence proved.

b)

Q.11.

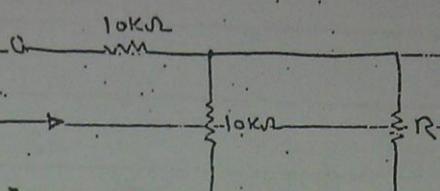

a) when $R = 30\text{ kN}$

$$R_{eq} = 10 + \left[\frac{10 \times 30}{10 + 30} \right]$$

$$R_{eq} = 10 + 7.5$$

$$R_{eq} = 17.5 \text{ kN}$$

b) $R = ?$ when $R_{eq} = 18 \text{ kN}$

$$R_{eq} = 10 + \left[\frac{10 \times R}{10 + R} \right]$$

$$18 = 10 + \left[\frac{10R}{10 + R} \right]$$

$$8(10 + R) = 10R$$

$$80 + 8R = 10R$$

$$2R = 80$$

$$R = 40 \text{ kN}$$

c) $R = ?$ when $R_{eq} = R$

$$R_{eq} = 10 + \left[\frac{10R}{10 + R} \right]$$

$$(R - 10) = \frac{10R}{10 + R}$$

$$(R - 10)(R + 10) = 10R$$

$$R^2 - 100 = 10R$$

$$R^2 - 10R - 100 = 0 \Rightarrow a=1, b=-10, c=-100$$

$$R = \frac{10 \pm \sqrt{100 + 400}}{2}$$

$$R = \frac{10 \pm \sqrt{500}}{2}$$

$$R = \left(\frac{1.23}{2}\right) R_1$$

$$R = 0.615 R_1 \quad \text{(i)}$$

b) when $R_1 = 10 \text{ kV}\Omega$

Find $R = ?$

Putting in Eq. (i)

$$R = 0.615 \times 10$$

$$R = 6.15 \text{ kV}\Omega$$


Q.13

$$R = 10 \text{ kV}\Omega$$

a) when $R_{eq} = 7.5 \text{ kV}\Omega$

$$10+10+10 = 30$$


$$\frac{30 \times 10}{30} = 10$$

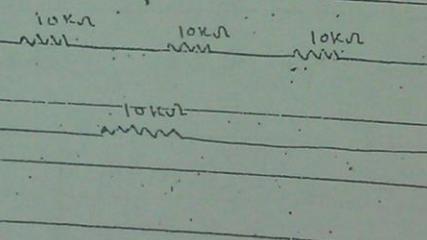


b) when $R_{eq} = 15 \text{ kV}\Omega$

$$\frac{10 \times 10}{10 + 10} = 5$$


$$10 + 5 = 15$$

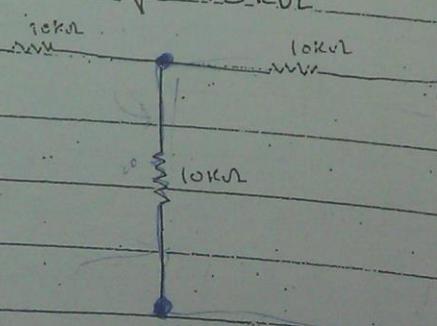

c) when $R_{eq} = 25 \text{ kV}\Omega$

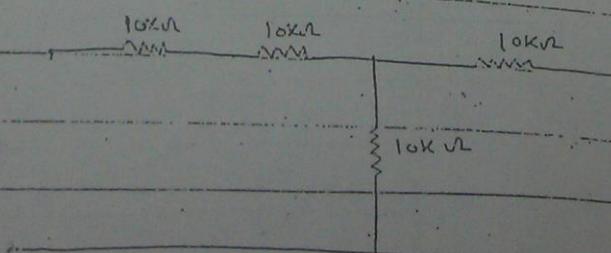

2.14

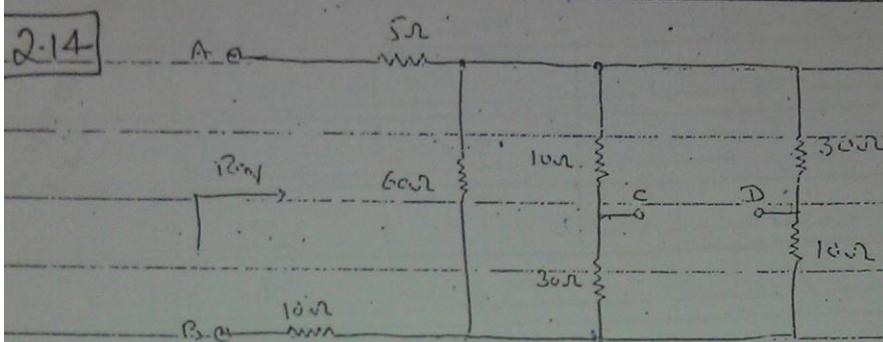


$$R_{eq} = 5 + \left[\frac{1}{60} + \frac{1}{40} + \frac{1}{40} \right]^{-1} + 10$$

$$R_{eq} = 5 + \left[\frac{2+3+3}{120} \right]^{-1} + 10$$

$$R_{eq} = 5 + 15 + 10$$

$$R_{eq} = 30\Omega$$

b) when C and D short circuited

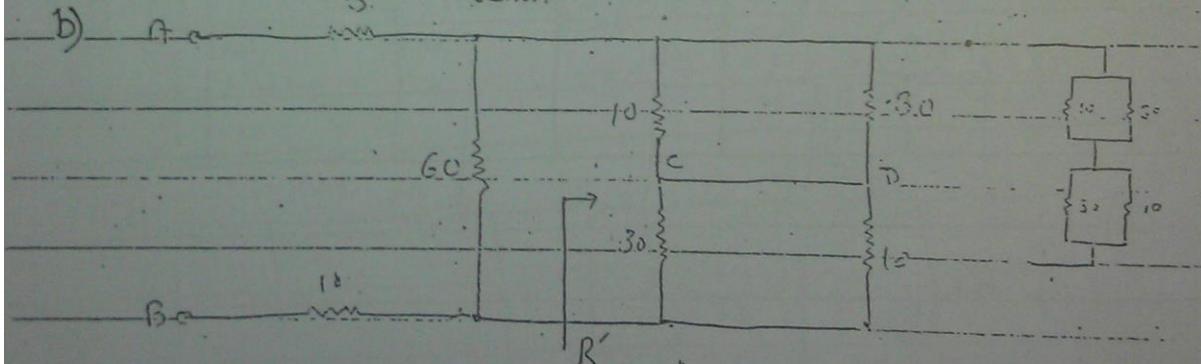

$$R' = \left[\frac{1}{10} + \frac{1}{30} \right]^{-1} + \left[\frac{1}{30} + \frac{1}{10} \right]^{-1}$$

$$R' = 7.5 + 7.5 = 15$$

$$R_{eq3} = \left(\frac{1}{20} + \frac{1}{60} \right)^{-1}$$

$$R_{eq3} = \frac{20 \times 60}{20 + 60} = \frac{1200}{80}$$

$$R_{eq2} = 15 \Omega$$

$$\rightarrow R_{eq} = R_{eq3} + 10 = 25 \Omega$$

$$R_{eq} = 10 + 15 = 25 \Omega$$

b)

$$R_{eq} = 25 \Omega \quad V = 15 \text{ V}$$

$$P = \frac{V^2}{R} = \frac{225}{25}$$

$$P = 9 \text{ watt}$$


2.16

Proportionality Analysis $\Rightarrow X$ (Not done)

By Majeed Shahid

06-CE-11

2.17

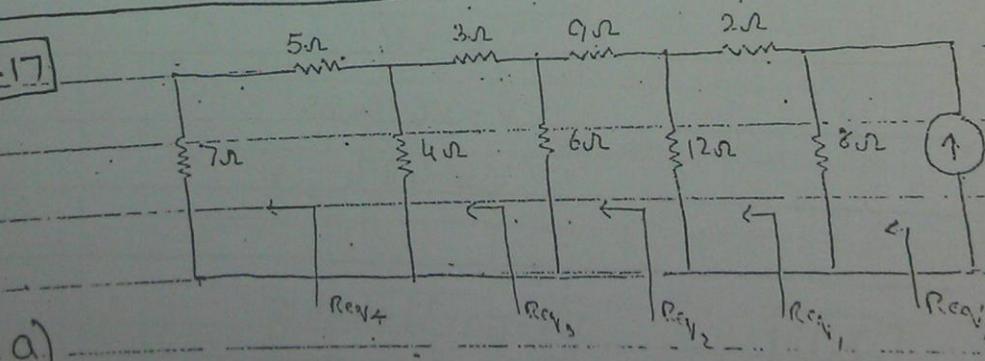

$$R_{eq1} = \left(\frac{1}{10} + \frac{1}{12} \right)^{-1}$$

$$R_{eq1} = \frac{10 \times 12}{10 + 12} = \frac{120}{22} = 5.45$$

نے حسیں شاید اے۔

اے۔ میں کوئی 0.1

لے کر ترددیں لے سکے۔

$$R_{eq_2} = \left[\frac{1}{14.45} + \frac{1}{6} \right]^{-1}$$

$$\Rightarrow R_{eq_2} = \frac{14.45 \times 6}{14.45 + 6} = \frac{86.7}{20.45} = 4.24$$

$$R_{eq_3} = \left[\frac{1}{7.24} + \frac{1}{4} \right]^{-1}$$

$$\Rightarrow R_{eq_3} = \frac{7.24 \times 4}{7.24 + 4} = \frac{28.96}{11.24} = 2.57$$

$$R_{eq} = \left[\frac{1}{7.57} + \frac{1}{7} \right]^{-1}$$

$$R_{eq} = \frac{7.57 \times 7}{7.57 + 7} = \frac{52.99}{15.57} = 4.03 \Omega$$

$$R_{eq} = 4.03 \Omega$$

b)

$$R_{eq} = 4.03 \Omega, I = 12 \text{ A}$$

$$V = ?$$

$$V = IR$$

$$V = 12 \times 4.03$$


$$V = 48.4 \text{ V}$$

2.18

Proportionality

X (Not done)

2.19

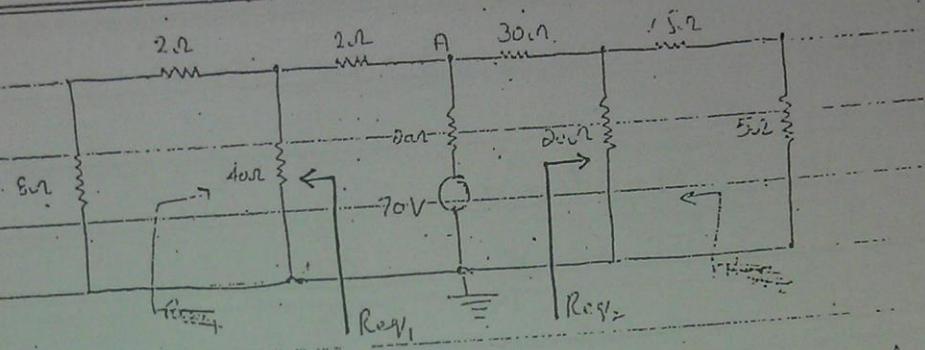

First we reduce resistances left of $\frac{70V}{R_{eq}}$.

$$R_{eq_1} = \left[\frac{1}{10} + \frac{1}{40} \right]^{-1} + 2$$

$$R_{eq_1} = \frac{10 \times 40}{10 + 40} + 2$$

$$R_{eq_1} = 8 + 2 = 10 \Omega$$



Now we reduce resistances from right of $\frac{70V}{R_{eq}}$.

$$R_{eq_2} = \left[\frac{1}{20} + \frac{1}{20} \right]^{-1} + 3.0$$

$$R_{eq_2} = \frac{20 \times 20}{20 + 20} + 3.0$$

$$R_{eq_2} = 10 + 3.0 = 13 \Omega$$

Now circuit becomes:-

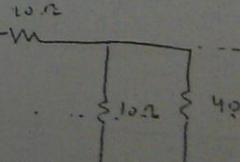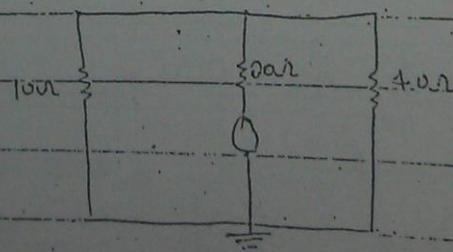

$$R_{eq} = \left[\frac{1}{10} + \frac{1}{4} \right]^{-1} + 2.0$$

$$R_{eq} = 8 + 20 = 28 \Omega$$

$$V = 70 \text{ V}$$

$$I = \frac{V}{R_{eq}} = \frac{70}{28}$$


$$I = 2.5 \text{ A}$$

2.20

2.21

} X (Not done)


2.22

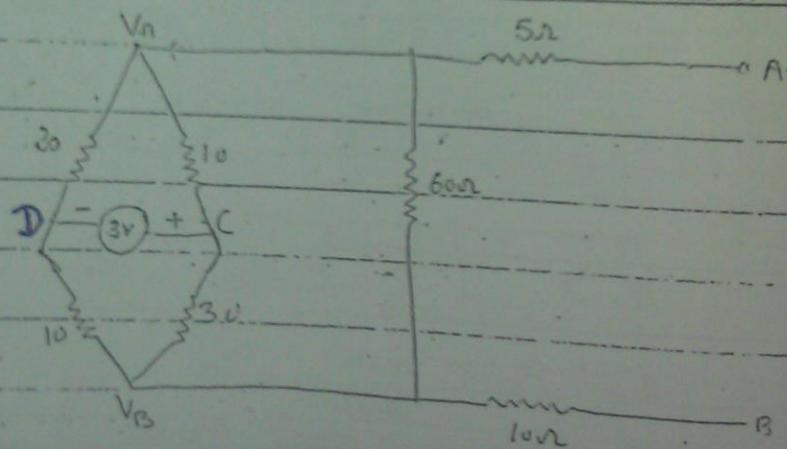

$$V_A = \frac{30}{40} \times 3 = 2.25 \text{ V}$$

$$V_B = \frac{10}{40} \times 3 = 0.75 \text{ V}$$
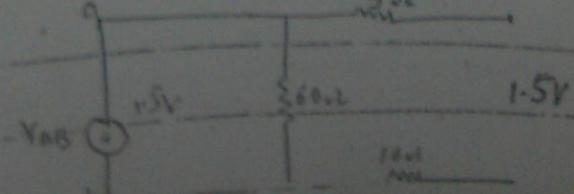
$$V_{AB} = V_A - V_B = 2.25 - 0.75 = 1.5 \text{ V}$$




Voltage and Current Dividers.

2.24

$$R_1 = 15 \text{ k}\Omega, R_2 = 3 \text{ k}\Omega$$

a) $V_o = ?$ if $V_i = 12 \text{ V}$

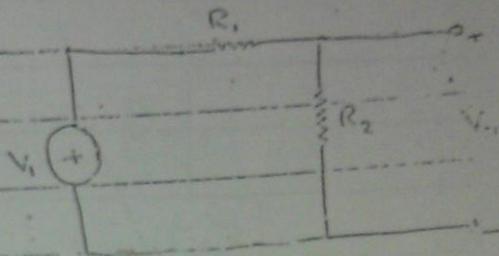

$$V_o = \frac{3}{15+3} \times 12$$

$$V_o = \frac{1}{6} \times 12 = 2 \text{ V}$$

b) find $V_i = ?$ when $V_o = 1 \text{ V}$

$$V_o = \frac{R_2}{R_1 + R_2} \times V_i$$

$$1 = \frac{3}{18} \times V_i$$

By Khalid Shahid
03/CE-11.

$$G = V_o$$

$$V_i = 6 \text{ V}$$

2.25

$$R_1 = 1 \text{ k}\Omega \pm 5\%$$

$$R_2 = 3 \text{ k}\Omega \pm 5\%$$

$$\text{Gain} = \frac{V_o}{V_i} = \frac{1}{1 + \frac{R_1}{R_2}} = \frac{R_2}{R_1 + R_2}$$

$$R'_1 = 1000 \times 5 = 50 \text{ }\Omega$$

$$R'_2 = 3000 \times 5 = 150 \text{ }\Omega$$


$$R_1 + R_2 = 4 \text{ k}\Omega \pm 200 \text{ }\Omega$$

Voltage and Current Dividers.

24

$$R_1 = 15 \text{ k}\Omega, R_2 = 3 \text{ k}\Omega$$

a) $V_o = ?$ if $V_i = 12 \text{ V}$

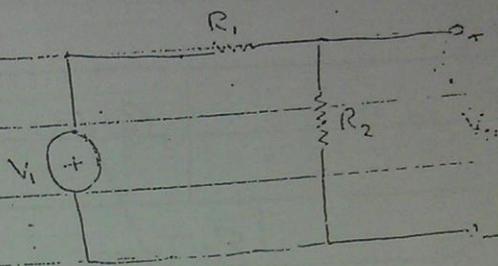

$$V_o = \frac{3}{15+3} \times 12$$

$$V_o = \frac{1}{6} \times 12 = 2 \text{ V}$$

b) Find $V_i = ?$ when $V_o = 1 \text{ V}$

$$V_o = \frac{R_2}{R_1 + R_2} \times V_i$$

$$1 = \frac{3}{18} \times V_i$$

By class 2b Shabid
CE-11

$$6 = V_i$$

$$V_i = 6 \text{ V}$$

2.25

$$R_1 = 1 \text{ k}\Omega \pm 5\%$$

$$R_2 = 3 \text{ k}\Omega \pm 5\%$$

$$\text{Gain} = \frac{V_o}{V_i} = \frac{1}{1 + \frac{R_1}{R_2}} = \frac{R_2}{R_1 + R_2} \quad (1)$$

$$R'_1 = \frac{1000 \times 5}{100} = 50 \text{ }\Omega$$

$$R'_2 = \frac{3000 \times 5}{100} = 150 \text{ }\Omega$$

$$R_1 + R_2 = 4 \text{ k}\Omega + 200 \text{ }\Omega$$

$$4R_1 + 8 = 20$$

$$4R_1 = 12$$

$$R_1 = 3 \text{ k}\Omega$$

c) $V_o = 5V$, $P_{V_1} = 50 \times 10^3 \text{ mW}$, $R_1 = ?$, $R_2 = ?$
 $V_1 = 10V$

$$P_{V_1} = \frac{(V_1)^2}{R}$$

$$50 \times 10^3 = \frac{100}{R_1 + R_2} \quad (i)$$

Also

$$V_o = \frac{R_1}{R_1 + R_2} \times V_1$$

$$5 = \frac{10R_1}{R_1 + R_2}$$

Wd. 26/CE-11
Haseeb Shahid

$$5R_1 + 5R_2 = 10R_1$$

$$5R_2 = 5R_1$$

$$R_2 = R_1 \quad (ii)$$

From Eq. (i)

$$50 \times 10^3 (R_1 + R_2) = 100$$

$$R_1 + R_2 = 2 \times 10^3 \quad (iii)$$

From Eq. (ii) put $R_2 = R_1$ in Eq. (iii)

$$R_1 + R_1 = 2 \times 10^3$$

$$R_1 = 1 \times 10^3$$

$$R_1 = R_2 = 1 \text{ k}\Omega$$


2.27

$$V_1 = 12 \text{ V}, P_{V_1} = 100 \text{ mW}$$

$$V_0 = 5 \text{ V}$$

We Know

$$P_{V_1} = \frac{V_1^2}{R_1}$$

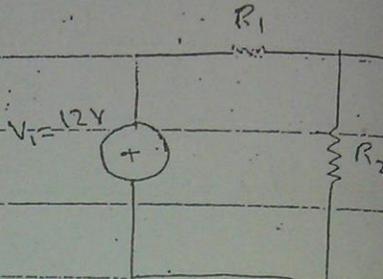

$$\frac{100 \times 10^{-3}}{R_1 + R_2} = 144$$

$$R_1 + R_2 = 1.44 \times 10^3 \quad (\text{I})$$

Also

$$V_0 = \frac{R_2}{R_1 + R_2} \times V_1$$

$$5(R_1 + R_2) = 12R_2$$

$$5R_1 + 5R_2 = 12R_2$$

$$R_1 = \frac{7}{5}R_2$$

put in Eq: (i)

(ii)

$$R_2 + \frac{7}{5}R_2 = 1.44 \times 10^3$$


$$\frac{12}{5}R_2 = 1.44 \times 10^3$$

$$R_2 = 600 \Omega$$

put in Eq: (ii)

$$R_1 = \frac{7}{5} \times 600$$

$$R_1 = 840 \Omega$$

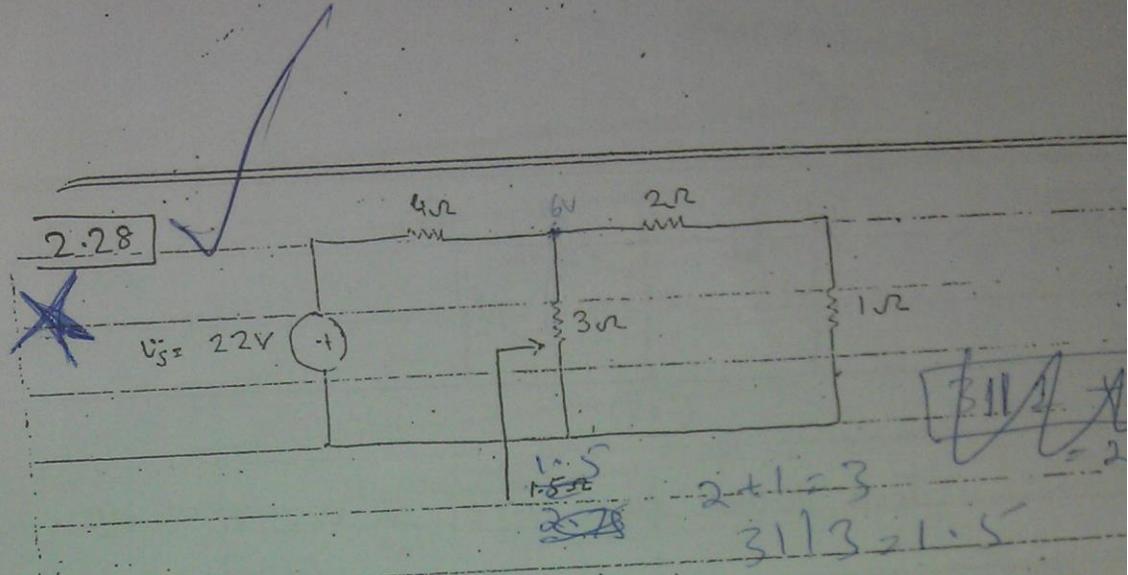

$$\begin{aligned}
 V_4 &= \frac{4}{2.75+4} \times 22 \quad V_4 = \frac{4}{1.5+4} \times 22 (V_S) \quad \checkmark \\
 V_4 &= 13V \quad \boxed{V_4 = 16V} \quad \text{across } 4\Omega \\
 V_2 &= \frac{2}{2+1} \times 13 \\
 V_2 &= 8.6 = 9V \quad \dots \\
 V_{1.5} &= \frac{1.5}{1.5+4} \times 22 \quad \checkmark \\
 V_{1.5} &= 6V \quad \boxed{V_{1.5} = 6V}
 \end{aligned}$$


A circuit diagram for problem 1.5. It features a 6V DC voltage source in series with a 4Ω resistor. This combination is in parallel with a 2Ω resistor. A 3Ω resistor is connected in series with the 2Ω resistor. A dependent current source, labeled i_1 , is connected in parallel with the 3Ω resistor. The dependent source is controlled by a voltage across the 3Ω resistor, with a value of $2i_1$. The circuit is completed with a 1Ω load resistor at the bottom right.

$$V_{2n} = \frac{2}{2+1} \times 96 \quad V_2 = \frac{2}{2+1} \times 6 = \frac{2}{3} \times 6 = 4 \text{ V}$$


$$\sqrt{2}r = 4V \quad \boxed{v_2 = 4V}$$

By Hattie Shick
76-C.E.-11


2.29

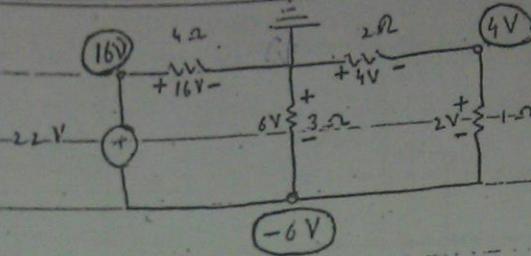

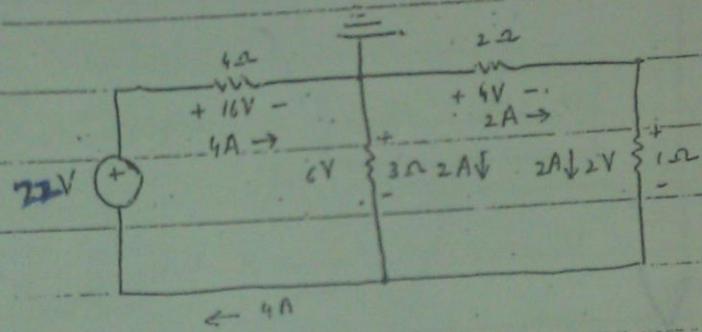Took Helped from [2.28] in $V_1 = 16V$ $V_2 = 4V$
 (By Black colour)



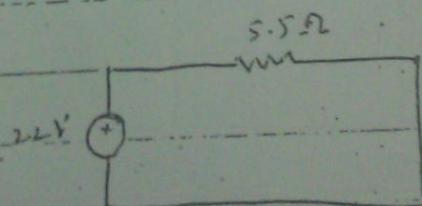By Ohm's law we can write branch currents
 (By Black colour)



$$P = \frac{V^2}{R_{\text{eq}}} = \frac{(22)^2}{5.5} = 88W$$

Power delivered by source = $P = 88W$

KHALID PHOTO STATE
U.E.T

230

$$V_s = 220 \text{ V}$$

$$V_o = 132 \text{ V}$$

$$V_s = 220 \text{ V}$$

R_1

$\approx R_2$

$$V_o = 132 \text{ V}$$

a) If $R_2 = 11$ with R_1 then $V_o = 60 \text{ V}$

From 1st circuit

$$V_o = \frac{R_2}{R_1 + R_2} \times V_s$$

$$132(R_1 + R_2) = 220R_2$$

$$132R_1 + 132R_2 = 220R_2$$

$$132R_1 = 88R_2$$

$$R_1 = \frac{2}{3} R_2$$

KHALID PHOTO STATE
U.E.T
Composing And Photo Copy
Student Services Centre
U.E.T. LHR

(i)

Now

$$V_s = 220 \text{ V}$$

R_1

$\approx 16 \text{ k}\Omega$

$$V_o = 60 \text{ V}$$

$$V_o = \frac{\frac{10 \times 10^3 \cdot R_2}{10 \times 10^3 + R_2} \times 220}{R_1 + \frac{10 \times 10^3 \cdot R_2}{10 \times 10^3 + R_2}}$$

$$V_o = \frac{10 \times 10^3 R_2}{(10 \times 10^3 + R_1) R_1 + 10 \times 10^3 R_2} \times 220$$

$$V_o = \frac{10 \times 10^3 R_2}{10 \times 10^3 R_1 + R_1 R_2 + 10 \times 10^3 R_2} \times 220$$

$$60 = \frac{10 \times 10^3 R_2}{10 \times 10^3 R_1 + R_1 R_2} \times 220$$

$$\frac{3}{11} = \frac{10 \times 10^3 R_2}{10 \times 10^3 R_1 + R_1 R_2}$$

$$30 \times 10^3 R_1 + 3 R_1 R_2 = 110 \times 10^3 R_2 \quad (i)$$

7.8.0m Eq. (i) put $R_1 = \frac{2}{3} R_2$ in Eq. (ii)

$$30 \times 10^3 \left(\frac{2}{3} R_2 \right) + 3 \left(\frac{2}{3} R_2 \right) R_2 = 110 \times 10^3 R_2$$

$$20 \times 10^3 R_2 + 2 R_2^2 = 110 \times 10^3 R_2$$

$$2 R_2^2 = 90 \times 10^3 R_2$$

$$R_2 = 45 \text{ k}\Omega$$


put in Eq. (i)

$$R_1 = \frac{2}{3} \times 45 \text{ k}\Omega$$

COMPOSING AND PRINTING
STUDENT SERVICES
U.E.T. LHR

$$R_1 = 30 \text{ k}\Omega$$

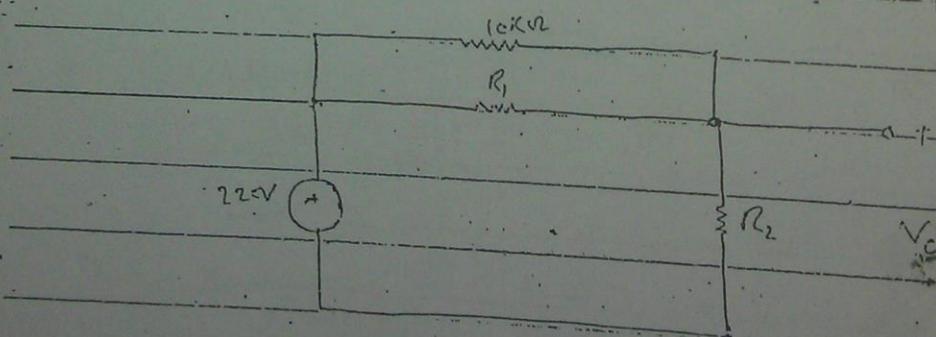b) $R_1 = 30 \text{ k}\Omega$; $R_2 = 4.5 \text{ k}\Omega$, $V_o = ?$, $V_i = 220 \text{ V}$



$$V_o = \frac{R_2}{R_1 + 10 \times 10^3 + R_2} \times 220$$

$$V_o = R_2 (R_1 + 10 \times 10^3)$$


$$V_o = \frac{45 (10 \times 10^3 + 30)}{10 \times 10^3 \times 30 + 45 (10 \times 10^3 + 30)} \times 220$$

$$V_o = \frac{45 (46)}{300 + 1800} \times 220$$

$$V_o = \frac{1800}{2100} \times 220$$

$$V_o = 188.5 V$$

2.31

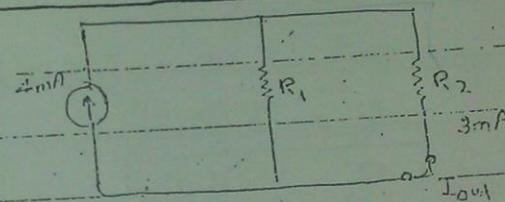

$$I_{out} = \frac{(R_1 \parallel R_2)}{R_2} \times I_{in}$$

$$I_{out} = \frac{R_1 \times R_2}{(R_1 + R_2) R_2} \times I_{in}$$

$$3 \times 10^3 = \frac{R_1}{R_1 + R_2} \times 4 \times 10^3$$

$$3R_1 + 3R_2 = 4R_1$$

$$R_1 = 3R_2$$

(i)

Also

$$P = I_{in}^2 R_p$$

KHALID PHOTO STATE
UET
KHALID PHOTO STATE
UET
Composing And Photo Copy
Student Services Centre
J.E.T. LHR

BD. Haib Shabid
06-CE-11

$$G_{cmW} = (4m)^2 \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$G_{cm} (R_1 + R_2) = 16m^2 R_1 R_2$$

$$G_0 R_1 + G_0 R_2 = 16m R_1 R_2$$

$$G_0 (3R_2) + G_0 R_1 = 16m (3R_1)(R_2)$$

$$240R_2 - 48mR_2$$


$$R_2 = 5\text{ k}\Omega$$

put in Eq. (i)

$$R_1 = 3(5\text{ k})$$

$$R_1 = 15\text{ k}\Omega$$


2.32

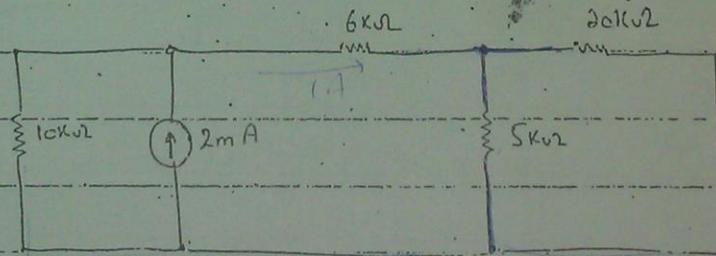


$$R_{eq1} = 6 + \left[\frac{1}{5} + \frac{1}{20} \right]^{-1}$$

$$R_{eq1} = 6 + \left[\frac{5 \times 20}{5 + 20} \right] = 6 + \frac{100}{25} = 6 + 4 = 10\text{ k}\Omega$$

Now circuit is.

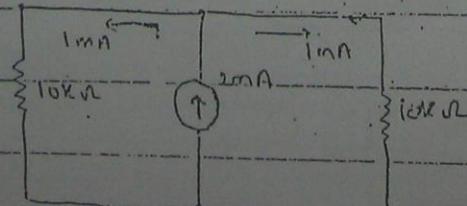

$$I_1 = \frac{R_1}{R_1 + R_2} I_1$$

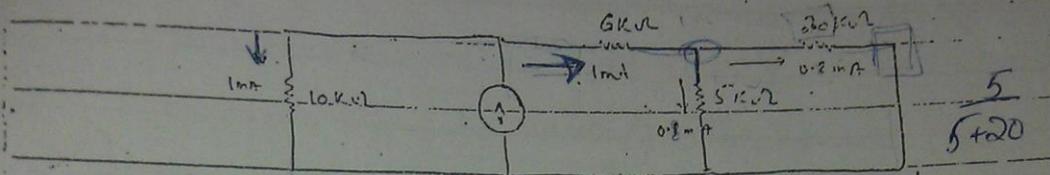

By current divider

$$I_1 = \frac{R_1}{R_1 + R_2}$$


$$= \frac{10}{10 + 5}$$

$$= \frac{10}{15} \left(\frac{R_1}{R_1 + R_2} \right)$$

$$= \frac{5}{5+20} \times 1 \times 10^3 \quad I_1 = \frac{20}{25} \times 10^3$$

$$I_1 = 0.8 \text{ mA}$$

Q.33

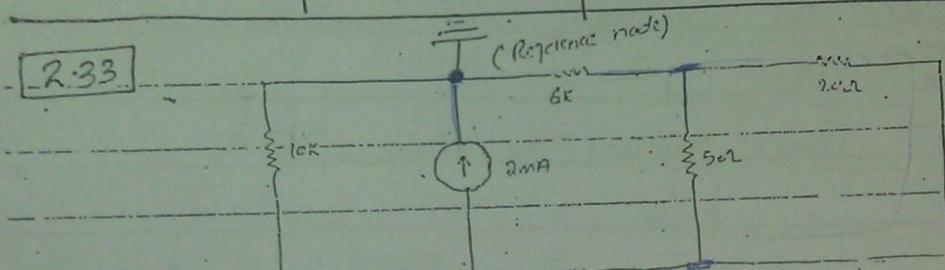


$$R_{eq1} = 6 + \left[\frac{1}{5} + \frac{1}{20} \right]$$

$$R_{eq2} = 6 + \left[\frac{5 \times 20}{5+20} \right]$$

$$R_{eq} = 6 + 4 = 10 \text{ k}\Omega$$

So, circuit becomes:

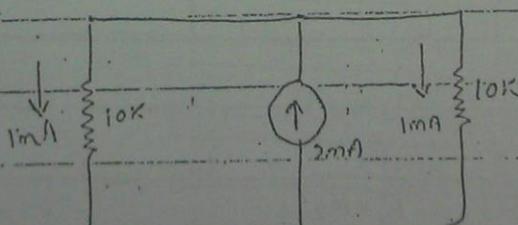

$$R_{eq} = \left[\frac{1}{10} + \frac{1}{10} \right]^{-1} = \frac{10 \times 10}{10+10} = \frac{100}{20} = 5 \text{ k}\Omega$$

$$R_{eq} = 5 \text{ k}\Omega$$


$$V = IR_{eq}$$

$$V = 2mA \times 5k\Omega$$

$$V = 10mV = 10V$$

Also
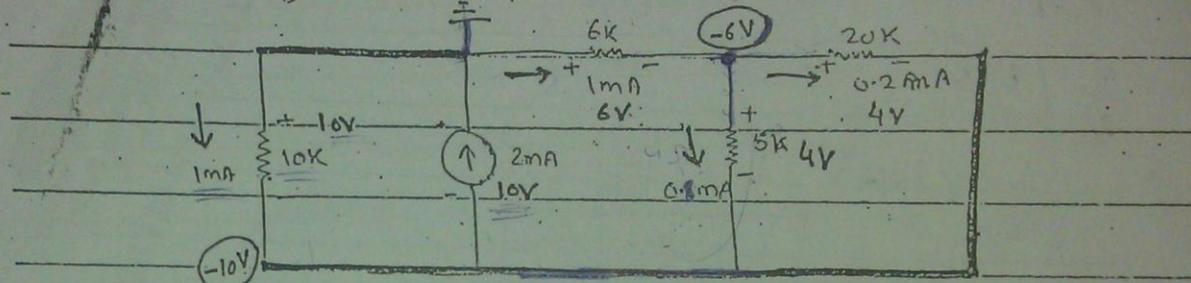
$$I_5 = 0.8 \text{ Amp} ; I_{20} = 0.2 \text{ Amp}$$




*) All voltages are measured using ohm's law
and

Power released by source = V_i

$$= 10 \times 2mA$$

$$\text{Power released} = 20mW$$

2.34

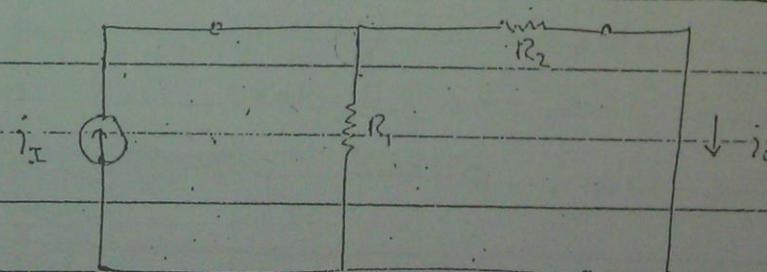

$$i_o = \frac{R_1}{R_1 + R_2} \times i_x$$


$$2 = \frac{R_1}{R_1 + R_2} \times 6$$

$$2R_1 + 2R_2 = 6R_1$$

$$2R_2 = 4R_1$$

$$R_2 = 2R_1$$

(i)

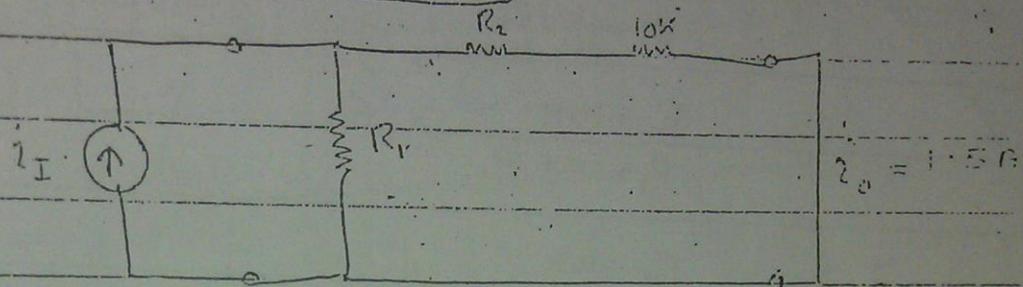

$$i_o = \frac{R_1}{R_1 + 10k + R_1} \times i_I$$

$$1.5 = \frac{R_1}{R_1 + R_2 + 10} \times 6$$

$$1.5R_1 + 1.5R_2 + 15 = 6R_1$$

$$1.5R_2 + 15 = 4.5R_1$$

putting $R_2 = 2R_1$ Eq. (i)

$$1.5(2R_1) + 15 = 4.5R_1$$


$$3R_1 + 15 = 4.5R_1$$

$$1.5R_1 = 15$$

$$R_1 = 10k\Omega$$

$$R_2 = 20k\Omega$$

b)

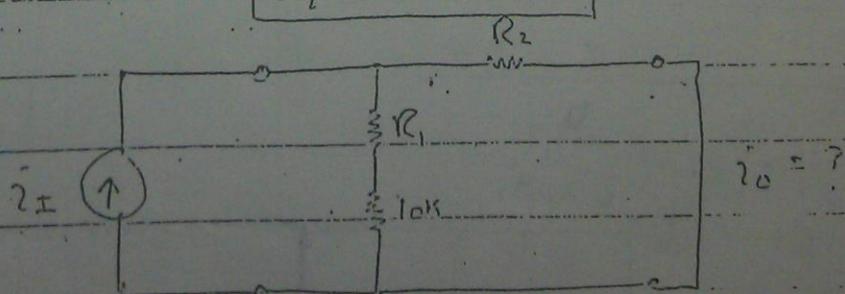

$$i_0 = \frac{R_1 + 10k}{R_1 + 10k + R_2} \times i_1$$


$$i_0 = \frac{R_1 + 10k}{R_1 + 10k + 2R_1} \times 6 \quad (\because R_2 = 2R_1)$$

$$i_0 = \frac{R_1 + 10k}{3R_1 + 10k} \times 6$$

$$i_0 = \frac{20}{40} \times 6 \quad (\because R_1 = 10k, R_2 = 20k)$$

$$i_0 = 3.0A$$

Q.35

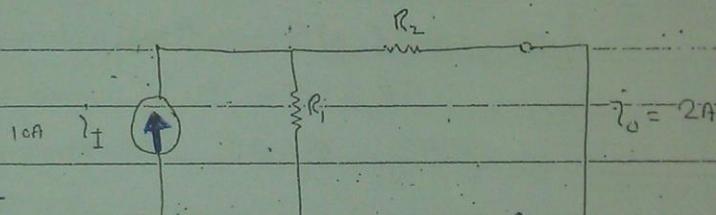

$$R_p = R_1 = \frac{2.4R_1}{2.4 + R_1}$$


Croffent divider

$$10 = \frac{\left(\frac{2.4R_1}{2.4 + R_1}\right)R_1}{\left(\frac{2.4R_1}{2.4 + R_1}\right) + R_2} \times 10 \times \frac{i_1}{R_1 + R_2} \times i_1$$

$$i_1 = \frac{R_1}{R_2} \times \frac{(R_1 + R_2)2.4}{R_1 + R_2 + 2.4}$$

$$2R_1 + 2R_2 = 10R_1$$
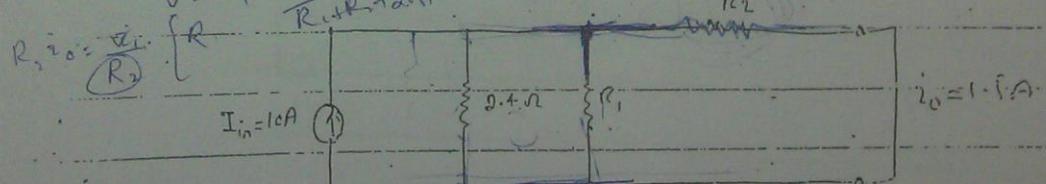
$$V = i_1 \times R_1 \times \frac{2.4}{R_1 + R_2 + 2.4} \times R_2 = 4R_1$$



$$R_1 = 15V$$

$$R_2 = 45V$$

$$\frac{R_P}{R_P + R_2} \times I_2$$

$$1.5/R_2 = \left[\frac{1}{2.4 + R_1 + R_2} \right] \times 2.4$$

$$R_2 I_2 = \left[\frac{R_1 + R_2 \times 2.4}{R_1 + R_2 + 2.4} \right] \times 10$$

$$1.5(R_2 - (R_1 + R_2 + 2.4)) = R_1 + R_2 \times 2.4$$

~~$$1.5R_1 R_2 + 3.6R_2 + 1.5R_2^2 = 2.4R_1 R_2$$~~

~~$$1.5R_1 + 3.6R_2 - 2.4R_1 R_2 = 4R_1$$~~

~~$$R_2 (1.5R_1 + 3.6 - 2.4R_1) + (R_1 + 4R_1 + 2.4) = 12.4R_1 - 2.4$$~~

~~$$1.5(4R_1) + 3.6 - 0.24(R_1) = 0$$~~

~~$$R_1 = 0.2 \sqrt{6R_1^2 + 24R_1^2 + 2.4R_1} = 4R_1^2 \cdot 2.4$$~~

~~$$R_2 = 0.8 \sqrt{6R_1^2 + 24R_1^2 - 6R_1^2 + 2.4R_1} = 2.4$$~~

~~$$26R_1^2 + 2.4R_1 - 24 = 0$$~~

~~$$13R_1^2 + 1.2R_1 - 12 = 0$$~~

$$R_1 = \frac{-1.2 \pm \sqrt{144 - 624}}{26}$$

$$R_1 = \frac{-1.2 \pm \sqrt{623.56}}{26}$$

$$R_1 = \frac{-1.2 + 25}{26}$$

$$R_1 = \frac{23.75}{26}$$

$$R_1 = 1.2 \sqrt{2}$$

$$R_1 = \frac{-1.2 - 25}{26}$$

Neglecting

$$R_2 = 4R_1$$


$$R_2 = 4(1)$$

$$R_2 = 4 \text{ k}\Omega$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 4 \text{ k}\Omega$$

2.36

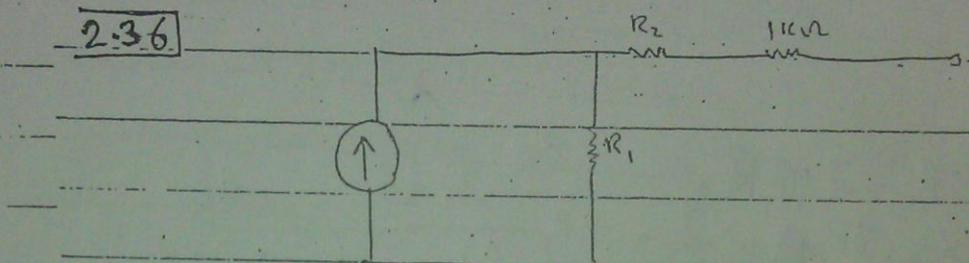

$$[2] \quad I_1 = 5 \text{ mA} \quad ; \quad i_1 = 1 \text{ mA}$$

$$i_2 = \frac{R_1}{R_1 + R_2} \times i_1$$

$$I_1 = \frac{R_1}{R_1 + R_2} \times 5$$

$$R_1 + R_2 = 5R_1$$

$$R_2 = 4R_1$$

(i)

KHALID PHOTO STA
U.E.T

$$0.75 = \frac{R_1}{R_1 + 1 + R_2} \times 5$$

$$0.75R_1 + 0.75 + 0.75R_2 = 5R_1$$

$$0.75 + 3R_1 = 4.25R_1$$

$$R_2 = 4R_1$$

$$0.75 = 1.25R_1$$

$$R_2 = 4(0.6)$$

$$R_1 = 0.6 \text{ k}\Omega$$

$$I_1 = 0.1 \text{ mA}$$

KHALID PHOTO STA
U.E.T

KHALID PHOTO STATE

For v_o

Q3)

$R = \left(\left(2R_1 + R_L \right)^{-1} + R_2^{-1} \right)^{-1}$

2 $R = R_2 \left(2R_1 + R_L \right)$

$2R_1 + R_1 + R_2$

KHALID PHOTO STATE
U.E.T

$v_R = \frac{R}{2R_1 + R} v_I$

$\frac{R_2 (2R_1 + R_L)}{(2R_1 + R_L + R_2)} v_I$

$2R_1 + R_2 (2R_1 + R_L) / (2R_1 + R_L + R_2)$

$\frac{R_2 (2R_1 + R_L)}{2R_1 (2R_1 + R_2 + R_L) + R_2 (2R_1 + R_L)} v_I$

$\frac{R_2 (2R_1 + R_L)}{4R_1^2 + 2R_1 R_2 + 2R_1 R_L + 2R_1 R_2 + R_2 R_L} v_I$

$v_R = \frac{R_2 (2R_1 + R_L)}{4R_1^2 + 4R_1 R_2 + 2R_1 R_L + R_2 R_L} v_I$


$v_o = \frac{R_L}{2R_1 + R_2} \times v_R$

$\frac{R_L}{(2R_1 + R_2)} \frac{R_2 (2R_1 + R_L)}{(4R_1^2 + 4R_1 R_2 + 2R_1 R_L + R_2 R_L)} v_I$

$U_2 = U_1 (0.01)$

$10 = 2.4 \times 10$

(b)

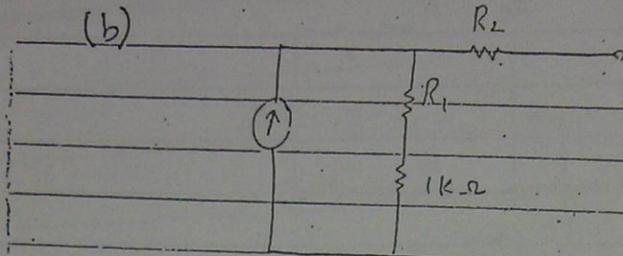

Mr. Haider Altaf
B/A ob-C E-14


$$2V_0 = R_L + 1 \times 5$$

$$R_L + 1 + R_1$$

$$\frac{1.6}{4} \times 5 = 2 \text{ mA}$$

$$I_0 = 2 \text{ mA}$$

[2.37] (a)

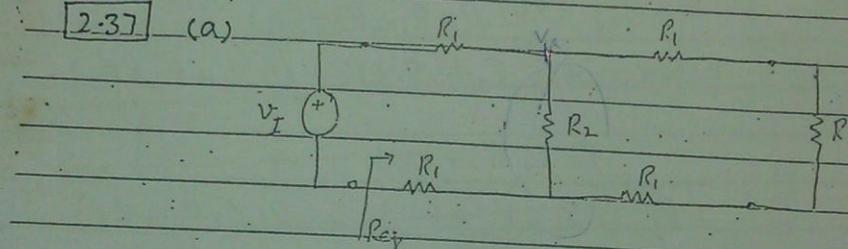

$$R_{eq} = \left((2R_1 + R_L)^{-1} + R_2^{-1} \right)^{-1} + 2R_1$$

$$R_2 = \frac{R_2(2R_1 + R_L)}{2R_1 + R_L + R_2} + 2R_1$$

$$R_{eq} = R_L$$

$$\frac{(R_L - 2R_1)}{2R_1 R_L + R_L^2 + R_1 R_2} (2R_1 + R_L + R_2) - R_2 (2R_1 + R_L)$$

$$-4R_1^2 - 2R_1 R_2 = 0$$

$$R_L^2 - 4R_1^2 - 2R_1 R_2 = 2R_1 R_2$$

$$R_1^2 = 4R_1(R_1 + R_2)$$



$$R_L^2 = 4R_1(R_1 + R_2)$$

①

$$\frac{V_o}{V_i} = \frac{R_2 R_L}{4R_1^2 + 4R_1 R_2 + 2R_1 R_L + R_2 R_L}$$

$$\text{from } ① \quad R_1^2 = 4R_1^2 + 4R_1 R_2$$

$$\frac{V_o}{V_i} = \frac{R_2 R_L}{R_L^2 + 2R_1 R_L + R_2 R_L}$$

$$\frac{V_o}{V_i} = \frac{R_2}{R_L + 2R_1 + R_2} \quad ②$$

$$(b) \quad R_2 = 600 \Omega$$

$$\frac{V_o}{V_i} = 0.5 \frac{V}{V}$$

$$R_1 = ? \quad \& \quad R_2 = ?$$

putting in ① & ②

$$360000 = 4R_1(R_1 + R_2)$$

$$90,000 = R_1^2 + R_1 R_2$$

$$R_1^2 + R_1 R_2 = 90,000 \quad ①'$$

$$0.5 = \frac{R_2}{600 + 2R_1 + R_2}$$

$$300 + R_1 + 0.5R_2 = R_2$$

$$R_1 - 0.5R_2 = 300 \quad ②'$$

$$R_1 = 2R_2 + 600 \quad \text{put in } ①'$$

$$R_1^2 + 2R_1 R_2 + 600R_1 = 90,000$$

$$3R_1^2 = 89400$$

$$R_1^2 = 29800$$

$$3R_1^2 + 600R_1 - 90,000 = 0$$

$$R_1^2 + 200R_1 - 30,000 = 0 \quad ③'$$

$$R_i = \frac{-200 \pm \sqrt{40,000 + 120,000}}{2}$$


$$R_1 = 100$$

$$R_1 = 100 \Omega$$

put in ②

$$R_2 = 800 \Omega$$

2.38

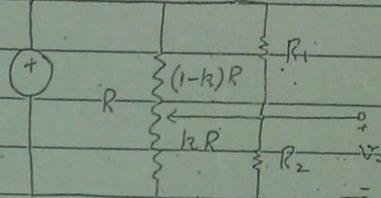


$$(a) R_1 = R_2 = \infty$$

$$V_O = \frac{R}{R + (1-R)R} V_I$$

$$\frac{V_O}{V_I} = R \quad \text{Sathe}$$

graph will be a straight line

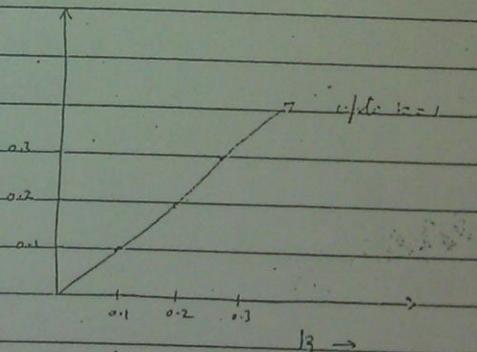

$$(b) R_1 = \infty, R_2 = 0.1R$$

$$(\text{say}) R_1' = \frac{(0.1R)(kR)}{0.1R + kR} = \frac{0.1kR}{0.1 + k}$$

$$V_O = \frac{0.1kR}{0.1 + k} = 0.1kR$$

$$(1-k)R + \frac{0.1kR}{0.1 + k} = (1-k)R(0.1 + k) + 0.1kR$$

$$112 = 4(0.1k)$$

$$k = 0.112$$

$$112 = 4(0.1k)$$

$$112 = 4(0.1k)$$

KHALID PHOTO STATE
Composing And Photo Copy
Student Services Centre
I.E.T. LHR

$$= 0.1/2$$

$$0.1 + k - 0.1k - k^2 + 0.1k$$

$$\left| \begin{array}{l} \frac{V_o}{V_I} = \frac{0.1k}{0.1 + k - k^2} \end{array} \right|$$

k	0	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1
$\frac{V_o}{V_I}$	0	0.05	0.07	0.09	0.11	0.13	0.17	0.22	0.30	0.47	1

Plot yourself

$$(c) R_1 = 0.1R, R_2 = 0.2$$

$$R'_1 = \frac{(0.1R)(1-k)R}{0.1R + (1-k)R} = \frac{(0.1 - 0.1k)R}{1.1 - k}$$

$$\frac{V_o}{V_I} = \frac{R'_1}{kR + R'_1} = \frac{(0.1 - 0.1k)R}{kR + (0.1 - 0.1k)R} = \frac{(0.1 - 0.1k)R}{(1.1 - k)R}$$

$$\frac{V_o}{V_I} = \frac{(0.1 - 0.1k)R}{(1.1 - k)kR + (0.1 - 0.1k)R} = \frac{0.1 - 0.1k}{1.1k - k^2 + 0.1 - 0.1k}$$

$$= \frac{0.1 - 0.1k}{0.1 + k - k^2}$$

$$\left| \begin{array}{l} \frac{V_o}{V_I} = \frac{0.1(1-k)}{0.1 + k - k^2} \end{array} \right|$$

Plot graph yourself

$$(d) R_1 = R_2 = 0.1R$$

$$R'_1 = \frac{0.1(1-k)R}{1.1 - k}$$

$$R'_2 = \frac{0.1(k)R}{0.1 + k}$$

$$\frac{V_o}{V_I} = \frac{R'_1 + R'_2}{R'_1 + R'_2}$$

given above

LIPPHOTO STATE
U.E.T

Hand Photo Copy
Services

KHALID PHOTOS
U.E.T

Composing And Photo Copy
Services
U.E.T. LHR

$$\frac{0.1kR}{(0.1+k)}$$

$$\frac{0.1kR}{(0.1+k)} + \frac{(0.1)(1-k)R}{(1-k)}$$

$$\frac{0.1kR}{(0.1+k)(1-1+k) + 0.1(1-k)R(0.1+k)}$$

$$\frac{0.1kR(1.1+k)}{[0.1k(1.1-k) + 0.1(1-k)(0.1+k)]R}$$

$$\frac{k(1.1+k)}{[k(1.1-k) + (1-k)(0.1+k)](0.1)}$$

$$= \frac{k(1.1+k)}{1.1k - k^2 + 0.1 + k - 0.1k - k^2}$$

$$= \frac{k(1.1+k)}{0.1 + 2k - 2k^2}$$

$$\left| \frac{V_o}{V_I} = \frac{k(1.1+k)}{0.1 + 2k - 2k^2} \right|$$

Plot graph yourself

M. Hussain Alvi
 B2
 06 CE-14

2.39


$$R = 100 \text{ k}\Omega$$

(a)

$$0 \rightarrow 0.75 \frac{V}{V}$$

For $0 \frac{V}{V}$ whiper at bottom

For $0.75 \frac{V}{V}$ we added R_1

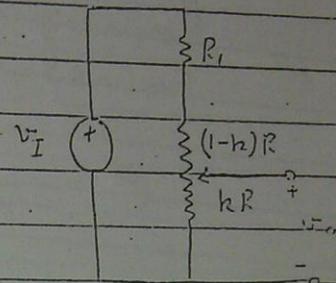

Now

$$\frac{V_0}{V_I} = \frac{R}{R + R_1}$$


$$0.75 = \frac{100}{100 + R_1}$$

$$R_1 = 33.3 \text{ k}\Omega$$

$$(b) 0.2 \frac{V}{V} \rightarrow 1 \frac{V}{V}$$

For $1 \frac{V}{V}$ whiper at tip

For $0.2 \frac{V}{V}$ we added R_2

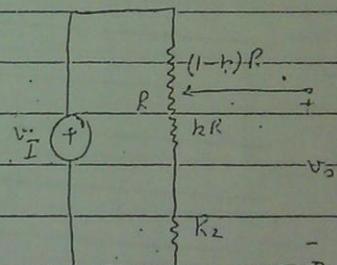

Now

$$\frac{V_0}{V_I} = \frac{R_L}{R_2 + R}$$

$$0.2 = \frac{R_L}{R_2 + 100}$$

$$R_L = 25 \text{ k}\Omega$$

$$(c) 0.1 \frac{V}{V} \text{ to } 0.9 \frac{V}{V}$$

Principle of power conservation proved.

For $\frac{V_o}{V}$ we add R_2

For $\frac{V_o}{V}$ we add R_1

$$\frac{V_o}{V_I} = \frac{R_2}{R + R_1 + R_2}$$

$$0.1 = \frac{R_2}{100 + R_1 + R_2}$$

$$10 + 0.1 R_1 - 0.9 R_1 = 0 \quad \text{--- (1)}$$

$$\frac{V_o}{V_I} = \frac{R + R_2}{R_1 + R + R_2}$$

$$0.9 = \frac{100 + R_2}{100 + R_1 + R_2}$$

$$10 + 0.1 R_2 - 0.9 R_1 = 0 \quad \text{--- (2)}$$

from (1) & (2)

$$R_1 = 12.5 \text{ K}\Omega$$

$$R_2 = 12.5 \text{ K}\Omega$$

M. Hais (Alt)
OG CE-14

$$R_o = 2.4 \text{ K}\Omega$$

Q. 40.


$$V_s = 18 \cos 2\pi \times 10^3 t \quad V$$

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = R_3 = R_4 = 30 \text{ k}\Omega$$

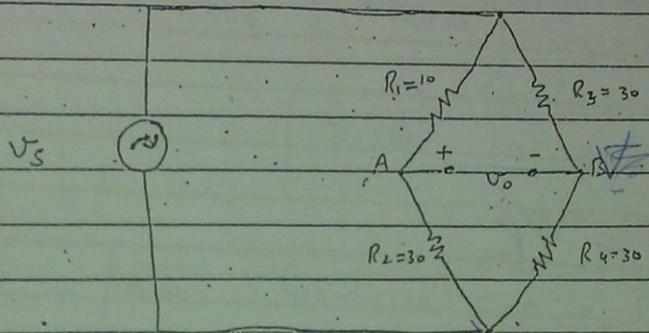(a) $V_o = ?$ as func of t

as resistance is a linear component
so the function (cos) will not change



$$V_A = \frac{R_2}{R_1 + R_2} (V_s)$$
$$= \frac{30}{40} (18 \cos 2\pi \times 10^3 t)$$

$$V_A = 13.5 \cos 2\pi \times 10^3 t$$

$$V_B = \frac{R_4}{R_3 + R_4} (V_s)$$
$$= \frac{30}{60} (18 \cos 2\pi \times 10^3 t)$$


$$V_B = 9 \cos 2\pi \times 10^3 t$$

$$V_o = V_A - V_B$$

$$V_o = 4.5 \cos 2\pi \times 10^3 t \quad V$$

(b) circuit becomes

$$\gamma_{AB} = ?$$

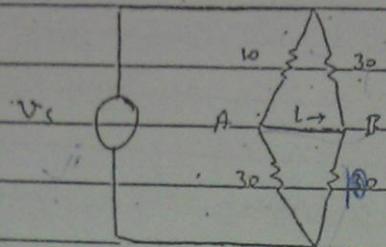


$$R_{eq} = \left(\frac{10 \times 30}{10 + 30} + \frac{30 \times 30}{30 + 30} \right)$$

Req - 22.5

$$i = \sqrt{R}$$
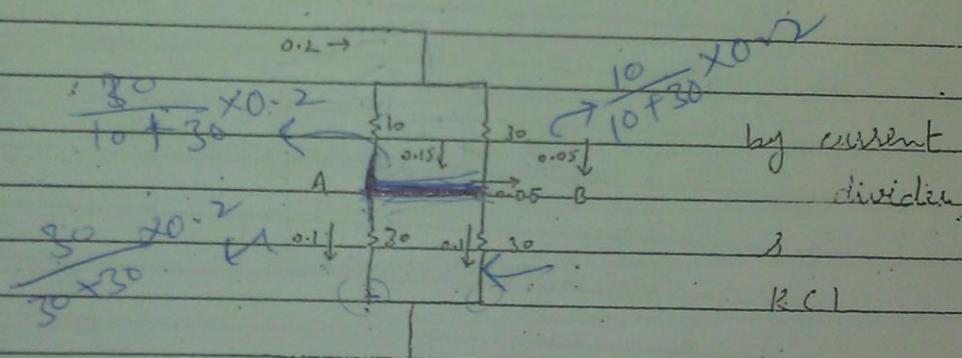
$$i = 0.2 \cos 2\pi \times 10^3 t \text{ mA} \quad \text{by n's law}$$




From A to B

$$0.15 - 0.1 = 0.05$$

$$i_{AB} = 0.05 \cos 2\pi \times 10^3 t \text{ mA}$$

KHALID PHOTO STATE
U.E.T

2.41

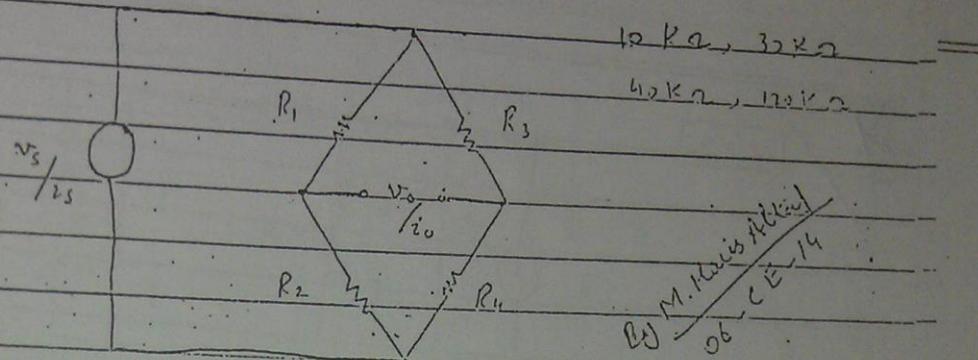

(a)

For balanced bridge

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \wedge (1)$$

only two possibilities are there

✓ (i)	$\frac{10}{40} = \frac{30}{120}$	$R_{eq_1} = 37.5 \text{ k}\Omega$
-------	----------------------------------	-----------------------------------

✓ (ii)	$\frac{10}{30} = \frac{40}{120}$	$R_{eq_2} = 30 \text{ k}\Omega$
--------	----------------------------------	---------------------------------

(b)

$$\rightarrow P = \frac{V^2}{R_{eq}} \quad \text{For emi voltage source}$$


If $R_{eq_1} > R_{eq_2}$ so (i) will consume less power

$$\Rightarrow P = i^2 R_{eq} \quad \text{For current source}$$

If $R_{eq_2} < R_{eq_1}$ so (ii) will consume less power

power conservation proved.

KHALID PHOTO STATE
U.E.T

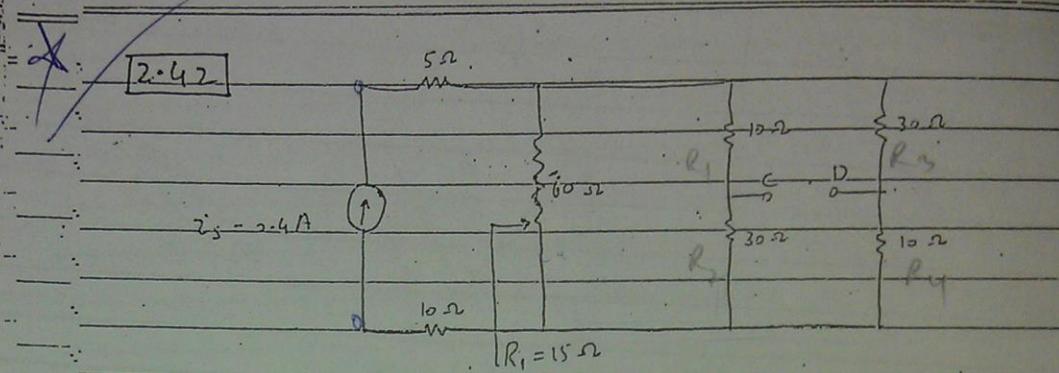

$$R_{eq} = 5 \parallel 10 + (60^{-1} + 40^{-1} + 40^{-1})$$

2

$$R_{eq} = 30\Omega$$

$$R_L = (60^{-1} + 40^{-1} + 40^{-1})$$


$$R_L = 15\Omega$$

M. Khalid Alvi
96-CE-14

$$V_{AB} = i_3 \times R_{eq} = 0.4 \times 30 = 12V$$

By

$$V_{AB} = 12V$$

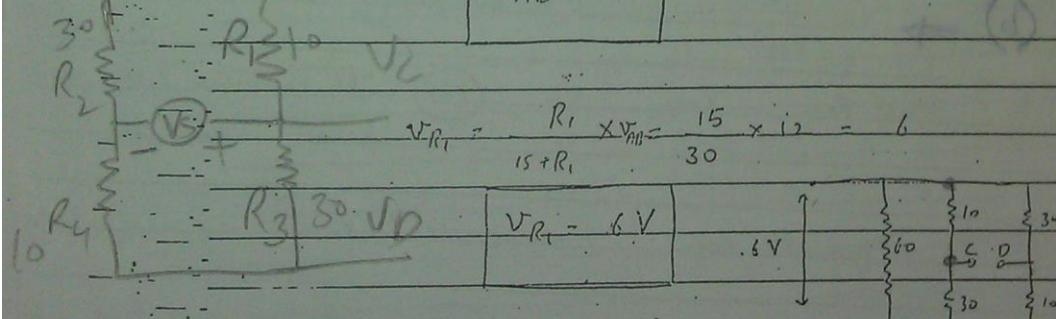


$$V_C = \frac{30}{40} \times V_{R_1} - \frac{3}{4} \times 6 = 4.5V$$

$$V_D = \frac{10}{40} \times V_{R_1} - \frac{1}{4} \times 6 = 1.5V$$

$$V_{CD} = V_C - V_D = 4.5 - 1.5 = 3V$$

$$V_{CD} = 3V$$

2.43

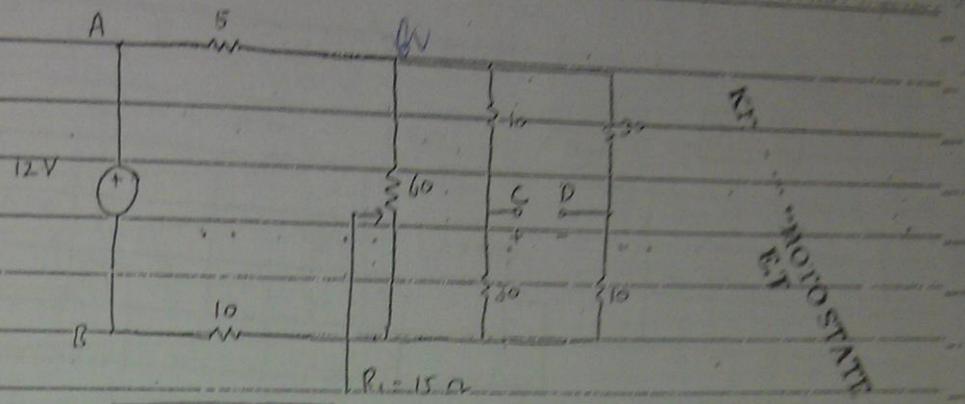

$$R_{eq} = 32 \Omega$$

$$R_1 = 15 \Omega$$

2.43

$$V_{f1} = \frac{15}{30} \times 12 = 6V$$

$$V_{R1} = 6V$$

$$V_C = \frac{30}{40} \times 6 = 4.5V \quad \because \text{Similar as}$$

2.43

$$V_D = \frac{10}{40} \times 6 = 1.5V$$

$$V_{CD} = V_C - V_D = 4.5 - 1.5$$

$$\Rightarrow V_{CD} = 3V$$

KHALID PHOTOSTATE
U.E.T

$$\Rightarrow \text{Power supplied by source} = P = \frac{V^2}{R_{eq}} = \frac{144}{30} = 4.8W$$

$$P = 4.8W$$

(a)

$$R_1 + R = \left(\frac{1-k}{k}\right) R + R$$


$$\Rightarrow R \cdot \left(\frac{1-k+k}{k}\right)$$

$$\boxed{R_1 + R = \frac{R}{k}} \quad \textcircled{1}$$

$$R_2 \parallel (R_1 + R) = \frac{\left(\frac{R}{1-k}\right) \left(\frac{R}{k}\right)}{\left(\frac{R}{1-k}\right) + \left(\frac{R}{k}\right)}$$

$$\boxed{R_2 \parallel (R_1 + R) = R} \quad \textcircled{2}$$

Now for R_{eq} the circuit will be:

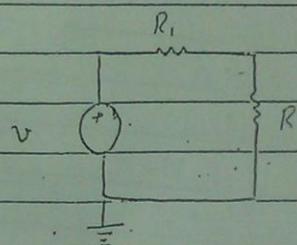

$$R_{eq} = R_1 + R$$

from \textcircled{1}


$$\boxed{R_{eq} = \frac{R}{k}} \quad \textcircled{3}$$

Now by voltage divider

$$V_{o1} = \frac{R}{R_1 + R} V$$

$$= \frac{R}{R/k} V$$

$$\boxed{V_{o1} = k V}$$

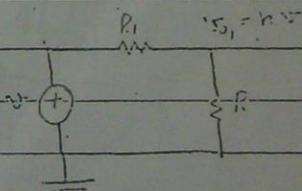

+ power conservation proved.

$$V_{O_2} = \frac{R}{R_1 + R} (kV)$$

$$= \frac{1}{2} (kV)$$

$$V_{O_2} = k^2 V$$

$$V \xrightarrow{R_1} \frac{kV}{R_1} \xrightarrow{R_2} \frac{k^2 V}{R_1 + R} \xrightarrow{R_2} V_{O_2} = k^2 V$$

$$V \xrightarrow{R_1} \frac{kV}{R_1} \xrightarrow{R_2} \frac{k^2 V}{R_1 + R} \xrightarrow{R_2} V_{O_2} = k^2 V$$

Similarly;


$$V_{O_3} = k^3 V$$

$$V_{O_4} = k^4 V$$

$$V_{O_5} = k^5 V$$


By M. Khalid Photo State
06-CE-14

So, circuit is verified

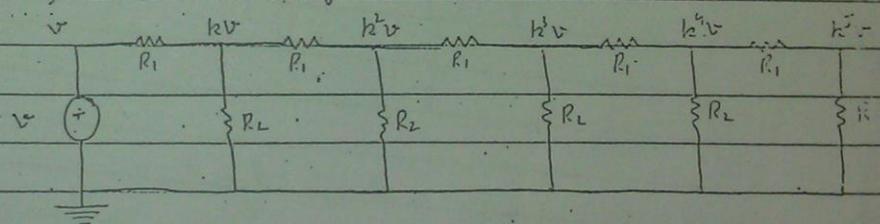

$$f = \left(\frac{1-k}{R_1} \right) R \Rightarrow \begin{cases} R_1 = R \\ R_2 = 2R \end{cases}$$

$$R_{eq} = 2R$$

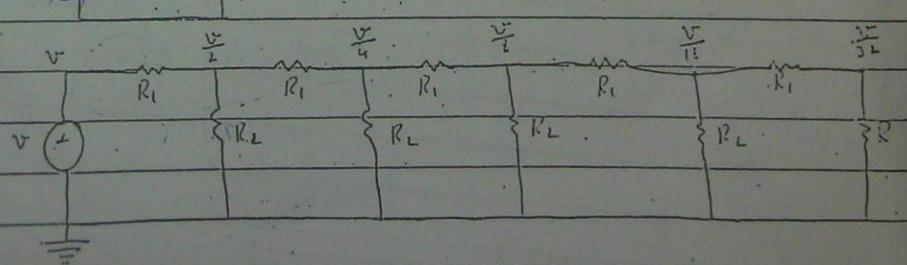

2.47

(a) $i_2 = 0.1$ $R_{eq} = 10 \text{ k}\Omega$

$$R_{eq} = \frac{R}{k}$$

from 2.61

$$R_1 = \frac{(1-k)}{k} R \quad \textcircled{2}$$


$$R_1 = \frac{1}{(1-k)} R \quad \textcircled{3}$$

putting the values in \textcircled{3}

$$10 \text{ k} = \frac{R}{0.1}$$

$$R = 1 \text{ k}\Omega$$

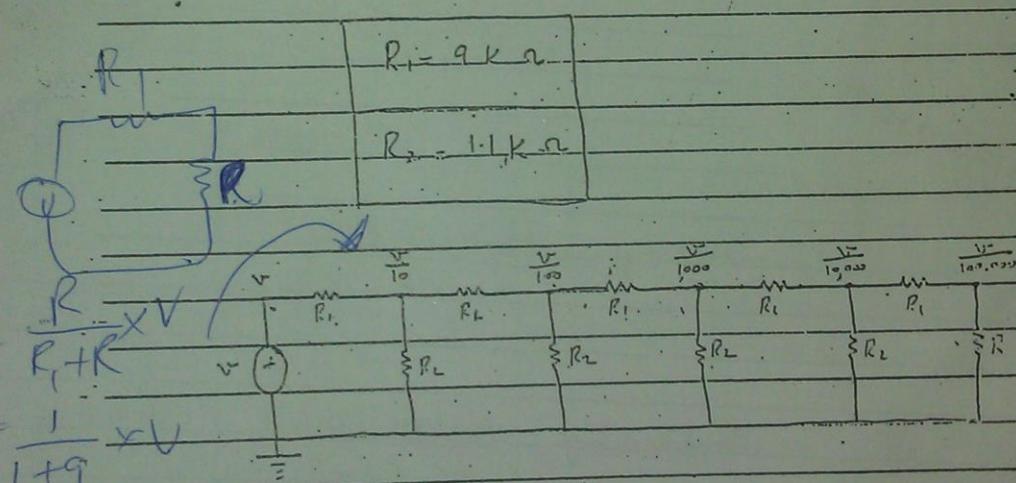by putting in \textcircled{2} & \textcircled{3} we get



$$\frac{V}{10} \quad (b) \quad k = \frac{1}{4} \quad R_{eq} = 10 \text{ k}\Omega$$

putting in \textcircled{1}

$$10 \text{ k}\Omega = \frac{R}{k}$$

$$R = 2.5 \text{ k}\Omega$$

hence this of power conservation is proved.