

3.1 Find both I_o and V_o in the network in Fig. P3.1 using nodal analysis.


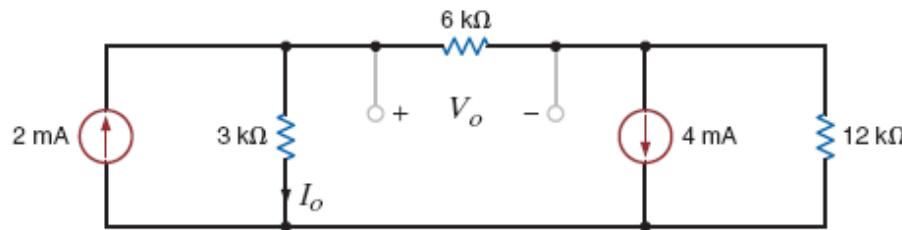


Figure P3.1

SOLUTION:

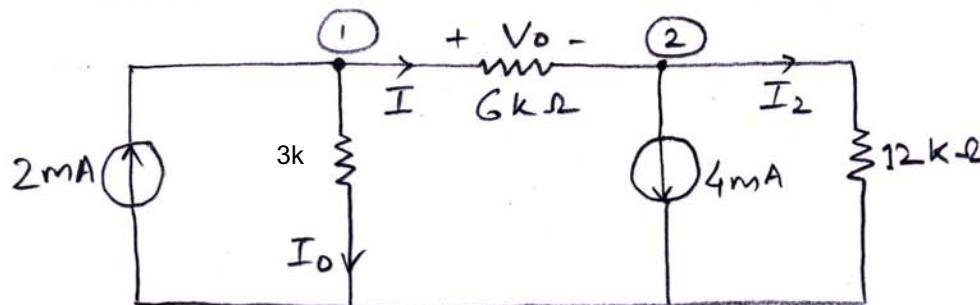

$$\text{KCL at } \textcircled{1} : 2m = I_o + I$$

$$\frac{V_1}{3k} + \frac{V_1 - V_2}{6k} = 2m$$

$$2V_1 + V_1 - V_2 = 12$$

$$\boxed{3V_1 - V_2 = 12}$$

$$\text{KCL at } \textcircled{2} : I = 4m + I_2$$

$$\frac{V_1 - V_2}{6k} = 4m + \frac{V_2}{12k}$$

$$2V_1 - 2V_2 = 48 + V_2$$

$$\boxed{2V_1 - 3V_2 = 48}$$

$$3V_1 - V_2 = 12$$

$$2V_1 - 3V_2 = 48$$

$$V_1 = -1.71 \text{ V}$$

$$V_2 = -17.14 \text{ V}$$

$$V_o = V_1 - V_2$$

$$V_o = -1.71 - (-17.14)$$
$$V_o = 15.43 \text{ V}$$

$$I_o = \frac{V_1}{3k}$$
$$= \frac{-1.71}{3k} = -0.57$$

$$I_o = -0.57 \text{ mA}$$

3.2 Use nodal analysis to find V_1 in the circuit in Fig. P3.2.


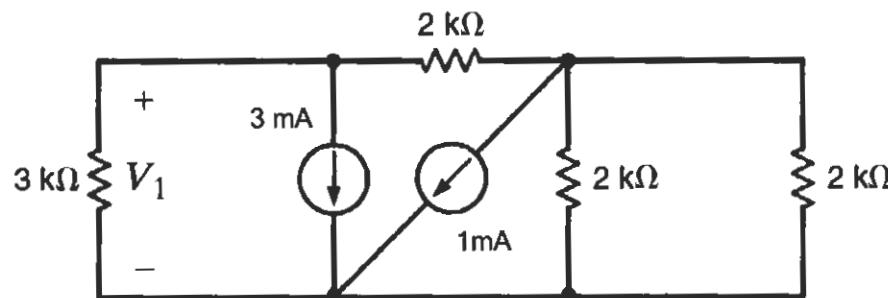


Figure P3.2

SOLUTION: 3.2

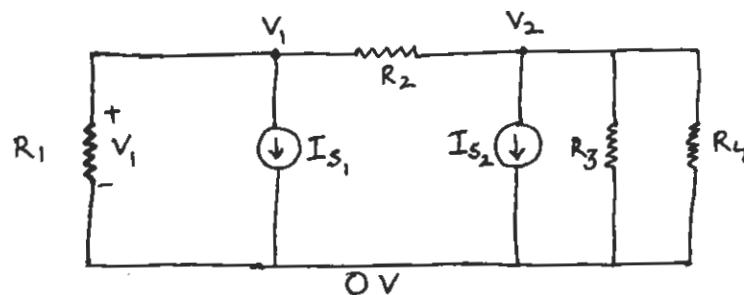

$$R_1 = 3 \text{ k}\Omega, R_2 = R_3 = R_4 = 2 \text{ k}\Omega, I_{s1} = 3 \text{ mA}, I_{s2} = 1 \text{ mA}$$

$$\text{KCL @ } V_1 : \frac{V_1}{R_1} + I_{s1} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1}{3 \times 10^3} + 3 \times 10^{-3} + \frac{V_1 - V_2}{2 \times 10^3} = 0$$

$$5V_1 - 3V_2 = -18 \quad \text{--- (1)}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_2} + I_{s2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} = 0$$

$$\frac{V_2 - V_1}{2 \times 10^3} + 1 \times 10^{-3} + \frac{V_2}{2 \times 10^3} + \frac{V_2}{2 \times 10^3} = 0$$

$$3V_2 - V_1 = -2 \quad \text{--- (2)}$$

Substituting equation (2) in (1), we get

$$V_2 = -\frac{28}{12}$$

$$V_1 = \frac{3V_2 - 18}{5} \Rightarrow V_1 = -5 \text{ V}$$

- 3.3 Find V_1 and V_2 in the circuit in Fig. P3.3 using nodal analysis. Then solve the problem using MATLAB and compare your answers.


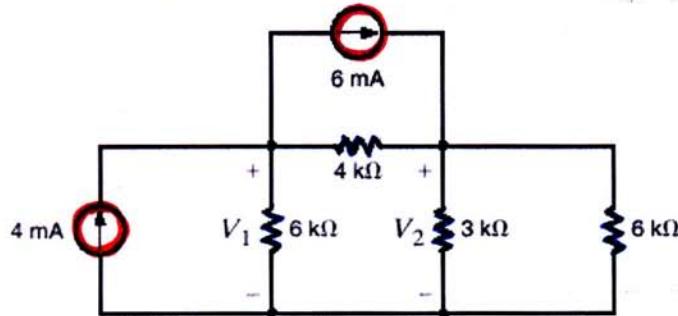


Figure P3.3

SOLUTION:

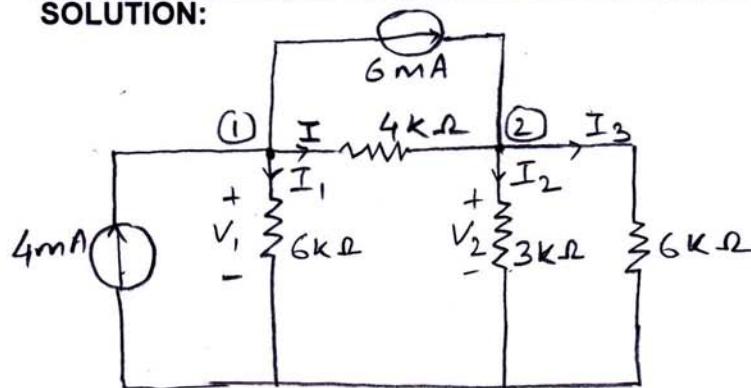

$$\text{KCL at } \textcircled{1}: 4m = 6m + I + I_1$$

$$\frac{V_1 - V_2}{4k} + \frac{V_1}{6k} = -2m$$

$$3V_1 - 3V_2 + 2V_1 = -24$$

$$\boxed{5V_1 - 3V_2 = -24}$$

$$\text{KCL at } \textcircled{2}: 6m + I = I_2 + I_3$$

$$\frac{V_2}{3k} + \frac{V_2}{6k} = 6m + \frac{V_1 - V_2}{4k}$$

$$4V_2 + 2V_2 = 72 + 3V_1 - 3V_2$$

$$\boxed{-3V_1 + 9V_2 = 72}$$

$$\begin{aligned}5V_1 - 3V_2 &= -24 \\-3V_1 + 9V_2 &= 72\end{aligned}$$

$$\begin{aligned}V_1 &= 0 \text{ V} \\V_2 &= 8 \text{ V}\end{aligned}$$

% MATLAB Code and solution for Problem 3.4

```
G = [ 5, -3; -3, 9];  
Imatrix = [-24; 72];  
V = inv (G) * Imatrix
```

>>

V =

0.00
8.00

3.4 Use nodal analysis to find both V_1 and V_o in the circuit in Fig. P3.4.


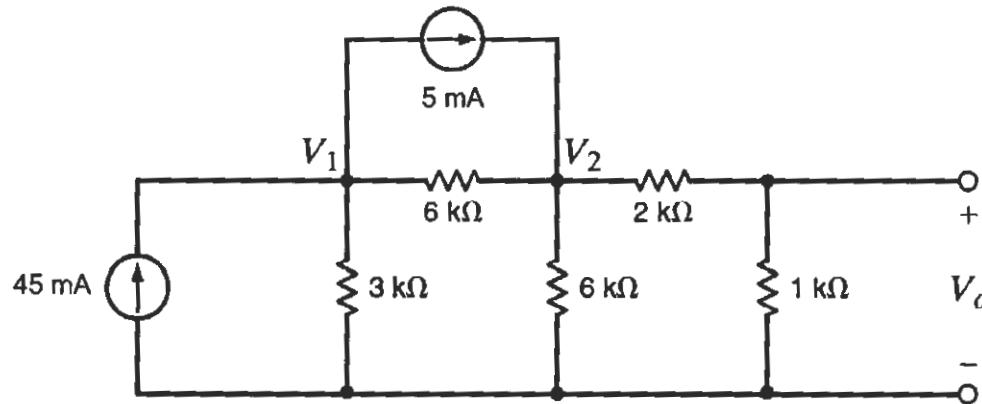


Figure P3.4

SOLUTION: 3.4

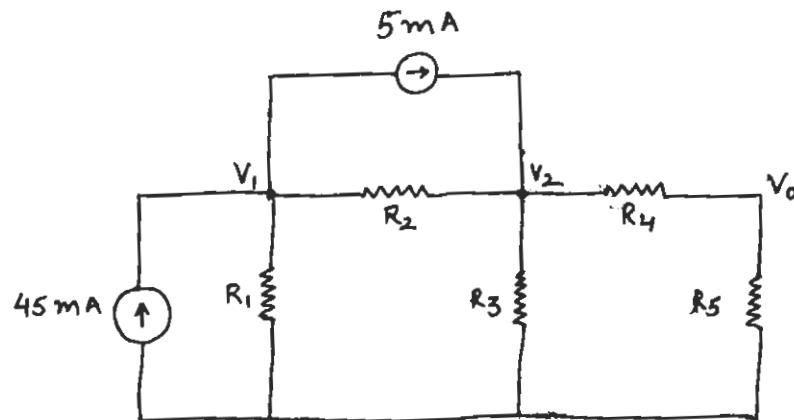

$$R_1 = 3 \text{ k}\Omega, R_2 = 6 \text{ k}\Omega, R_3 = 6 \text{ k}\Omega, R_4 = 2 \text{ k}\Omega, R_5 = 1 \text{ k}\Omega$$

$$\text{KCL @ } V_1 : \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_1} + I_{S_2} - I_{S_1} = 0$$

$$\frac{V_1 - V_2}{6 \times 10^3} + \frac{V_1}{3 \times 10^3} + 5 \times 10^{-3} - 45 \times 10^{-3} = 0$$

$$3V_1 - V_2 = 240 \quad \text{--- (1)}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_2} + \frac{V_2 - V_0}{R_4} + \frac{V_2}{R_3} - I_{S_2} = 0$$

$$\frac{V_2 - V_1}{6 \times 10^3} + \frac{V_2 - V_0}{2 \times 10^3} + \frac{V_2}{6 \times 10^3} - 5 \times 10^{-3} = 0$$

$$5V_2 - V_1 - 3V_0 = 30 \quad \text{--- (2)}$$

$$\text{KCL at } V_0 : \frac{V_2 - V_0}{R_4} - \frac{V_0}{R_5} = 0$$

$$\frac{V_2 - V_0}{2 \times 10^3} - \frac{V_0}{10^3} = 0$$

$$V_2 = 3V_0 \quad \text{--- (3)}$$

Substituting equation (3) in (2), we get

$$5(3V_0) - V_1 - 3V_0 = 30$$

$$12V_0 - 30 = V_1 \quad \text{--- (4)}$$

Substituting equations (3) and (4) in (1), we get

$$3(12V_0 - 30) - 3V_0 = 240$$

$$V_0 = 10V$$

Substituting the value of V_0 in equation (4), we get

$$12(10) - 30 = V_1$$

$$\Rightarrow V_1 = 90V$$

3.5 Find V_o in the network in Fig. P3.5.


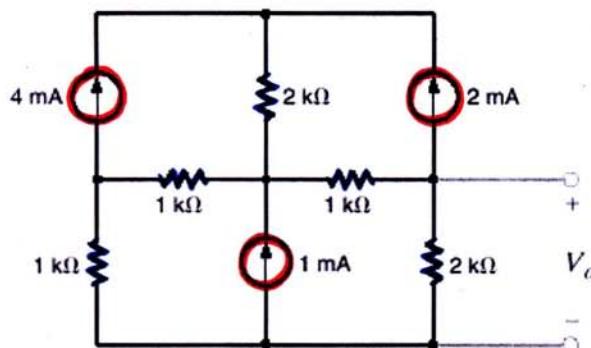


Figure P3.5

SOLUTION:

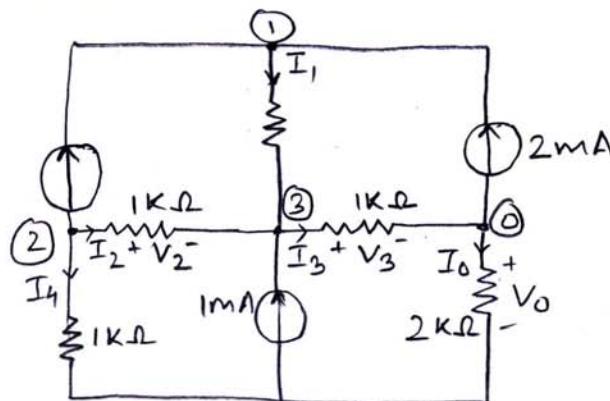

$$\text{KCL at } (2) : 4m + I_2 + I_4 = 0$$

$$\frac{V_2 - V_3}{1k} + \frac{V_2}{1k} = -4m$$

$$V_2 - V_3 + V_2 = -4$$

$$2V_2 - V_3 = -4$$

$$\text{KCL at } (3) : I_1 + 1m + I_2 = I_3$$

$$\frac{V_1 - V_3}{2k} + 1m + \frac{V_2 - V_3}{1k} = \frac{V_3 - V_0}{1k}$$

$$V_1 - V_3 + 2 + 2V_2 - 2V_3 = 2V_3 - 2V_0$$

$$-2V_0 + 5V_3 - 2V_2 - V_1 = 2$$

$$-2V_0 - V_1 - 2V_2 + 5V_3 = 2$$

$$KCL \text{ at } \textcircled{0} : I_3 = 2m + I_0$$

$$\frac{V_3 - V_0}{1k} = 2m + \frac{V_0}{2k}$$

$$\begin{aligned} 2V_3 - 2V_0 &= 4 + V_0 \\ -3V_0 + 2V_3 &= 4 \end{aligned}$$

$$KCL \text{ at } \textcircled{1} : 4m + 2m = I_1$$

$$\frac{V_1 - V_3}{2k} = 6m$$

$$V_1 - V_3 = 12$$

$$0V_0 + 0V_1 + 2V_2 - V_3 = -4$$

$$-2V_0 - V_1 - 2V_2 + 5V_3 = 2$$

$$-3V_0 + 0V_1 + 0V_2 + 2V_3 = 4$$

$$0V_0 + V_1 + 0V_2 - V_3 = 12$$

$$V_0 = 1.6 \text{ V}$$

$$V_1 = 16.4 \text{ V}$$

$$V_2 = 0.2 \text{ V}$$

$$V_3 = 4.4 \text{ V}$$

3.6 Use nodal analysis to find V_o in the circuit in Fig. P3.6.


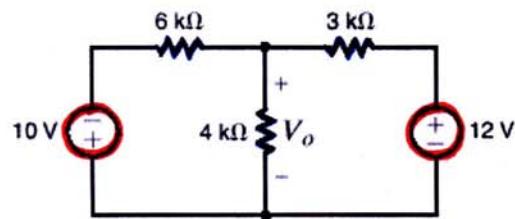


Figure P3.6

SOLUTION:

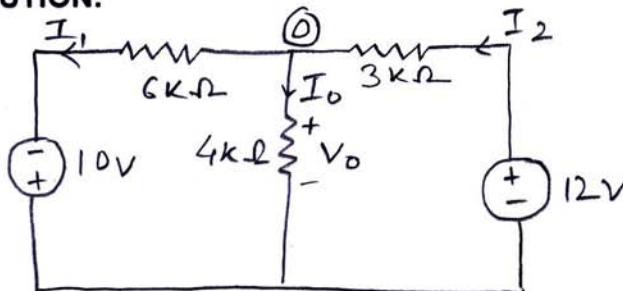

$$\text{KCL at } \textcircled{0}: \quad I_2 = I_0 + I_1$$

$$\frac{12 - V_o}{3k} = \frac{V_o}{4k} + \frac{V_o - (-10)}{6k}$$

$$48 - 4V_o = 3V_o + 2V_o + 20$$

$$9V_o = 28$$

$$V_o = 3.11 \text{ V}$$

3.7 Find V_o in the network in Fig. P3.7 using nodal analysis.


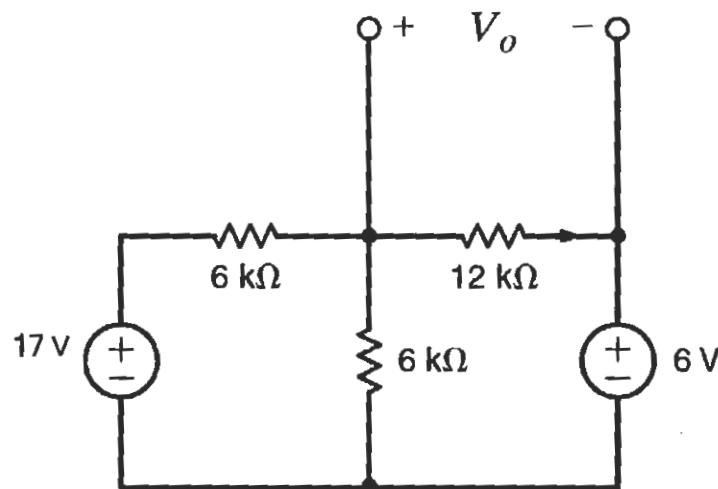


Figure P3.7

SOLUTION: 3.7

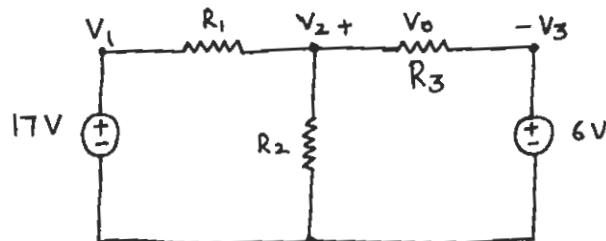

$$R_1 = R_2 = 6 \text{ k}\Omega, R_3 = 12 \text{ k}\Omega$$

$$@ V_1 : V_1 = 17 \text{ V}$$

$$\text{KCL} @ V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0 \quad \textcircled{1}$$

$$@ V_3 : V_3 = 6 \text{ V}$$

Substituting values of V_1 and V_3 in equation $\textcircled{1}$, we get

$$\frac{V_2}{R_1} - \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2}{R_3} - \frac{V_3}{R_3} = 0$$

$$V_2 \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{V_1}{R_1} - \frac{V_3}{R_3} = 0$$

$$V_2 \left[\frac{1}{6} + \frac{1}{6} + \frac{1}{12} \right] - \frac{17}{6} - \frac{6}{12} = 0$$

$$V_2 = 8 \text{ V}$$

$$V_0 = V_2 - V_3$$

$$\boxed{V_0 = 2 \text{ V}}$$

3.8 Use nodal analysis to find V_o in the circuit in Fig. P3.8.


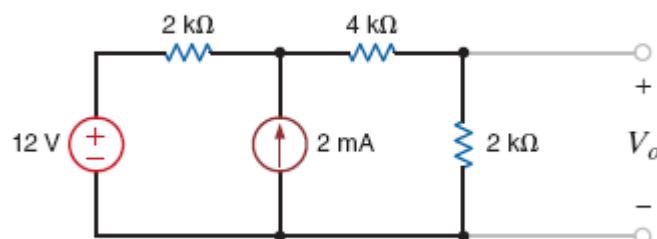


Figure P3.8

SOLUTION:

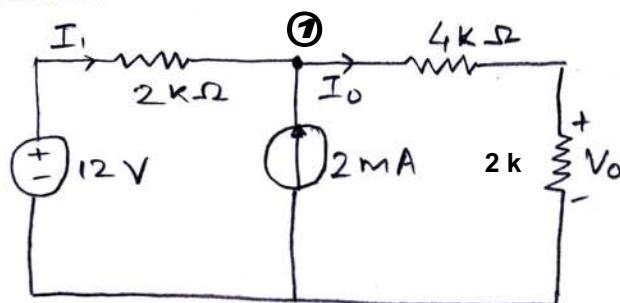

$$\text{KCL at } \textcircled{1} : I_1 + 2m = I_0$$

$$\frac{12 - V_1}{2k} + 2m = \frac{V_1}{4k + 2k}$$

$$36 - 3V_1 + 12 = V_1$$

$$4V_1 = 48$$

$$V_1 = 12 \text{ V}$$

$$I_0 = \frac{V_1}{4k + 2k}$$

$$= \frac{12}{6k}$$

$$I_0 = 2 \text{ mA}$$

$$V_o = I_0 (2k)$$

$$= 2m (2k)$$

$$V_o = 4 \text{ V}$$

3.9 Use nodal analysis to find V_o in the circuit in Fig. P3.9.


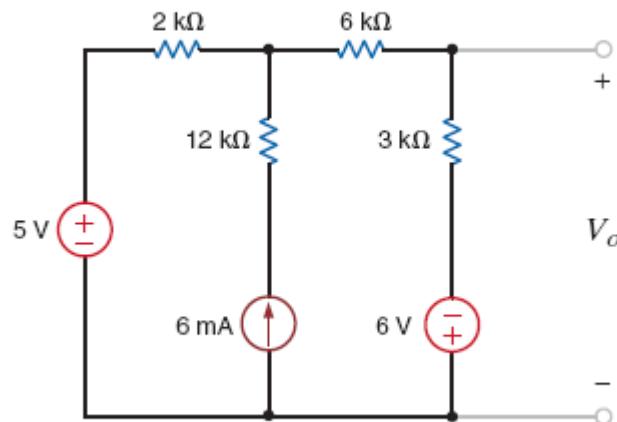


Figure P3.9

SOLUTION:

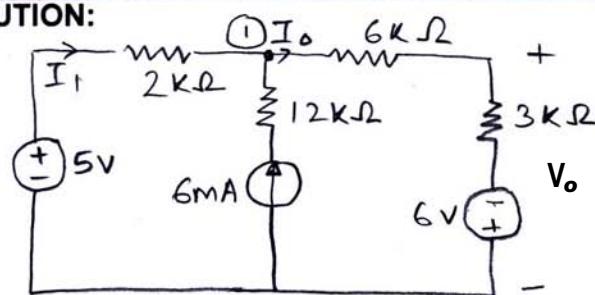

$$KCL \text{ at } \textcircled{1} : I_1 + 6m = I_o$$

$$\frac{5 - V_1}{2k} + 6m = \frac{V_1 - (-6)}{6k + 3k}$$

$$45 - 9V_1 + 108 = 2V_1 + 12$$

$$11V_1 = 141$$

$$V_1 = 12.82 \text{ V}$$

$$I_o = \frac{V_1 - (-6)}{6k + 3k}$$

$$= \frac{12.82 + 6}{9k}$$

$$I_o = 2.09 \text{ mA}$$

$$6 + V_o = 3k I_o$$

$$V_o = 3k(2.09m) - 6$$

$$V_o = 0.27 \text{ V}$$

3.10 Use nodal analysis to find V_o in the network in Fig. P3.10.


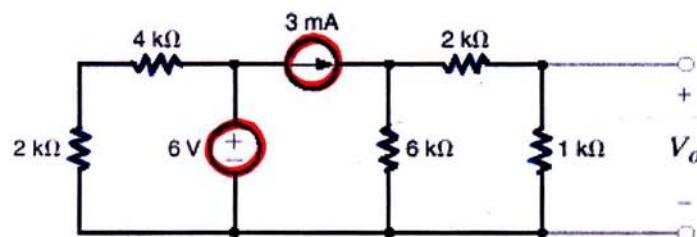


Figure P3.10

SOLUTION:

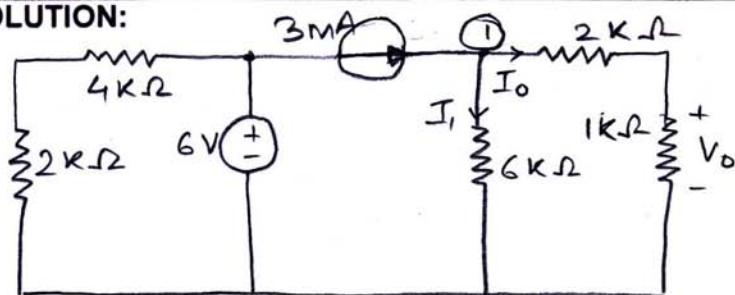

$$\text{KCL at } \textcircled{1}: \quad 3\text{mA} = I_1 + I_2$$

$$\frac{V_1}{6\text{k}} + \frac{V_1}{2\text{k}+1\text{k}} = 3\text{mA}$$

$$V_1 + 2V_1 = 18$$

$$3V_1 = 18$$

$$V_1 = 6 \text{ V}$$

$$I_2 = \frac{V_1}{2\text{k}+1\text{k}} = \frac{6}{3\text{k}}$$

$$I_2 = 2\text{mA}$$

$$V_o = I_2(1\text{k})$$

$$= 2\text{mA}(1\text{k})$$

$$V_o = 2 \text{ V}$$

- 3.11 Use nodal analysis to find V_o in the circuit in Fig. P3.11.


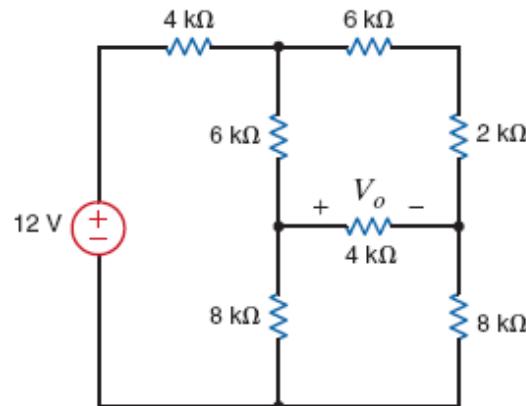


Figure P3.11

SOLUTION:

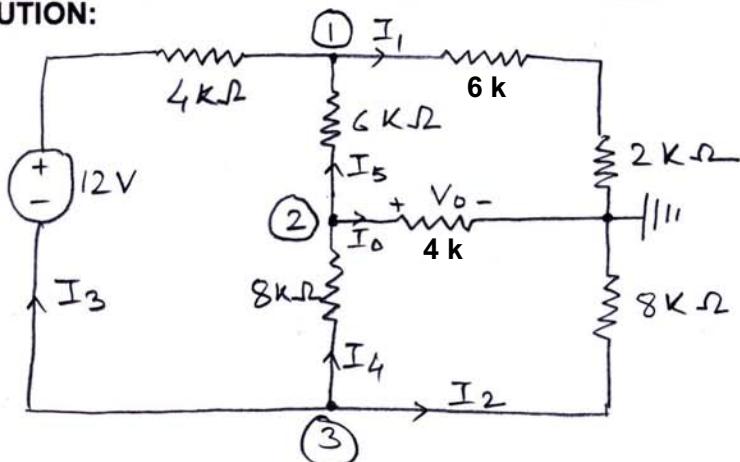

$$\text{KCL at } \textcircled{1} : I_3 + I_5 = I_1$$

$$\frac{12 - V_1}{4K} + \frac{V_2 - V_1}{6K} = \frac{V_1}{6K + 2K}$$

$$72 - 6V_1 + 4V_2 - 4V_1 = 3V_1$$

$$13V_1 - 4V_2 = 72$$

$$\text{KCL at } \textcircled{2} : I_4 = I_0 + I_5$$

$$\frac{V_3 - V_2}{8K} = \frac{V_2}{4K} + \frac{V_2 - V_1}{6K}$$

$$3V_3 - 3V_2 = 6V_2 + 4V_2 - 4V_1$$

$$4V_1 - 13V_2 + 3V_3 = 0$$

KCL at ③: $I_2 + I_3 + I_4 = 0$

$$\frac{-12 + V_1}{4K} + \frac{V_3}{8K} + \frac{V_3 - V_2}{8K} = 0$$

$$\frac{-24 + 2V_1 + V_3 + V_3 - V_2}{2V_1 - V_2 + 2V_3} = 0$$

$$2V_1 - V_2 + 2V_3 = 24$$

$$13V_1 - 4V_2 + 0V_3 = 72$$

$$4V_1 - 13V_2 + 3V_3 = 0$$

$$2V_1 - V_2 + 2V_3 = 24$$

$$V_1 = 6.68 \text{ V}$$

$$V_2 = 3.71 \text{ V}$$

$$V_3 = 7.18 \text{ V}$$

$$V_0 = V_2 = 3.71 \text{ V}$$

3.12 Find I_o in the network in Fig. P3.12 using nodal analysis.


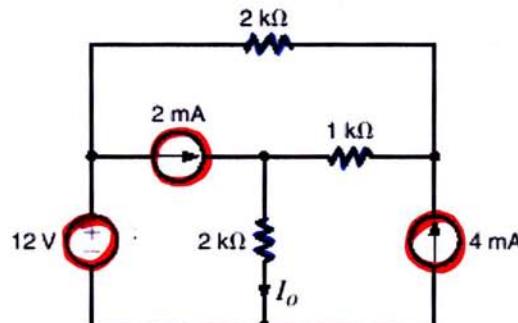


Figure P3.12

SOLUTION:

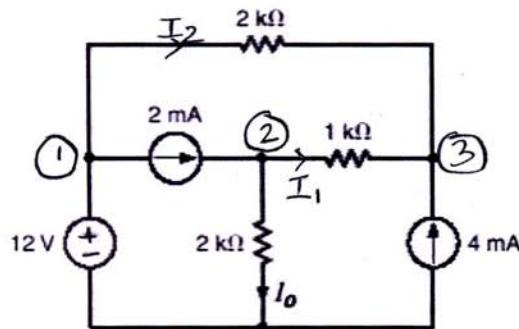

$$\text{KCL at } \textcircled{2} : 2m = \frac{V_2}{2k} + \frac{V_2 - V_3}{1k}$$

$$4 = V_2 + 2V_2 - 2V_3$$

$$\boxed{3V_2 - 2V_3 = 4}$$

$$\text{KCL at } \textcircled{3} : I_1 + I_2 + 4m = 0$$

$$\frac{V_2 - V_3}{1k} + \frac{V_1 - V_3}{2k} + 4m = 0$$

$$2V_2 - 2V_3 + V_1 - V_3 + 8 = 0$$

$$V_1 = 12V$$

$$\boxed{2V_2 - 3V_3 = -20}$$

$$3V_2 - 2V_3 = 4$$

$$2V_2 - 3V_3 = -20$$

$$V_2 = 10.4 \text{ V}$$

$$V_3 = 13.6 \text{ V}$$

$$I_0 = \frac{V_2}{2K}$$

$$= \frac{10.4}{2K}$$

$$I_0 = 5.2 \text{ mA}$$

- 3.13 Use nodal analysis to solve for the node voltages in the circuit in Fig. P3.13. Also calculate the power supplied by the 1-A current source.

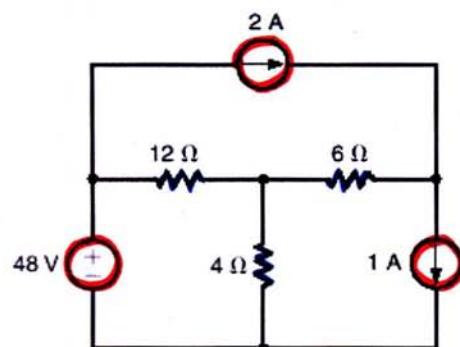
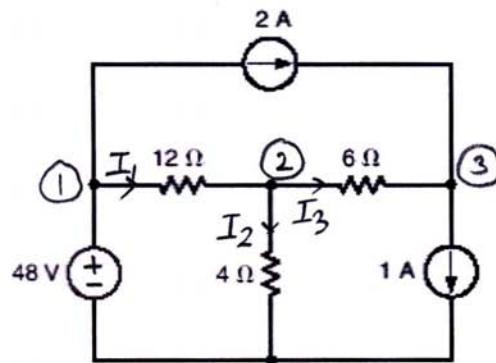


Figure P3.13

SOLUTION:

$$\text{KCL at } (2) : I_1 = I_2 + I_3$$

$$\frac{V_1 - V_2}{12} = \frac{V_2}{4} + \frac{V_2 - V_3}{6}$$

$$V_1 - V_2 = 3V_2 + 2V_2 - 2V_3$$

$$V_1 = 48 \text{ V}$$

$$6V_2 - 2V_3 = 48$$

$$\text{KCL at } (3) : 2 + I_3 - 1 = 0$$

$$\frac{V_2 - V_3}{6} = -1$$

$$V_2 - V_3 = -6$$

$$6V_2 - 2V_3 = 48$$

$$V_2 - V_3 = -6$$

$$V_2 = 15 \text{ V}$$

$$V_3 = 21 \text{ V}$$

$$\begin{aligned}P_{IA} &= V_3 (1) \\&= 21 (1)\end{aligned}$$

$$P_{IA} = 21 \text{ W}$$

- 3.14 Find V_o in the network in Fig. P3.14 using nodal equations.


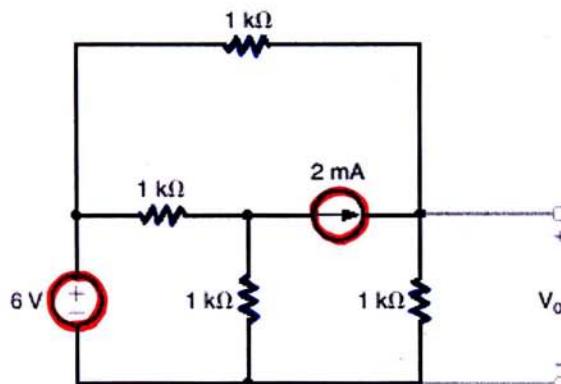


Figure P3.14

SOLUTION:

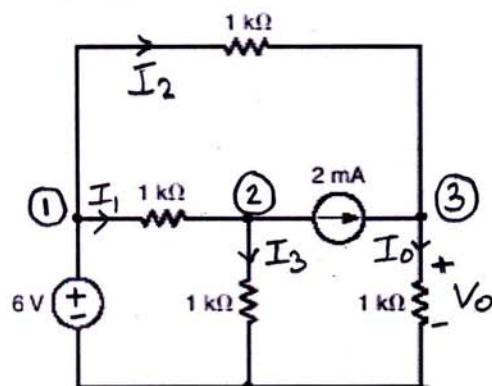

$$\text{KCL at } \textcircled{2} : I_1 = I_3 + 2\text{mA}$$

$$\frac{V_1 - V_2}{1\text{K}} = \frac{V_2}{1\text{K}} + 2\text{mA}$$

$$V_1 - V_2 = V_2 + 2$$

$$\boxed{V_1 - 2V_2 = 2}$$

$$V_1 = 6\text{V}$$

$$-2V_2 = -4$$

$$V_2 = 2\text{V}$$

$$\text{KCL at } \textcircled{3} : I_2 + 2\text{mA} = I_o$$

$$\frac{V_1 - V_3}{1\text{K}} + 2\text{mA} = \frac{V_3}{1\text{K}}$$

$$V_1 - V_3 + 2 = V_3$$

$$2V_3 = 8$$

$$V_3 = 4 \text{ V}$$

$$V_0 = V_3$$

$$V_0 = 4 \text{ V}$$

3.15 Find I_o in the network in Fig. P3.15 using nodal analysis.


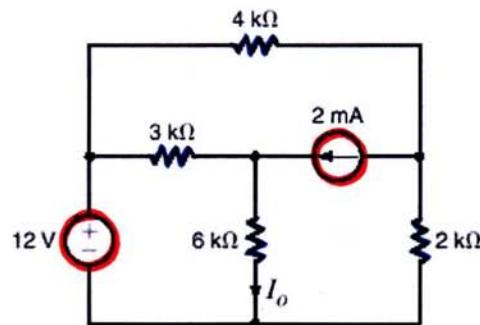


Figure P3.15

SOLUTION:

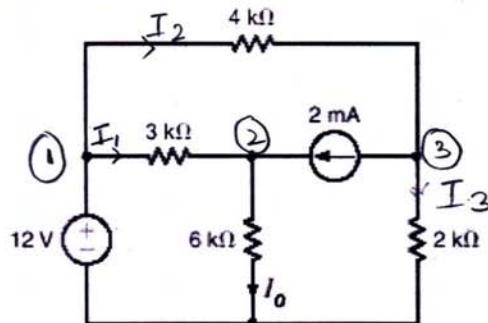

$$\text{KCL at } \textcircled{2} : I_1 + 2m = I_o$$

$$\frac{V_1 - V_2}{3k} + 2m = \frac{V_2}{6k}$$

$$\begin{aligned} 2V_1 - 2V_2 + 12 &= V_2 \\ \boxed{2V_1 - 3V_2 &= -12} \end{aligned}$$

$$\text{KCL at } \textcircled{3} : I_2 = 2m + I_3$$

$$\frac{V_1 - V_3}{4k} = 2m + \frac{V_3}{2k}$$

$$\begin{aligned} V_1 - V_3 &= 8 + 2V_3 \\ \boxed{V_1 - 3V_3 &= 8} \end{aligned}$$

$$V_1 = 12 \text{ V}$$

$$2(12) - 3V_2 = -12$$

$$-3V_2 = -36$$

$$V_2 = 12 \text{ V}$$

$$I_o = \frac{V_2}{6K}$$

$$= \frac{12}{6K}$$

$$I_o = 2 \text{ mA}$$

3.16 Use nodal analysis to find I_o in the circuit in Fig. P3.16.


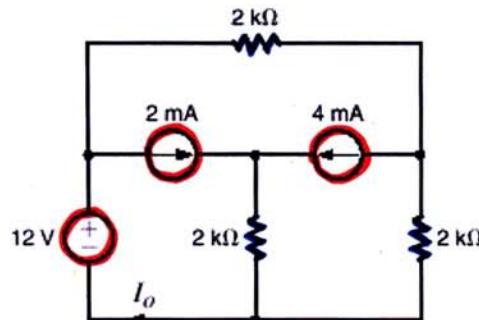


Figure P3.16

SOLUTION:

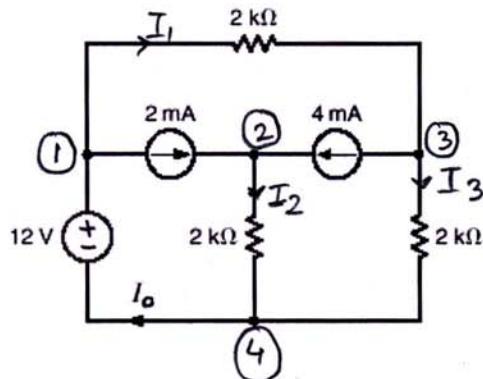

$$KCL \text{ at } (2) : 2m + 4m = I_2$$

$$\frac{V_2}{2k} = 6m$$

$$V_2 = 12V$$

$$KCL \text{ at } (3) : I_3 = 4m + I_3$$

$$\frac{V_1 - V_3}{2k} = 4m + \frac{V_3}{2k}$$

$$V_1 - V_3 = 8 + V_3$$

$$2V_3 = V_1 - 8$$

$$V_1 = 12V$$

$$2V_3 = 12 - 8$$

$$V_3 = 2V$$

$$I_2 = \frac{V_2}{2k}$$

$$I_2 = \frac{12}{2k} = 6mA$$

$$I_3 = \frac{V_3}{2k} = \frac{2}{2k} = 1mA$$

KCL at ④ : $I_2 + I_3 = I_o$
 $I_o = 6mA + 1mA$
 $I_o = 7mA$

3.17 Find V_o in the circuit in Fig. P3.17 using nodal analysis.

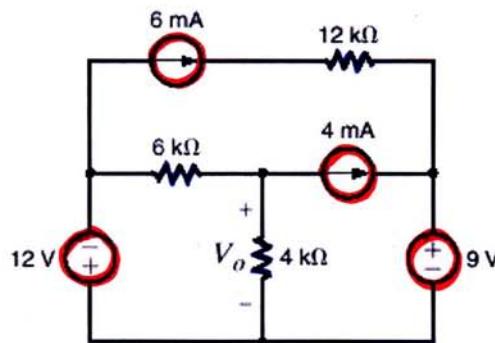


Figure P3.17

SOLUTION:

$$KCL \text{ at } (2) : I_1 = I_o + 4m$$

$$\frac{V_1 - V_2}{6K} = \frac{V_2}{4K} + 4m$$

$$2V_1 - 2V_2 = 3V_2 + 48$$

$$2V_1 - 5V_2 = 48$$

$$V_1 = -12V$$

$$2(-12) - 5V_2 = 48$$

$$V_2 = -14.4V$$

$$V_o = V_2 = -14.4V$$

$$V_o = -14.4V$$

3.18 Use nodal analysis to find V_o in the network in Fig. P3.18.

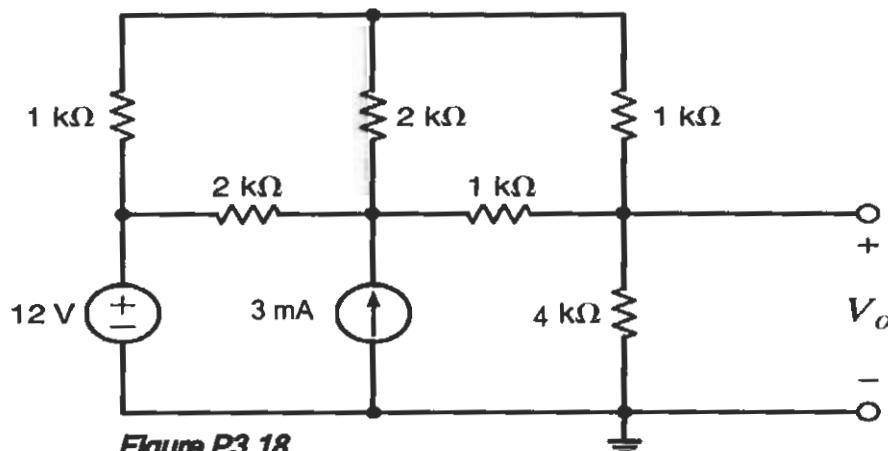
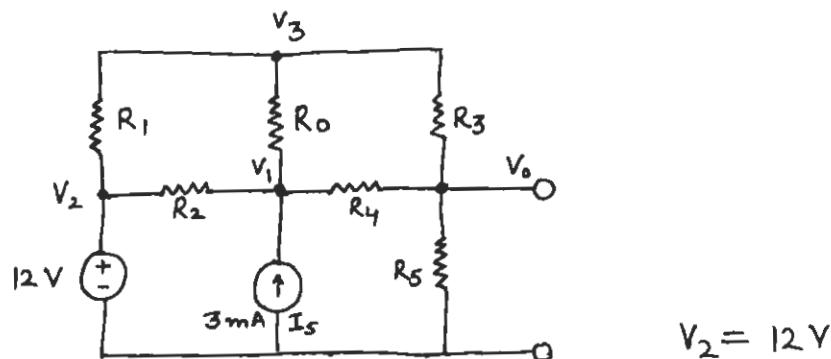


Figure P3.18

SOLUTION: 3.18

$$R_S = 4 \text{ k}\Omega, R_1 = 1 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega, R_3 = 1 \text{ k}\Omega, R_4 = 1 \text{ k}\Omega, R_0 = 2 \text{ k}\Omega$$

$$\text{KCL at } V_1 : \frac{V_1 - V_0}{R_4} + \frac{V_1 - V_3}{R_0} + \frac{V_1 - V_2}{R_2} = I_s$$

$$\frac{V_1 - V_0}{1 \times 10^3} + \frac{V_1 - V_3}{2 \times 10^3} + \frac{V_1 - 12}{2 \times 10^3} = 3 \times 10^{-3}$$

$$2V_1 - 2V_0 + V_1 - V_3 + V_1 - 12 = 6$$

$$4V_1 - V_3 - 2V_0 = 18 \quad \text{--- } ①$$

$$\text{KCL @ } V_3 : \frac{V_3 - V_2}{R_1} + \frac{V_3 - V_1}{R_0} + \frac{V_3 - V_0}{R_3} = 0$$

$$\frac{V_3 - 12}{1 \times 10^3} + \frac{V_3 - V_1}{2 \times 10^3} + \frac{V_3 - V_0}{1 \times 10^3} = 0$$

$$-V_1 + 5V_3 - 2V_0 = 24 \quad \text{--- } (2)$$

$$\text{KCL @ } V_0 : \frac{V_0 - V_3}{R_3} + \frac{V_0 - V_1}{R_4} + \frac{V_0}{R_5} = 0$$

$$\frac{V_0 - V_3}{1 \times 10^3} + \frac{V_0 - V_1}{1 \times 10^3} + \frac{V_0}{4 \times 10^3} = 0$$

$$-4V_1 - 4V_3 + 9V_0 = 0 \quad \text{--- } (3)$$

From equation (1)

$$V_1 = \frac{18 + V_3 + 2V_0}{4} \quad \text{--- } (4)$$

Substituting equation (4) in (2), we get

$$19V_3 - 10V_0 = 114 \quad \text{--- } (5)$$

Substituting equation (4) in (3), we get

$$-4V_1 - 4V_3 + 9V_0 = 0$$

$$-4\left[\frac{18 + V_3 + 2V_0}{4}\right] - 4V_3 + 9V_0 = 0$$

$$-5V_3 + 7V_0 = 18 \quad \text{--- } (6)$$

From equations (5) and (6), we get

$$83V_0 = 912$$

$$V_0 = \frac{912}{83} = 10.99$$

$$\boxed{V_0 = 11.0V}$$

3.19 Find I_o in the circuit in Fig. P3.19 using nodal analysis.


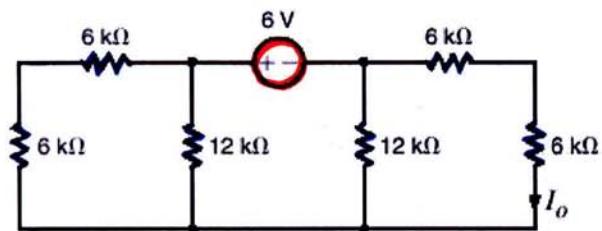


Figure P3.19

SOLUTION:

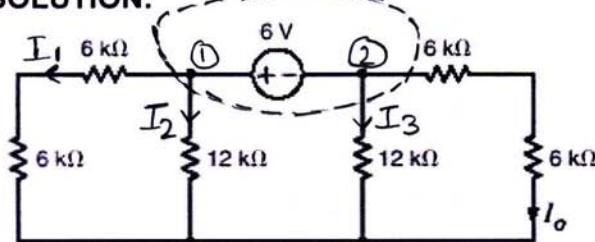

KCL at supernode: $I_1 + I_2 + I_3 + I_o = 0$

$$\frac{V_1}{6K+6K} + \frac{V_1}{12K} + \frac{V_2}{12K} + \frac{V_2}{6K+6K} = 0$$

$$\frac{V_1 + V_1 + V_2 + V_2}{2V_1 + 2V_2} = 0$$

$$2V_1 + 2V_2 = 0$$

$$V_1 - V_2 = 6$$

$$2V_1 + 2V_2 = 0$$

$$V_1 - V_2 = 6$$

$$V_1 = 3 \text{ V}$$

$$V_2 = -3 \text{ V}$$

$$I_o = \frac{V_2}{12K}$$

$$= \frac{-3}{12K}$$

$$I_o = -0.25 \text{ mA}$$

3.20 Use nodal analysis to find I_o in the circuit in Fig. P3.20.


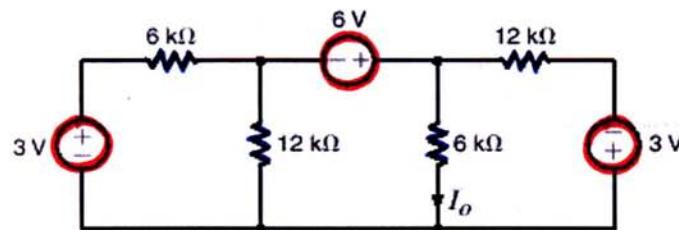


Figure P3.20

SOLUTION:

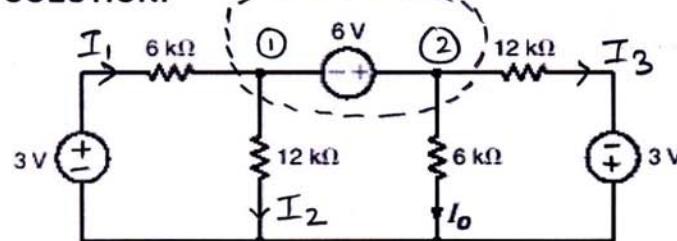

$$\text{KCL at supernode : } I = I_2 + I_o + I_3$$

$$\frac{3 - V_1}{6K} = \frac{V_1}{12K} + \frac{V_2}{6K} + \frac{V_2 - (-3)}{12K}$$

$$6 - 2V_1 = V_1 + 2V_2 + V_2 + 3$$

$$\boxed{3V_1 + 3V_2 = 3}$$

$$V_2 - V_1 = 6$$

$$\boxed{-V_1 + V_2 = 6}$$

$$\begin{aligned} 3V_1 + 3V_2 &= 3 \\ -V_1 + V_2 &= 6 \end{aligned}$$

$$V_1 = -2.5 \text{ V}$$

$$V_2 = 3.5 \text{ V}$$

$$I_o = \frac{V_2}{6K}$$

$$= \frac{3.5}{6K}$$

$$I_o = 0.583 \text{ mA}$$

- 3.21 Using nodal analysis, find V_o in the network in Fig. P3.21.


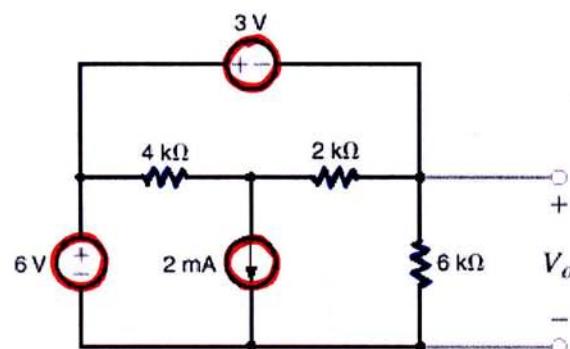


Figure P3.21

SOLUTION:

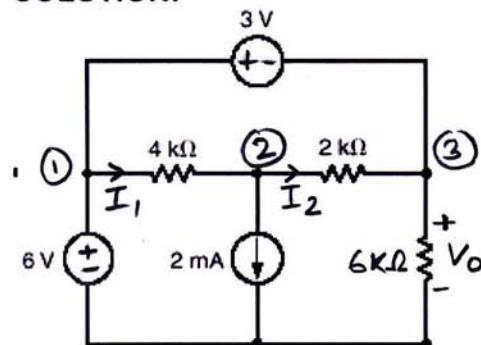

$$KCL \text{ at } (2) : I_1 = 2m + I_2$$

$$\frac{V_1 - V_2}{4K} = 2m + \frac{V_2 - V_3}{2K}$$

$$V_1 - V_2 = 8 + 2V_2 - 2V_3$$

$$3V_2 - 2V_3 = -2$$

$$V_1 - V_3 = 3$$

$$-V_3 = 3 - 6$$

$$V_3 = 3V$$

$$V_o = V_3 = 3V$$

$$V_o = 3V$$

3.22 Find V_o in the network in Fig. P3.22 using nodal analysis.


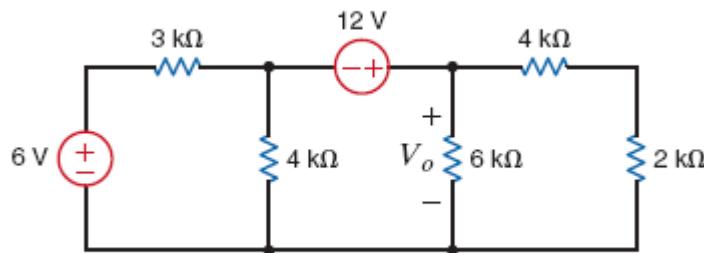


Figure P3.22

SOLUTION:

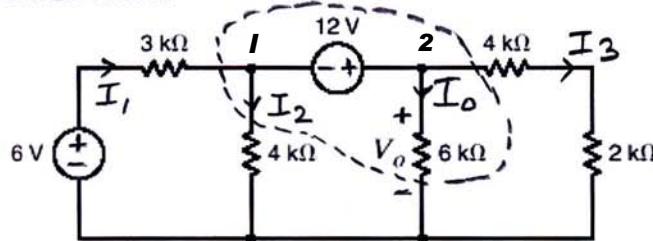

$$\text{KCL at supernode: } I_1 = I_2 + I_o + I_3$$

$$\frac{6 - V_1}{3k} = \frac{V_1}{4k} + \frac{V_2}{6k} + \frac{V_2}{4k + 2k}$$

$$24 - 4V_1 = 3V_1 + 2V_2 + 2V_2$$

$$\boxed{7V_1 + 4V_2 = 24}$$

$$V_2 - V_1 = 12$$

$$\boxed{-V_1 + V_2 = 12}$$

$$\begin{aligned} 7V_1 + 4V_2 &= 24 \\ -V_1 + V_2 &= 12 \end{aligned}$$

$$V_1 = -2.18 \text{ V}$$

$$V_2 = 9.82 \text{ V}$$

$$V_o = V_2 = 9.82 \text{ V}$$

$$V_o = 9.82 \text{ V}$$

3.23 Find V_o in the circuit in Fig. P3.23 using nodal analysis.


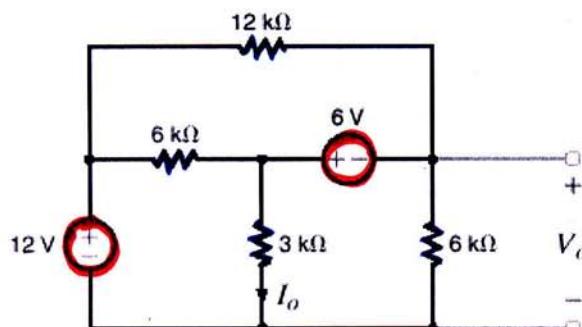


Figure P3.23

SOLUTION:

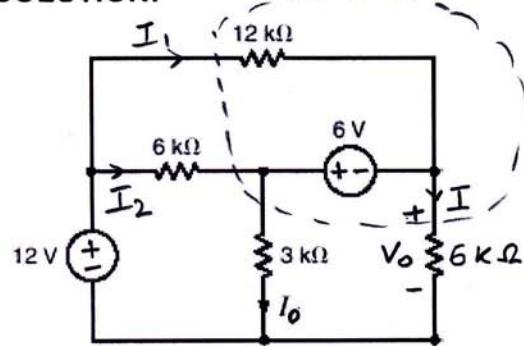

$$\text{KCL at supernode: } I_1 + I_2 = I_o + I$$

$$\frac{V_1 - V_3}{12\text{K}} + \frac{V_1 - V_2}{6\text{K}} = \frac{V_2}{3\text{K}} + \frac{V_3}{6\text{K}}$$

$$V_1 - V_3 + 2V_1 - 2V_2 = 4V_2 + 2V_3$$

$$V_1 = 12\text{V}$$

$$6V_2 + 3V_3 = 36$$

$$V_2 - V_3 = 6$$

$$6V_2 + 3V_3 = 36$$

$$V_2 - V_3 = 6$$

$$V_2 = 6\text{V}$$

$$V_3 = 0\text{V}$$

$$V_o = V_3 - 0\text{V}$$

$$V_o = 0\text{V}$$

3.24 Use nodal analysis to find V_o in the circuit in Fig. P3.24.


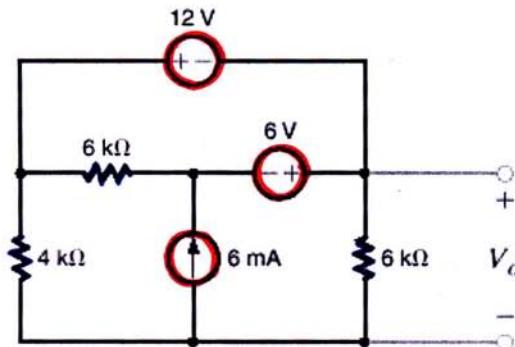


Figure P3.24

SOLUTION:

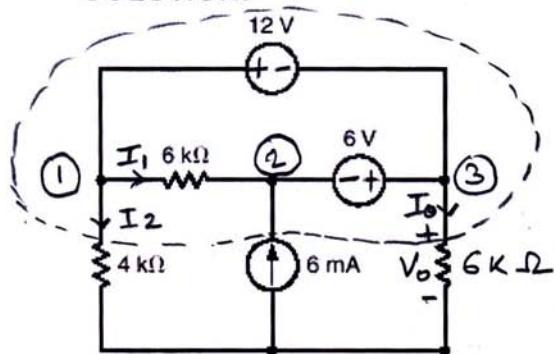

$$\text{KCL at supernode: } 6m = I_2 + I_o$$

$$\frac{V_1}{4K} + \frac{V_3}{6K} = 6m$$

$$3V_1 + 2V_3 = 72$$

$$V_1 - V_3 = 12$$

$$\begin{aligned} 3V_1 + 2V_3 &= 72 \\ V_1 - V_3 &= 12 \end{aligned}$$

$$V_1 = 19.2 \text{ V}$$

$$V_3 = 7.2 \text{ V}$$

$$V_o = V_3 = 7.2 \text{ V}$$

$$V_o = 7.2 \text{ V}$$

3.25 Find V_o in the circuit in Fig. P3.25.


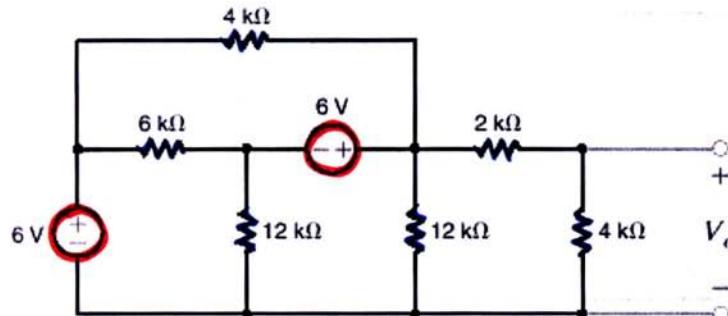


Figure P3.25

SOLUTION:

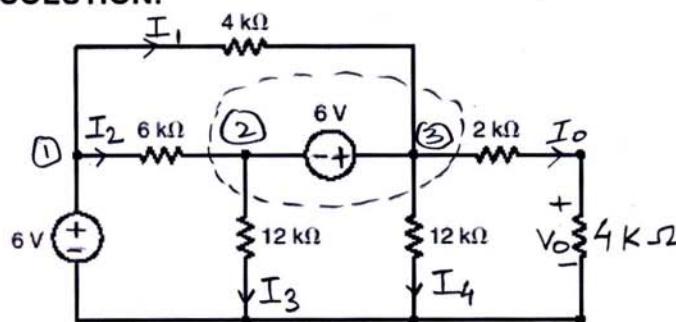

$$\text{KCL at super node: } I_1 + I_2 = I_3 + I_4 + I_o$$

$$\frac{V_1 - V_3}{4K} + \frac{V_1 - V_2}{6K} = \frac{V_2}{12K} + \frac{V_3}{12K} + \frac{V_3}{2K + 4K}$$

$$3V_1 - 3V_3 + 2V_1 - 2V_2 = V_2 + V_3 + 2V_3$$

$$V_1 = 6V$$

$$3V_2 + 6V_3 = 30$$

$$V_3 - V_2 = 6$$

$$-V_2 + V_3 = 6$$

$$3V_2 + 6V_3 = 30$$

$$-V_2 + V_3 = 6$$

$$V_2 = -0.667V$$

$$V_3 = 5.33V$$

$$I_o = \frac{V_3}{2K + 4K} = \frac{5.33}{6K} = 0.888mA$$

$$V_o = I_o(4K) = 0.888(4) = 3.55V$$

3.26 Find V_o in the circuit in Fig. P3.26 using nodal analysis.


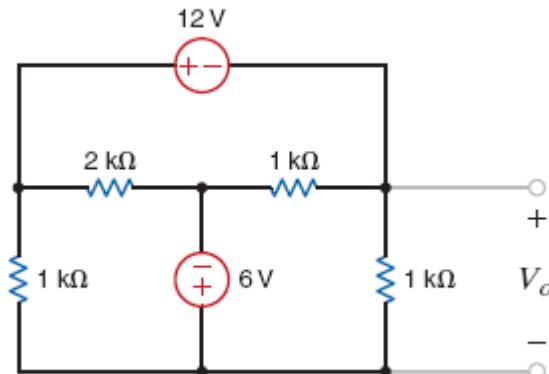


Figure P3.26

SOLUTION:

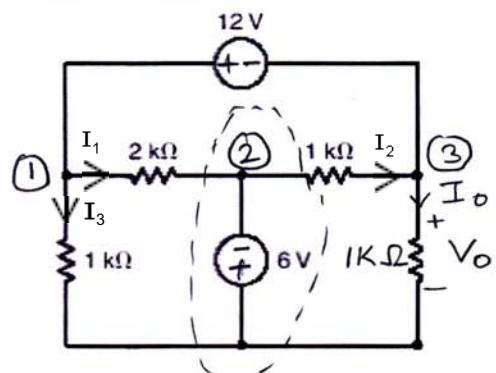

$$\text{KCL at supernode: } I_1 + I_3 + I_o = I_2$$

$$\frac{V_1 - V_2}{2k\Omega} + \frac{V_1}{1k\Omega} + \frac{V_3}{1k\Omega} = \frac{V_2 - V_3}{1k\Omega}$$

$$V_1 - V_2 + 2V_1 + 2V_3 = 2V_2 - 2V_3$$

$$V_2 = -6V$$

$$3V_1 + 4V_3 = -18$$

$$V_1 - V_3 = 12$$

$$V_1 = 4.29 V$$

$$V_3 = -7.71 V$$

$$V_o = V_3 = -7.71 V$$

$$V_o = -7.71 V$$

3.27 Use nodal analysis to find V_o in the circuit in Fig. P3.27.


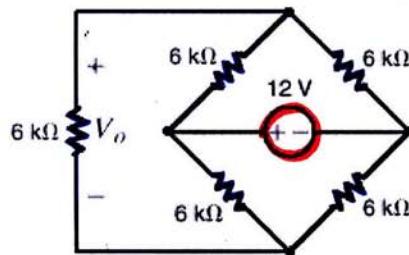


Figure P3.27

SOLUTION:

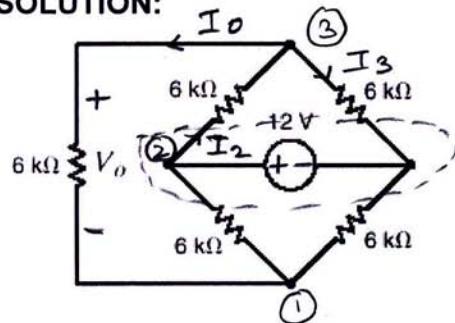

$$\text{KCL at supernode: } I_1 + I_4 + I_3 = I_2$$

$$\frac{V_1}{6k} + \frac{V_1 - V_2}{6k} + \frac{V_3}{6k} = \frac{V_2 - V_3}{6k}$$

$$V_1 + V_1 - V_2 + V_3 = V_2 - V_3$$

$$\boxed{2V_1 - 2V_2 + 2V_3 = 0}$$

$$\text{KCL at } \textcircled{1} : I_0 = I_1 + I_4$$

$$\frac{V_3 - V_1}{6k} = \frac{V_1}{6k} + \frac{V_1 - V_2}{6k}$$

$$V_3 - V_1 = V_1 + V_1 - V_2$$

$$\boxed{3V_1 - V_2 - V_3 = 0}$$

$$\boxed{V_2 = 12V}$$

$$\boxed{2V_1 + 2V_3 = 24}$$

$$\boxed{3V_1 - V_3 = 12}$$

$$2V_1 + 2V_3 = 24$$

$$3V_1 - V_3 = 12$$

$$\begin{aligned}2V_1 + 2V_3 &= 24 \\3V_1 - V_3 &= 12\end{aligned}$$

$$V_1 = 6 \text{ V}$$

$$V_3 = 6 \text{ V}$$

$$\begin{aligned}V_o &= V_3 - V_1 = 6 - 6 \\V_o &= 0 \text{ V}\end{aligned}$$

It should be noted that this circuit is a balanced Wheatstone bridge. Therefore, the output voltage is zero.

3.28 Use nodal analysis to find V_o in the circuit in Fig. P3.28.


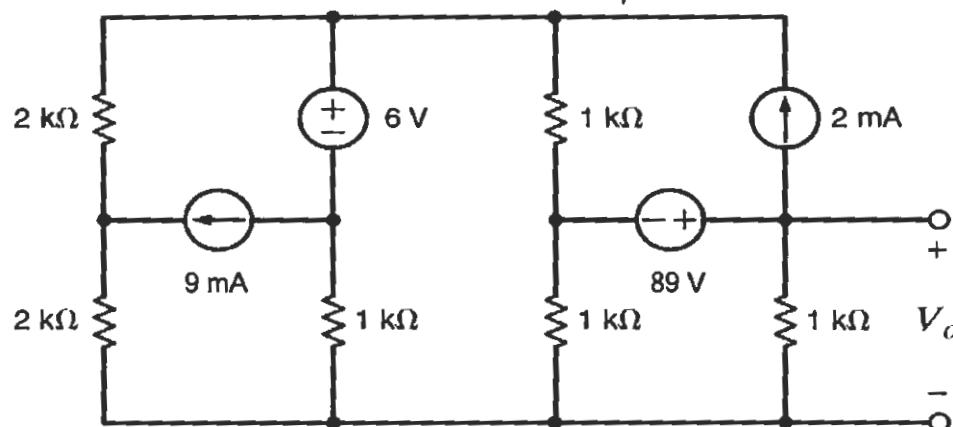


Figure P3.28

SOLUTION: 3.28

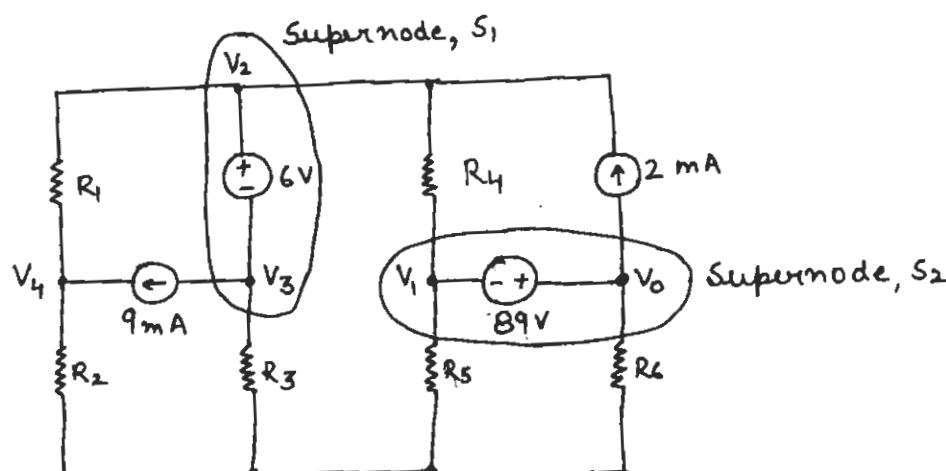

$$R_1 = R_2 = 2 \text{ k}\Omega, R_3 = R_4 = R_5 = R_6 = 1 \text{ k}\Omega$$

$$V_2 - V_3 = 6 \text{ V} \quad \text{--- } (1)$$

$$V_0 - V_1 = 89 \text{ V} \quad \text{--- } (2)$$

$$\text{KCL @ } S_1: \frac{V_2 - V_4}{R_1} + \frac{V_2 - V_1}{R_4} - 2 \times 10^{-3} + 9 \times 10^{-3} + \frac{V_3}{R_3} = 0$$

$$-2V_1 + 3V_2 + 2V_3 - V_4 = -14 \quad \text{--- } (3)$$

$$\text{KCL @ } S_2: 2 \times 10^{-3} + \frac{V_0}{R_6} + \frac{V_1 - V_2}{R_4} + \frac{V_1}{R_5} = 0$$

$$V_0 + 2V_1 - V_2 = -2 \quad \text{--- } (4)$$

$$\text{KCL at } V_4: \frac{V_4 - V_2}{R_1} - 9 \times 10^{-3} + \frac{V_4}{R_2} = 0$$

$$V_4 = 9 + \frac{V_2}{2} \quad \text{---} \quad (5)$$

Substituting equations (1), (2) and (5) in (3), we get

$$-2(V_0 - 89) + 3V_2 + 2(V_2 - 6) - \left(9 + \frac{V_2}{2}\right) = -14$$

$$-4V_0 + 9V_2 = -342 \quad \text{---} \quad (6)$$

Substituting equation (1) in (4), we get

$$V_2 = 3V_0 - 176$$

Substituting the value of V_2 in equation (6), we get

$$-4V_0 + 9(3V_0 - 176) = -342$$

$$V_0 = 53.7 \text{ V}$$

$$\boxed{V_0 = 54.0 \text{ V}}$$

3.29 Find V_o in the network in Fig. P3.29.


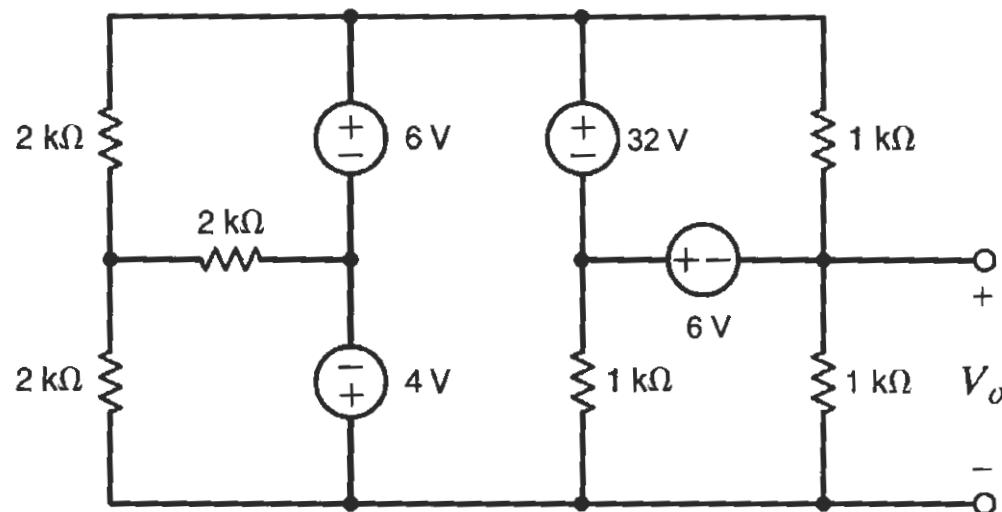


Figure P3.29

SOLUTION: 3.29

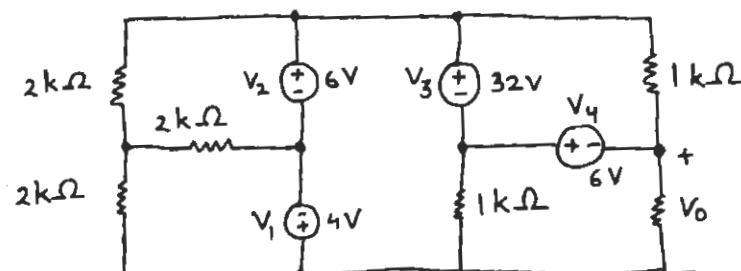

$$\begin{aligned} \text{KVL : } & V_1 - V_2 + V_3 + V_4 + V_o = 0 \\ & 4 - 6 + 32 + 6 + V_o = 0 \\ & 36 + V_o = 0 \\ & V_o = -36.0 \text{ V} \end{aligned}$$

3.30 Find I_o in the circuit in Fig. P3.30 using nodal analysis.


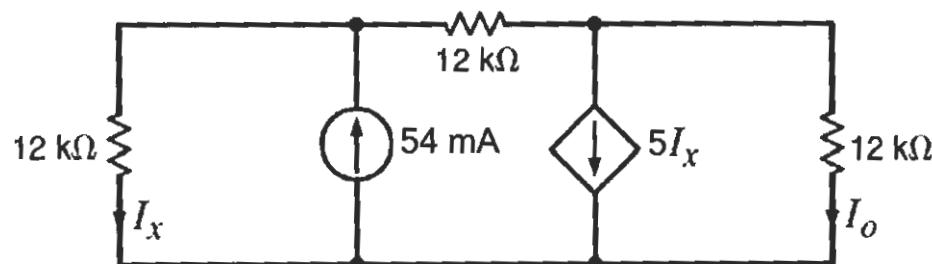


Figure P3.30

SOLUTION: 3.30

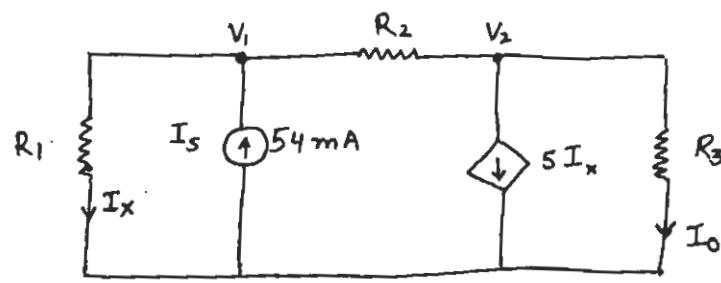

$$R_1 = R_2 = R_3 = 12 \text{ k}\Omega$$

$$\text{KCL @ } V_1 : \frac{V_1}{R_1} - I_s + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1}{12 \times 10^3} - 54 \times 10^{-3} + \frac{V_1 - V_2}{12 \times 10^3} = 0$$

$$2V_1 - V_2 = 648 \quad \text{--- } ①$$

$$I_x = \frac{V_1}{R_1}$$

$$I_o = \frac{V_2}{R_3} \quad \text{--- } ②$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_2} + 5I_x + \frac{V_2}{R_3} = 0$$

$$\frac{V_2 - V_1}{12 \times 10^3} + 5 \cdot \frac{V_1}{12 \times 10^3} + \frac{V_2}{12 \times 10^3} = 0$$

$$2V_1 + V_2 = 0 \quad \text{---} \quad (3)$$

From equations (1) and (3), we get

$$V_2 = -324 \text{ V}$$

Substituting the value of V_2 in equation (2), we get

$$I_0 = \frac{V_2}{R_3}$$

$$\boxed{I_0 = -27.0 \text{ mA}}$$

3.31 Find V_o in the circuit in Fig. P3.31 using nodal analysis.


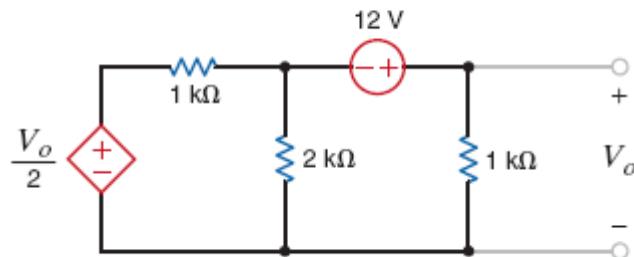


Figure P3.31

SOLUTION:

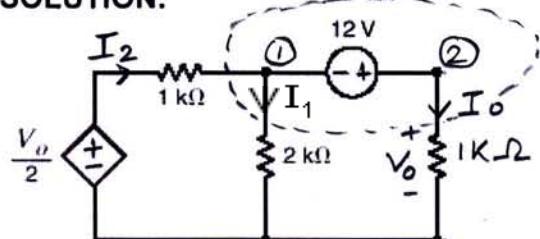

$$\text{KCL at supernode: } I_2 = I_1 + I_o$$

$$\frac{\frac{V_o}{2} - V_1}{1\text{ k}\Omega} = \frac{V_1}{2\text{ k}\Omega} + \frac{V_2}{1\text{ k}\Omega}$$

$$V_o = V_2$$

$$\frac{\frac{V_2}{2} - V_1}{1\text{ k}\Omega} = \frac{V_1}{2\text{ k}\Omega} + \frac{V_2}{1\text{ k}\Omega}$$

$$V_2 - 2V_1 = V_1 + 2V_2$$

$$\boxed{3V_1 + V_2 = 0}$$

$$V_2 - V_1 = 12$$

$$\boxed{-V_1 + V_2 = 12}$$

$$3V_1 + V_2 = 0$$

$$-V_1 + V_2 = 12$$

$$V_1 = -3V$$

$$V_2 = 9 \text{ V}$$

$$V_o = V_2 = 9 \text{ V}$$

$$V_o = 9 \text{ V}$$

3.32 Find V_o in the circuit in Fig. P3.32.


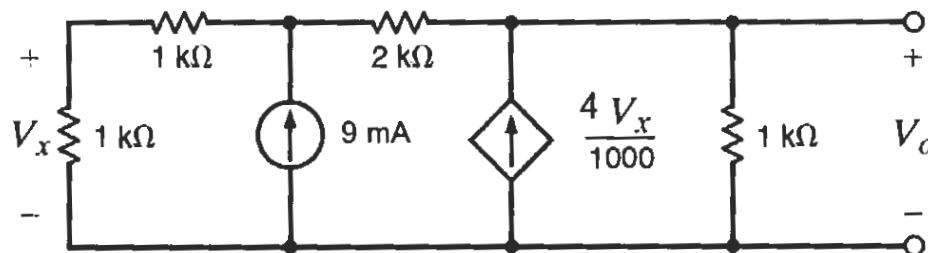


Figure P3.32

SOLUTION: 3.32

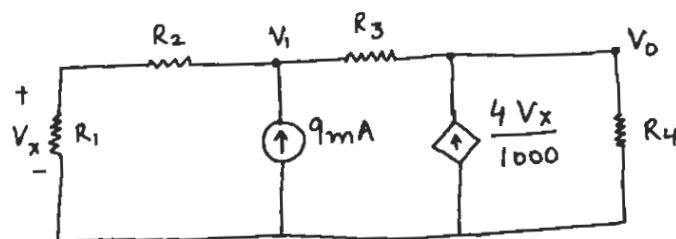

$$R_1 = R_2 = 1 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega$$

$$\text{KCL @ } V_1 : \frac{V_1}{R_1 + R_2} - 9 \times 10^{-3} + \frac{V_1 - V_o}{R_3} = 0$$

$$\frac{V_1}{2 \times 10^3} + \frac{V_1 - V_o}{2 \times 10^3} = 9 \times 10^{-3}$$

$$2V_1 - V_o = 18 \quad \text{--- (1)}$$

$$\text{Voltage Division : } V_x = V_1 \frac{R_1}{R_1 + R_2}$$

$$V_x = \frac{V_1}{2} \quad \text{--- (2)}$$

$$\text{KCL @ } V_o : \frac{-4V_x}{1000} + \frac{V_o - V_1}{R_3} + \frac{V_o}{R_4} = 0$$

$$\frac{V_o - V_1}{2 \times 10^3} + \frac{V_o}{1 \times 10^3} = \frac{4V_x}{1000} \quad \text{--- (3)}$$

Substituting equation (2) in (3), we get

$$5V_1 - 3V_o = 0 \quad \text{--- (4)}$$

From equation (1) and (4), we get

$V_o = 90.0 \text{ V}$

3.33 Use nodal analysis to find V_o in the circuit in Fig. P3.33.


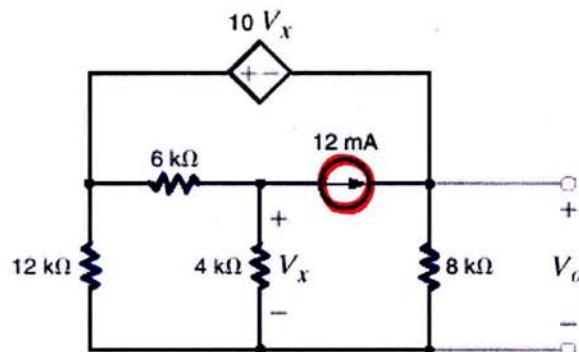


Figure P3.33

SOLUTION:

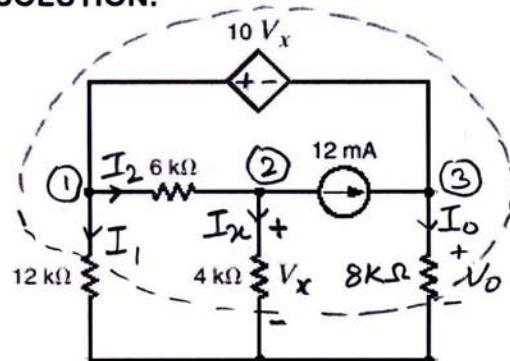

$$\text{KCL at supernode: } I_1 + I_x + I_o = 0$$

$$\frac{V_1}{12\text{K}} + \frac{V_2}{4\text{K}} + \frac{V_3}{8\text{K}} = 0$$

$$\boxed{2V_1 + 6V_2 + 3V_3 = 0}$$

$$\text{KCL at } \textcircled{2}: I_2 = I_x + 12\text{mA}$$

$$\frac{V_1 - V_2}{6\text{K}} = \frac{V_2}{4\text{K}} + 12\text{mA}$$

$$2V_1 - 2V_2 = 3V_2 + 144$$

$$\boxed{2V_1 - 5V_2 = 144}$$

$$V_1 - V_3 = 10V_x$$

$$V_x = V_2$$

$$V_1 - V_3 = 10V_2$$

$$\boxed{V_1 - 10V_2 - V_3 = 0}$$

$$2V_1 + 6V_2 + 3V_3 = 0$$

$$2V_1 - 5V_2 + 0V_3 = 144$$

$$V_1 - 10V_2 - V_3 = 0$$

$$V_1 = 150.26 \text{ V}$$

$$V_2 = 31.3 \text{ V}$$

$$V_3 = -162.78 \text{ V}$$

$$V_0 = V_3 = -162.78 \text{ V}$$

$$V_0 = -162.78 \text{ V}$$

3.34 Use nodal analysis to find V_o in the circuit in Fig. P3.34.


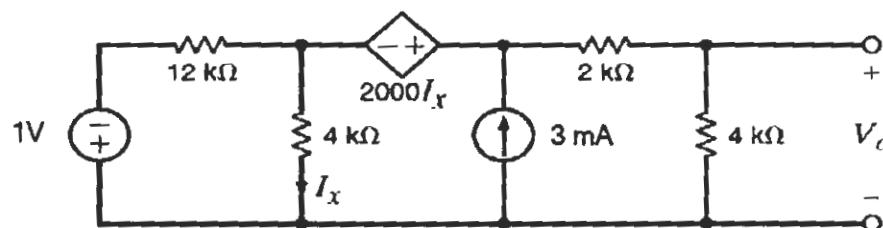


Figure P3.34

SOLUTION: 3.34

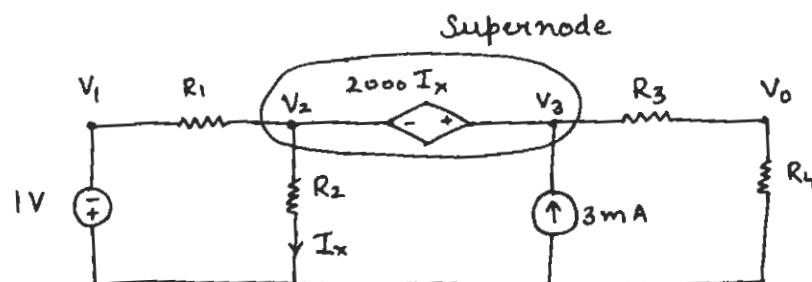

$$R_1 = 12 \text{ k}\Omega, R_2 = R_4 = 4 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega$$

$$V_1 = -1 \text{ V} \quad \text{--- } ①$$

$$V_3 - V_2 = 2000 I_x \quad \text{--- } ②$$

$$I_x = \frac{V_2}{R_2} = \frac{V_2}{4 \times 10^3} \quad \text{--- } ③$$

Substituting equation ③ in ②, we get

$$V_3 - \frac{3}{2} V_2 = 0 \\ V_2 = \frac{2}{3} V_3 \quad \text{--- } ④$$

KCL @ Supernode:

$$\frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3 - V_0}{R_3} - 3 \times 10^{-3} = 0$$

$$\frac{V_2 - V_1}{12 \times 10^3} + \frac{V_2}{4 \times 10^3} + \frac{V_3 - V_0}{2 \times 10^3} - 3 \times 10^{-3} = 0$$

$$6 V_3 + 4 V_2 - V_1 - 6 V_0 = 36 \quad \text{--- } ⑤$$

KCL @ V_0 :

$$\frac{V_0}{R_4} + \frac{V_0 - V_3}{R_3} = 0$$

$$\frac{V_0}{4 \times 10^3} + \frac{V_0 - V_3}{2 \times 10^3} = 0$$

$$3V_0 - 2V_3 = 0$$

$$V_3 = \frac{3}{2}V_0 \quad \text{---} \quad (6)$$

Substituting equations (1) and (4) in (5), we get

$$26V_3 - 18V_0 = 105 \quad \text{---} \quad (7)$$

Substituting equation (6) in (7), we get

$$21V_0 = 105$$

$$\boxed{V_0 = 5.00 \text{ V}}$$

- 3.35 Determine V_o in the network in Fig. P3.35 using nodal analysis.


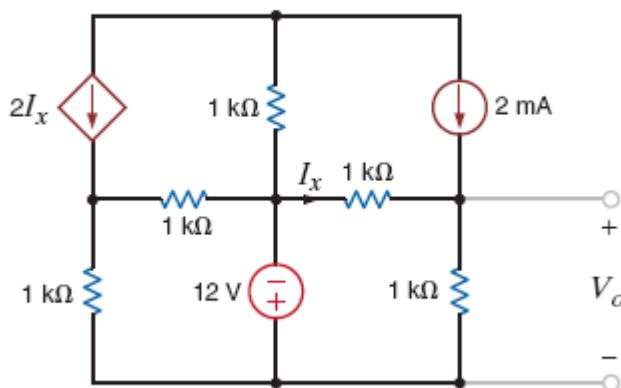


Figure P3.35

SOLUTION:

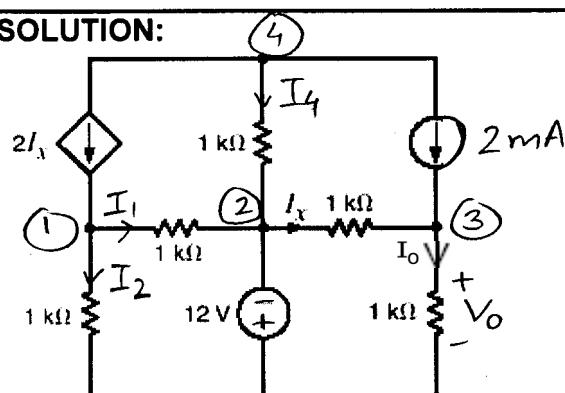

$$\text{KCL at } (4) : 2I_x + I_4 + 2m = 0$$

$$I_x = \frac{V_2 - V_3}{1k}$$

$$2 \left[\frac{V_2 - V_3}{1k} \right] + \frac{V_4}{1k} + 2m = 0$$

$$2V_2 - 2V_3 + V_4 + 2 = 0$$

$$2V_2 - 2V_3 + V_4 = -2$$

$$\text{KCL at } \textcircled{3}: I_x + 2m = I_0$$

$$\frac{V_2 - V_3}{1k} + 2m = \frac{V_3}{1k}$$

$$V_2 - V_3 + 2 = V_3$$

$$V_2 - 2V_3 = -2$$

$$\text{KCL at } \textcircled{1}: 2I_x = I_1 + I_2$$

$$2 \left[\frac{V_2 - V_3}{1k} \right] = \frac{V_1 - V_2}{1k} + \frac{V_1}{1k}$$

$$2V_2 - 2V_3 = V_1 - V_2 + V_1$$

$$2V_1 - 3V_2 + 2V_3 = 0$$

$$V_2 = -12V$$

$$-12 - 2V_3 = -2$$

$$-2V_3 = 10$$

$$V_3 = -5V$$

$$V_0 = V_3 = -5V$$

$$V_0 = -5V$$

3.36 Determine V_o in the network in Fig. P3.36.


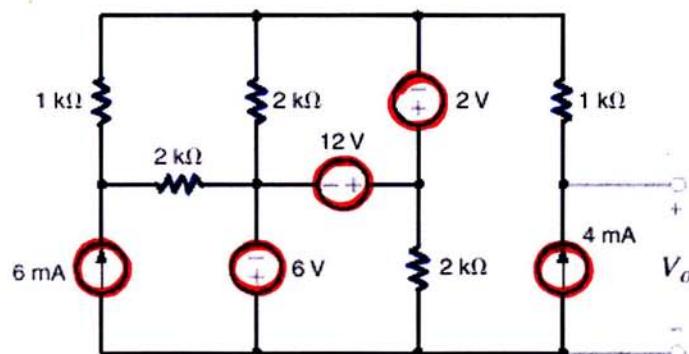


Figure P3.36

SOLUTION:

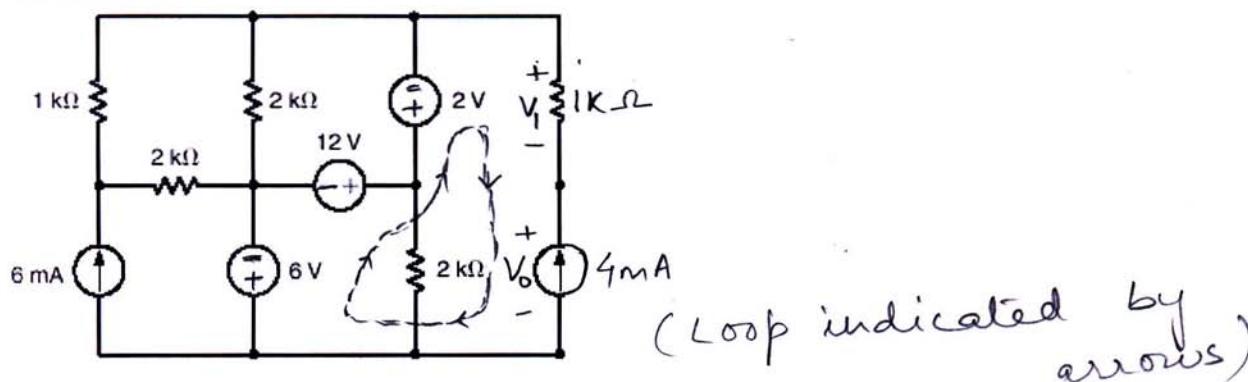

$$V_1 = 1k(-4m) = -4V$$

$$\begin{aligned} \text{KVL: } 12 &= 6 + 2 + V_1 + V_o \\ \text{in loop} \quad V_o &= 12 - 8 + 4 \end{aligned}$$

$$V_o = 8V$$

3.37 Find I_o in the circuit in Fig. P3.37.


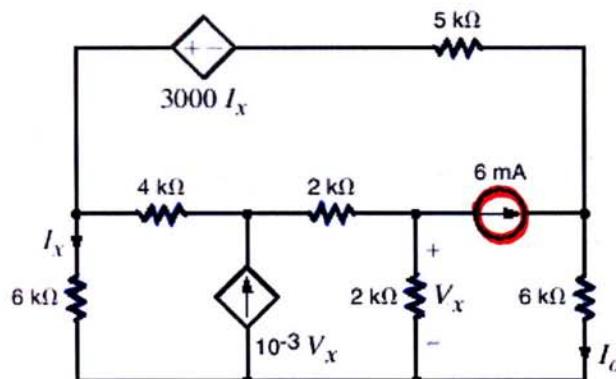


Figure P3.37

SOLUTION:

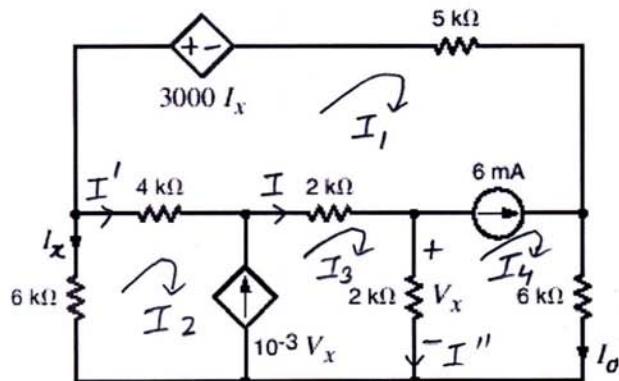

$$I_2 = -I_x \quad ; \quad I_4 = I_o$$

$$\text{KCL} : I_2 = I' + I''$$

$$I' = I_2 - I_1$$

$$\text{KCL} : I'' + I_4 = I_3$$

$$I'' = I_3 - I_4$$

$$\text{KCL} : I = I'' + 6\text{mA}$$

$$I = I_3 - I_4 + 6\text{mA}$$

$$\text{KCL} : I_3 = 10^{-3} V_x + I_2$$

$$-I_2 + I_3 = 10^{-3} V_x$$

$$V_x = 2k I''$$

$$V_x = 2k (I_3 - I_4)$$

$$-I_2 + I_3 = 10^{-3} (2K) (I_3 - I_4)$$

$$\boxed{I_2 + I_3 - 2I_4 = 0}$$

$$KCL : I_1 + 6m = I_4$$

$$\boxed{I_1 - I_4 = -6m}$$

$$KVL : 3000I_x + 5KI_1 + 6KI_4 + 6KI_2 = 0$$

$$3000(-I_2) + 5KI_1 + 6KI_4 + 6KI_2 = 0$$

$$\boxed{5KI_1 + 3KI_2 + 6KI_4 = 0}$$

$$KVL : 4KI' + 2KI + 2KI'' + 6KI_2 = 0$$

$$0 = 4K(I_2 - I_1) + 2K(I_3 - I_4 + 6m) + 2K(I_3 - I_4) + 6KI_2$$

$$\boxed{-4KI_1 + 10KI_2 + 4KI_3 - 4KI_4 = -12}$$

$$I_2 + I_3 - 2I_4 = 0$$

$$I_1 - I_4 = -6m$$

$$5KI_1 + 3KI_2 + 6KI_4 = 0$$

$$-4KI_1 + 10KI_2 + 4KI_3 - 4KI_4 = -12$$

$$I_1 = -1.64 \text{ mA}$$

$$I_2 = -6 \text{ mA}$$

$$I_3 = 14.7 \text{ mA}$$

$$I_4 = 4.36 \text{ mA}$$

$$I_o = I_4$$

$$I_o = 4.36 \text{ mA}$$

- 3.38 Use nodal analysis to solve for I_A in the network in Fig. P3.38.


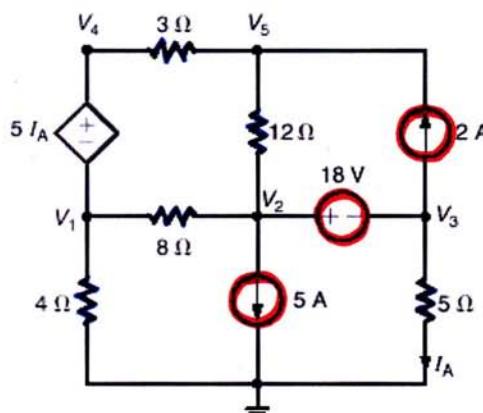


Figure P3.38

SOLUTION:

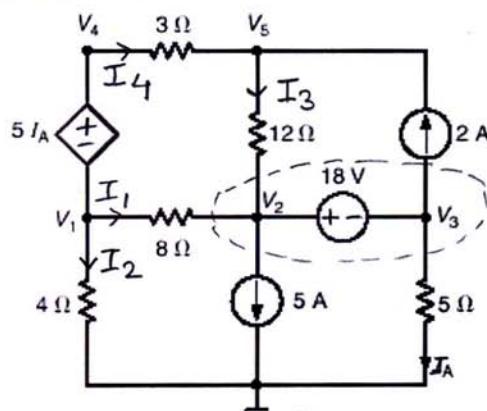

$$\text{KCL at } \textcircled{5} : \quad -I_4 + 2 = I_3$$

$$\frac{V_4 - V_5}{3} + 2 = \frac{V_5 - V_2}{12}$$

$$4V_4 - 4V_5 + 24 = V_5 - V_2$$

$$\boxed{V_2 + 4V_4 - 5V_5 = -24}$$

$$\text{KCL at supernode: } I_3 + I_1 = 5 + I_A + 2$$

$$\frac{V_5 - V_2}{12} + \frac{V_1 - V_2}{8} = 5 + \frac{V_3}{5} + 2$$

$$5V_5 - 5V_2 + 7.5V_1 - 7.5V_2 = 300 + 12V_3 + 120$$

$$\boxed{-7.5V_1 - 12.5V_2 - 12V_3 + 5V_5 = 420}$$

$$V_4 - V_1 = 5I_A$$

$$I_A = \frac{V_3}{5}$$

$$V_4 - V_1 = 5(V_3/5)$$

$$V_4 - V_1 = V_3$$

$$\boxed{V_2 - V_3 = 18}$$

$$\boxed{-V_1 - V_3 + V_4 = 0}$$

KCL at reference: $I_2 + 5 + I_A = 0$

$$\frac{V_1}{4} + 5 + \frac{V_3}{5} = 0$$

$$5V_1 + 100 + 4V_3 = 0$$

$$\boxed{5V_1 + 4V_3 = -100}$$

$$0V_1 + V_2 + 0V_3 + 4V_4 - 5V_5 = -24$$

$$7.5V_1 - 12.5V_2 - 12V_3 + 0V_4 + 5V_5 = 120$$

$$-V_1 + 0V_2 - V_3 + V_4 + 0V_5 = 0$$

$$0V_1 + V_2 - V_3 + 0V_4 + 0V_5 = 18$$

$$5V_1 + 0V_2 + 4V_3 + 0V_4 + 0V_5 = -100$$

$$V_1 = 3.22 \text{ V}$$

$$V_2 = -11.02 \text{ V}$$

$$V_3 = -29.02 \text{ V}$$

$$V_4 = -25.81 \text{ V}$$

$$V_5 = -18.05 \text{ V}$$

$$I_A = \frac{V_3}{5} = \frac{-29.02}{5}$$

$$I_A = -5.8 \text{ A}$$

- 3.39 Use nodal analysis to find V_1 , V_2 , V_3 , and V_4 in the circuit in Fig. P3.39.

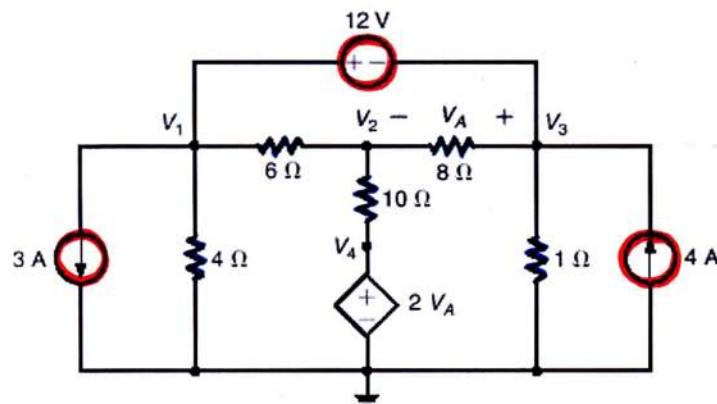
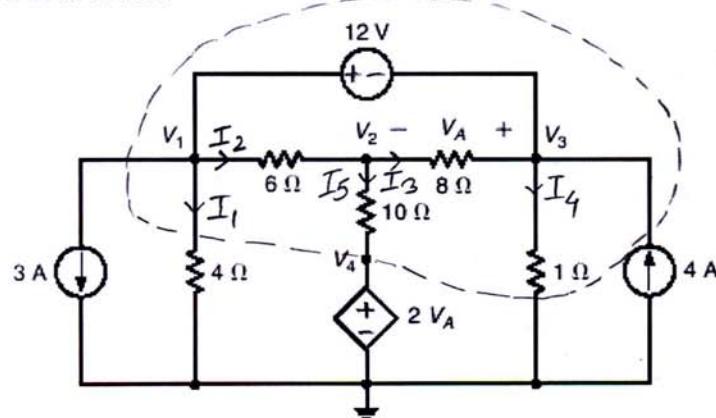


Figure P3.39

SOLUTION:

$$KCL \text{ at } (2): I_2 = I_5 + I_3$$

$$\frac{V_1 - V_2}{6} = \frac{V_2 - V_4}{10} + \frac{V_2 - V_3}{8}$$

$$\begin{aligned} 5V_1 - 5V_2 &= 3V_2 - 3V_4 + 3.75V_2 - 3.75V_3 \\ 5V_1 - 11.75V_2 + 3.75V_3 + 3V_4 &= 0 \end{aligned}$$

$$KCL \text{ at supernode: } 3 + I_1 + I_5 + I_4 = 4$$

$$\frac{V_1}{4} + \frac{V_2 - V_4}{10} + \frac{V_3}{1} = 1$$

$$5V_1 + 2V_2 - 2V_4 + 20V_3 = 20$$

$$5V_1 + 2V_2 + 20V_3 - 2V_4 = 20$$

$$V_1 - V_3 = 12$$

$$V_4 = 2V_A$$

$$V_A = V_3 - V_2$$

$$V_4 = 2(V_3 - V_2)$$

$$-2V_2 + 2V_3 - V_4 = 0$$

$$5V_1 - 11.75V_2 + 3.75V_3 + 3V_4 = 0$$

$$5V_1 + 2V_2 + 20V_3 - 2V_4 = 20$$

$$V_1 + 0V_2 - V_3 + 0V_4 = 12$$

$$0V_1 - 2V_2 + 2V_3 - V_4 = 0$$

$$V_1 = 9.68 \text{ V}$$

$$V_2 = 1.45 \text{ V}$$

$$V_3 = -2.32 \text{ V}$$

$$V_4 = -7.54 \text{ V}$$

- 3.40 Use nodal analysis to find V_1 , V_2 , V_3 , and V_4 in the network in Fig. P3.40


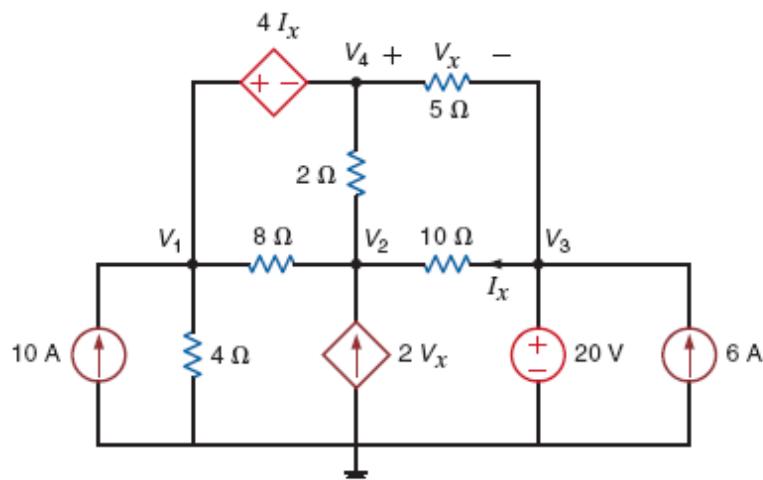


Figure P3.40

SOLUTION:

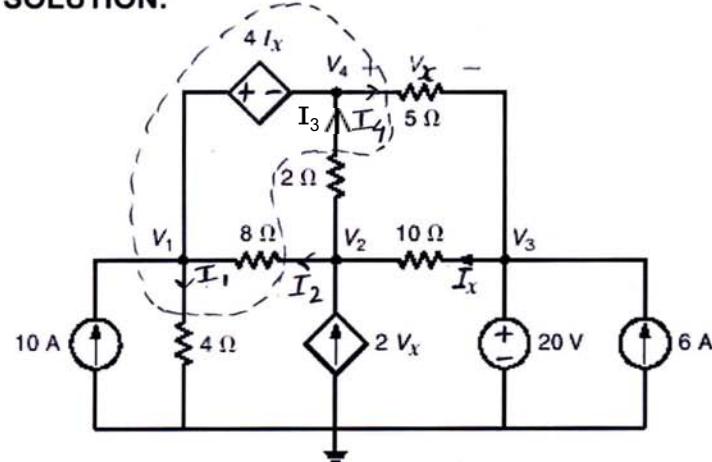

$$KCL \text{ at } (2) : 2V_x + I_x = I_2 + I_3$$

$$V_x = V_4 - V_3$$

$$2(V_4 - V_3) + \frac{V_3 - V_2}{10} = \frac{V_2 - V_1}{8} + \frac{V_2 - V_4}{2}$$

$$80V_4 - 80V_3 + 4V_3 - 4V_2 = 5V_2 - 5V_1 + 20V_2 - 20V_4$$

$$\boxed{5V_1 - 29V_2 - 76V_3 + 100V_4 = 0}$$

$$V_3 = 20V$$

$$\boxed{5V_1 - 29V_2 + 100V_4 = 1520}$$

$$KCL \text{ at supernode} : 10 + I_2 + I_3 = I_1 + I_4$$

$$10 + \frac{V_2 - V_1}{8} + \frac{V_2 - V_4}{2} = \frac{V_1}{4} + \frac{V_4 - V_3}{5}$$

$$400 + 5V_2 - 5V_1 + 20V_2 - 20V_4 = 10V_1 + 8V_4 - 8V_3$$

$$\boxed{-15V_1 + 25V_2 + 8V_3 - 28V_4 = -400}$$

$$\boxed{-15V_1 + 25V_2 - 28V_4 = -560}$$

$$V_1 - V_4 = 4I_x$$

$$I_x = \frac{V_3 - V_2}{10}$$

$$V_1 - V_4 = 4 \left(\frac{V_3 - V_2}{10} \right)$$

$$10V_1 - 10V_4 = 4V_3 - 4V_2$$

$$\boxed{10V_1 + 4V_2 - 4V_3 - 10V_4 = 0}$$

$$\boxed{10V_1 + 4V_2 - 10V_4 = 80}$$

$$5V_1 - 24V_2 + 100V_4 = 1520$$

$$-15V_1 + 25V_2 - 28V_4 = -560$$

$$10V_1 + 4V_2 - 10V_4 = 80$$

$$V_1 = 21.14 \text{ V}$$

$$V_2 = 9.07 \text{ V}$$

$$V_4 = 16.77 \text{ V}$$

$$V_3 = 20 \text{ V}$$

3.41 Find I_o in the network in Fig. P3.41 using nodal analysis.


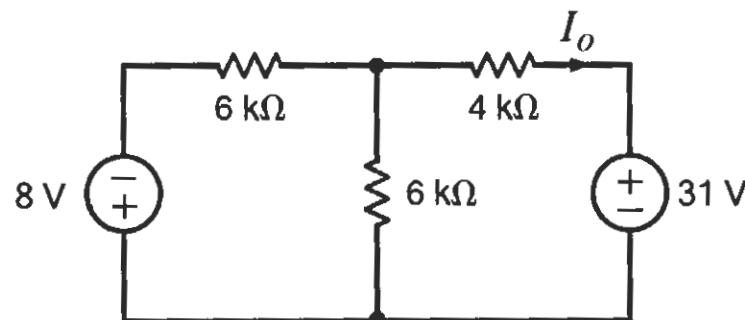


Figure P3.41

SOLUTION: 3.41

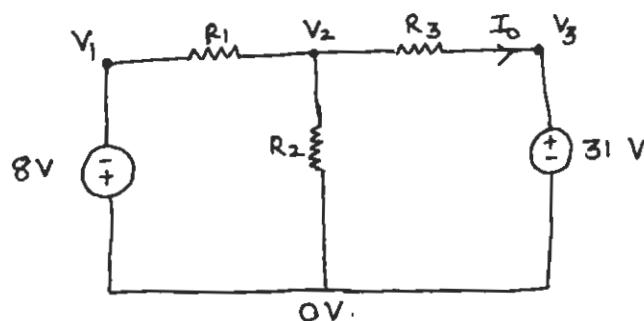

$$R_1 = R_2 = 6 \text{ k}\Omega, \quad R_3 = 4 \text{ k}\Omega, \quad I_o = \frac{V_2 - V_3}{R_3} \quad \text{--- (1)}$$

$$@ V_1 : \quad V_1 = -8 \text{ V} \quad \text{--- (2)}$$

$$\text{KCL @ } V_2 : \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$

$$\frac{V_2 - V_1}{6 \times 10^3} + \frac{V_2}{6 \times 10^3} + \frac{V_2 - V_3}{4 \times 10^3} = 0$$

$$7V_2 - 3V_3 - 2V_1 = 0 \quad \text{--- (3)}$$

$$@ V_3 : \quad V_3 = 31 \text{ V} \quad \text{--- (4)}$$

Substituting equations (4) and (2) in (3), we get

$$7V_2 - 3V_3 - 2V_1 = 0$$

$$7V_2 - 3(31) - 2(-8) = 0$$

$$V_2 = 11 \text{ V} \quad \text{--- (5)}$$

Substituting equations ④ and ⑤ in ①, we get

$$I_0 = \frac{V_2 - V_3}{R_3}$$

$$I_0 = -5.00 \text{ mA}$$

3.42 Use nodal analysis to find V_o in the circuit in Fig. P3.42.


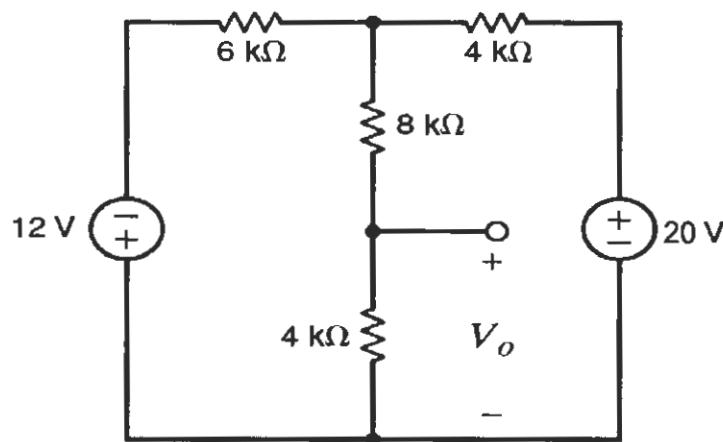


Figure P3.42

SOLUTION: 3.42

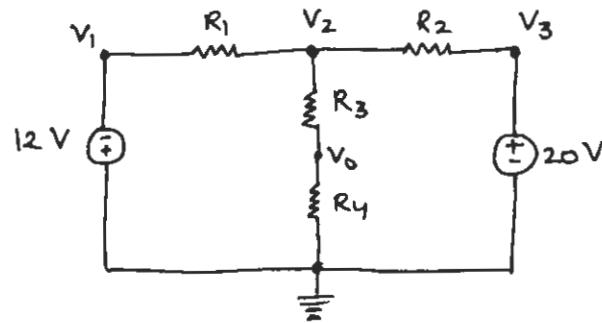

$$R_1 = 6 \text{ k}\Omega, R_2 = R_4 = 4 \text{ k}\Omega, R_3 = 8 \text{ k}\Omega$$

$$V_1 = -12 \text{ V} ; V_3 = 20 \text{ V}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_0}{R_3} + \frac{V_2 - V_3}{R_2} = 0$$

$$\frac{V_2 + 12}{6 \times 10^3} + \frac{V_2 - V_0}{8 \times 10^3} + \frac{V_2 - 20}{4 \times 10^3} = 0$$

$$\Rightarrow 13V_2 - 3V_0 = 72 \quad \text{---} \quad (1)$$

$$\text{KCL @ } V_0 : \frac{V_0}{R_4} + \frac{V_0 - V_2}{R_3} = 0$$

$$\frac{V_0}{4 \times 10^3} + \frac{V_0 - V_2}{8 \times 10^3} = 0$$

$$\Rightarrow 3V_0 - V_2 = 0 \quad \text{---} \quad (2)$$

From equations ① and ②, we get

$$12 V_2 = 72$$

$$V_2 = 6 \text{ V}$$

Substituting the value of V_2 in equation ②, we get

$$3 V_0 - V_2 = 0$$

$$\boxed{V_0 = 2.00 \text{ V}}$$

3.43 Find I_o in the circuit in Fig. P3.43.


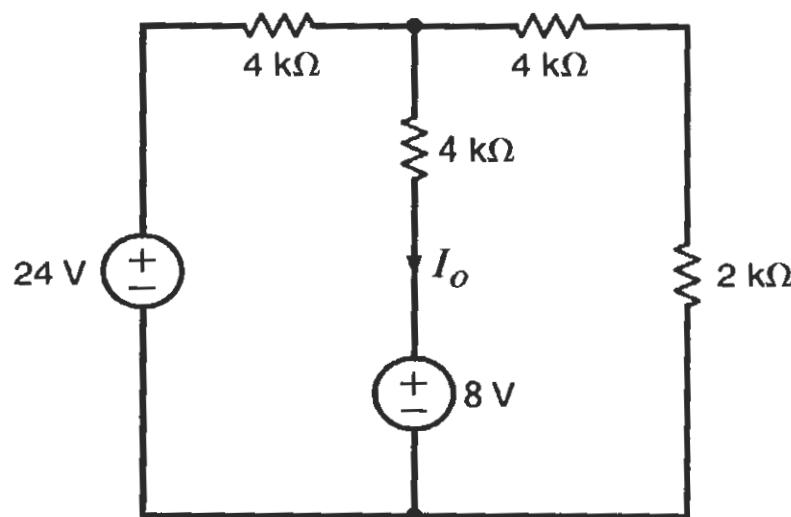


Figure P3.43

SOLUTION: 3.43

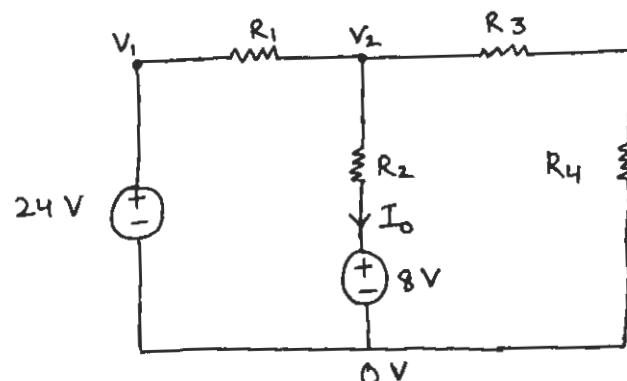

$$R_1 = R_2 = R_3 = 4 \text{ k}\Omega, R_4 = 2 \text{ k}\Omega$$

$$@ V_1 : V_1 = 24 \text{ V} \quad \text{--- (1)}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2 - 8}{R_2} + \frac{V_2}{R_3 + R_4} = 0$$

$$\frac{V_2 - 24}{4 \times 10^3} + \frac{V_2 - 8}{4 \times 10^3} + \frac{V_2}{6 \times 10^3} = 0$$

$$\Rightarrow 8V_2 - 3V_1 = 24 \quad \text{--- (2)}$$

Substituting equation (1) in (2), we get

$$8V_2 - 3 \cdot 24 = 24$$

$$\Rightarrow V_2 = 12 \text{ V}$$

$$I_0 = \frac{V_2 - 8}{R_2}$$

$$I_0 = 1.00 \text{ mA}$$

3.44 Find V_o in the network in Fig. P3.44 using mesh equations.


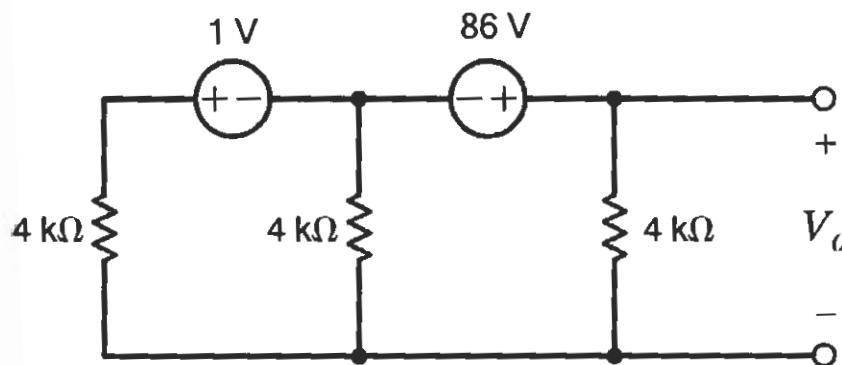


Figure P3.44

SOLUTION: 3.44

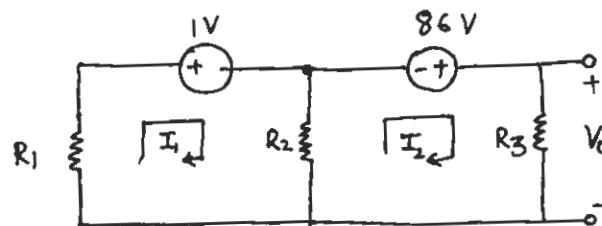

$$R_1 = R_2 = R_3 = 4 \text{ k}\Omega$$

$$\text{KVL @ } I_1 : I_1 R_1 + 1 + (I_1 - I_2) R_2 = 0$$

$$I_1 (4 \times 10^3) + (I_1 - I_2)(4 \times 10^3) = -1$$

$$8 I_1 - 4 I_2 = -1 \times 10^{-3} \quad \textcircled{1}$$

$$\text{KVL @ } I_2 : (I_2 - I_1) R_2 - 86 + I_2 R_3 = 0$$

$$(I_2 - I_1)(4 \times 10^3) + I_2 (4 \times 10^3) = 86$$

$$-8 I_1 + 16 I_2 = 172 \times 10^{-3} \quad \textcircled{2}$$

From equations $\textcircled{1}$ and $\textcircled{2}$, we get

$$12 I_2 = 171 \times 10^{-3}$$

$$I_2 = \frac{171}{12} \times 10^{-3} \text{ A}$$

$$\begin{aligned}V_0 &= I_2 R_3 \\&= \frac{17}{12} \times 10^{-3} \times 4 \times 10^3 \\V_0 &= 57.0V\end{aligned}$$

3.45 Find V_o in the network in Fig. P3.45 using mesh equations.


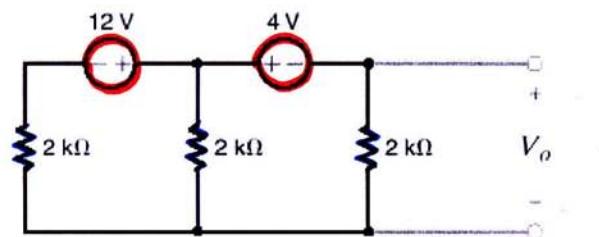


Figure P3.45

SOLUTION:

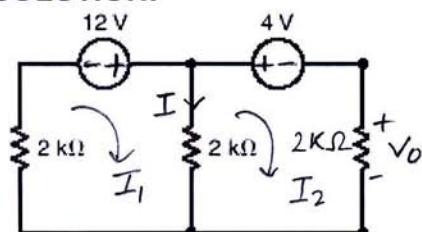

$$I_1 = I + I_2$$

$$I = I_1 - I_2$$

$$\text{KVL left loop: } 12 = 2KI_1 + 2KI$$

$$2KI_1 + 2K(I_1 - I_2) = 12$$

$$\boxed{4KI_1 - 2KI_2 = 12}$$

$$\text{KVL right loop: } 4 + 2KI_2 + 2K(-I) = 0$$

$$2KI_2 - 2K(I_1 - I_2) = -4$$

$$\boxed{-2KI_1 + 4KI_2 = -4}$$

$$4KI_1 - 2KI_2 = 12$$

$$-2KI_1 + 4KI_2 = -4$$

$$I_1 = 3.333 \text{ mA} ; I_2 = 0.667 \text{ mA}$$

$$V_o = I_2(2K) = 0.667 \text{ mA} (2K)$$

$$V_o = 1.33 \text{ V}$$

3.46 Find I_o in the circuit in Fig. P3.46.


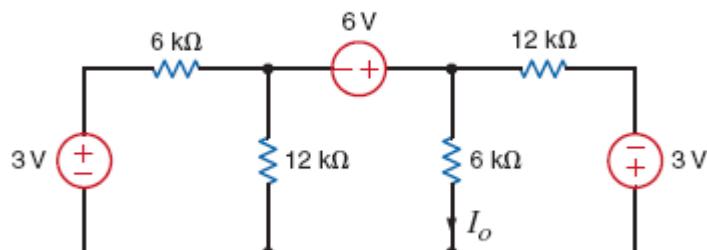


Figure P3.46

SOLUTION:

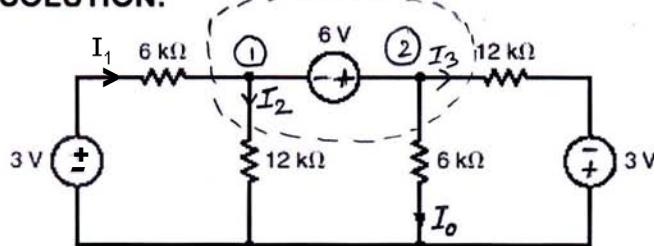

$$\text{KCL at supernode: } I_1 = I_2 + I_o + I_3$$

$$\frac{3 - V_1}{6K} = \frac{V_1}{12K} + \frac{V_2}{6K} + \frac{V_2 - (-3)}{12K}$$

$$6 - 2V_1 = V_1 + 2V_2 + V_2 + 3$$

$$3V_1 + 3V_2 = 3$$

$$V_2 - V_1 = 6$$

$$-V_1 + V_2 = 6$$

$$\begin{aligned} 3V_1 + 3V_2 &= 3 \\ -V_1 + V_2 &= 6 \end{aligned}$$

$$V_1 = -2.5 \text{ V}$$

$$V_2 = 3.5 \text{ V}$$

$$I_o = \frac{V_2}{6K} = \frac{3.5}{6K}$$

$$I_o = 0.5833 \text{ mA}$$

3.47 Find V_o in the circuit in Fig. P3.47 using nodal analysis.


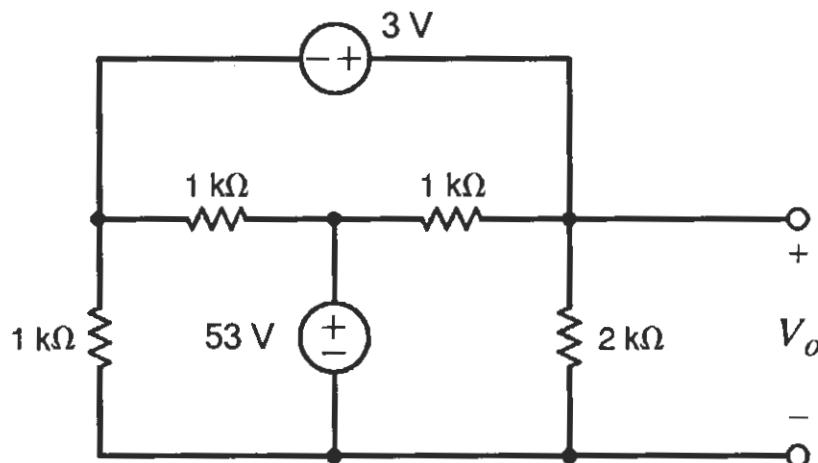


Figure P3.47

SOLUTION: 3.47

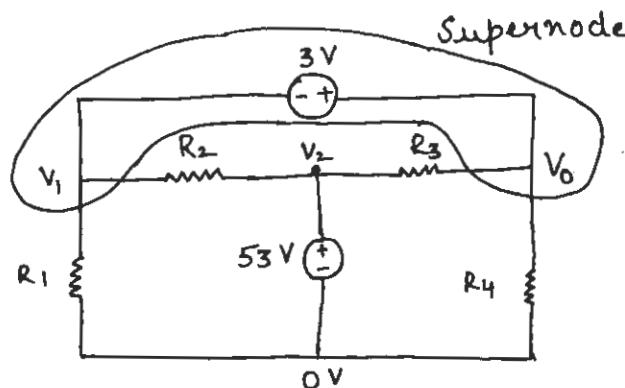

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega, R_4 = 2 \text{ k}\Omega$$

$$V_o - V_1 = 3 \text{ V} \quad \textcircled{1} \qquad V_2 = 53 \text{ V}$$

KVL @ supernode,

$$\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_o}{R_4} + \frac{V_o - V_2}{R_3} = 0$$

$$4V_1 + 3V_o = 212 \quad \textcircled{2}$$

Substituting equation ① in ②, we get

$$4(V_o - 3) + 3V_o = 212$$

$$V_o = 32.0 \text{ V}$$

3.48 Solve Problem 3.23 using loop analysis.


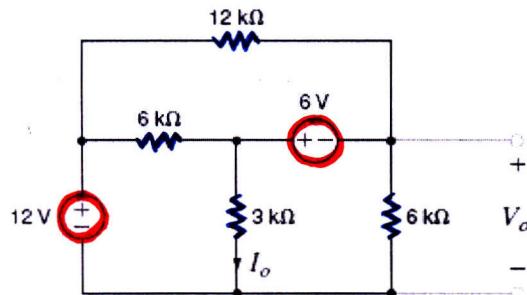


Figure P3.23

SOLUTION:

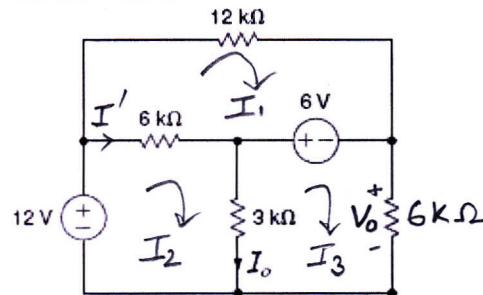

$$\text{KCL: } I_2 = I' + I_1 \\ I' = I_2 - I_1$$

$$\text{KVL: } \boxed{12K I_1 + 6K I_3 = 12}$$

$$\text{KCL: } I_0 + I_3 = I_2 \\ I_0 = I_2 - I_3$$

$$\text{KVL: } 6 + 6K I_3 + 3K(-I_0) = 0 \\ 6 + 6K I_3 - 3K(I_2 - I_3) = 0 \\ \boxed{-3K I_2 + 9K I_3 = -6}$$

$$\text{KVL: } 12 = 6K I_1 + 6 + 6K I_3 \\ 6K(I_2 - I_1) + 6K I_3 = 6 \\ \boxed{-6K I_1 + 6K I_2 + 6K I_3 = 6}$$

$$12K I_1 + 0I_2 + 6K I_3 = 12 \\ 0I_1 - 3K I_2 + 9K I_3 = -6 \\ -6K I_1 + 6K I_2 + 6K I_3 = 6$$

$$I_1 = 1 \text{ mA}$$

$$I_2 = 2 \text{ mA}$$

$$I_3 = 0 \text{ A}$$

$$V_o = 6K I_3$$

$$V_o = 6K(0)$$

$$V_o = 0 \text{ V}$$

3.49 Solve Problem 3.27 using loop analysis.


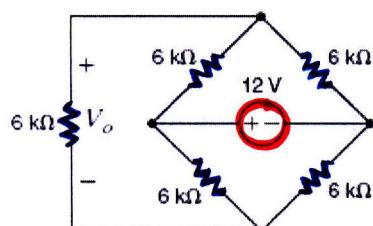


Figure P3.27

SOLUTION:

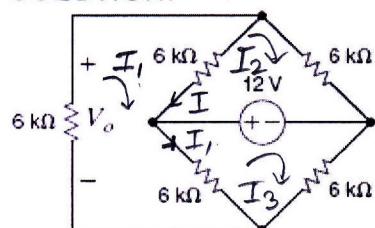

$$\text{KCL} : \quad I_1 = I + I_2 \\ I = I_1 - I_2$$

$$\text{KCL} : \quad I' + I_3 = I_1 \\ I' = I_1 - I_3$$

$$\text{KVL} : \quad \boxed{6KI_1 + 6KI_2 + 6KI_3 = 0}$$

$$\begin{aligned} \text{KVL} : \quad 12 &= 6K(-I) + 6K I_2 \\ &- 6K(I_1 - I_2) + 6K I_2 = 12 \\ &\boxed{-6KI_1 + 12KI_2 = 12} \end{aligned}$$

$$\begin{aligned} 6KI_1 + 6KI_2 + 6KI_3 &= 0 \\ 18KI_1 - 6KI_2 - 6KI_3 &= 0 \\ -6KI_1 + 12KI_2 + 0I_3 &= 12 \end{aligned}$$

$$I_1 = 0 \text{ A}$$

$$I_2 = 1 \text{ mA}$$

$$I_3 = -1 \text{ mA}$$

$$V_o = -I_1(6K)$$

$$V_o = 0 \text{ V}$$

3.50 Use loop analysis to find V_o in the network in Fig. P3.50.


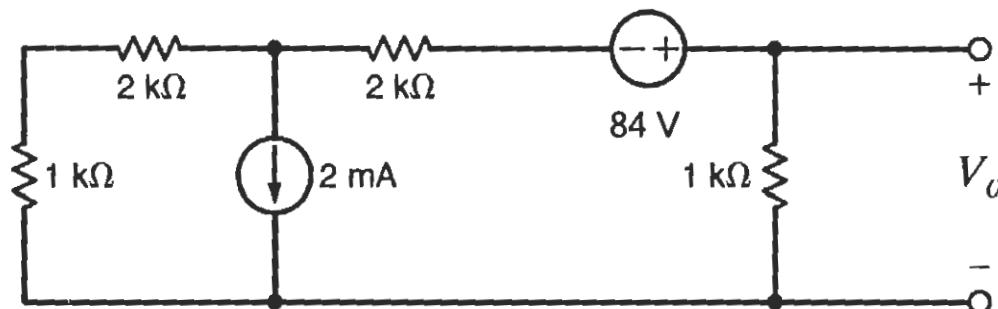


Figure P3.50

SOLUTION: 3.50

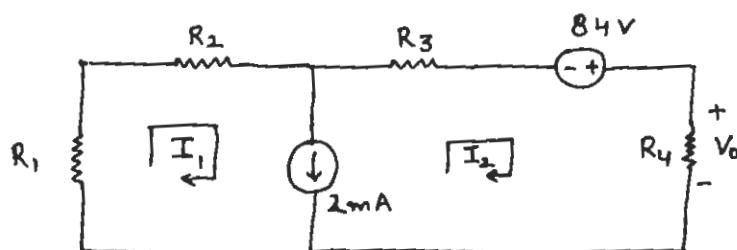

$$R_1 = R_4 = 1 \text{ k}\Omega, R_2 = R_3 = 2 \text{ k}\Omega$$

$$V_o = I_2 R_4$$

$$I_1 - I_2 = 2 \times 10^{-3} \text{ A} \quad \text{--- (1)}$$

$$I_1 R_1 + I_1 R_2 + I_2 R_3 - 84 + I_2 R_4 = 0$$

$$I_1 (R_1 + R_2) + I_2 (R_3 + R_4) = 84$$

$$(3 \times 10^3) I_1 + (3 \times 10^3) I_2 = 84$$

$$I_1 + I_2 = 28 \times 10^{-3} \quad \text{--- (2)}$$

From equations (1) and (2), we get

$$2 I_1 = 30 \times 10^{-3}$$

$$I_1 = 15 \text{ mA} \text{ and } I_2 = 13 \text{ mA}$$

$$\begin{aligned} V_o &= I_2 R_4 \\ &= 13 \times 10^{-3} \times 1 \times 10^3 \end{aligned}$$

$$\boxed{V_o = 13.0 \text{ V}}$$

3.51 Use mesh analysis to find V_o in the network in Fig. P3.51.


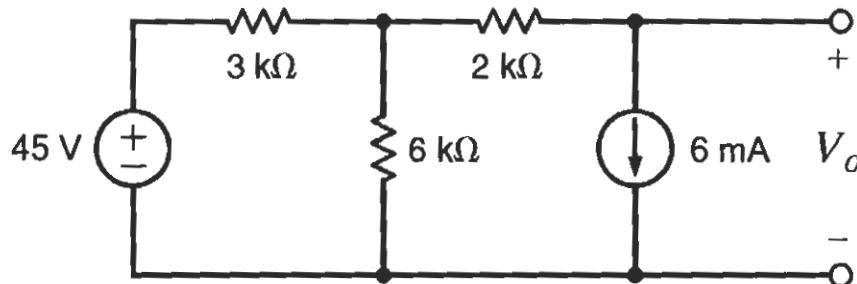


Figure P3.51

SOLUTION: 3.51

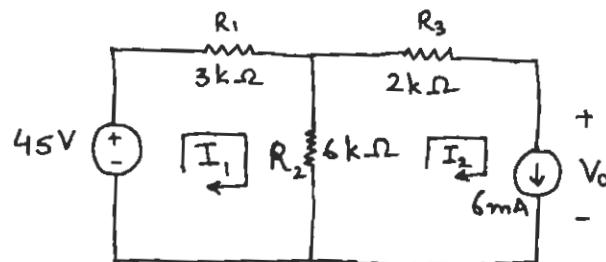

$$I_2 = 6 \text{ mA}$$

$$\text{KVL @ } I_1: -45 + I_1 R_1 + (I_1 - I_2) R_2 = 0$$

$$I_1 (R_1 + R_2) - I_2 R_2 = 45$$

$$9 \times 10^3 (I_1) - 6 \times 10^3 (I_2) = 45$$

$$I_1 = 9 \times 10^{-3}$$

$$= 9 \text{ mA}$$

$$\text{KVL @ } I_2: -45 + I_1 R_1 + I_2 R_3 + V_o = 0$$

$$-45 + [9 \times 10^{-3} \times 3 \times 10^3] + [(6 \times 10^{-3}) \times (2 \times 10^3)] + V_o = 0$$

$$\boxed{V_o = 6.00 \text{ V}}$$

- 3.52 Find I_o in the circuit in Fig. P3.52 using mesh analysis.


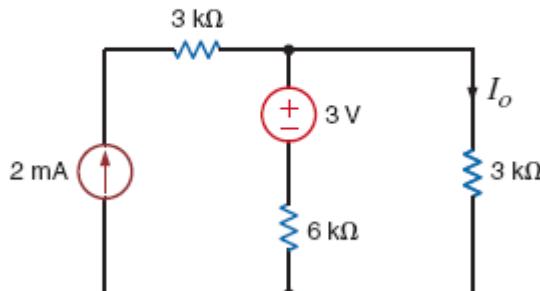


Figure P3.52

SOLUTION:

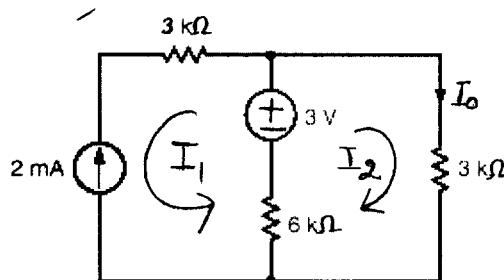

Let the loop currents be I_1 & I_2 mA

From loop 1 :

$$I_1 = -2 \text{ mA} \quad \textcircled{1}$$

Applying KVL in second loop :

$$3 = 3I_2 + 6(I_1 + I_2)$$

$$\Rightarrow 3 = 9I_2 + 6I_1 \quad \textcircled{2}$$

From equation $\textcircled{1}$ & $\textcircled{2}$

$$3 = 9(I_2) + 6I_1 = 9I_2 + 6(-2)$$

$$\Rightarrow I_2 = \frac{15}{9}$$

$$\Rightarrow I_2 = \frac{5}{3} = 1.667 \text{ mA}$$

$$I_o = I_2 = 1.67 \text{ mA}$$

3.53 Find V_o in the circuit in Fig. P3.53 using mesh analysis.


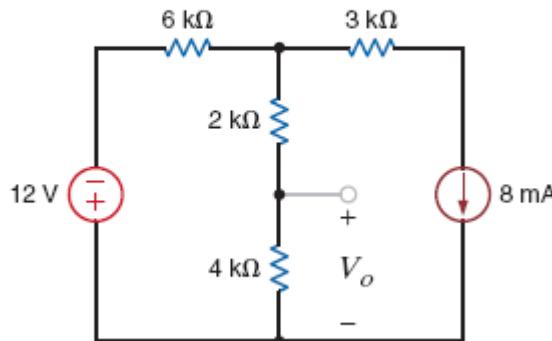


Figure P3.53

SOLUTION:

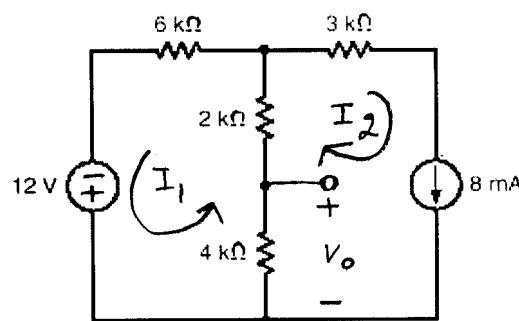

Let I_1 & I_2 be two loop currents in mA.

From loop 2 :

$$I_2 = 8 \text{ mA} \quad - \textcircled{1}$$

KVL in the loop 1 :

$$I_2 = 4(I_1 + I_2) + 2(I_1 + I_2) + 6I_1$$

$$\Rightarrow I_2 = 12I_1 + 6I_2 \quad - \textcircled{2}$$

Substituting the value of I_2 from ① in ②

$$\Rightarrow I_2 = 12I_1 + 6(8)$$

$$\Rightarrow I_1 = -3 \text{ mA} \quad - \textcircled{3}$$

$$V_o = -4 \times (I_1 + I_2)$$

$$\Rightarrow V_o = -4(-3 + 8)$$

$$\Rightarrow V_o = -4(5)$$

$$V_o = -20 \text{ Volts}$$

3.54 Use mesh analysis to find V_o in the circuit in Fig. P3.54.


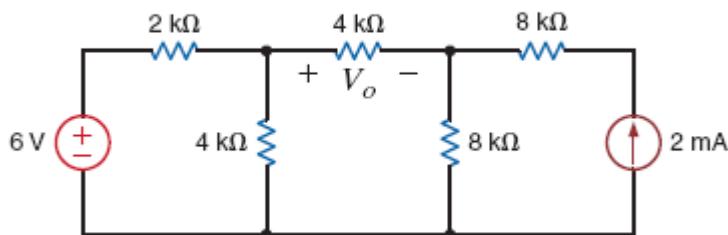


Figure P3.54

SOLUTION:

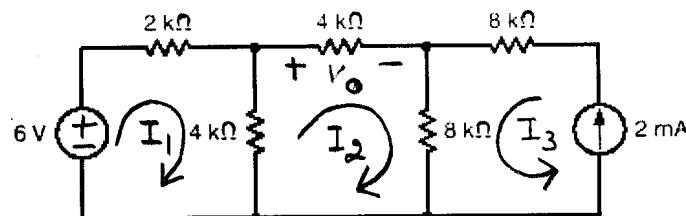

Let the loop currents be I_1 , I_2 and I_3 mA as shown in the diagram.

KVL in the first loop gives :

$$6 = 2I_1 + 4(I_1 - I_2)$$

$$\Rightarrow 6 = 6I_1 - 4I_2 \quad - \textcircled{1}$$

KVL in the second loop gives :

$$0 = 4(I_2 - I_1) + 4I_2 + 8(I_2 + I_3)$$

$$\Rightarrow 0 = 16I_2 - 4I_1 + 8I_3 \quad - \textcircled{2}$$

From the third loop:

$$I_3 = 2 \text{ mA} \quad - \textcircled{3}$$

From equation $\textcircled{2}$ & $\textcircled{3}$

$$0 = 16I_2 - 4I_1 + 8(2)$$

$$\Rightarrow 16 = 4I_1 - 16I_2 \quad - \textcircled{4}$$

$$\Rightarrow 4 = I_1 - 4I_2$$

$$6 = 6I_1 - 4I_2 \quad - \textcircled{1}$$

Solving these two equations

$$2 = 5I_1 \quad \therefore I_1 = \frac{2}{5} = 0.4 \text{ mA}$$

$$I_2 = -0.9 \text{ mA}$$

$$V_o = I_2 \times 4K = 4 \times (-0.9) = -3.6 \text{ Volts.}$$

3.55 Use mesh analysis to find I_o in the network in Fig. P3.55.


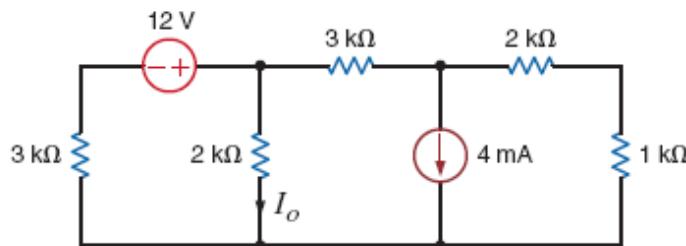


Figure P3.55

SOLUTION:

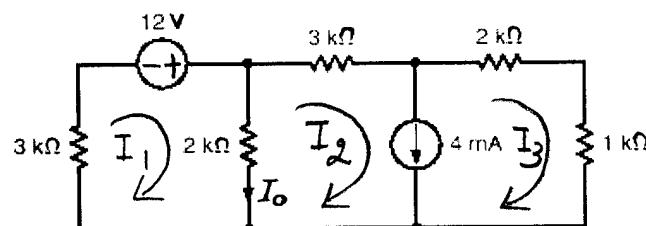

Let I_1 , I_2 and I_3 be the loop currents (in mA) as shown in the diagram.

KVL in the first loop:

$$12 = 2(I_1 - I_2) + 3I_1, \\ \Rightarrow 12 = 5I_1 - 2I_2 \quad \text{--- } ①$$

From the second loop:

$$I_2 - I_3 = 4 \quad \text{--- } ②$$

KVL in the loop outer to loop 2 & 3

$$0 = 3I_2 + 2I_3 + I_3 + 2(I_2 - I_1)$$

$$\Rightarrow 0 = 5I_2 + 3I_3 - 2I_1 \quad \text{--- } ③$$

Upon solving these three equations, we get

$$I_1 = \frac{10}{3} \text{ mA}, \quad I_2 = \frac{7}{3} \text{ mA}, \quad I_3 = -\frac{5}{3} \text{ mA}$$

$$I_o = I_1 - I_2$$

$$\Rightarrow I_o = \frac{10}{3} - \frac{7}{3} = \frac{3}{3} = 1 \text{ mA}$$

$I_o = 1 \text{ mA}$

3.56 Find I_o in the network in Fig. P3.56 using loop analysis.


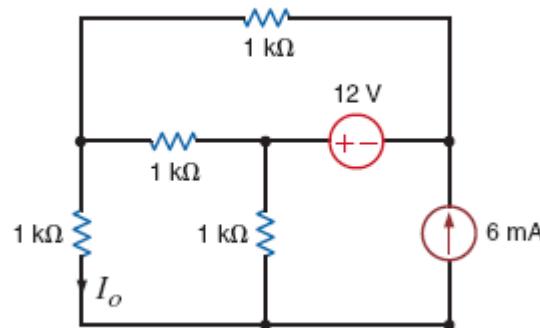


Figure P3.56

SOLUTION:

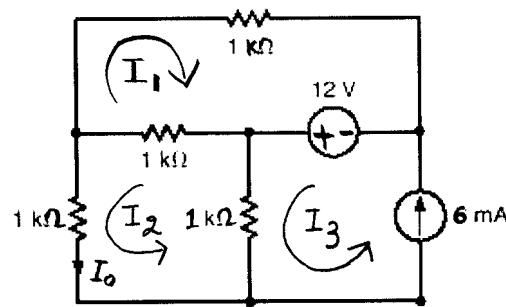

Let I_1 , I_2 and I_3 be the loop currents (in mA).

KVL in the first loop:

$$12 = 1(I_1 + I_2) + 1 \times I_1$$

$$\Rightarrow 12 = 2I_1 + I_2 \quad \text{--- } ①$$

From the third loop:

$$I_3 = 6 \text{ mA} \quad \text{--- } ②$$

KVL in the second loop:

$$1(I_1 + I_2) + 1(I_2) + 1(I_2 - I_3) = 0$$

$$\Rightarrow I_1 + 3I_2 - I_3 = 0 \quad — \quad (3)$$

From equation (2) & (3), we get :

$$I_1 + 3I_2 = I_3 = 6 \quad — \quad (4)$$

From equation (1) & (4) :

$$I_2 = 2I_1 + I_2 \quad — \quad (1)$$

$$6 = I_1 + 3I_2$$

$$\Rightarrow I_2 = 2I_1 + 6I_2 \quad — \quad (5)$$

$$5I_2 = 0 \quad \{ \text{eq. (5)} - \text{eq. (1)} \}$$

or I₂ = 0 mA

- 3.57 Use loop analysis to find I_o and I_1 in the network in Fig. P3.57.


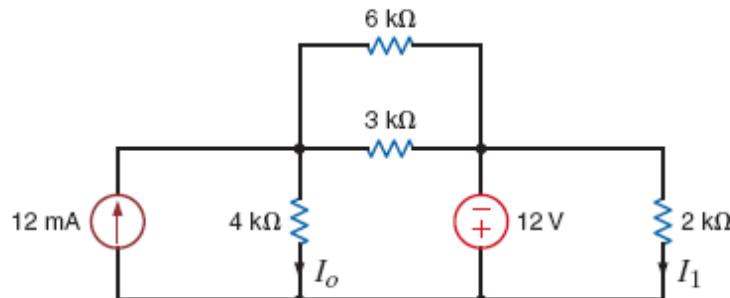


Figure P3.57

SOLUTION:

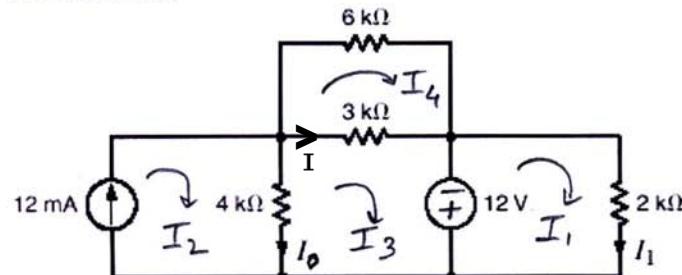

$$I_2 = 12 \text{ mA}$$

$$\text{KCL : } I_o + I_3 = I_2 \\ I_o = I_2 - I_3$$

$$\begin{aligned} \text{KCL : } I_2 &= I + I_o + I_4 \\ I &= I_2 - I_2 + I_3 - I_4 \\ I &= I_3 - I_4 \end{aligned}$$

$$\text{KVL : } 12 = -2KI_1 \\ I_1 = -6 \text{ mA}$$

$$\begin{aligned} \text{KVL : } 12 &= 4K(-I_o) + 6KI_4 \\ -4K(-I_o) + 6KI_4 & \\ -4K(I_2 - I_3) + 6KI_4 &= 12 \\ -4KI_2 + 4KI_3 + 6KI_4 &= 12 \end{aligned}$$

$$[4KI_3 + 6KI_4 = 60]$$

$$\text{KVL: } 12 = 4K(-I_0) + 3K I_1 \\ -4K(I_2 - I_3) + 3K(I_3 - I_4) = 12$$

$$7I_3 - 4I_2 - 3I_4 = 12$$

$$\text{KVL: } 6kI_4 + 3k(I_4 - I_3) = 0 \\ I_4 = I_3/3$$

$$I_3 = 10\text{mA}$$

$$I_4 = 3.33\text{mA}$$

$$I_0 = I_2 - I_3 = 12\text{mA} - 10\text{mA} = 2\text{mA}$$

$$I_0 = 2\text{mA}$$

3.58 Find I_o in the network in Fig. P3.58 using loop analysis.

Then solve the problem using MATLAB and compare your answers.


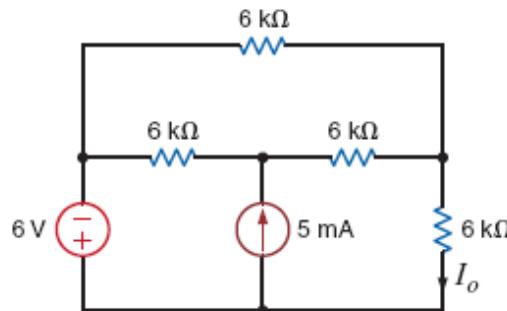


Figure P3.58

SOLUTION:

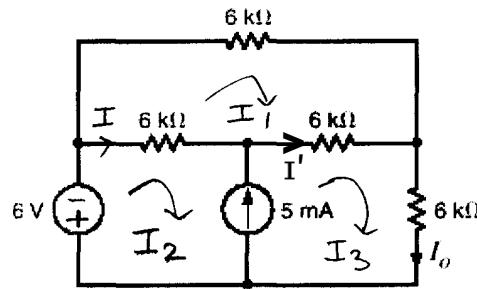

$$I_3 = I_o$$

$$KCL: I_2 = I + I_1$$

$$I = I_2 - I_1$$

$$KCL: I_1 + I' = I_3$$

$$I' = I_3 - I_1$$

KVL:

KVL in the top loop:

$$18I_1 - 6I_2 - 6I_3 = 0$$

$$\boxed{3I_1 - I_2 - I_3 = 0}$$

$$KVL: 6 + 6KI + 6KI' + 6KI_o = 0$$

$$6K(I_2 - I_1) + 6K(I_3 - I_1) + 6KI_3 = -6$$

$$\boxed{-12KI_1 + 6KI_2 + 12KI_3 = -6} \Rightarrow \boxed{2I_1 - I_2 - 2I_3 = 1}$$

$$KCL: I_3 = 5m + I_2$$

$$\boxed{-I_2 + I_3 = 5m}$$

upon solving these equations we get, $i_3 = 2/5 = 0.4\text{mA}$

% MATLAB code and solution for Problem 3.65

$$R = [3, -1, -1; 2, -1, -2; 0, -2, 1];$$

$$V = [0; 1; 5]$$

$$I_{matrix} = \text{inv}(R) * V$$

\Rightarrow

$$I_{matrix} =$$

$$-0.0016$$

$$-0.0044$$

$$0.0006$$

3.59 Use nodal analysis to find V_o in the circuit in Fig. P3.59.


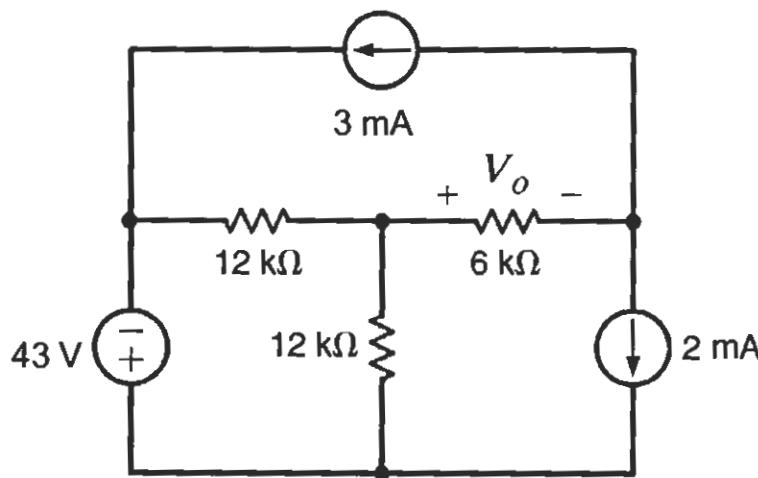


Figure P3.59

SOLUTION: 3.59

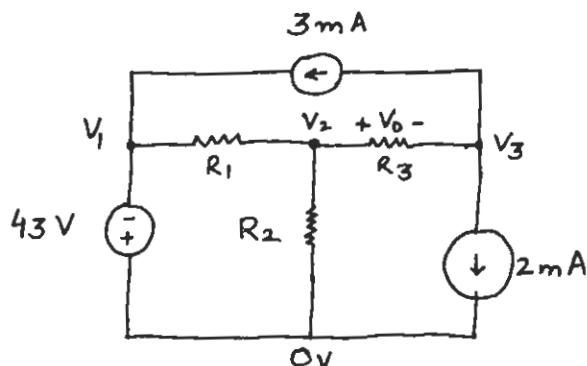

$$R_1 = R_2 = 12 \text{ k}\Omega, R_3 = 6 \text{ k}\Omega$$

$$V_1 = -43 \text{ V}$$

$$V_2 - V_3 = V_o \quad \text{---} \quad (1)$$

$$\text{KCL at } V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_3} + \frac{V_2}{R_2} = 0$$

$$\text{KCL at } V_3 : \frac{V_3 - V_2}{R_3} + 2 \times 10^{-3} + 3 \times 10^{-3} = 0$$

$$V_2 - V_3 = 30 \quad \text{---} \quad (2)$$

From equations (1) and (2), we get

$$V_o = 30.0 \text{ V}$$

3.60 Determine V_o in the circuit in Fig. P3.60 using loop analysis.


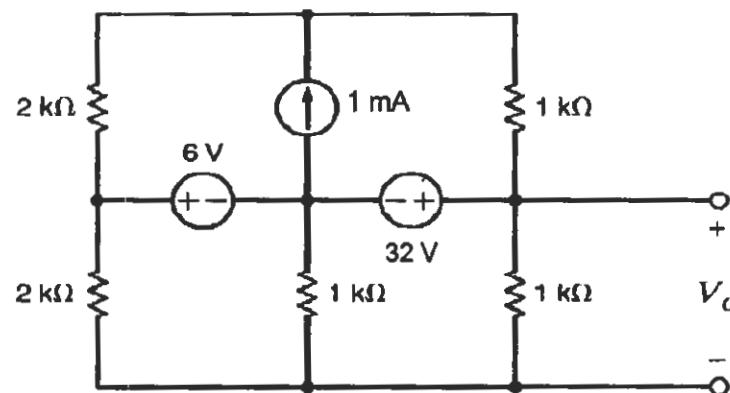


Figure P3.60

Solution: 3.60

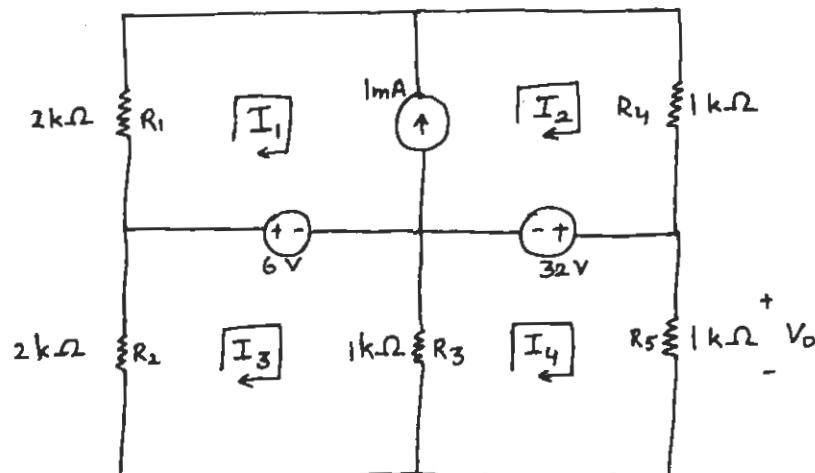

$$V_o = I_4 R_5 \quad I_2 - I_1 = 1 \text{ mA}$$

$$\text{KVL @ } I_3 : I_3 R_2 + 6 + (I_3 - I_4) R_3 = 0$$

$$I_3 (R_2 + R_3) - I_4 R_3 = -6$$

$$I_3 (3 \times 10^3) - I_4 (10^3) = -6$$

$$3I_3 - I_4 = -6 \times 10^{-3} \quad \textcircled{1}$$

$$\text{KVL @ } I_4 : (I_4 - I_3) R_3 - 32 + I_4 R_5 = 0$$

$$2I_4 - I_3 = 32 \times 10^{-3} \quad \textcircled{2}$$

$$5I_4 = 90 \times 10^{-3}$$

$$I_4 = 18 \text{ mA}$$

$$V_o = I_4 R_5$$

$$V_o = 18 \times 10^{-3} \times 10^3$$

$$\boxed{V_o = 18.0 \text{ V}}$$

3.61 Find I_o in the circuit in Fig. P3.61.


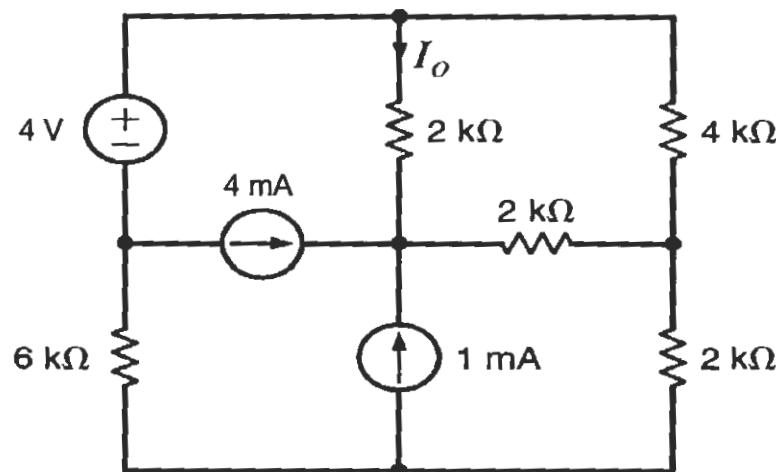


Figure P3.61

SOLUTION: 3.61

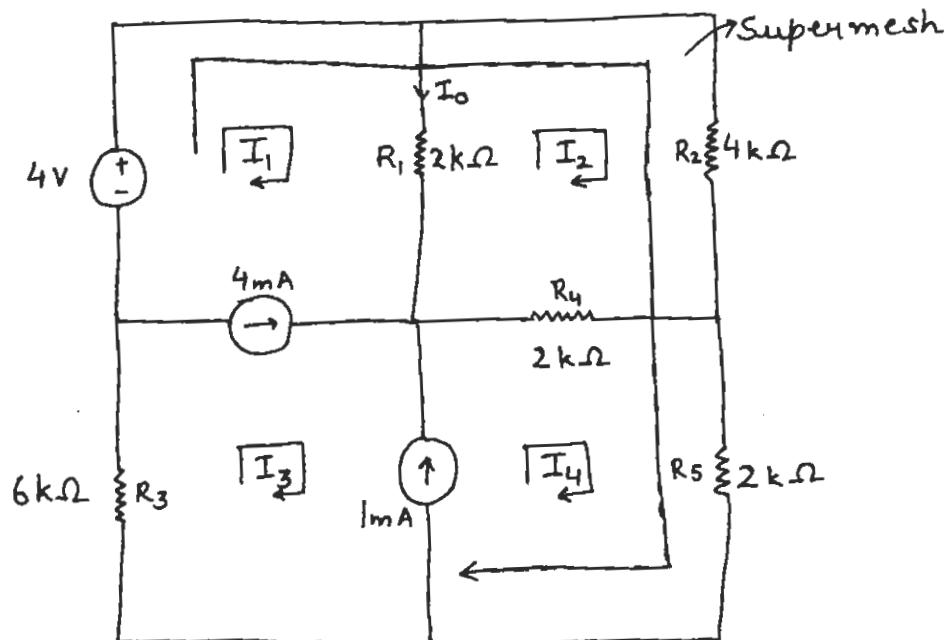

$$I_3 - I_1 = 4 \times 10^{-3} \text{ A} = 4 \text{ mA}$$

$$\Rightarrow I_3 = 4 \text{ mA} + I_1 \quad \textcircled{1}$$

$$I_4 - I_3 = 1 \times 10^{-3} \text{ A} = 1 \text{ mA}$$

$$\Rightarrow I_4 = 1 \text{ mA} + I_3 = 5 \text{ mA} + I_1 \quad \textcircled{2}$$

$$I_1 - I_2 = I_0$$

$$\Rightarrow I_2 = I_1 - I_0 \quad \text{---} \quad (3)$$

KVL for I_2 : $(I_2 - I_1)R_1 + I_2 R_2 + (I_2 - I_4)R_4 = 0$

$$I_2(R_1 + R_2 + R_4) - I_1 R_1 - I_4 R_4 = 0$$

$$I_2(8 \times 10^3) - 2 \times 10^3 I_1 - (2 \times 10^3) I_4 = 0$$

$$\Rightarrow 4I_2 - I_1 - I_4 = 0 \quad \text{---} \quad (4)$$

KVL for supermesh: $-4 + I_2 R_2 + I_4 R_5 + I_3 R_3 = 0$

$$I_2(4 \times 10^3) + I_4(2 \times 10^3) + I_3(6 \times 10^3) = 4$$

$$\Rightarrow 2I_2 + I_4 + 3I_3 = 2 \times 10^{-3} \quad \text{---} \quad (5)$$

Substituting equations (2) and (3) in (4), we get

$$4(I_1 - I_0) - I_1 - [(5 \times 10^{-3}) + I_1] = 0$$

$$2I_1 - 4I_0 = 5 \times 10^{-3} \quad \text{---} \quad (6)$$

Substituting equations (1), (2) and (3) in (5), we get

$$2(I_1 - I_0) + 5 \times 10^{-3} + I_1 + 3(4 \times 10^{-3} + I_1) = 2 \times 10^{-3}$$

$$6I_1 - 2I_0 = -15 \times 10^{-3} \quad \text{---} \quad (7)$$

From equations (6) and (7), we get

$I_0 = -3.00 \text{ mA}$

3.62 Use loop analysis to find I_o in the network in Fig. P3.62.


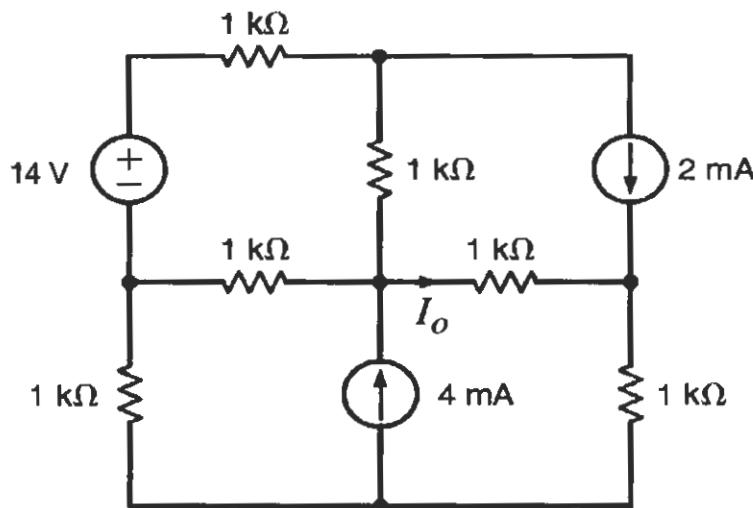


Figure P3.62

SOLUTION: 3-62

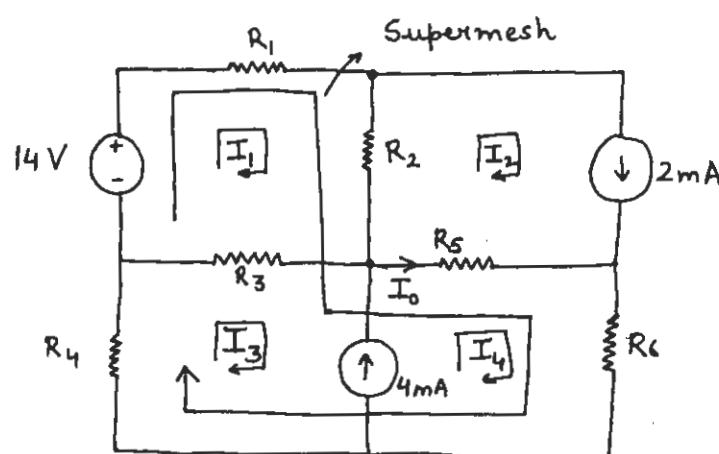

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 1 \text{ k}\Omega$$

$$I_2 = 2 \text{ mA}$$

$$I_4 - I_2 = I_o \Rightarrow I_4 = I_o + 2 \text{ mA} \quad \text{---} \quad (1)$$

$$I_4 - I_3 = 4 \text{ mA}$$

$$I_3 = I_4 - 4 \times 10^{-3}$$

$$= I_0 + 2 \times 10^{-3} - 4 \times 10^{-3}$$

$$I_3 = I_0 - 2 \times 10^{-3} \quad \text{---} \quad (2)$$

KVL @ I_1 : $-14 + I_1 R_1 + (I_1 - I_2) R_2 + (I_1 - I_3) R_3 = 0$

$$I_1 (R_1 + R_2 + R_3) - I_2 R_2 - I_3 R_3 = 14$$

Substituting $I_2 = 2 \text{ mA}$, $I_3 = I_0 - 2 \text{ mA}$ in above equation, we get

$$3I_1 - I_0 = 14 \times 10^{-3} \quad \text{---} \quad (3)$$

KVL @ Supermesh: $-14 + I_1 R_1 + (I_1 - I_2) R_2 + (I_4 - I_2) R_5 + I_4 R_6 + I_3 R_4 = 0$

$$I_1 (R_1 + R_2) - I_2 (R_2 + R_5) + I_3 R_4 + I_4 (R_5 + R_6) = 14$$

$$2I_1 - 2I_2 + I_3 + 2I_4 = 14 \times 10^{-3}$$

$$2I_1 - 2(2 \times 10^{-3}) + I_0 - 2 \times 10^{-3} + 2(I_0 + 2 \times 10^{-3}) = 14 \times 10^{-3}$$

$$2I_1 + 3I_0 = 16 \times 10^{-3} \quad \text{---} \quad (4)$$

From equations (3) and (4), we get

$$I_0 = 1.82 \text{ mA}$$

3.63 Use loop analysis to find I_o in the network in Fig. P3.63.


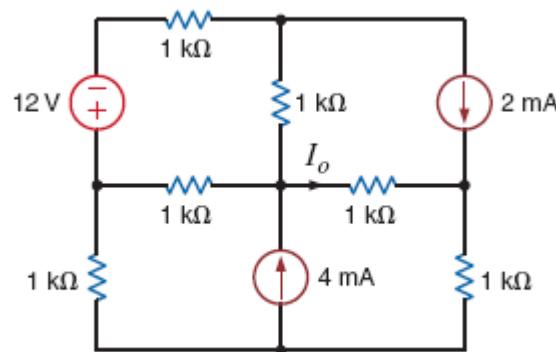


Figure P3.63

SOLUTION:

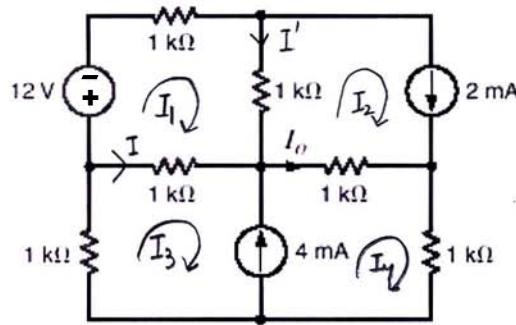

$$I_2 = 2\text{mA}$$

$$\text{KCL: } I_3 = I + I_1$$

$$I = I_3 - I_1$$

$$\text{KCL: } I' + I_2 = I_1$$

$$I' = I_1 - I_2$$

$$\text{KCL: } I_o + 2\text{mA} = I_4$$

$$I_o = I_4 - 2\text{mA}$$

$$\text{KVL: } 0 = 12 + 1kI_1 + 1kI' + 1k(-I)$$

$$1kI_1 + 1k(I_1 - I_2) - 1k(I_3 - I_1) = -12$$

$$3kI_1 - 1kI_2 - 1kI_3 = -12$$

$$\boxed{3kI_1 - 1kI_3 = -10}$$

$$\text{KVL: } 1kI_3 + 1kI + 1kI_o + 1kI_4 = 0$$

$$1kI_3 + 1k(I_3 - I_1) + 1k(I_4 - 2\text{mA}) + 1kI_4 = 0$$

$$\boxed{-1kI_1 + 2kI_3 + 2kI_4 = 2}$$

KCL: $I_4 = 4m + I_3$

$$\boxed{-I_3 + I_4 = 4m}$$

KVL: $0 = 12 + 1kI_1 + 1kI_1 + 1kI_0 + 1kI_4 + 1kI_3$
 $1kI_1 + 1k(I_1 - I_2) + 1k(I_4 - 2m) + 1kI_4 + 1kI_3 = -12$
 $2kI_1 - 1kI_2 + 1kI_3 + 2kI_4 = -10$

$$\boxed{2kI_1 + 1kI_3 + 2kI_4 = -8}$$

$$3kI_1 - 1kI_3 = -10$$

$$-1kI_1 + 2kI_3 + 2kI_4 = 2$$

$$-I_3 + I_4 = 4m$$

$$I_1 = -4.18mA$$

$$I_3 = -2.55mA$$

$$I_4 = 1.45mA$$

$$I_0 = I_4 - 2m$$

$$I_0 = 1.45m - 2m$$

$$I_0 = -0.55mA$$

3.64 Use loop analysis to find V_o in the network in the Fig. P3.64.


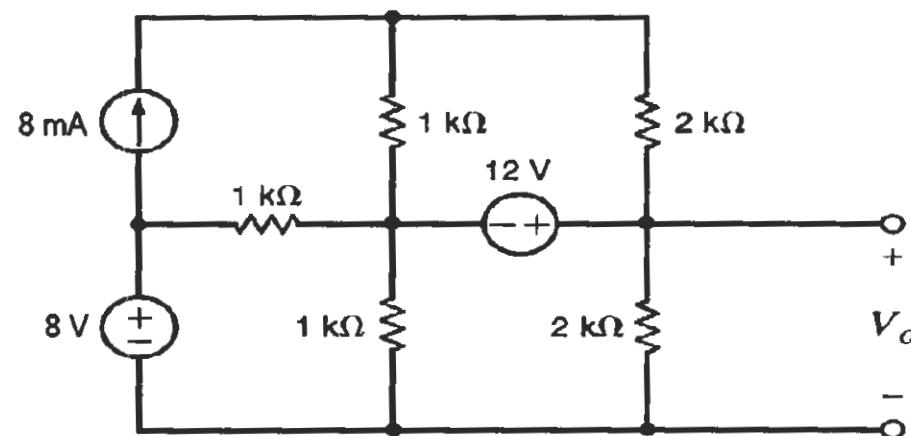


Figure P3.64

Solution: 3-64

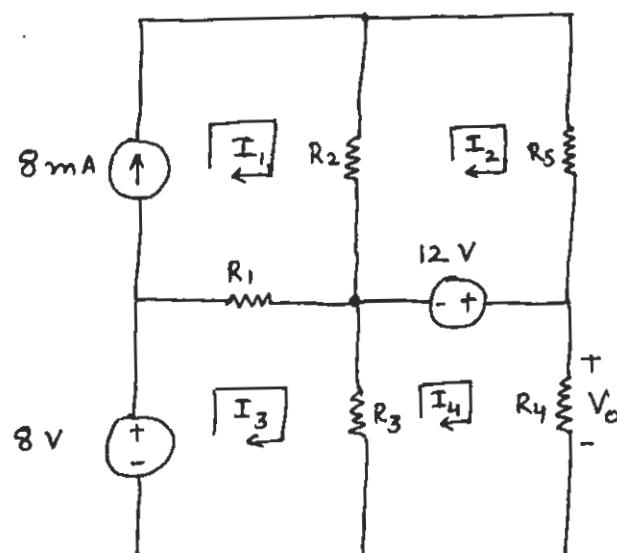

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega, R_5 = R_4 = 2 \text{ k}\Omega$$

$$V_o = I_4 R_4 \quad \text{---} \quad (1)$$

$$I_1 = 8 \text{ mA}$$

$$\text{kVL @ } I_2: (I_2 - I_1) R_2 + I_2 R_5 + 12 = 0$$

$$I_2 = -2 \text{ mA}$$

$$\text{KVL @ } I_3 : -8 + (I_3 - I_1) R_1 + (I_3 - I_4) R_3 = 0$$

$$I_3(R_1 + R_3) - I_1 R_1 - I_4 R_3 = 8$$

$$I_3(2 \times 10^3) - (8 \times 10^{-3})(10^3) - I_4(10^3) = 8$$

$$2I_3 - I_4 = 16 \times 10^{-3} \quad \text{--- } \textcircled{2}$$

$$\text{KVL @ } I_4 : (I_4 - I_3) R_3 - 12 + I_4 R_4 = 0$$

$$I_4(R_3 + R_4) - I_3 R_3 = 12$$

$$(3 \times 10^3) I_4 - (10^3) I_3 = 12$$

$$3I_4 - I_3 = 12 \times 10^{-3} \quad \text{--- } \textcircled{3}$$

From equations $\textcircled{2}$ and $\textcircled{3}$, we get

$$I_4 = 8 \text{ mA}$$

Substituting the value of I_4 in equation $\textcircled{1}$, we get

$$V_0 = (8 \times 10^{-3})(2 \times 10^3)$$

$$\boxed{V_0 = 16.0 \text{ V}}$$

3.65 Using loop analysis, find V_o in the network in Fig. P3.65.


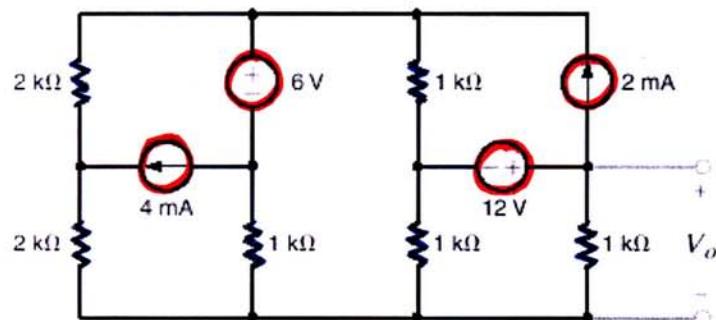


Figure P3.65

SOLUTION:

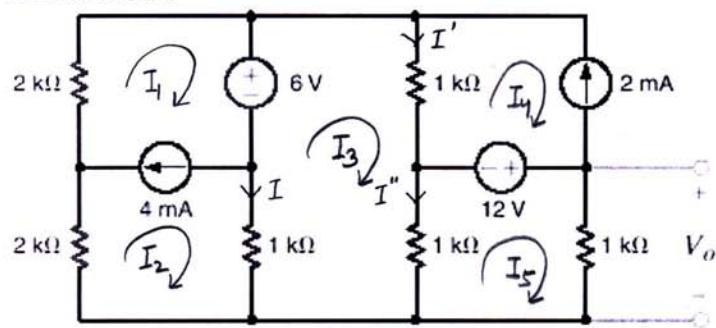

$$\text{KCL: } I_3 + I = I_2 \\ I = I_2 - I_3$$

$$\text{KCL: } I_3 = I' + I_4 \\ I' = I_3 - I_4$$

$$\text{KCL: } I'' + I_5 = I_3 \\ I'' = I_3 - I_5$$

$$\begin{aligned} \text{KVL: } 12 &= 1k I_5 + 1k(-I'') \\ -1k(I_3 - I_5) + 1k I_5 &= 12 \\ \boxed{-1k I_3 + 2k I_5 = 12} \end{aligned}$$

$$\begin{aligned} \text{KVL: } 6 &= 1k I' + 1k I'' + 1k(-I) \\ 1k(I_3 - I_4) + 1k(I_3 - I_5) - 1k(I_2 - I_3) &= 6 \end{aligned}$$

$$-1kI_2 + 3kI_3 - 1kI_4 - 1kI_5 = 6$$

$$\text{KVL: } 2kI_1 + 1kI + 1kI_5 + 2kI_2 = 12$$

$$2kI_1 + 1k(I_3 - I_4) + 1kI_5 + 2kI_2 = 12$$

$$2kI_1 + 2kI_2 + 1kI_3 - 1kI_4 + 1kI_5 = 12$$

$$\text{KCL: } I_2 + 4m = I_1$$

$$-I_1 + I_2 = -4m$$

$$I_4 = -2mA$$

$$-1kI_2 + 3kI_3 - 1k(-2m) - 1kI_5 = 6$$

$$-1kI_2 + 3kI_3 - 1kI_5 = 4$$

$$2kI_1 + 2kI_2 + 1kI_3 - 1k(-2m) + 1kI_5 = 12$$

$$2kI_1 + 2kI_2 + 1kI_3 + 1kI_5 = 10$$

$$0I_1 + 0I_2 - 1kI_3 - 1k(-2m) + 1kI_5 = 12$$

$$-I_1 + I_2 + 0I_3 + 0I_5 = -4m$$

$$0I_1 - 1kI_2 + 3kI_3 - 1kI_5 = 4$$

$$2kI_1 + 2kI_2 + 1kI_3 + 1kI_5 = 10$$

$$I_1 = 1.83mA$$

$$I_2 = -2.17mA$$

$$I_3 = 3.13mA$$

$$I_5 = 7.57mA$$

$$V_o = 1k(I_5) = 1k(7.57mA)$$

$$V_o = 7.57V$$

3.66 Using loop analysis, find I_o in the circuit in Fig. P3.66.


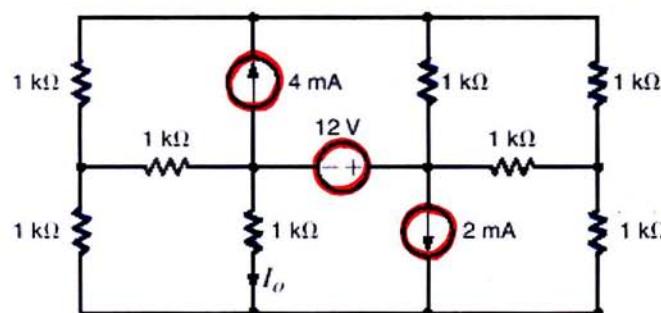


Figure P3.66

SOLUTION:

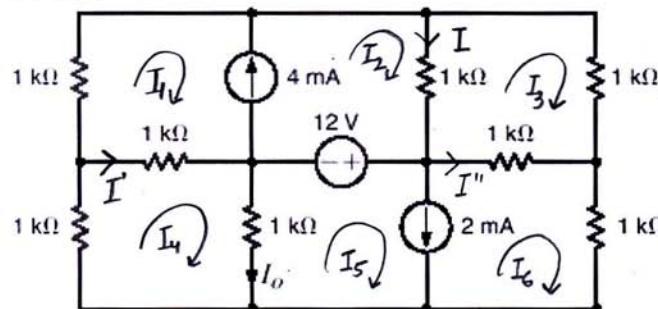

$$\text{KCL: } I_2 = I + I_3 \\ I = I_2 - I_3$$

$$\text{KCL: } I_3 + I'' = I_6$$

$$I'' = I_6 - I_3$$

$$\text{KCL: } I_4 = I_1 + I'$$

$$I' = I_4 - I_1$$

$$\text{KCL: } I_0 + I_5 = I_4$$

$$I_0 = I_4 - I_5$$

$$\text{KVL: } 12 = 1k I'' + 1k I_6 + 1k(-I_0)$$

$$1k(I_6 - I_3) + 1k I_6 - 1k(I_4 - I_5) = 12$$

$$-1kI_3 - 1kI_4 + 1kI_5 + 2kI_6 = 12$$

$$\begin{aligned} \text{KVL: } & 1kI' + 1kI_0 + 1kI_4 = 0 \\ & 1k(I_4 - I_1) + 1k(I_4 - I_5) + 1kI_4 = 0 \\ & \boxed{-1kI_1 + 3kI_4 - 1kI_5 = 0} \end{aligned}$$

$$\begin{aligned} \text{KCL: } & I_6 + 2m = I_5 \\ & \boxed{-I_5 + I_6 = -2m} \end{aligned}$$

$$\begin{aligned} \text{KCL: } & I_1 + 4m = I_2 \\ & \boxed{I_1 - I_2 = -4m} \end{aligned}$$

$$\begin{aligned} \text{KVL: } & 1kI_1 + 1kI_3 + 1k(-I'') + 12 + 1k(-I') = 0 \\ & 1kI_1 + 1kI_3 - 1k(I_6 - I_3) - 1k(I_4 - I_1) = -12 \\ & \boxed{2kI_1 + 2kI_3 - 1kI_4 - 1kI_6 = -12} \end{aligned}$$

$$\begin{aligned} \text{KVL: } & 1kI_3 + 1k(-I'') + 1k(-I) = 0 \\ & 1kI_3 - 1k(I_6 - I_3) - 1k(I_2 - I_3) = 0 \\ & \boxed{-1kI_2 + 3kI_3 - 1kI_6 = 0} \end{aligned}$$

$$\begin{aligned} 0I_1 + 0I_2 - 1kI_4 + 1kI_5 + 2kI_6 &= 12 \\ -1kI_1 + 0I_2 + 0I_3 + 3kI_4 - 1kI_5 + 0I_6 &= 0 \\ 0I_1 + 0I_2 + 0I_3 + 0I_4 - I_5 + I_6 &= -2m \\ I_1 - I_2 + 0I_3 + 0I_4 + 0I_5 + 0I_6 &= -4m \\ 2kI_1 + 0I_2 + 2kI_3 - 1kI_4 + 0I_5 - 1kI_6 &= -12 \\ 0I_1 - 1kI_2 + 3kI_3 + 0I_4 + 0I_5 - 1kI_6 &= 0 \end{aligned}$$

$$I_1 = -4.93 \text{ mA}$$

$$I_2 = -0.933 \text{ mA}$$

$$I_3 = 0.933 \text{ mA}$$

$$I_4 = 0.267 \text{ mA}$$

$$I_5 = 5.73 \text{ mA}$$

$$I_6 = 3.73 \text{ mA}$$

$$I_0 = I_4 - I_5 = 0.267 \text{ mA} - 5.73 \text{ mA}$$

$$I_0 = -5.46 \text{ mA}$$

3.67 Use MATLAB to find the mesh currents in the network in Fig. P3.6.


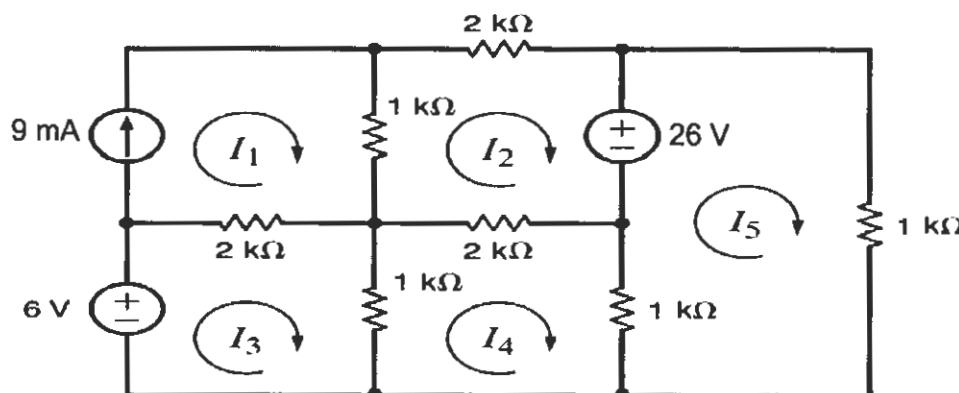


Figure P3.67

SOLUTION: 3.67

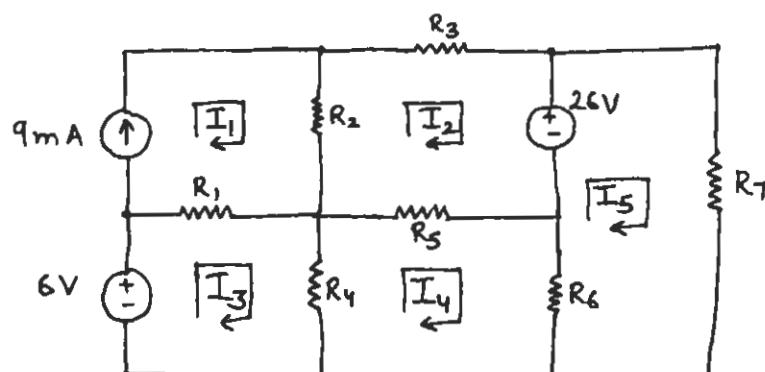

$$R_1 = R_3 = R_5 = 2 \text{ k}\Omega, R_2 = R_4 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$I_1 = 9 \times 10^{-3} \text{ A}$$

$$\begin{aligned} \text{KVL @ } I_2: & (I_2 - I_1)R_2 + I_2R_3 + 26 + (I_2 - I_4)R_5 = 0 \\ & -I_1(R_2) + I_2(R_2 + R_3 + R_5) - I_4R_5 = -26 \\ & -I_1(10^3) + I_2(5 \times 10^3) - I_4(2 \times 10^3) = -26 \\ & -I_1 + 5I_2 - 2I_4 = -26 \times 10^{-3} \end{aligned}$$

$$\begin{aligned} \text{KVL @ } I_3: & -6 + (I_3 - I_1)R_1 + (I_3 - I_4)R_4 = 0 \\ & -I_1R_1 + I_3(R_1 + R_4) - I_4(R_4) = 6 \\ & -I_1(2 \times 10^3) + I_3(3 \times 10^3) - I_4(10^3) = 6 \\ & -2I_1 + 3I_3 - I_4 = 6 \times 10^{-3} \end{aligned}$$

$$\text{KVL @ } I_4: (I_4 - I_3)R_4 + (I_4 - I_2)R_5 + (I_4 - I_5)R_6 = 0$$

$$-I_2R_5 - I_3R_4 + I_4(R_4 + R_5 + R_6) - I_5R_6 = 0$$

$$-I_2(2 \times 10^3) - I_3(10^3) + I_4(4 \times 10^3) - I_5(10^3) = 0$$

$$-2I_2 - I_3 + 4I_4 - I_5 = 0$$

$$\text{KVL @ } I_5: -26 + I_5R_7 + (I_5 - I_4)R_6 = 0$$

$$-I_4R_6 + I_5(R_6 + R_7) = 26$$

$$-I_4(10^3) + I_5(2 \times 10^3) = 26$$

$$-I_4 + 2I_5 = 26 \times 10^{-3}$$

In matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ -1 & 5 & 0 & -2 & 0 \\ -2 & 0 & 3 & -1 & 0 \\ 0 & -2 & -1 & 4 & -1 \\ 0 & 0 & 0 & -1 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 0.009 \\ -0.026 \\ 0.006 \\ 0 \\ 0.026 \end{bmatrix}$$

- 3.68 Use loop analysis to find V_o in the network in Fig. P3.68.


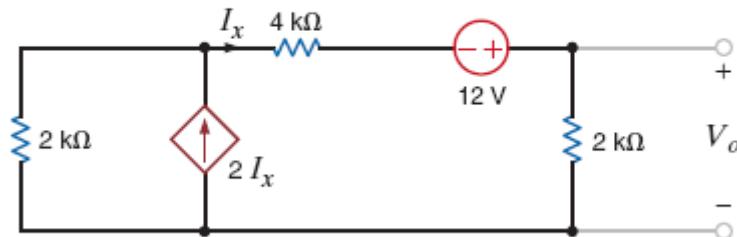


Figure P3.68

SOLUTION:

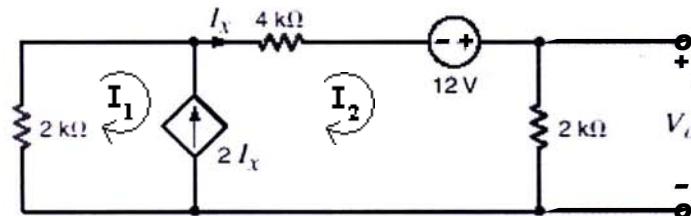

$$\text{KCL: } I_1 + 2I_x = I_x$$

$$I_1 = -I_x \text{ and } I_2 = I_x$$

$$\text{KVL: } 12 = 2kI_1 + 4kI_2 + 2kI_2$$

$$2kI_1 + 6kI_2 = 12$$

$$2k(-I_x) + 6k(I_x) = 12$$

$$4kI_x = 12$$

$$I_x = 3\text{mA}$$

$$V_o = 2kI_x = 2k(3m)$$

$$V_o = 6\text{V}$$

- 3.69 Find V_o in the circuit in Fig. P3.69 using nodal analysis.


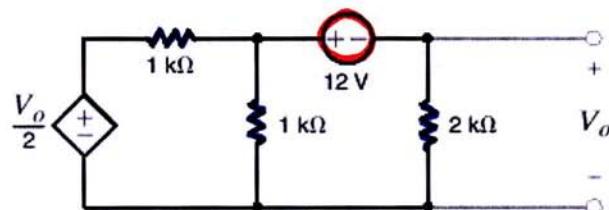


Figure P3.69

SOLUTION:

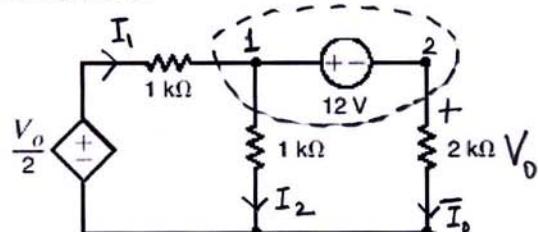

KCL at supernode:

$$I_1 = I_2 + I_o$$

$$\frac{\frac{V_o}{2} - V_1}{1k} = \frac{V_1}{1k} + \frac{V_2}{2k}$$

$$V_o - 2V_1 = 2V_1 + V_2$$

$$V_2 = V_o$$

$$V_1 = 0V$$

$$V_1 - V_2 = 12$$

$$V_2 = -12V$$

$$V_o = -12V$$

3.70 Use nodal analysis to find V_o in Fig. P3.70.


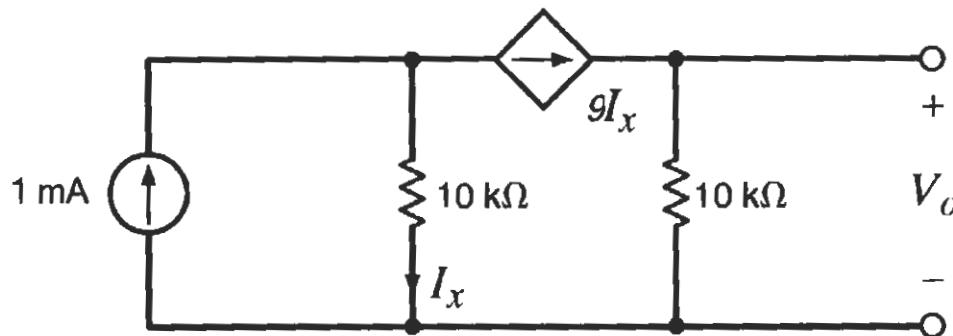


Figure P3.70

SOLUTION: 3.70

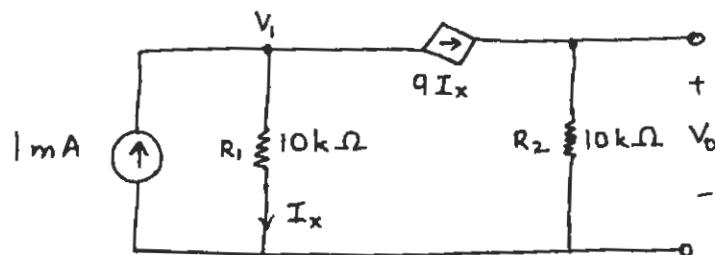

$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$I_x = \frac{V_i}{R_1} \Rightarrow I_x = \frac{V_i}{10 \times 10^3} = \frac{V_i}{10} \times 10^{-3}$$

$$\text{KCL at } V_i : -1 \times 10^{-3} + \frac{V_i}{R_1} + 9 I_x = 0$$

$$V_i = 1 \text{ V}$$

$$\text{KCL at } V_o : -9 I_x + \frac{V_o}{R_2} = 0$$

$$V_o = 9 V_i$$

$$\boxed{V_o = 9 V}$$

3.71 Use nodal analysis to find V_o in the network in Fig. P3.71.


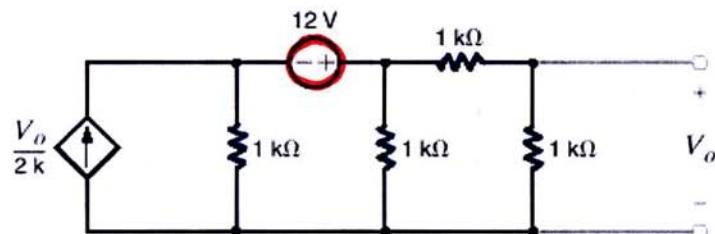


Figure P3.71

SOLUTION:

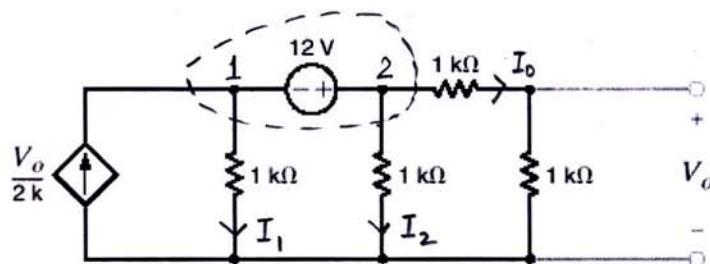

KCL at supernode:

$$\frac{V_o}{2k} = I_1 + I_2 + I_0$$

$$\frac{V_1}{1k} + \frac{V_2}{1k} + \frac{V_2}{1k+1k} = \frac{V_o}{2k}$$

$$2V_1 + 2V_2 + V_2 = V_o$$

$2V_1 + 3V_2 = V_o$

$-V_1 + V_2 = 12$

$$V_o = I_0(1k)$$

$$I_0 = \frac{V_2}{1k+1k} = \frac{V_2}{2k}$$

$V_o = \frac{V_2}{2}$

$$2V_1 + 3V_2 = \frac{V_2}{2}$$

$$4V_1 + 6V_2 = V_2$$

$$\boxed{4V_1 + 5V_2 = 0}$$

$$-V_1 + V_2 = 12$$

$$4V_1 + 5V_2 = 0$$

$$V_1 = -6.67V$$

$$V_2 = 5.33V$$

$$V_o = \frac{V_2}{2} = \frac{5.33}{2}$$

$$V_o = 2.67V$$

3.72 Find the power supplied by the 4 A current source in the network in Fig. P3.72 using nodal analysis.


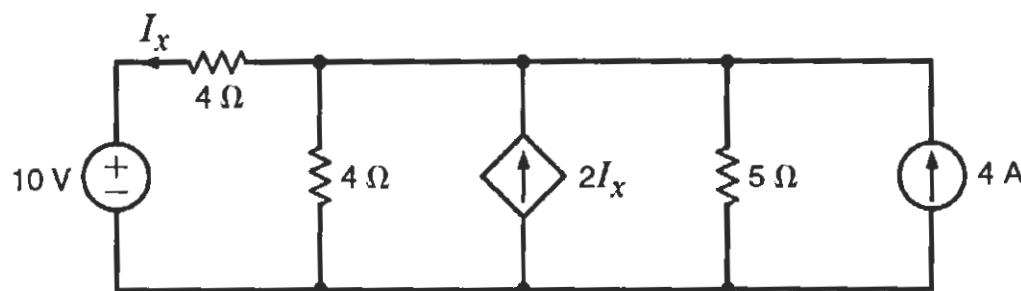


Figure P3.72

SOLUTION: 3.72

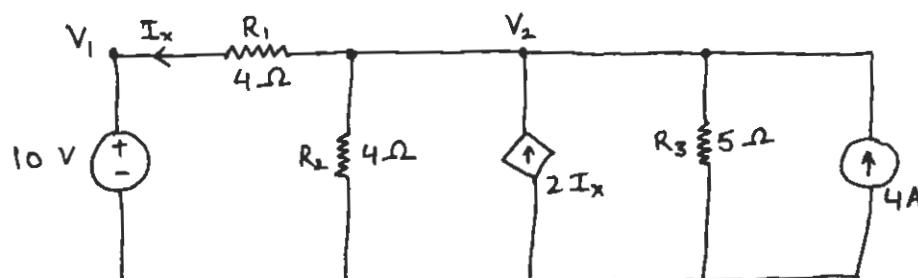

$$R_1 = R_2 = 4 \Omega, \quad R_3 = 5 \Omega$$

$$V_1 = 10 \text{ V}; \quad I_x = \frac{V_2 - V_1}{R_1} = \frac{V_2 - 10}{4} = \frac{V_2 - 10}{4} \text{ A}$$

$$\text{KCL @ } V_2: \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} - 2I_x + \frac{V_2}{R_3} - 4 = 0$$

$$\frac{V_2 - 10}{4} + \frac{V_2}{4} - 2\left(\frac{V_2 - 10}{4}\right) + \frac{V_2}{5} - 4 = 0$$

$$V_2 = 7.5 \text{ V}$$

Power supplied by 4-A source,

$$P_{4A} = 4 \times 7.5$$

$P_{4A} = 30.0 \text{ W}$

3.73 Find I_o in the network in Fig. P3.73.


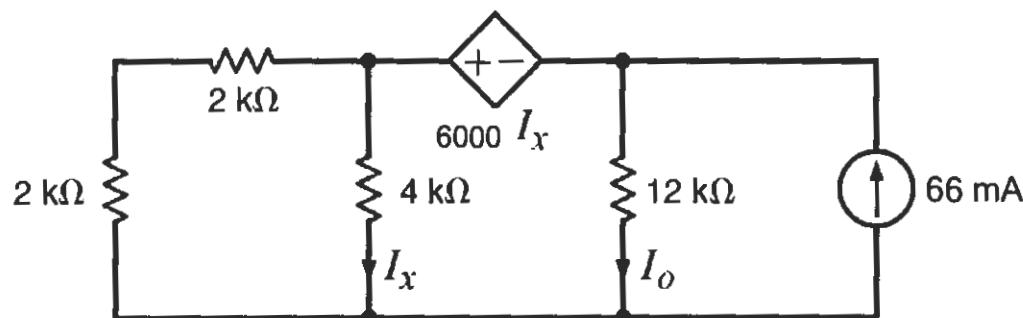


Figure P3.73

SOLUTION: 3.73

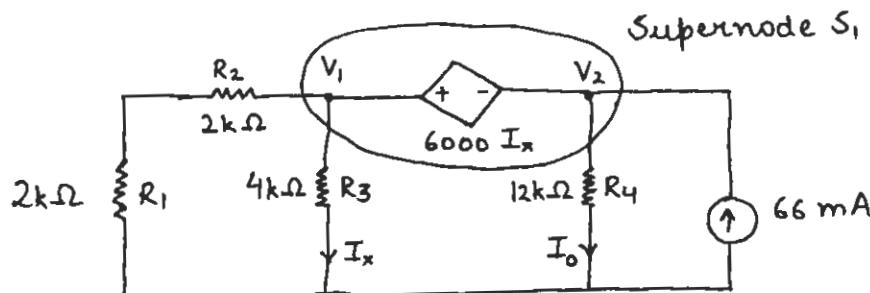

$$R_1 = R_2 = 2 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, R_4 = 12 \text{ k}\Omega$$

$$V_1 - V_2 = 6000 I_x$$

$$\text{Using } I_x = \frac{V_1}{R_3},$$

$$V_1 - V_2 = \frac{3}{2} V_1 \Rightarrow V_1 = -2 V_2 \quad \text{--- (1)}$$

$$\text{KCL @ } S_1 : \frac{V_1}{R_1 + R_2} + \frac{V_1}{R_3} + \frac{V_2}{R_4} - 66 \times 10^{-3} = 0$$

$$6V_1 + V_2 = 792 \quad \text{--- (2)}$$

From equations (1) and (2) we get,

$$-11V_2 = 792$$

$$V_2 = -72.0 \text{ V}$$

$$\begin{aligned}I_0 &= \frac{V_2}{R_4} \\&= \frac{-72}{12 \times 10^3}\end{aligned}$$

$$\boxed{I_0 = -6 \text{ mA}}$$

3.74 Find V_o in the circuit in Fig. P3.74 using nodal analysis.


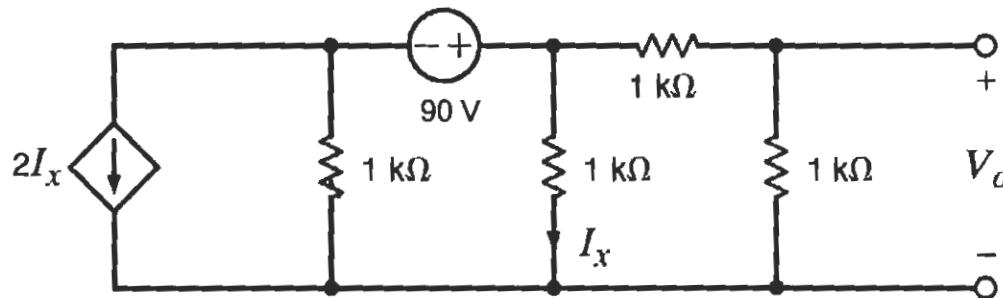


Figure P3.74

SOLUTION: 3.74

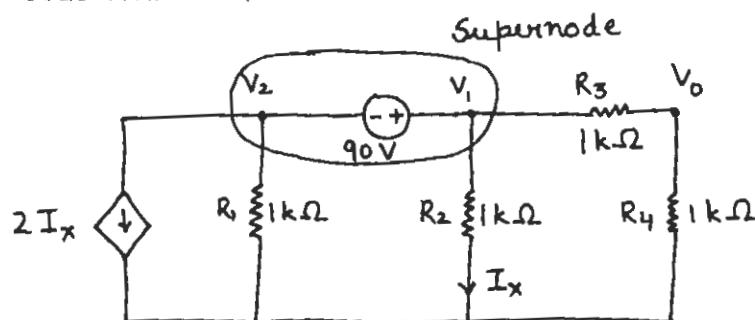

$$R_1 = R_2 = R_3 = R_4 = 1\text{k}\Omega$$

$$V_1 - V_2 = 90\text{ V} \quad \text{---} \quad (1)$$

$$I_x = \frac{V_1}{R_2} = \frac{V_1}{10^3}$$

$$\text{KCL @ Supernode: } 2I_x + \frac{V_2}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_o}{R_3} = 0$$

$$4V_1 + V_2 - V_o = 0 \quad \text{---} \quad (2)$$

$$\text{KCL @ } V_o : \frac{V_o}{R_4} + \frac{V_o - V_1}{R_3} = 0$$

$$V_o = \frac{V_1}{2} \quad \text{---} \quad (3)$$

Substituting equation (3) in (2), we get

$$4V_1 + V_2 - \frac{V_1}{2} = 0$$

$$7V_1 + 2V_2 = 0 \quad \text{---} \quad (4)$$

From equations (1) and (4), we get

$$V_1 = 20 \text{ V}$$

$$V_0 = \frac{V_L}{2}$$

$$\boxed{V_0 = 10 \text{ V}}$$

3.75 Find V_o in the network in Fig. P3.75 using nodal analysis.


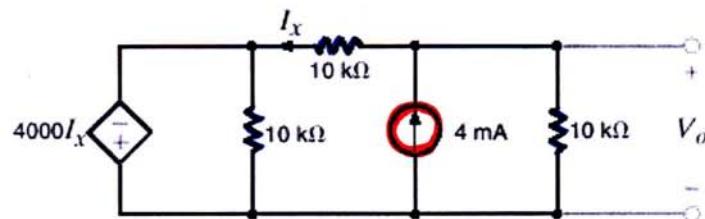


Figure P3.75

SOLUTION:

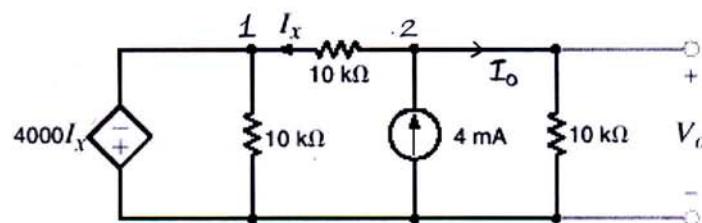

$$V_1 = -4000 I_x$$

$$I_x = \frac{V_2 - V_1}{10k}$$

$$\text{KCL at } 2: 4m = I_x + I_o$$

$$\frac{V_2 - V_1}{10k} + \frac{V_2}{10k} = 4m$$

$$V_2 - V_1 + V_2 = 40$$

$$\boxed{-V_1 + 2V_2 = 40}$$

$$V_1 = -4000 \left(\frac{V_2 - V_1}{10k} \right)$$

$$V_1 = -2/5 V_2 + 2/5 V_1$$

$$5V_1 = -2V_2 + 2V_1$$

$$\boxed{-3V_1 - 2V_2 = 0}$$

$$-V_1 + 2V_2 = 40$$

$$-3V_1 - 2V_2 = 0$$

$$V_1 = -10V$$

$$V_2 = 15V$$

$$V_0 = V_2 = 15V$$

$$V_0 = 15V$$

3.76 Use both nodal analysis and mesh analysis to find V_o in the circuit in Fig. P3.76.


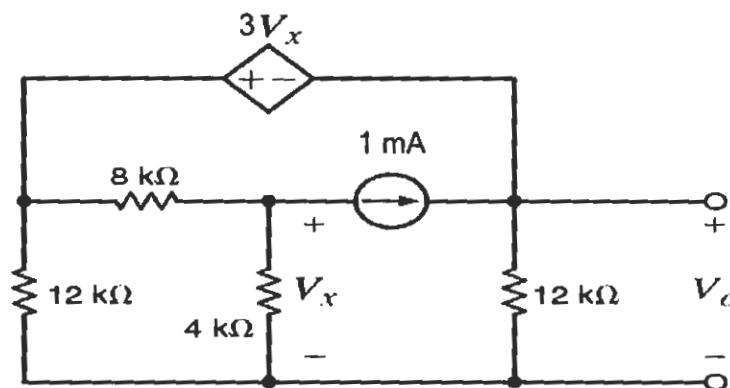


Figure P3.76

SOLUTION: 3.76 (a)

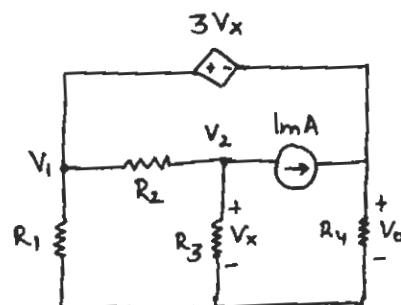

$$R_1 = R_4 = 12 \text{ k}\Omega, R_2 = 8 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, V_x = V_2$$

$$V_1 - V_o = 3V_x$$

$$\Rightarrow V_1 - V_o = 3V_2 \quad \text{---} \quad (1)$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + 1 \times 10^{-3} = 0$$

$$3V_2 - V_1 = -8$$


$$V_2 = \frac{-8 + V_1}{3} \quad \text{---} \quad (2)$$

Substituting equation (2) in (1), we get

$$V_1 - V_o = \frac{3(V_1 - 8)}{3}$$

$$V_o = 8.00 \text{ V}$$

3.76(b)

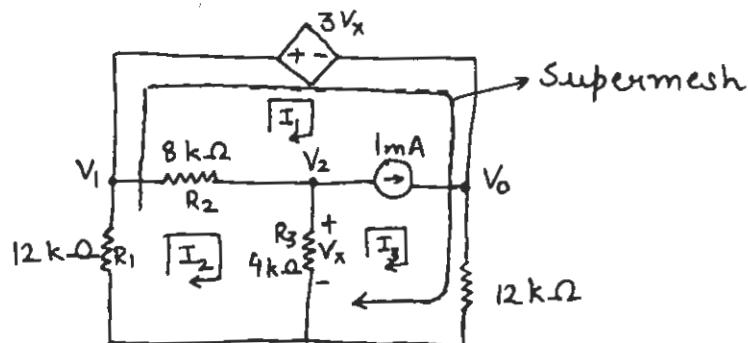

$$R_1 = R_4 = 12\text{k}\Omega, R_2 = 8\text{k}\Omega, R_3 = 4\text{k}\Omega$$

$$I_3 - I_1 = 10^{-3}\text{A} \quad \text{---} \quad (1)$$

$$V_x = (I_2 - I_3) R_3$$

$$V_0 = I_3 R_4$$

$$\text{KVL @ Supermesh: } 3V_x + I_3 R_4 + I_2 R_1 = 0$$

$$3I_2 R_3 - 3I_3 R_3 + I_3 R_4 + I_2 R_1 = 0$$

$$I_2 = 0\text{A} \quad \text{---} \quad (2)$$

$$\text{KVL @ } I_2 : I_2 R_1 + (I_2 - I_1) R_2 + (I_2 - I_3) R_3 = 0$$

$$2I_1 + I_3 = 0$$

$$I_1 = -\frac{I_3}{2} \quad \text{---} \quad (3)$$

Substituting equation (3) in (2), we get

$$I_3 = \frac{2}{3} \times 10^{-3}\text{A}$$

$$V_0 = I_3 R_4$$

$$\boxed{V_0 = 8.00\text{V}}$$

3.77 Find V_x in the circuit in Fig. P3.77.


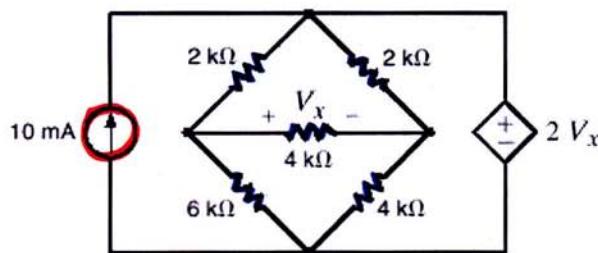


Figure P3.77

SOLUTION:

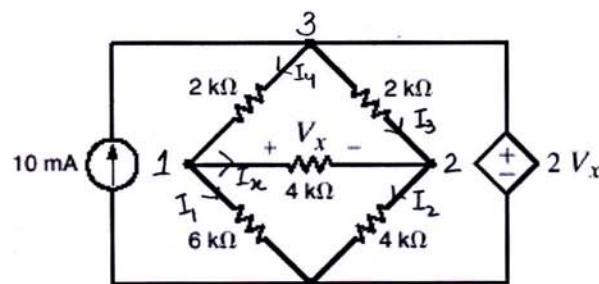

$$\text{KCL at } 1: I_4 = I_x + I_1$$

$$\frac{V_3 - V_1}{2k} = \frac{V_1 - V_2}{4k} + \frac{V_1}{6k}$$

$$6V_3 - 6V_1 = 3V_1 - 3V_2 + 2V_1$$

$$\boxed{11V_1 - 3V_2 - 6V_3 = 0}$$

$$\text{KCL at } 2: I_x + I_3 = I_2$$

$$\frac{V_1 - V_2}{4k} + \frac{V_3 - V_2}{2k} = \frac{V_2}{4k}$$

$$V_1 - V_2 + 2V_3 - 2V_2 = V_2$$

$$\boxed{V_1 - 4V_2 + 2V_3 = 0}$$

$$V_3 = 2V_x$$

$$V_x = V_1 - V_2$$

$$V_3 = 2(V_1 - V_2)$$

$$\boxed{2V_1 - 2V_2 - V_3 = 0}$$

$$11V_1 - 3V_2 - 6V_3 = 0$$

$$V_1 - 4V_2 + 2V_3 = 0$$

$$2V_1 - 2V_2 - V_3 = 0$$

$$V_1 = 0V$$

$$V_2 = 0V$$

$$V_3 = 0V$$

$$V_x = V_1 - V_2$$

$$V_x = 0V$$

3.78 Using mesh analysis, find V_o in the circuit in Fig. P3.78.


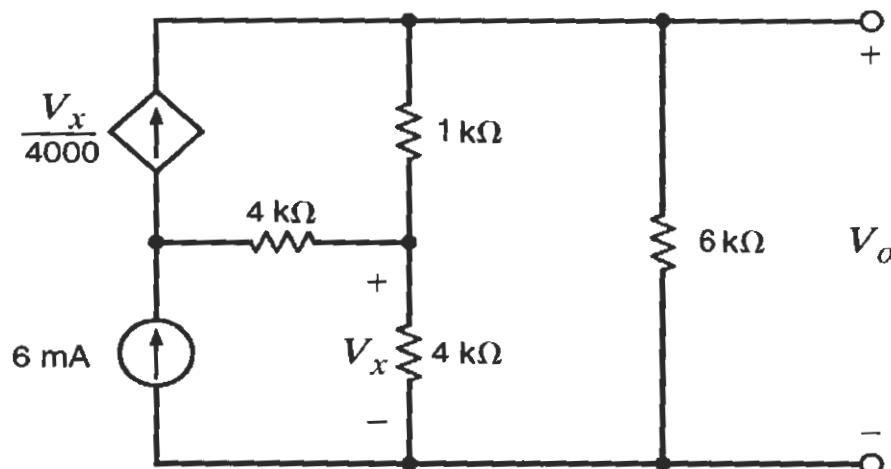


Figure P3.78

SOLUTION: 3.78

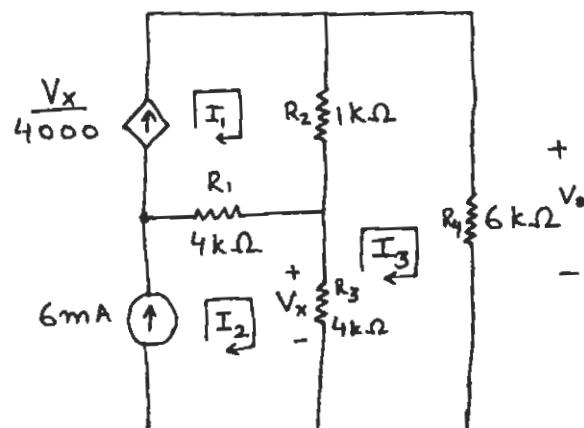

$$R_1 = R_3 = 4 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_4 = 6 \text{ k}\Omega$$

$$I_2 = 6 \times 10^{-3} \text{ A} \quad \text{---} \quad (1)$$

$$V_x = (I_2 - I_3) R_3 \quad \text{---} \quad (2)$$

$$I_1 = \frac{V_x}{4000} \quad \text{---} \quad (3)$$

$$V_o = I_3 R_4$$

$$\text{KVL @ } I_3: (I_8 - I_1)R_2 + I_3R_4 + (I_3 - I_2)R_3 = 0$$

$$11 I_3 - I_1 = 24 \times 10^{-3} \quad \text{--- (4)}$$

Substituting equations (1) and (2) in (3), we get

$$I_1 = 6 \times 10^{-3} - I_3 \quad \text{--- (5)}$$

Substituting equation (5) in (4), we get

$$I_3 = \frac{30}{12} \times 10^{-3} A$$

$$\begin{aligned} V_0 &= I_3 R_4 \\ &= \frac{30}{12} \times 10^{-3} \times 6 \times 10^3 \end{aligned}$$

$V_0 = 15.0V$

3.79 Find I_o in the circuit in Fig. P3.79.


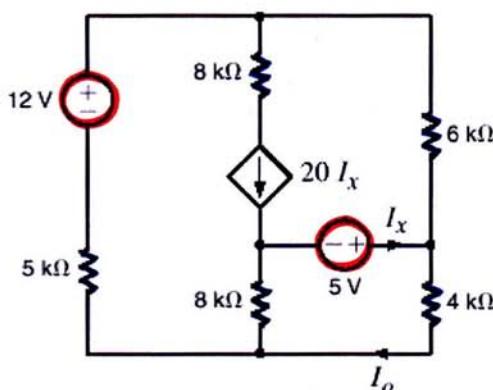


Figure P3.79

SOLUTION:

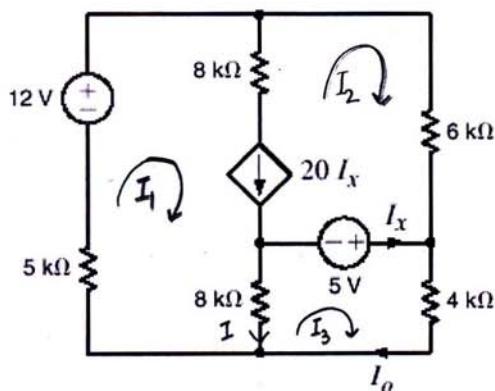

$$\text{KVL: } \boxed{12 = 5kI_1 + 6kI_2 + 4kI_3}$$

$$\begin{aligned} \text{KCL: } I + I_3 &= I_1 \\ I &= I_1 - I_3 \end{aligned}$$

$$\begin{aligned} \text{KVL: } 5 &= 4kI_3 + 8k(-I) \\ 4kI_3 - 8k(I_1 - I_3) &= 5 \\ \boxed{-8kI_1 + 12kI_3 = 5} \end{aligned}$$

$$\begin{aligned} \text{KCL: } I_1 &= 20I_x + I_2 \\ I_1 - I_2 - 20(I_3 - I_2) &= 0 \end{aligned}$$

$$\boxed{I_1 + 19I_2 - 20I_3 = 0}$$

$$5kI_1 + 6kI_2 + 4kI_3 = 12$$

$$-8kI_1 + 0I_2 + 12kI_3 = 5$$

$$I_1 + 19I_2 - 20I_3 = 0$$

$$I_1 = 0.66\text{mA}$$

$$I_2 = 0.871\text{mA}$$

$$I_3 = 0.861\text{mA}$$

$$I_0 = I_3$$

$$I_0 = 0.861\text{mA}$$

- 3.80 Write mesh equations for the circuit in Fig. P3.80 using the assigned currents.


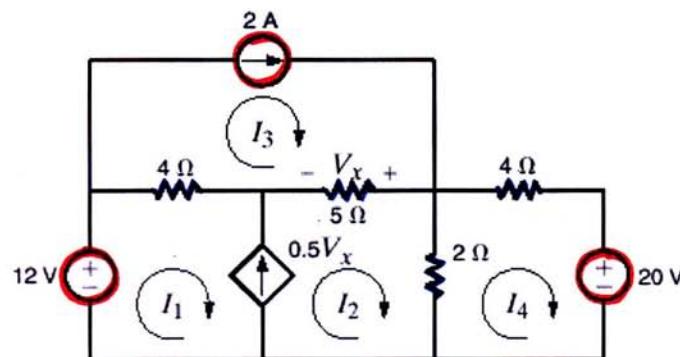


Figure P3.80

SOLUTION:

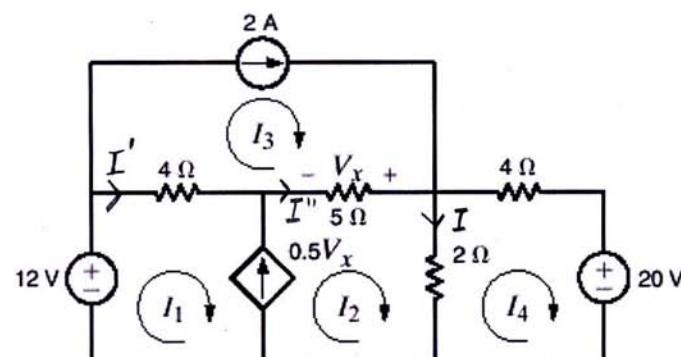

$$KCL: I_1 = I' + I_3$$

$$I' = I_1 - I_3$$

$$KCL: I + I_4 = I_2$$

$$I = I_2 - I_4$$

$$KCL: I'' + I_3 = I + I_4$$

$$I'' = -I_3 + I_4 + I_2 - I_4$$

$$I'' = I_2 - I_3$$

$$KCL: I_2 = 0.5V_x + I_1$$

$$-I_1 + I_2 - 0.5V_x = 0$$

$$V_x = -I''(5) = -5(I_2 - I_3)$$

$$V_x = -5I_2 + 5I_3$$

$$-I_1 + I_2 - 0.5(-5I_2 + 5I_3) = 0$$

$$\boxed{-I_1 + 3.5I_2 - 2.5I_3 = 0}$$

$$I_3 = 2A$$

$$KVL: 4I_4 + 20 + 2(-I) = 0$$

$$4I_4 - 2(I_2 - I_4) = -20$$

$$\boxed{-2I_2 + 16I_4 = -20}$$

$$KVL: 12 = 4I' + 5I'' + 4I_4 + 20$$

$$4(I_1 - I_3) + 5(I_2 - I_3) + 4I_4 = -8$$

$$4I_1 + 5I_2 - 9I_3 + 4I_4 = -8$$

$$\boxed{4I_1 + 5I_2 + 4I_4 = 10}$$

$$-I_1 + 3.5I_2 - 2.5I_3 = 0$$

$$-2I_2 + 6I_4 = -20$$

$$4I_1 + 5I_2 + 4I_4 = 10$$

$$I_3 = 2A$$

$$-I_1 + 3.5I_2 = 5$$

$$-2I_2 + 6I_4 = -20$$

$$4I_1 + 5I_2 + 4I_4 = 10$$

$$I_1 = 2.46A$$

$$I_2 = 2.13A$$

$$I_4 = -2.62A$$

3.81 Find V_o in the network in Fig. P3.81.


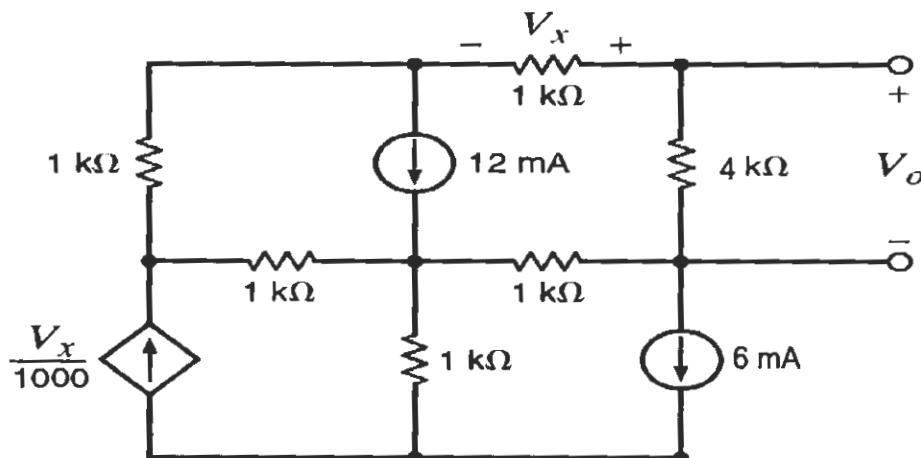


Figure P3.81

SOLUTION: 3.81

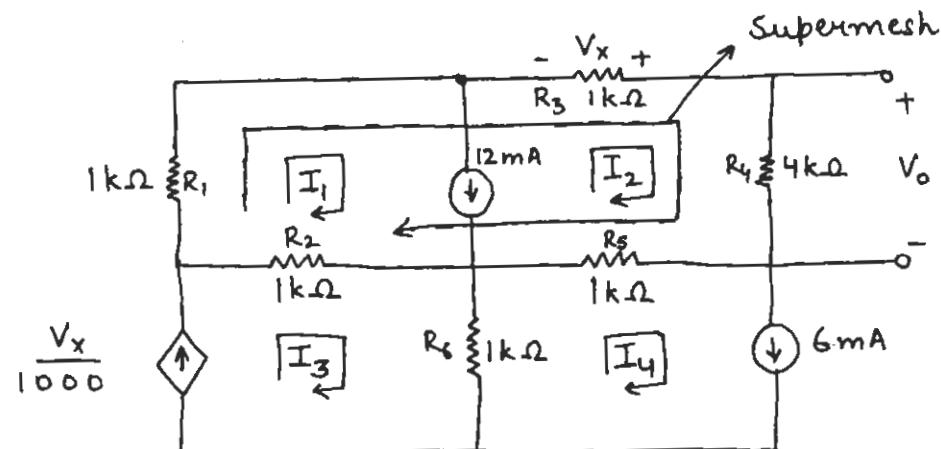

$$R_1 = R_2 = R_3 = R_5 = R_6 = 1 \text{ k}\Omega, R_4 = 4 \text{ k}\Omega$$

$$I_1 - I_2 = 12 \text{ mA} \quad \text{---}$$

$$I_4 = 6 \text{ mA}$$

$$V_x = -I_2 R_3$$

$$I_3 = \frac{V_x}{1000}$$

$$V_0 = I_2 R_4$$

$$KVL @ \text{supermesh: } I_1 R_1 + I_2 R_3 + I_2 R_4 + (I_2 - I_4) R_5 + (I_1 - I_3) R_2 = 0$$

$$I_1(R_1+R_2) + I_2(R_3+R_4+R_5) - I_3 R_2 - I_4 R_5 = 0$$

$$2 \times 10^3 I_1 + 6 \times 10^3 I_2 - 10^3 I_3 - 10^3 I_4 = 0$$

$$2I_1 + 6I_2 - I_3 - I_4 = 0$$

Substituting $I_3 = \frac{V_x}{1000}$ and $V_x = -I_2 R_3$

$$2I_1 + 7I_2 = 6 \times 10^{-3} \quad \text{---} \quad (2)$$

From equations (1) and (2), we get

$$I_2 = -2 \text{ mA}$$

$$V_o = I_2 R_4$$

$$V_o = -2 \times 10^{-3} \times 4 \times 10^3$$

$$V_o = -8.00 \text{ V}$$

3.82 Using nodal analysis, find V_o in the circuit in Fig. P3.82.


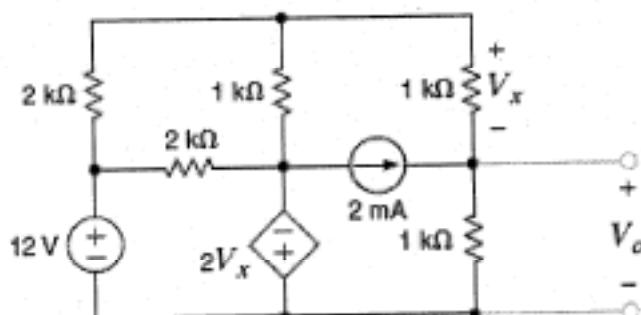


Figure P3.82

Solution : 3.82

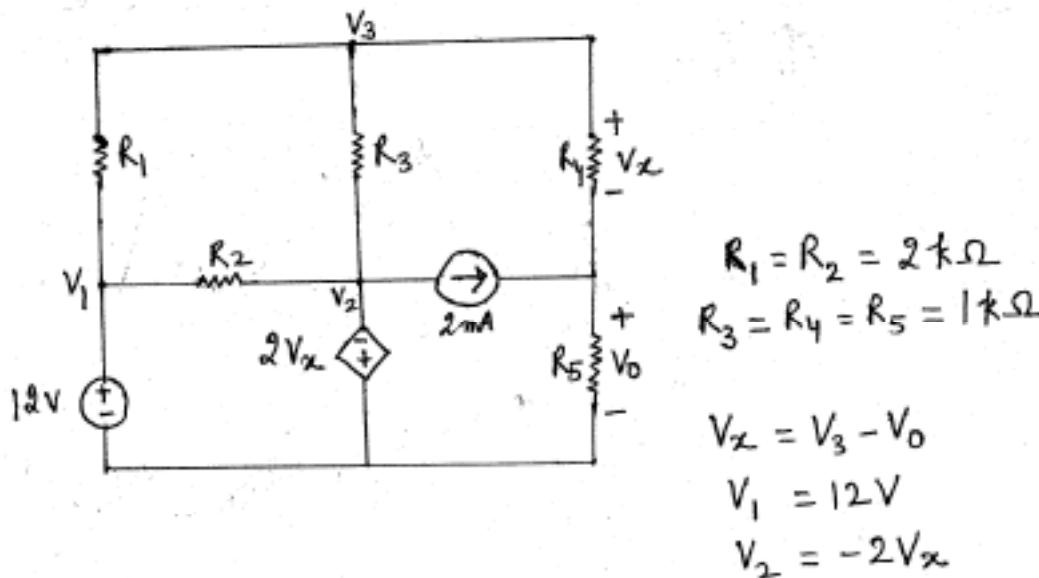

$$\text{at } V_3 : \frac{V_3 - V_1}{R_1} + \frac{V_3 - V_2}{R_3} + \frac{V_3 - V_o}{R_4} = 0$$

$$\text{at } V_o : \frac{V_3 - V_o}{R_4} + 2 \times 10^{-3} = \frac{V_o}{R_5}$$

Solve for V_o : $V_o = 2.5 \text{ V}$

- 3.83 Solve for the assigned mesh currents in the network in Fig. P3.83.


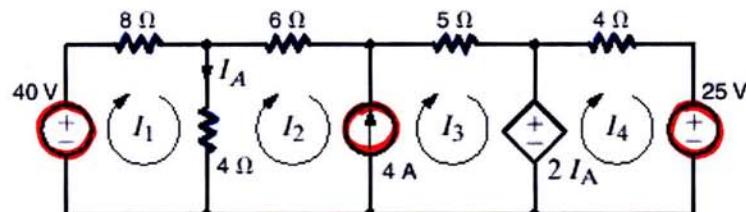


Figure P3.83

SOLUTION:

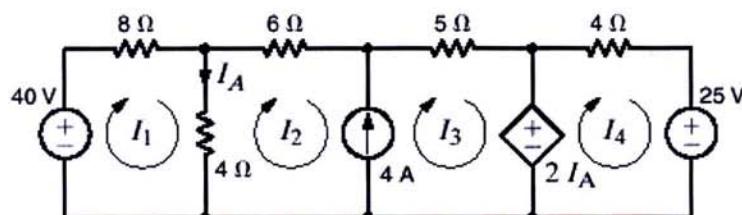

$$\text{KCL: } I_1 = I_A + I_2$$

$$I_A = I_1 - I_2$$

$$\text{KVL: } 8I_1 + 4I_A = 40$$

$$8I_1 + 4(I_1 - I_2) = 40$$

$$\boxed{12I_1 - 4I_2 = 40}$$

$$\text{KVL: } 2I_A = 4I_4 + 25$$

$$2(I_1 - I_2) = 4I_4 + 25$$

$$\boxed{2I_1 - 2I_2 - 4I_4 = 25}$$

$$\text{KVL: } 8I_1 + 6I_2 + 5I_3 + 4I_4 + 25 = 40$$

$$\boxed{8I_1 + 6I_2 + 5I_3 + 4I_4 = 15}$$

$$\text{KCL: } I_2 + 4 = I_3$$

$$\boxed{-I_2 + I_3 = 4}$$

$$12I_1 - 4I_2 + 0I_3 + 0I_4 = 40$$

$$2I_1 - 2I_2 + 0I_3 - 4I_4 = 25$$

$$8I_1 + 6I_2 + 5I_3 + 4I_4 = 15$$

$$0I_1 - I_2 + I_3 + 0I_4 = 4$$

$$I_1 = 2.97A$$

$$I_2 = -1.08A$$

$$I_3 = 2.92A$$

$$I_4 = -4.22A$$

- 3.84 Using the assigned mesh currents shown in Fig. P3.84 solve for the power supplied by the dependent voltage source.

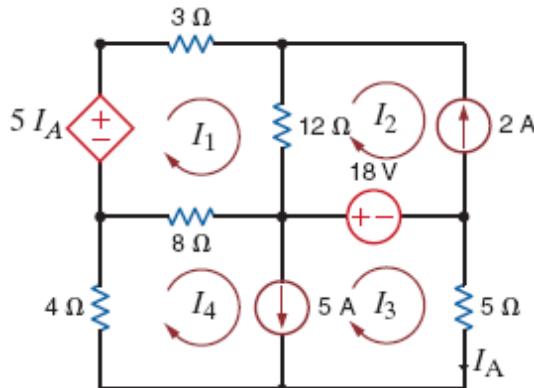
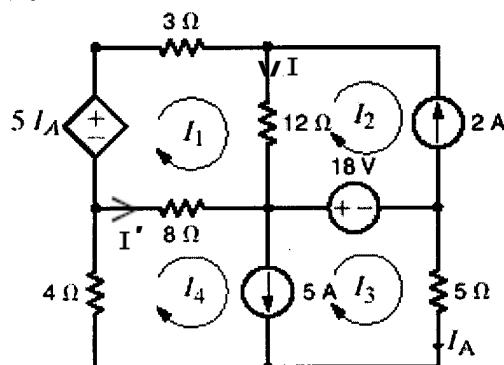


Figure P3.84

SOLUTION:

$$\text{KCL: } I_1 = I + I_2$$

$$I = I_1 - I_2$$

$$\text{KCL: } I_4 = I' + I_1$$

$$I' = I_4 - I_1$$

$$\text{KVL: } 3I_1 + 12I + 8(-I') = 5I_A$$

$$I_A = I_3$$

$$3I_1 + 12(I_1 - I_2) - 8(I_4 - I_1) = 5I_3$$

$$\boxed{23I_1 - 12I_2 - 5I_3 - 8I_4 = 0}$$

$$\text{KVL: } 8I' + 5I_3 + 4I_4 + 18 = 0$$

$$8(I_4 - I_1) + 5I_3 + 4I_4 = -18$$

$$\boxed{-8I_1 + 5I_3 + 12I_4 = -18}$$

$$\text{KCL: } I_3 + 5 = I_4$$

$$I_2 = -2A \quad \boxed{I_3 - I_4 = -5}$$

$$\boxed{23I_1 - 5I_3 - 8I_4 = -24}$$

$$23I_1 - 5I_3 - 8I_4 = -24$$

$$-8I_1 + 5I_3 + 12I_4 = -18$$

$$0I_1 + I_3 - I_4 = -5$$

$$I_1 = -2.59A$$

$$I_3 = -5.8A$$

$$I_4 = -0.8A$$

and $I_2 = -2A$

$$\therefore P_{SIA} = (5 \times -5.8)(-2.59) = 75W$$

3.85 Determine V_o in the network in the Fig. P3.85 using loop analysis.


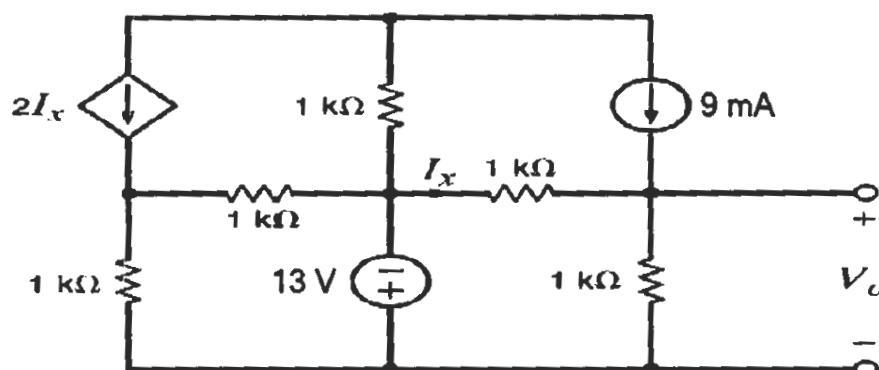


Figure P3.85

Solution: 3.85

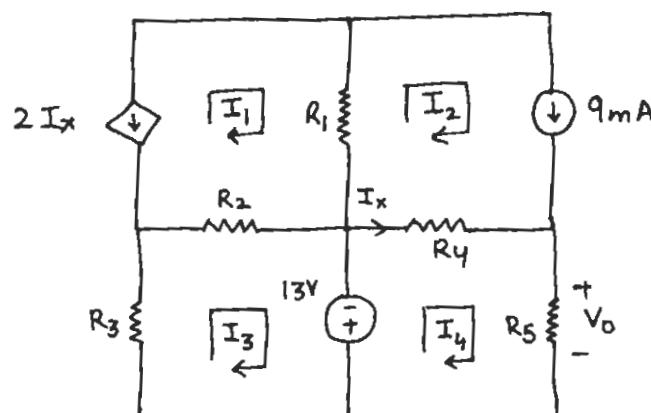

$$R_1 = R_2 = R_3 = R_4 = R_5 = 1 \text{ k}\Omega$$

$$I_2 = 9 \text{ mA}$$

$$I_x = (I_4 - I_2)$$

$$I_1 = -2I_x$$

$$= -2(I_4 - I_2)$$

$$V_o = I_4 R_5$$

$$\text{KVL } @ I_4 : 13 + (I_4 - I_2)R_4 + I_4 R_5 = 0$$

$$13 + 10^3 I_4 - 10^3 I_2 + 10^3 I_4 = 0$$

$$I_4 = -2 \times 10^{-3} \text{ A}$$

$$V_o = I_4 R_5 = -2 \times 10^{-3} \times 1 \times 10^3$$

$V_o = -2.00 \text{ V}$

- 3.86 Using loop analysis, find V_o in the network in Fig. P3.86.


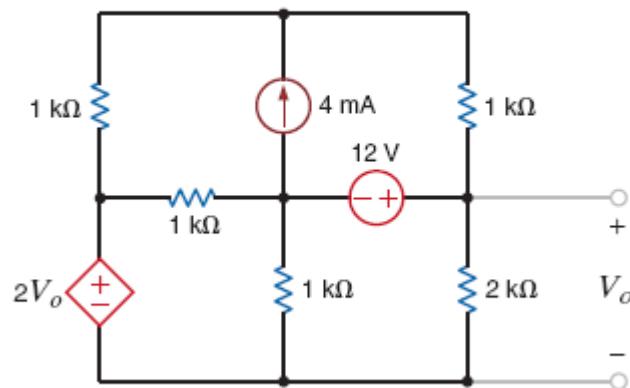


Figure P3.86

SOLUTION:

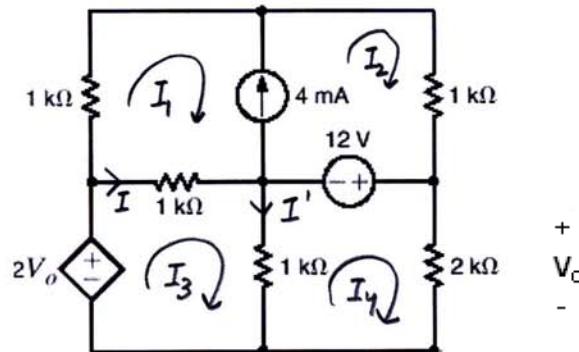

$$\text{KCL: } I_1 + 4\text{mA} = I_2$$

$$\boxed{I_1 - I_2 = -4\text{mA}}$$

$$\text{KCL: } I_3 = I + I_1$$

$$I = I_3 - I_1$$

$$\text{KCL: } I' + I_4 = I_3$$

$$I' = I_3 - I_4$$

$$\text{KVL: } 2kI_4 + 1k(-I') = 12$$

$$-1k(I_3 - I_4) + 2kI_4 = 12$$

$$\boxed{-1kI_3 + 3kI_4 = 12}$$

$$KVL: 1k I + 1k I' = 2V_0$$

$$V_0 = 2k I_4$$

$$\boxed{1k(I_3 - I_1) + 1k(I_3 - I_4) = 2(2k I_4)}$$

$$\boxed{-1k I_1 + 2k I_3 - 5k I_4 = 0}$$

$$KVL: 2V_0 = 1k I_1 + 1k I_2 + 2k I_4$$

$$V_0 = 2k I_4$$

$$\boxed{1k I_1 + 1k I_2 - 2k I_4 = 0}$$

$$I_1 - I_2 + 0I_3 + 0I_4 = -4m$$

$$0I_1 + 0I_2 - 1k I_3 + 3k I_4 = 12$$

$$-1k I_1 + 0I_2 + 2k I_3 - 5k I_4 = 0$$

$$1k I_1 + 1k I_2 + 0I_3 - 2k I_4 = 0$$

In the matrix form the equation can be represented/restructured as:

$$\begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 2 & 0 & -2 \\ 0 & 0 & 4 & -12 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -4 \\ 4 \\ -4 \\ 44 \end{bmatrix}$$

$$V_0 = \infty$$

Since there are only 3 independent equations for 4 unknowns (11 to 14), it can be not be solved for a unique solution.

This is because current equations are contradictory.
 $\therefore V_0$ = not defined (open circuit).

- 3.87 Using loop analysis, find V_o in the circuit in Fig. P3.87.


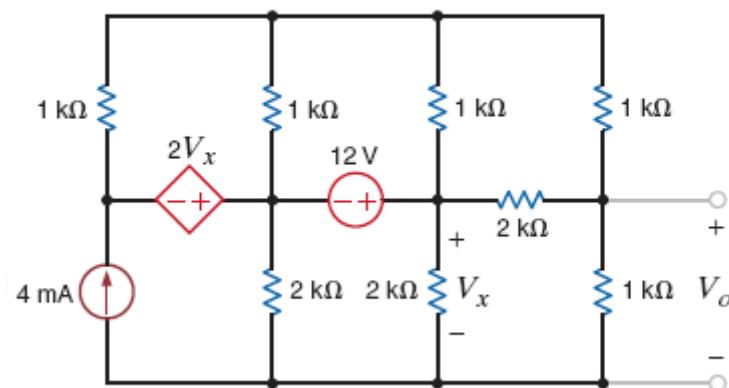


Figure P3.87

SOLUTION:

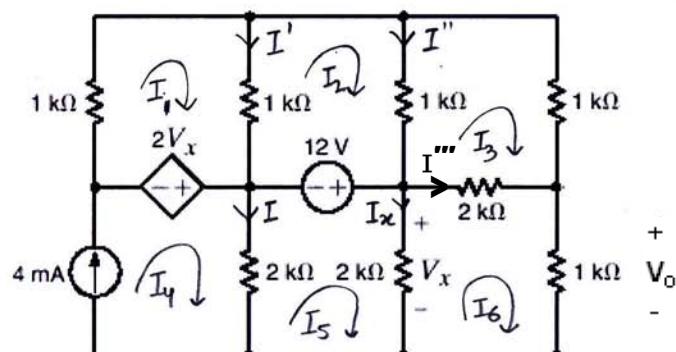

$$\text{KCL: } I_1 = I' + I_2$$

$$I' = I_1 - I_2$$

$$\text{KCL: } I_2 = I'' + I_3$$

$$I'' = I_2 - I_3$$

$$\text{KCL: } I + I_5 = I_4$$

$$I = I_4 - I_5$$

$$\text{KCL: } I_x + I_6 = I_5$$

$$I_x = I_5 - I_6$$

$$\text{KCL: } I_3 + I''' = I_6$$

$$I''' = I_6 - I_3$$

$$\text{KVL: } 2V_x + 1kI_1 + 1kI' = 0$$

$$\begin{aligned} V_x &= I_x(2k) = (I_5 - I_6)2k \\ 2(2k)(I_5 - I_6) + 1kI_1 + 1k(I_1 - I_2) &= 0 \\ 4kI_5 - 4kI_6 + 2kI_1 - 1kI_2 &= 0 \end{aligned}$$

$$2kI_1 - 1kI_2 + 4kI_5 - 4kI_6 = 0$$

$$\begin{aligned} \text{KVL: } 12 + 1k(-I') + 1kI'' &= 0 \\ -1k(I_1 - I_2) + 1k(I_2 - I_3) &= -12 \\ -1kI_1 + 2kI_2 - 1kI_3 &= -12 \end{aligned}$$

$$\begin{aligned} \text{KVL: } 1k(-I'') + 1kI_3 + 2k(-I''') &= 0 \\ -1k(I_2 - I_3) + 1kI_3 - 2k(I_6 - I_3) &= 0 \\ -1kI_2 + 4kI_3 - 2kI_6 &= 0 \end{aligned}$$

$$\begin{aligned} \text{KVL: } 12 &= 2k(-I) + 2kI_x \\ -2k(I_4 - I_5) + 2k(I_5 - I_6) &= 12 \end{aligned}$$

$$I_4 = \frac{4\text{mA}}{4kI_5 - 2kI_6 = 20}$$

$$\begin{aligned} \text{KVL: } 2kI''' + 1kI_6 + 2k(-I_x) &= 0 \\ 2k(I_6 - I_3) + 1kI_6 - 2k(I_5 - I_6) &= 0 \\ -2kI_3 - 2kI_5 + 5kI_6 &= 0 \end{aligned}$$

$$\begin{aligned} 2kI_1 - 1kI_2 + 0I_3 + 4kI_5 - 4kI_6 &= 0 \\ -1kI_1 + 2kI_2 - 1kI_3 + 0I_5 + 0I_6 &= -12 \\ 0I_1 - 1kI_2 + 4kI_3 + 0I_5 - 2kI_6 &= 0 \\ 0I_1 + 0I_2 + 0I_3 + 4kI_5 - 2kI_6 &= 20 \\ 0I_1 + 0I_2 - 2kI_3 - 2kI_5 + 5kI_6 &= 0 \end{aligned}$$

$$I_1 = -18mA$$

$$I_2 = -17mA$$

$$I_3 = -4mA$$

$$I_5 = 5.25mA$$

$$I_6 = 0.5mA$$

$$V_o = 1k(I_6) = 1k(0.5m)$$

$$V_o = 0.5V$$

3.88 Use loop analysis to determine I_o in the circuit in the Fig. P3.88.


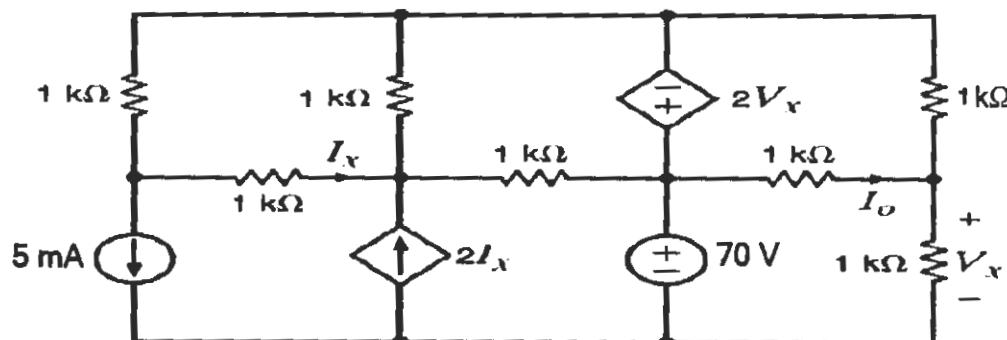


Figure P3.88

Solution: 3.88

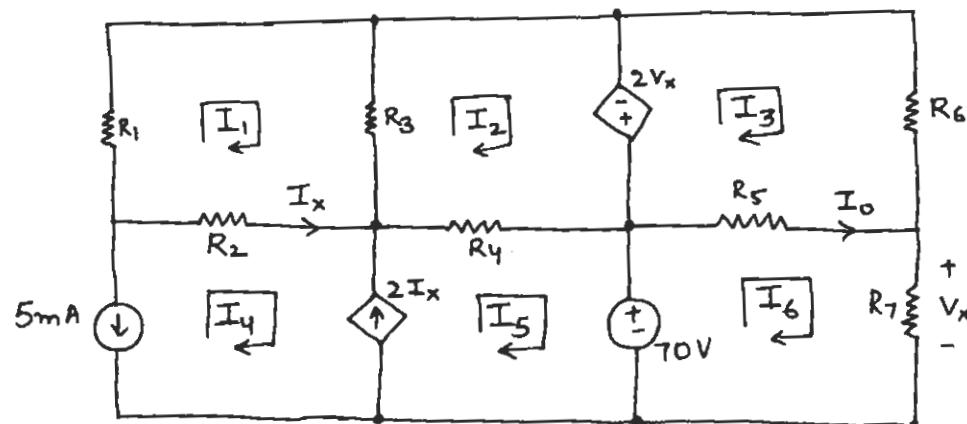

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$I_4 = 5 \text{ mA}$$

$$2I_x = I_5 - I_4$$

$$I_x = I_4 - I_1$$

$$I_6 = I_6 - I_3$$

$$V_x = I_6 R_7$$

$$\text{KVL @ } I_1 : I_1 R_1 + (I_1 - I_2) R_3 + (I_1 - I_4) R_2 = 0$$

$$3I_1 - I_2 = 5 \times 10^{-3}$$

$$\text{KVL @ } I_2: (I_2 - I_1)R_3 - 2V_x + (I_2 - I_5)R_4 = 0$$

$$-I_1 + 2I_2 - I_5 - 2I_6 = 0$$

$$\text{KVL @ } I_3: 2V_x + I_3R_6 + (I_3 - I_6)R_5 = 0$$

$$2I_3 + I_6 = 0 \quad \textcircled{1}$$

$$\text{KVL @ } I_6: -70 + (I_6 - I_3)R_5 + I_6R_7 = 0$$

$$-I_3 + 2I_6 = 70 \times 10^{-3} \quad \textcircled{2}$$

From equations $\textcircled{1}$ and $\textcircled{2}$, we get

$$I_6 = 28 \text{ mA}$$

Substituting the value of I_6 in $\textcircled{1}$, we get

$$2I_3 = -28 \times 10^{-3}$$

$$I_3 = -14 \text{ mA}$$

$$I_0 = I_6 - I_3$$

$$\boxed{I_0 = 42.0 \text{ mA}}$$

- 3.89 Using loop analysis, find I_o in the circuit in Fig. P3.89.

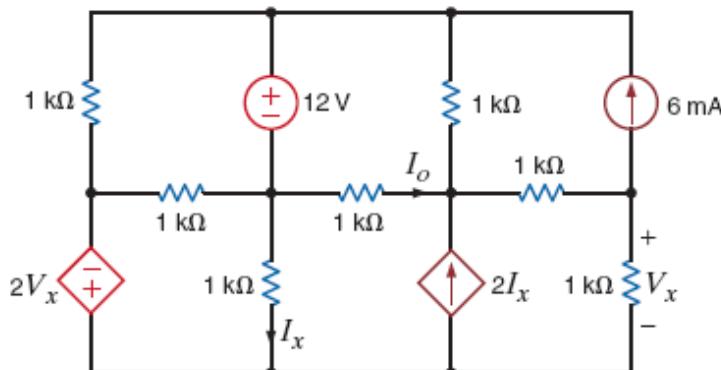
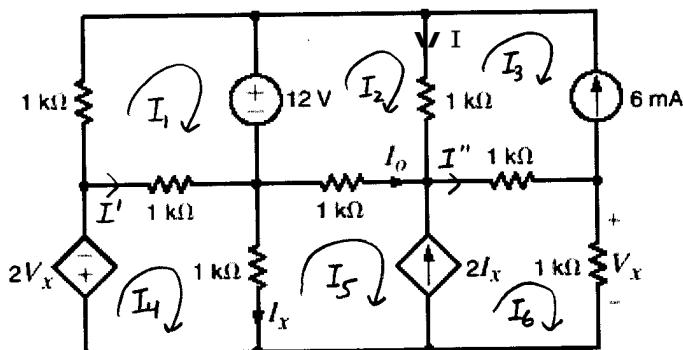


Figure P3.89

SOLUTION:

$$\text{KCL: } I_2 = I + I_3$$

$$I = I_2 - I_3$$

$$\text{KCL: } I_4 = I' + I_1$$

$$I' = I_4 - I_1$$

$$\text{KCL: } I_3 + I'' = I_6$$

$$I'' = I_6 - I_3$$

$$\text{KCL: } I_5 + I_x = I_4$$

$$I_x = I_4 - I_5$$

$$\text{KCL: } I_0 + I + 2I_x = I''$$

$$I_0 = I'' - I - 2I_x = I_6 - I_3 - I_2 + I_3 - 2I_x$$

$$I_0 = I_6 - I_2 - 2(I_4 - I_5)$$

$$I_0 = -I_2 - 2I_4 + 2I_5 + I_6$$

$$\text{KVL: } 1k I_1 + 12 + 1k(-I') = 0$$

$$1k I_1 - 1k(I_4 - I_1) = -12$$

$$\boxed{2k I_1 - 1k I_4 = -12}$$

$$\text{KVL: } 1k I + 1k(-I_0) = 12$$

$$1k(I_2 - I_3) - 1k(-I_2 - 2I_4 + 2I_5 + I_6) = 12$$

$$\boxed{2k I_2 - 1k I_3 + 2k I_4 - 2k I_5 - 1k I_6 = 12}$$

$$\text{KVL: } 2V_x + 1k I' + 1k I_x = 0$$

$$V_x = 1k I_6$$

$$2(1k I_6) + 1k(I_4 - I_1) + 1k(I_4 - I_5) = 0$$

$$\boxed{-1k I_1 + 2k I_4 - 1k I_5 + 2k I_6 = 0}$$

$$\text{KCL: } I_6 = 2I_x + I_5$$

$$I_5 - I_6 + 2(I_4 - I_5) = 0$$

$$\boxed{2I_4 - I_5 - I_6 = 0}$$

$$\text{KVL: } 2V_x + 1k I' + 1k I_0 + 1k I'' + 1k I_6 = 0$$

$$2(1k I_6) + 1k(I_4 - I_1) + 1k(-I_2 - 2I_4 + 2I_5 + I_6) + 1k(I_6 - I_3) + 1k I_8$$

$$\boxed{-1k I_1 - 1k I_2 - 1k I_3 - 1k I_4 + 2k I_5 + 5k I_6 = 0}$$

$$I_3 = -6 \text{ mA}$$

$$\boxed{2k I_2 + 2k I_4 - 2k I_5 - 1k I_6 = 6}$$

$$\boxed{-1k I_1 - 1k I_2 - 1k I_4 + 2k I_5 + 5k I_6 = -6}$$

$$\begin{aligned}
 2kI_1 + 0I_2 - 1kI_4 + 0I_5 + 0I_6 &= -12 \\
 0I_1 + 2kI_2 + 2kI_4 - 2kI_5 - 1kI_6 &= 6 \\
 -1kI_1 + 0I_2 + 2kI_4 - 1kI_5 + 2kI_6 &= 0 \\
 0I_1 + 0I_2 + 2I_4 - I_5 - I_6 &= 0 \\
 -1kI_1 - 1kI_2 - 1kI_4 + 2kI_5 + 5kI_6 &= -6
 \end{aligned}$$

$$I_1 = -6.48\text{mA}$$

$$I_2 = 3.12\text{mA}$$

$$I_4 = -0.96\text{mA}$$

$$I_5 = 0.24\text{mA}$$

$$I_6 = -2.16\text{mA}$$

$$I_0 = -I_2 - 2I_4 + 2I_5 + I_6$$

$$I_0 = -3.12m - 2(-0.96m) + 2(0.24m) - 2.16m$$

$$I_0 = -2.88\text{mA}$$

- 3.90 Use mesh analysis to determine the power delivered by the independent 3-V source in the network in Fig. P3.90.


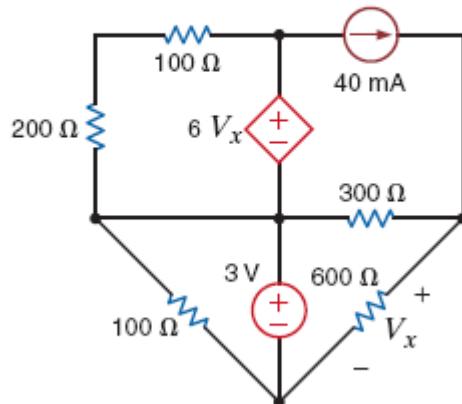


Figure P3.90

SOLUTION:

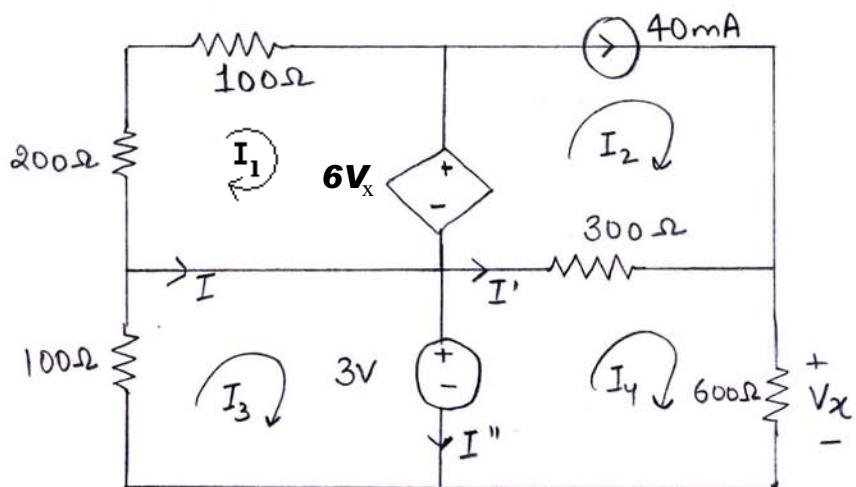

$$I_2 = 40 \text{ mA}$$

$$\text{KCL: } I_3 = I + I_1$$

$$I = I_3 - I_1$$

$$\text{KCL: } 40 \text{ mA} + I' = I_4$$

$$I' = I_4 - 40 \text{ mA}$$

$$\text{KVL: } 200I_1 + 100I_3 + 6V_x = 0$$

$$V_x = 600I_4$$

$$300I_1 + 3600I_4 = 0$$

$$\text{KVL: } 100I_3 + 3 = 0$$

$$I_3 = -30 \text{ mA}$$

KVL: $3 = 300 I' + 600 I_y$

$$600 I_y + 300 (I_y - 40 \text{ m}) = 3$$

$$900 I_y = 15$$

$$I_y = 16.67 \text{ mA}$$

KCL: $I_y + I'' = I_3$

$$I'' = I_3 - I_y$$

$$P_{3V} = I''(3) = 3(I_3 - I_y)$$

$$P_{3V} = 3(-30 \text{ m} - 16.67 \text{ m})$$

$$P_{3V} = -140.01 \text{ mW}$$

$$P_{3V} = 140.01 \text{ mW}$$

3.91 Use mesh analysis to find the power delivered by the current-controlled voltage source in the circuit in Fig. P3.91.


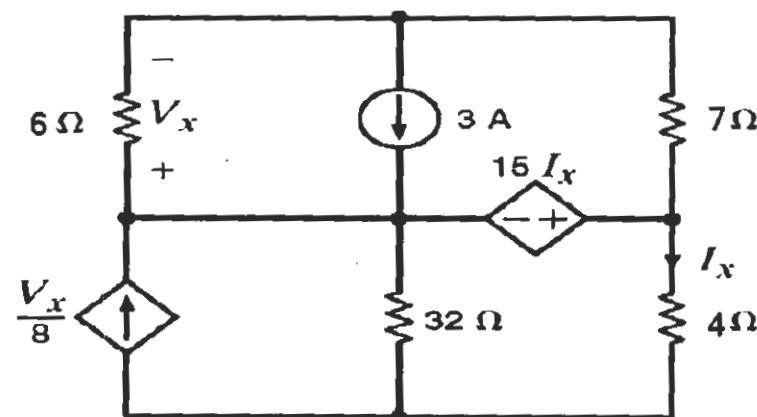


Figure P3.91

Solution: 3.91

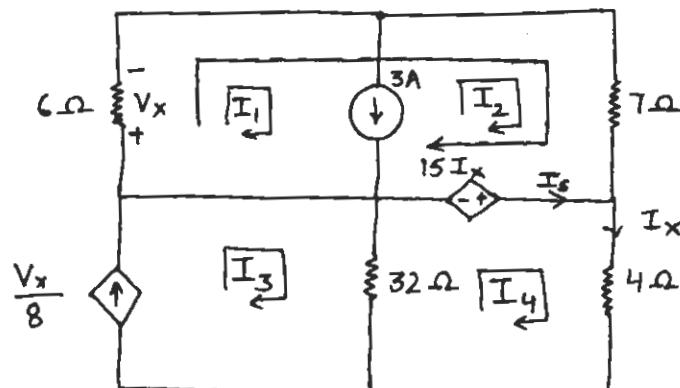

$$I_1 - I_2 = 3 \quad \text{---} \quad (1)$$

$$V_x = 6 I_1$$

$$I_5 = I_4 - I_2$$

$$I_x = I_4$$

$$I_3 = \frac{V_x}{8} = \frac{3}{4} I_1$$

$$\text{KVL @ } I_4 : 32(I_4 - I_3) - 15I_x + 4I_4 = 0$$

$$21I_4 - 32I_3 = 0$$

$$I_4 = 1.52 I_3$$

KVL @ Supermesh : $6I_1 + 7I_2 + 15I_x = 0$

$$23 \cdot 18 I_1 + 7I_2 = 0 \quad \text{--- } (2)$$

From equations (1) and (2), we get

$$I_1 = 0.696 \text{ A}$$

$$I_3 = \frac{3}{4} I_1 = 0.522 \text{ A}$$

$$I_4 = 1.52 I_3 = 0.793 \text{ A}$$

$$I_s = I_4 - I_2 = 3.09 \text{ A}$$

$$P_{CCVS} = (15I_x) I_s$$

$P_{CCVS} = 37.0 \text{ W}$

3.92 Use nodal analysis to determine I_o in the circuit in Fig. P3.92.


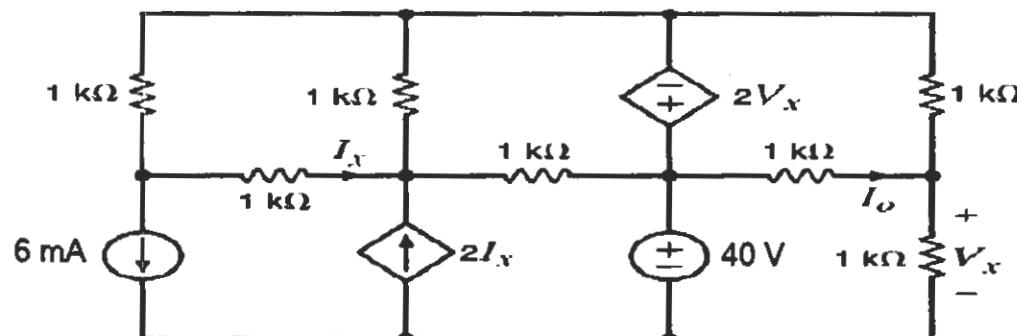


Figure P3.92

Solution: 3.92

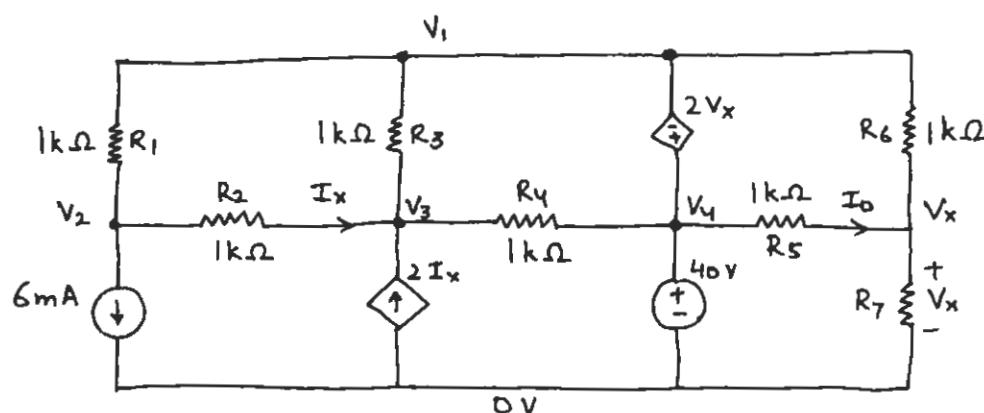

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$V_4 = 40 \text{ V}$$

$$V_4 - V_1 = 2V_x \quad \text{--- (1)}$$

$$\frac{V_2 - V_3}{R_2} = I_x$$

$$I_o = \frac{V_4 - V_x}{R_5}$$

$$\text{KCL at } V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_2} + 6 \times 10^{-3} = 0$$

$$-V_1 + 2V_2 - V_3 = -6$$

$$\text{KCL @ } V_3 : \frac{V_3 - V_2}{R_2} - 2 I_x + \frac{V_3 - V_1}{R_3} + \frac{V_3 - V_4}{R_4} = 0$$

$$-V_1 - 3V_2 + 5V_3 = 40 \quad (\text{Using } V_4 = 40 \text{ V})$$

$$\text{KCL @ } V_x : \frac{V_x - V_4}{R_5} + \frac{V_x - V_1}{R_6} + \frac{V_x}{R_7} = 0$$

$$3V_x - V_4 - V_1 = 0 \quad \text{--- (2)}$$

Substituting equation (1) in (2), we get

$$3\left(\frac{V_4 - V_1}{2}\right) - V_4 - V_1 = 0$$

$$-\frac{5}{2}V_1 + \frac{1}{2}V_4 = 0$$

$$-5V_1 + 40 = 0$$

$$V_1 = 8 \text{ V}$$

$$(\text{Using } V_4 = 40 \text{ V})$$

$$V_x = \frac{V_4 - V_1}{2} = \frac{40 - 8}{2}$$

$$V_x = 16 \text{ V}$$

$$I_0 = \frac{V_4 - V_x}{R_5}$$

$$= \frac{40 - 16}{1 \times 10^3}$$

$$\boxed{I_0 = 24.0 \text{ mA}}$$

3.93 Use nodal analysis to find V_o in the circuit in Fig. P3.93.


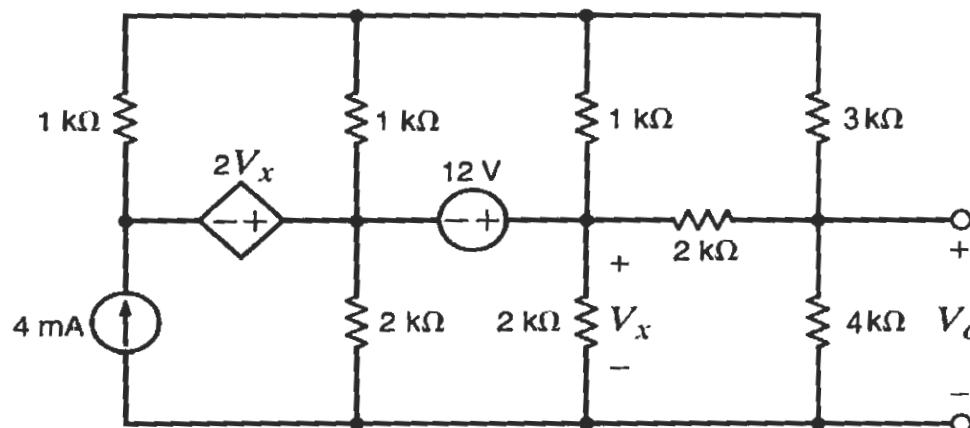


Figure P3.93

SOLUTION: 3.93

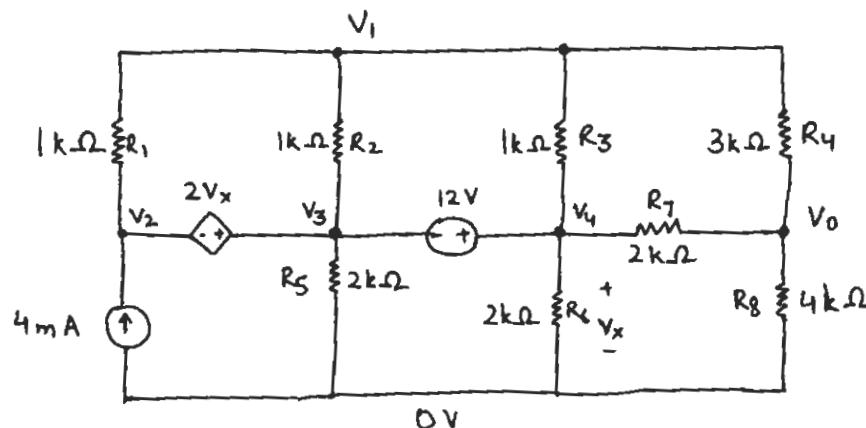

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega, R_4 = 3 \text{ k}\Omega, R_5 = R_6 = R_7 = 2 \text{ k}\Omega, R_8 = 4 \text{ k}\Omega$$

$$V_3 - V_2 = 2V_x \quad \text{---} \quad (1)$$

$$V_4 - V_3 = 12 \text{ V} \quad \text{---} \quad (2)$$

$$V_x = V_4 \quad \text{---} \quad (3)$$

$$\text{KCL @ } V_1: \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_3}{R_2} + \frac{V_1 - V_4}{R_3} + \frac{V_1 - V_0}{R_4} = 0$$

$$-3V_4 - 3V_3 - 3V_2 + 10V_1 - V_0 = 0 \quad \text{---} \quad (4)$$

$$\text{KCL @ reference: } \frac{V_3}{R_5} + \frac{V_4}{R_6} + \frac{V_0}{R_8} = 4 \times 10^{-3}$$

$$4V_3 + V_0 = -8 \quad \text{---} \quad (5)$$

$$\text{KCL at } V_0 : \frac{V_0 - V_1}{3 \times 10^3} + \frac{V_0 - V_4}{2 \times 10^3} + \frac{V_0}{4 \times 10^3} = 0$$

$$V_1 = \frac{13V_0 - 6V_4}{4} \quad \text{---} \quad (6)$$

Substituting equations ①, ②, ③ and ⑥ in ④, we get

$$-3V_4 - 3V_3 - 3V_2 + 10 \cdot \frac{13V_0 - 6V_4}{4} - V_0 = 0$$

$$-18(12 + V_3) - 3V_3 - 3(V_3 - 2(12 + V_3)) + \frac{63}{2}V_0 = 0$$

$$-4V_3 + 7V_0 = 32 \quad \text{---} \quad (7)$$

From equations ⑤ and ⑦ we get

$$V_0 = 3.00 \text{ V}$$

3.94 Find I_o in the network in Fig. P3.94 using nodal analysis.


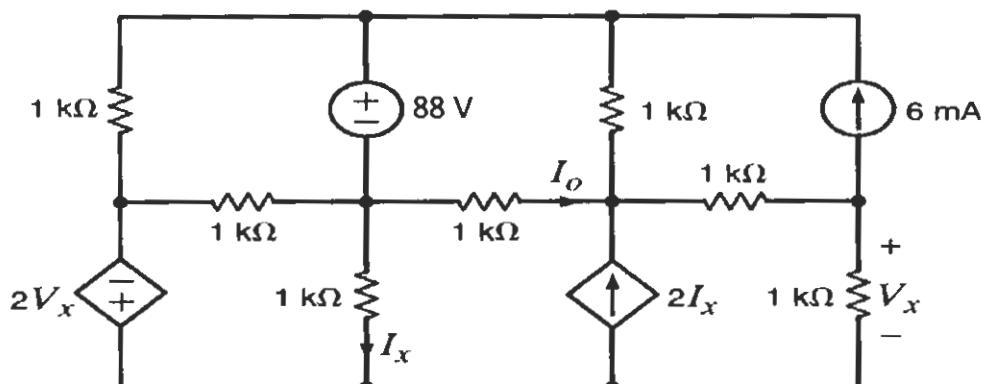


Figure P3.94

SOLUTION: 3.94

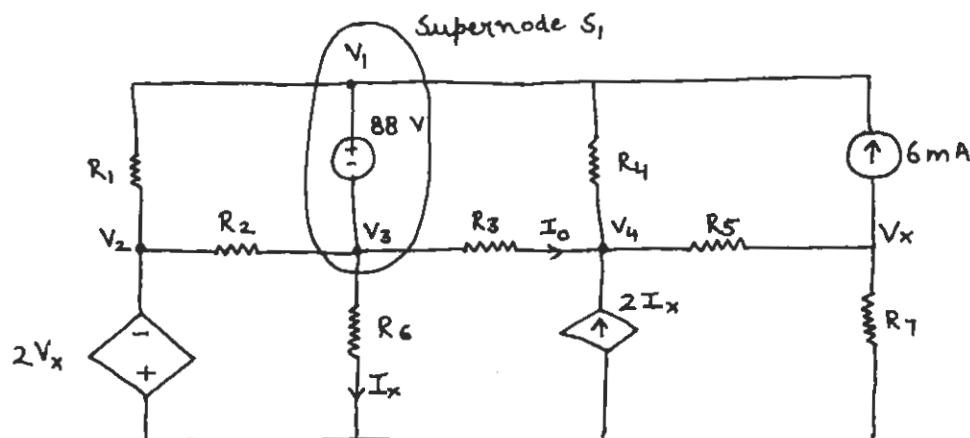

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$I_x = \frac{V_3}{R_6} \quad \text{--- } ①$$

$$V_1 - V_3 = 88 \text{ V} \quad \text{--- } ②$$

$$V_2 = -2V_x \Rightarrow V_x = -\frac{V_2}{2}$$

$$\text{KCL @ } S_1: \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_4}{R_4} - 6 \times 10^{-3} + \frac{V_3 - V_2}{R_2} + \frac{V_3}{R_6} + \frac{V_3 - V_4}{R_3} = 0$$

$$2V_1 - 2V_2 + 3V_3 - 2V_4 = 6 \quad \text{--- } ③$$

$$\text{KCL @ } V_4: \frac{V_4 - V_3}{R_3} - 2I_x + \frac{V_4 - V_x}{R_5} + \frac{V_4 - V_1}{R_4} = 0$$

$$-2V_1 + V_2 - 6V_3 + 6V_4 = 0 \quad \text{---} \quad (4)$$

$$\text{KCL at } V_x : \frac{V_x - V_4}{R_5} + \frac{V_x}{R_7} + 6 \times 10^{-3} = 0$$

$$V_2 + V_4 = 6 \quad \text{---} \quad (5)$$

Substituting equations (2) and (5) in (3), we get

$$2V_1 - 2V_2 + 3V_3 - 2V_4 = 6$$

$$V_3 = -31.6 \text{ V}$$

Substituting equations (2) and (5) in (4), we get

$$-2V_1 + V_2 - 6V_3 + 6V_4 = 0$$

$$V_4 = -16.56$$

$$\begin{aligned} I_0 &= \frac{V_3 - V_4}{R_3} \\ &= -\frac{31.6 + 16.56}{10^3} \end{aligned}$$

$I_0 = -15.04 \text{ mA}$