

In operational amp:-

$$a = 10^3 \frac{V}{V}$$


a) $v_N = ?$ $v_p = 0$ $v_o = 3V$

$$v_o = a(v_p - v_N) \quad (1)$$

$$\frac{v_o}{a} = v_p - v_N \rightarrow v_N = -\frac{v_o}{a}$$

$$v_N = -3 \times 10^{-3} V$$

b), c), (d) do yourself -

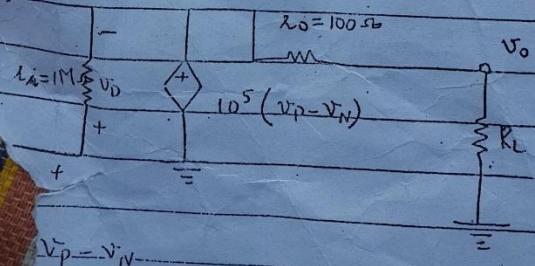

$$v_p = v_N$$


$$(v_p = v_N)$$

$$(0 = v_N)$$

$$-\frac{10}{10^5} = -10^{-4}$$

KHALID PHOTO STALE
U.E.T

KHALID PHOTO STALE
U.E.T

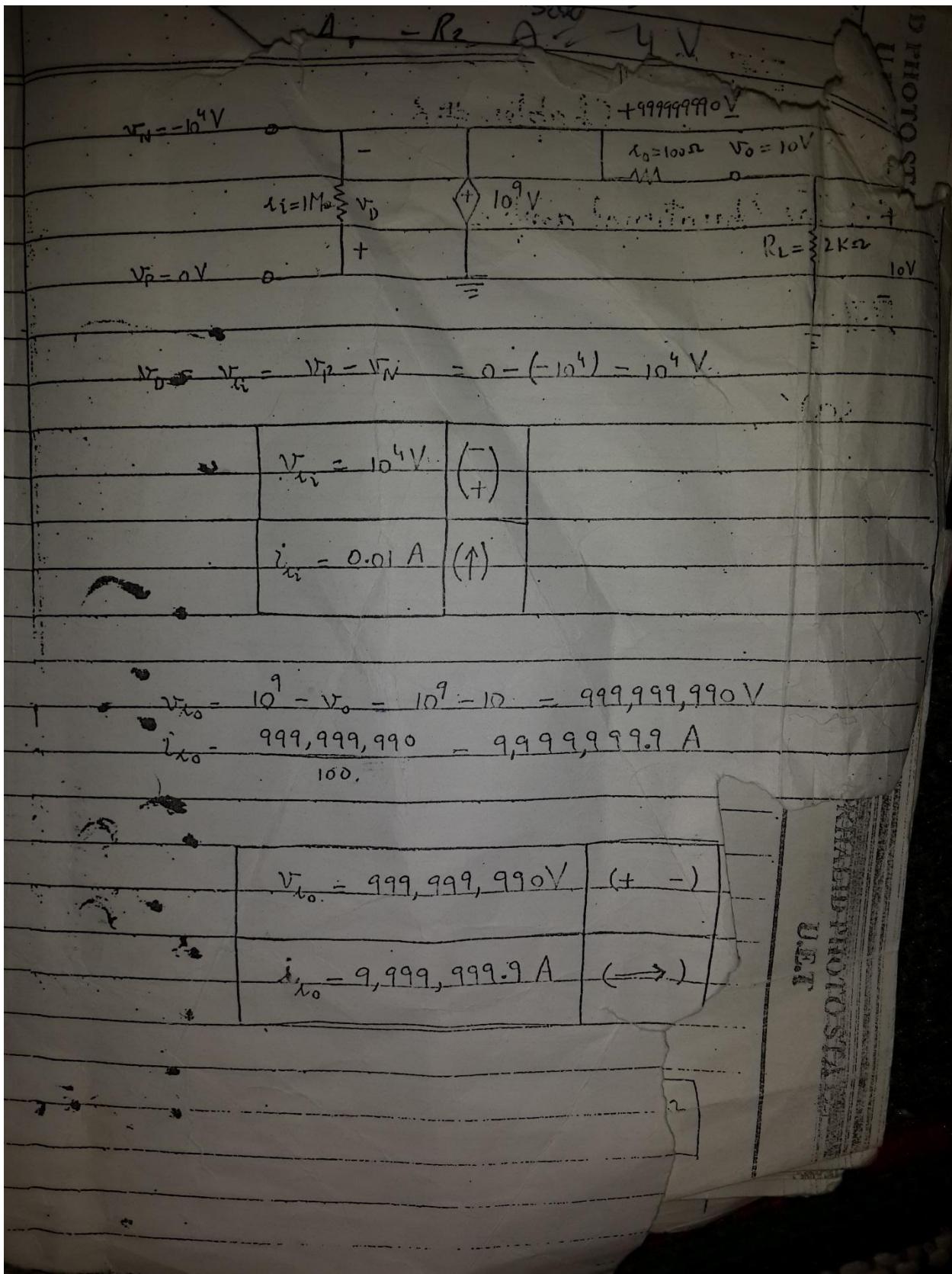

3:

6.2 Basic Op Amp Configuration

$$6.3 (a) R_1 = 10 \text{ k}\Omega$$

$$R_2 = 20 \text{ k}\Omega$$

For non inverting amplifier

$$A = \frac{1 + R_2}{R_1}$$

$$= 1 + \frac{20 \text{ k}}{10 \text{ k}}$$

$$A = 3 \frac{V}{V}$$

$$(b) R_3 = 10 \text{ k}\Omega$$

Case I: In series with R_1

$$R_1' = R_1 + R_3 = 10 \text{ k} + 10 \text{ k} = 20 \text{ k}$$

$$A = \frac{1 + R_2}{R_1'} = \frac{1 + 1}{20 \text{ k}} = \frac{20 \text{ k}}{20 \text{ k}} = 1 + 1 = 2$$

$$A = 2 \frac{V}{V}$$

Case II: In parallel with R_1

$$R_1' = \left(R_1^{-1} + R_3^{-1} \right)^{-1} = \left(10 \text{ k}^{-1} + 10 \text{ k}^{-1} \right)^{-1}$$

$$R_1' = 5 \text{ k}$$

$$A = \frac{1 + R_2}{R_1'} = \frac{1 + 20 \text{ k}}{5 \text{ k}} = 1 + 4$$

$$A = 5 \frac{V}{V}$$

6.4 do yourself: $A = -2$ V

By $A = -\frac{R_2}{R_1}$ $A = -4$ V

6.5 (a) $A = 5$ V (for non-inverting)
 $R_1 + R_2 = 100 \text{ k}\Omega$ ①

$$A = 1 + \frac{R_2}{R_1}, 5 = 1 + \frac{R_2}{R_1}, 4 = \frac{R_2}{R_1}$$

$$R_2 = 4R_1 \quad \text{②}$$

put in ①

$$R_1 + 4R_1 = 100 \text{ k}\Omega$$

$$5R_1 = 100 \text{ k}\Omega$$

$$R_1 = 20 \text{ k}\Omega$$

$$R_2 = 80 \text{ k}\Omega$$

(b) $A = -5$ V (for inverting)
 $R_1 + R_2 = 100 \text{ k}\Omega$ ①

$$A = -\frac{R_2}{R_1}$$


$$-5 = -\frac{R_2}{R_1}$$

$$R_2 = 5R_1 \quad \text{②} \quad \text{put in ①}$$

$$6R_1 = 100 \text{ k}\Omega$$

$$R_1 = \frac{50}{3} \text{ k}\Omega$$

$$R_2 = \frac{250}{3} \text{ k}\Omega$$

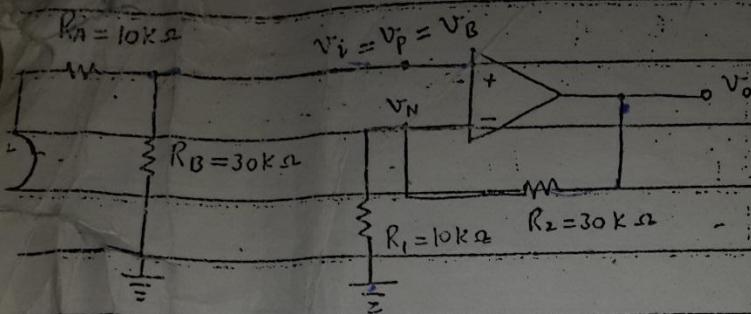

$$A = 4 \frac{V}{V}$$

$$V_B = \frac{R_B}{R_A + R_B} \times 1 = \frac{30K}{10K + 30K} = \frac{3}{4} V$$


$$V_i = V_p = V_B = \frac{3}{4} V, \quad V_o = \frac{3}{4} V$$

$$A = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$

$$4 = \frac{V_o}{\frac{3}{4}} \Rightarrow V_o = 4 \times \frac{3}{4} = 3$$

$$V_o = 3 V$$

(b)

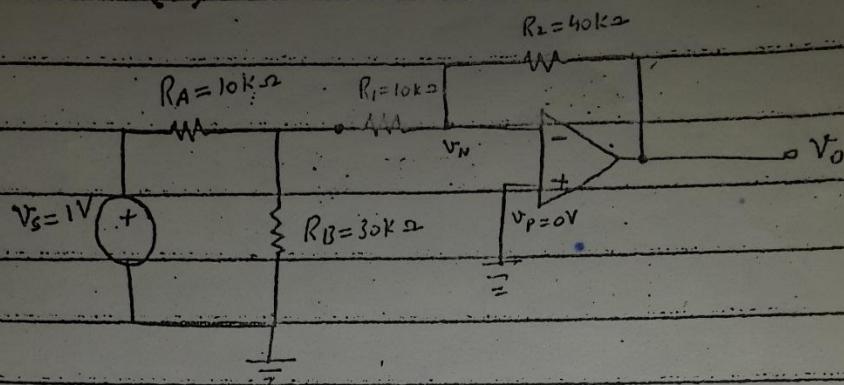

$$A = -\frac{V_o}{V_i}$$

$$V_B = \frac{R_B}{R_A + R_B} \times V_s = \frac{30k}{10k + 30k} \times 1 = \frac{3}{4} V$$

$$V_B = \frac{3}{4} V$$

$$V_B = V_i$$

$$V_i = \frac{3}{4} V$$


$$A = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

$$-4 = \frac{V_o}{V_i}, \quad -4 = \frac{V_o}{\frac{3}{4}} \Rightarrow V_o = -4 \times$$

$$V_o = -3V$$

\Rightarrow In case (b) the output is inverted.

7

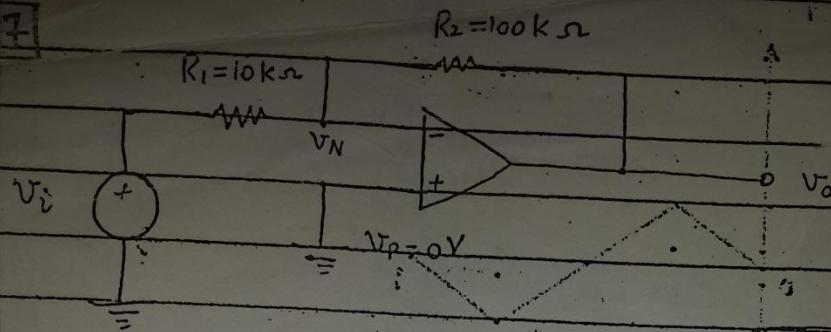

$$R_2 = 100 \text{ k}\Omega$$

$$R_1 = 10 \text{ k}\Omega$$

$$V_N$$

$$V_P = 0V$$

$$f = 1 \text{ kHz}$$

$$T = 1 \text{ msec}$$

$$V_o = \alpha (V_P - V_N)$$

$$V_o = 10^3 (0 - V_N)$$

$$V_o = -10^3 V_N$$

①

at V_N :

$$\frac{V_N - V_i}{10 \text{ k}\Omega} + \frac{V_N - V_o}{100 \text{ k}\Omega} + 0 = 0$$

$$10V_N - 10V_i + V_N - V_o = 0$$

$$10V_N = 10V_i + V_N - (-10^3 V_N) = 0$$

$$11V_N = 10V_i + 10^3 V_N$$

$$101V_N = 10V_i$$

$$V_N = 9.891 \text{ mV}_i$$

②

put in ①

$$V_o = -9.891 V_i$$

③

Extreme values of V_i 1 V -1 V

$$V_o = -9.891 \text{ V} \quad 9.891 \text{ V}$$

$$V_N = 9.891 \text{ mV} \quad -9.891 \text{ mV}$$

$$V_o = a (V_p - V_N) - \alpha \quad (ii)$$

$$V_o = 10^3 \left(0 - \frac{(V_o + 10)}{101} \right)$$

$$V_o = -1000 \frac{(V_o + 10)}{101}$$

$$V_o = -1000 \frac{V_o}{101} - \frac{100,000 V_i}{101}$$

$$V_o \left(1 + \frac{1000}{101} \right) = -\frac{100,000 V_i}{101}$$

$$V_o \left(\frac{101 + 1000}{101} \right) = -\frac{100,000 V_i}{101}$$

$$V_o \frac{1101}{101} = -\frac{100,000 V_i}{101}$$

$$\frac{V_o}{V_i} = -100,000$$

$$\frac{V_o}{V_i} = -90.83$$

$$A = \frac{V_o}{V_i} = -90.83$$

$$A_{\text{ideal}} = -\frac{R_2}{R_1} = -\frac{10^3}{10k} = -\frac{1000 \times 10^{-3}}{10 \times 10^{-3}}$$

$$A_{\text{ideal}} = -100$$


$$\% \text{ deviation} = \frac{A_{\text{ideal}} - A}{A_{\text{ideal}}} \times 100 = 9.17\%$$

$$\% \text{ deviation} = 9.17\%$$

8

(V)


F.3

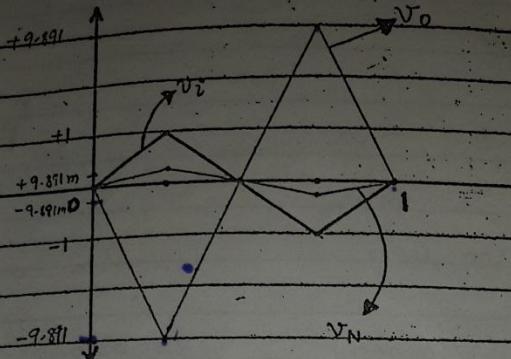

U.E.T

6.8

$$R_2 = 1 \text{ M}\Omega$$

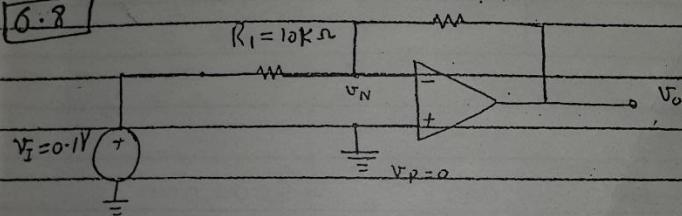

$$A = ?$$

$$(i) \alpha = 10^3 \frac{V}{V}$$

$$V_P = 0 \text{ V}$$

$$V_N =$$

$$\frac{V_N - V_i}{10K} + \frac{V_N - V_o}{1M} = 0$$

$$100(V_N - 0.1) + (V_N - V_o) = 0$$

$$101V_N = V_o + 100V_i$$

$$V_N = \frac{V_o + 100V_i}{101}$$

$$V_P = 0 \text{ V}$$

U.E.T


KARACHI INSTITUTE OF STATE

(ii) $a = 10^4$

(iii) $a = 10^5$

do yourself

[6.9] (a)

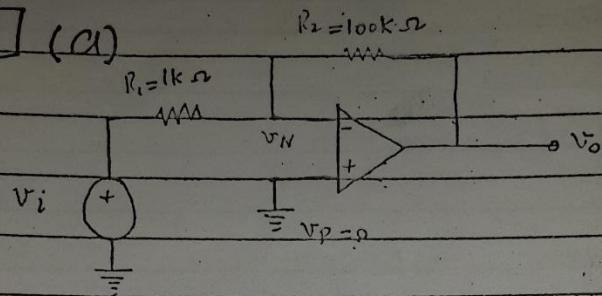

at V_N :

$$\frac{V_N - V_i}{1k} + \frac{V_N - V_o}{100k} = 0$$

$$100 V_P = 100 V_i + V_N - V_o = 0$$

$$100 V_N = V_o + 100 V_i$$

$$V_N = \frac{V_o + 100 V_i}{101}$$

$$V_P = 0$$

$$V_o = a (V_P - V_N)$$

$$\therefore V_P = 0 \quad V_N = \frac{V_o + 100 V_i}{101}$$

$$V_o = -a (V_o + 100 V_i)$$

$$V_o = -\frac{a}{101} V_o - \frac{a \cdot 100}{101} V_i$$

$$V_o \left(\frac{101 + a}{101} \right) = -\frac{100}{101} a V_i$$

$$\frac{V_o}{V_i} = \frac{-100a}{(101+a)}$$

$$A = \frac{-100a}{101+a}$$

$$\text{Now } a_1 = 200,000$$

$$A_1 = \frac{-100(200,000)}{101 + 200,000} = \frac{-20,000,000}{200,101}$$

$$A_1 = -99.95$$

$$a_2 = 50,000$$

$$A_2 = \frac{-100(50,000)}{101 + 50,000} = \frac{-5,000,000}{50,101}$$


$$A_2 = -99.82$$

$$\Rightarrow \% \text{ change} = \frac{A_2 - A_1}{A_1} \times 100 = -0.15\%$$

* -ve means decrease

12

(b)

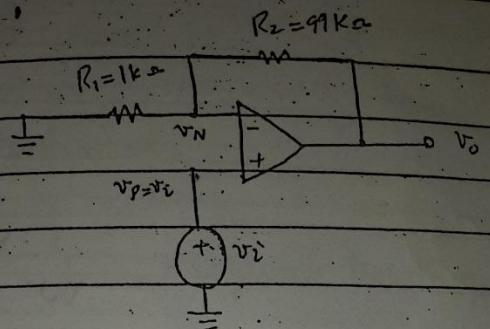at v_N :

$$v_N = 0 + \frac{v_N - v_o}{1k} = 0$$

$$99v_N + v_N - v_o = 0$$

$$100v_N = v_o$$

$$v_N = \frac{v_o}{100}$$

$$v_p = v_N$$

$$v_o = a(v_p - v_N)$$

$$v_o = a \left(v_i - \frac{v_o}{100} \right)$$

$$v_o + \frac{av_o}{100} = av_i$$

$$v_o \left(\frac{100 + a}{100} \right) = av_i$$

$$\frac{v_o}{v_i} = \frac{a100}{a + 100}$$

$$A = \frac{a100}{a + 100}$$

13. ...

$A_1 = 200,000$ (1)

$$A_1 = \frac{200,000 \times 100}{200,000 + 100} = 99.95$$

$A_1 = 99.95$


$A_2 = 50,000$

$$A_2 = \frac{50,000 \times 100}{50,000 + 100} = 99.80$$


$A_2 = 99.80$

$\rightarrow \text{% change} = \frac{A_2 - A_1}{A_1} \times 100 = -0.15 \%$

\leftarrow -ve means decrease

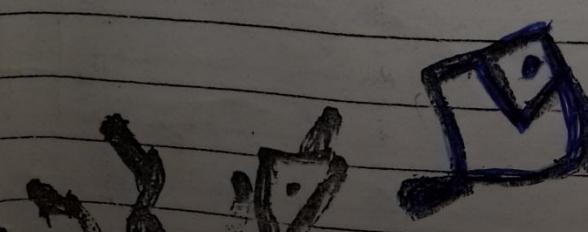

(c)

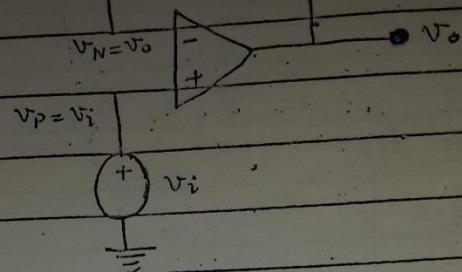

$$v_o = a(v_p - v_N)$$

$$v_o = a(v_i - v_N)$$

$$v_o = av_i - av_N$$

$$v_o(1+a) = av_i$$

$$\frac{v_o}{v_i} = \frac{a}{1+a}$$

$$A = \frac{a}{1+a}$$

when $a_1 = 200,000$

$$A_1 = \frac{200,000}{200,001} = 0.999995$$

$$A_1 = 0.999995$$

when $a_2 = 50,000$

$$A_2 = \frac{50,000}{50,001} = 0.99998$$

$$A_2 = 0.99998$$


15

$$\rightarrow \% \text{ change} = \frac{A_2 - A_1}{A_1} \times 100 = -0.0015 \quad [1.3]$$

-ve means decrease

6.3 4 ideal Op-Amp Circuit Analysis:-

[6.10]

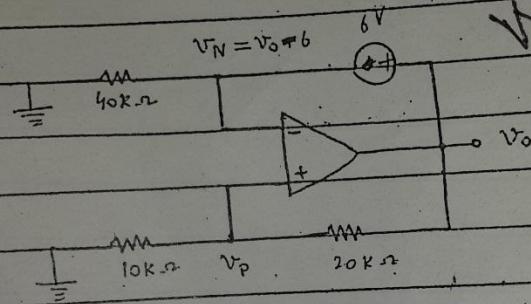

$$V_0, V_N^2 + 6$$

$$V_N^2$$

$$V_0, 6$$

$$V_p = \frac{10k}{10k+20k} \times V_0 = \frac{1}{3} V_0 \quad (1)$$

$$V_N = V_0 + 6$$

(2)

$$V_p = V_N$$


$$\frac{1}{3} V_0 = V_0 + 6$$

$$V_0 = 3V_0 + 18$$

$$2V_0 = 18$$

$V_0 = 9V$	$V_p = V_N = 3V$
------------	------------------

6.11

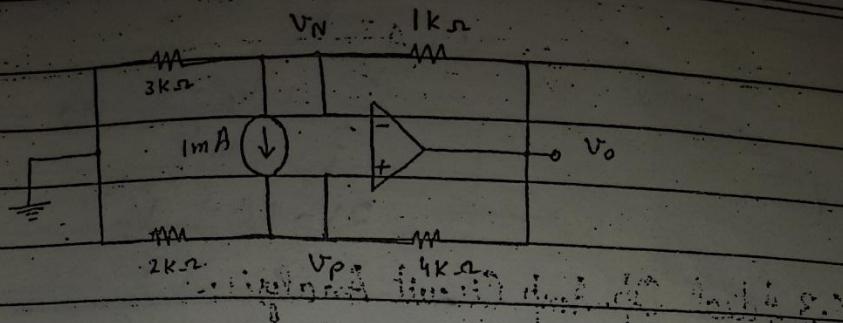

at V_N :

$$\frac{V_N - 0}{3k} + 1mA + \frac{V_N - V_o}{1k} = 0$$

$$V_N + 3 + 3V_N - 3V_o = 0$$

$$4V_N + 3 - 3V_o = 0$$

$$4V_N = 3V_o - 3$$

$$V_N = \frac{3}{4}(V_o - 1) \quad (1)$$

at V_p :

$$\frac{V_p - 0}{2k} + \frac{V_p - V_o}{4k} = 1mA$$

$$2V_p + V_p - V_o = 4$$

$$3V_p - V_o = 4$$

$$V_p = \frac{V_o + 4}{3} \quad (2)$$

$$V_N = V_p$$

(3)

$$\frac{3}{4}(V_o - 1) = \frac{1}{3}(V_o + 4)$$

$$9(V_o - 1) = 4(V_o + 4)$$


$$9V_o - 9 = 4V_o + 16$$

$$5V_o = 25$$

$$V_o = 5V$$

17

$$V_N = V_P = 3V$$

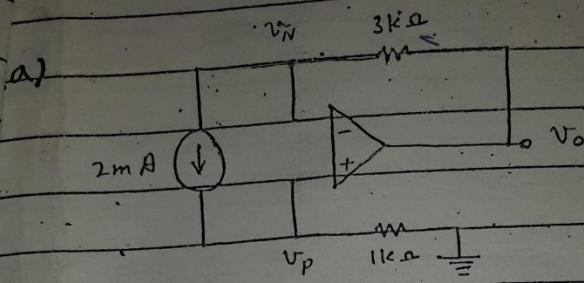

I_N :

$$I = 2m + \frac{V_N - V_o}{3k}$$

$$I = 6 + V_N - V_o$$

$$V_N = V_o + 6 \quad (1)$$

I_{V_P} :

$$2m = \frac{V_P - 0}{1k}$$

$$V_P = 2V$$


(2)

$$V_P = V_N = 2V$$

put in (1)

$$I = V_o - 6$$

$$V_o = 8V$$

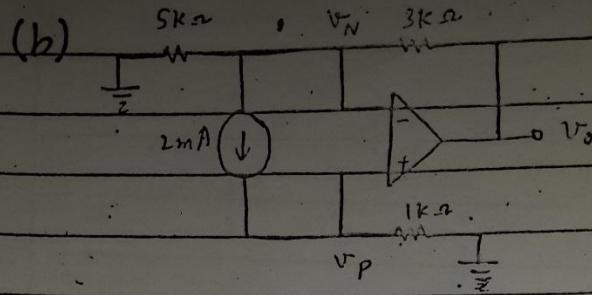

at V_N :

$$0 = 2mA + \frac{V_N - 0}{5k} + \frac{V_N - V_o}{3k}$$

$$0 = 30 + 3V_N + 5V_N - 5V_o$$

$$0 = 30 + 8V_N - 5V_o$$

$$V_N = \frac{5V_o - 30}{8}$$

(1)

at V_P :

$$2mA = \frac{V_P - 0}{1k}$$

$$2 = V_P$$

$$V_P = 2V$$

(2)

as

$$V_P = V_N = 2V$$

(3) put in (1)

$$16 = 5V_o - 30$$

$$16 + 30 = 5V_o$$

$$46 = 5V_o$$

$$V_o = \frac{46}{5} V$$

$$\text{At } V_N, V_N - 1 + V_N = V_{O20}$$


$$V_N = \frac{2V_o + 6}{3}$$

6.13

6.14 (a)

$$V_o = 6V$$

$$V_p - V_N = -2V$$

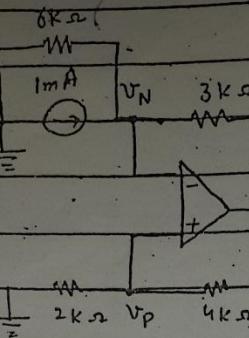

$$\text{At } V_p, V_p + V_p - V_o = 0$$

$$V_p = \frac{V_o}{4}$$


$$\frac{2V_o + 6}{3} = \frac{V_o}{3}$$

$$-1 + V_N - V_o = 0$$

(b)

$$V_o = 6.5V$$

$$V_p = V_N = 3.5V$$

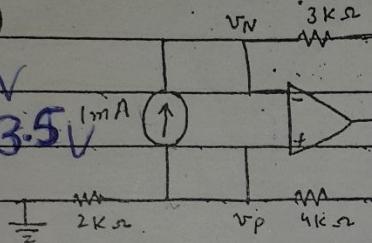

$$V_N = \frac{3}{4} + 3 \quad \text{--- (1)}$$



$$-1 + V_p + V_p - V_o = 0$$

$$V_p = \frac{V_o}{4}$$

$$V_o - 6.5 = \frac{V_o}{4}$$

do yourself

6.15

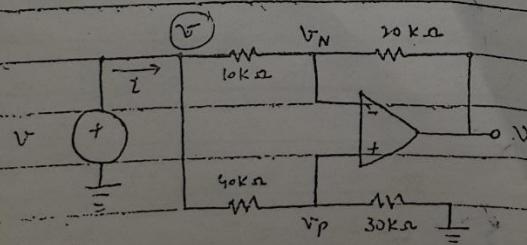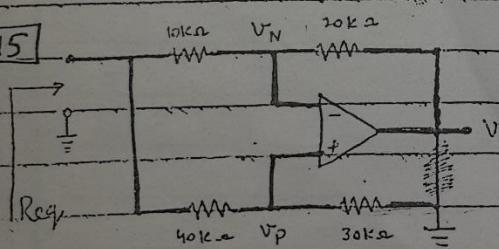

20%

at v_N :

$$\frac{v_N - v_0}{20k} + \frac{v_N - v}{40k} = 0$$

$$v_N - v_0 + 2v_N - 2v = 0$$

$$3v_N - 2v = v_0 \rightarrow 0$$

$$v_N = \frac{2v + v_0}{3} \quad (1)$$

at v_P :

$$\frac{v_P - 0}{30k} + \frac{v_P - v}{40k} = 0$$

$$4v_P + 3v_P - 3v = 0$$

$$7v_P = 3v$$

$$v_P = \frac{3}{7}v \quad (2)$$

at v :

$$i = \frac{v - v_N}{10k} \left[+ \frac{v - v_P}{40k} \right]$$

$$40ki = 4v - 4v_N + v - v_P$$

$$40ki = 5v - 4v_N - v_P \quad (3)$$

as $v_N = v_P$

$$40ki = 5v - 4v_N - v_N \quad (4)$$

$$40ki = 5v - 5v_N = 5v_N \quad \text{just in (3)}$$

SSKR

$$40kI = 5V - \frac{3}{7}(4V) - \frac{3}{7}V$$

Ans

at V_N :

$$40kI = 5V - \frac{15}{7}V - \frac{35V - 15V}{7}$$


$$40kI = \frac{20}{7}V$$

$$I = \frac{40k \times 7}{20}$$

at V_P :

Reg 2 14K 2

do yourself

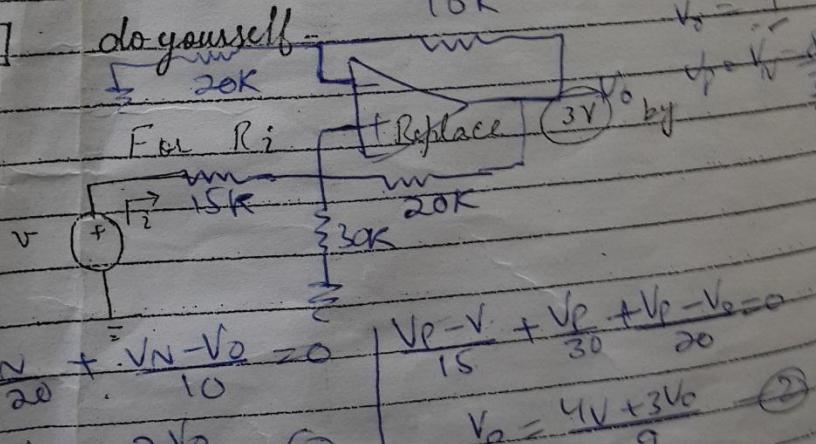

$$V_P = \frac{4}{3}V$$

at r_i

$$\frac{V_N}{20} + \frac{V_N - V_P}{10} = 0 \quad \left| \begin{array}{l} V_P = \frac{4}{3}V \\ \frac{V_P - V}{15} + \frac{V_P - V_0}{30} = 0 \end{array} \right.$$

$$V_N = \frac{2V_0}{3} \quad (1) \quad V_P = \frac{4V + 3V_0}{9} \quad (2)$$

$$V_N = V_P$$

$$\frac{2V_0}{3} = 4V + 3V_0$$

$$\frac{3}{2}V_0 = \frac{4}{3}V$$

$$\frac{2}{3}V - \frac{4}{3}V = I \Rightarrow \frac{V - V_P}{15} = I \Rightarrow \frac{V - \frac{4}{3}V}{15} = 15I \quad (3)$$

$$(2) \Rightarrow V_P = \frac{4V + 3(\frac{4}{3}V)}{9}$$


$$V_P = \frac{8}{9}V$$

$$V_P = \frac{4V + 3V_0}{9}$$

$$V = \frac{8}{9}V = 15I \quad \rightarrow I = 15k\Omega$$

22

6.17

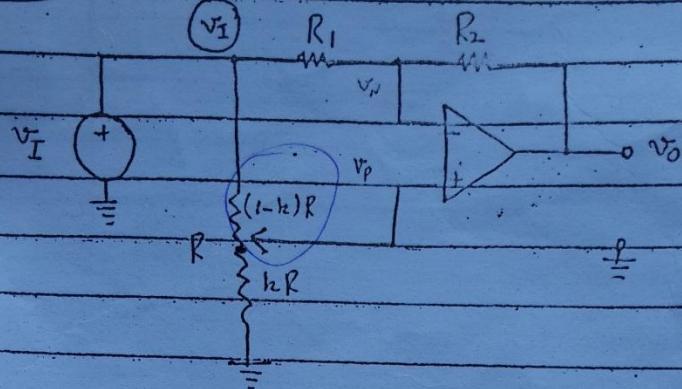

$$R_1 = R_2 = 10k\Omega$$

at $V_N =$

$$\frac{V_N - V_T}{R_1} + \frac{V_N - V_O}{R_2} = 0$$

$$\frac{V_N - V_T}{10k} + \frac{V_N - V_O}{10k} = 0$$

$$V_N - V_T + V_N - V_O = 0$$

$$2V_N = V_T + V_O$$

$$V_N = \frac{V_T + V_O}{2}$$

(1)

at $V_P =$

$$\frac{V_P - V_I}{(1-h)R} + \frac{V_P - 0}{hR} = 0$$

$$\frac{h(V_P - V_I) + (1-h)(V_P)}{(1-h)hR} = 0$$

$$h(V_P - V_I) + V_P(1-h) = 0$$

$$hV_P - hV_I + V_P - hV_P = 0$$

$$hV_I = V_P$$

(2)

23

at $V_P = V_N$

from ① & ②

pt. 2

$$kV_I = \frac{V_I + V_0}{2}$$

$$2kV_I = V_I + V_0$$

$$V_0 = 2kV_I - V_I$$

$$V_0 = (2k-1)V_I$$

$$\frac{V_0}{V_I} = 2k-1$$

$$A = 2k-1$$

⇒ when whiper at top means $k = \underline{\underline{1}}$

$$A = +1$$

⇒ " at mid " $k = \frac{1}{2}$


$$A = 0$$

⇒ " at bottom " $k = 0$

$$A = -1$$

2.4.5.5

6.18

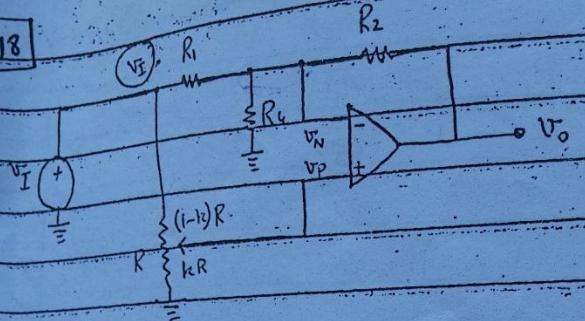

$V_N + R_2 R_4$

at V_N :

$$\frac{V_N - 0}{R_4} + \frac{V_N - V_O}{R_2} + \frac{V_N - V_I}{R_1} = 0$$

(3)

$$R_1 R_2 V_N + R_1 R_4 (V_N - V_O) + R_2 R_4 (V_N - V_I) = 0$$

$$R_1 R_2 V_N + R_1 R_4 V_N - R_1 R_4 V_O + R_2 R_4 V_N - R_2 R_4 V_I = 0$$

$$(R_1 R_2 + R_1 R_4 + R_2 R_4) V_N = R_1 R_4 V_O + R_2 R_4 V_I$$

$$V_N = \frac{R_1 R_4 V_O + R_2 R_4 V_I}{(R_1 R_2 + R_1 R_4 + R_2 R_4)}$$

(1)

in (3)

at V_P :

$$\frac{V_P - V_I}{(1-k)R} + \frac{V_P - 0}{kR} = 0$$

$$k(V_P - V_I) + (1-k)V_P = 0$$

$$kV_P - kV_I + V_P - kV_P = 0$$

$$V_P = kV_I$$

(2)

25

6.18

$$V_N = V_P$$

$$R_1 R_4 V_0 + R_2 R_4 V_I = k_2 V_I$$

$$(R_1 R_2 + R_1 R_4 + R_2 R_4)$$

$$\frac{R_1 R_4}{R_2 + R_1 R_4 + R_2 R_4} V_0 = V_I \left(\frac{R_2 - R_2 R_4}{R_1 R_2 + R_1 R_4 + R_2 R_4} \right)$$

$$\frac{V_0}{V_I} = \left(\frac{k_2 (R_1 R_2 + R_1 R_4 + R_2 R_4) - R_2 R_4}{R_1 R_2 + R_1 R_4 + R_2 R_4} \right) \left(\frac{R_1 R_2 + R_1 R_4 + R_2 R_4}{R_1 R_4} \right)$$

$$A = \frac{k_2 (R_1 R_2 + R_1 R_4 + R_2 R_4)}{R_1 R_4} - \frac{R_2}{R_1} \quad (3)$$

$$-100 \leq A \leq +100$$

at bottom as $V_N > V_P$ at top as $V_P > V_N$

at bottom when $k=0$ & $A = -100$ put in (3)

$$-100 = 0 + \frac{R_2}{R_1}$$

$$R_2 = 100 R_1 \quad (4)$$

at top when $k=1$ & $A = 100$ put in (3)

$$100 = \frac{R_1 R_2 + R_1 R_4 + R_2 R_4}{R_1 R_4} - \frac{R_2}{R_1}$$

$$100 = \frac{R_2}{R_4} + 1 + \frac{R_L}{R_1} - \frac{R_L}{R_1}$$

$$100 - 1 = \frac{R_2}{R_4}$$

$$R_2 = 99 R_4$$

(5)

\Rightarrow at halfway $I_3 = \frac{1}{2}$ & $A = 0$ put in (3)

$$0 = \frac{R_1 R_2 + R_1 R_4 + R_2 R_4}{2 R_1 R_4} - \frac{R_2}{R_1}$$

$$0 = \frac{1}{2} \frac{R_2}{R_4} + \frac{1}{2} + \frac{1}{2} \frac{R_2}{R_1} - \frac{R_2}{R_1}$$

$$0 = \frac{1}{2} \frac{R_2}{R_4} + \frac{1}{2} - \frac{1}{2} \frac{R_2}{R_1}$$

$$0 = \frac{R_2}{R_4} + 1 - \frac{R_2}{R_1}$$

$$0 = \frac{R_1 R_2 + R_1 R_4 - R_2 R_4}{R_1 R_4}$$

$$R_1 R_2 + R_1 R_4 - R_2 R_4 = 0$$

(6)

from (4) & (5)

$$\frac{100 R_1}{R_1} = \frac{99 R_4}{100}$$

(7)

27

we have the relation:-

$$R_3 = 100 R_1 \quad (4)$$

$$R_4 = \frac{1}{99} R_2 \quad (5)$$

If we take $R_1 = 1 \text{ k}\Omega$ then

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

$$R_4 = 1.01 \text{ k}\Omega$$

\Rightarrow when at half way put $k = \frac{1}{2}$ in (3)

$$A = \frac{\frac{1}{2} \left((1)(100) + (1)(1.01) + (100)(1.01) \right)}{(1)(1.01)} - (100) \quad (1)$$

$$= 100. - 100$$

$$A = 0 \text{ V}$$

6.19


2.8

As we know

$$R_{eq} = - \frac{R_1 R}{R_2} \quad \text{so we should}$$

change R_1

So

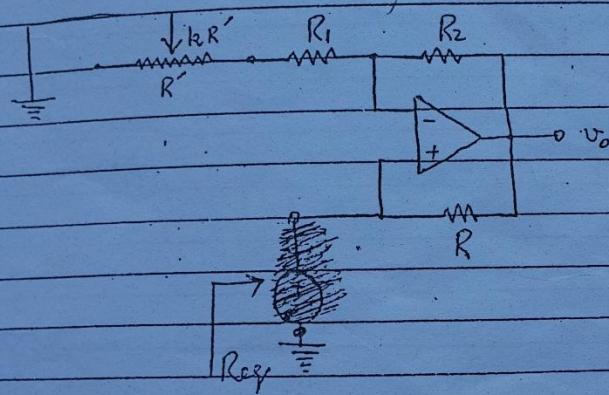


Now we have

$$R_{eq} = - \frac{(R_1 + kR')}{R_2} R$$

$$R_{eq} = - \frac{(R_1 + k(100))}{R_2} R \quad R' = 100k\Omega \quad (\text{given})$$

\Rightarrow By given conditions

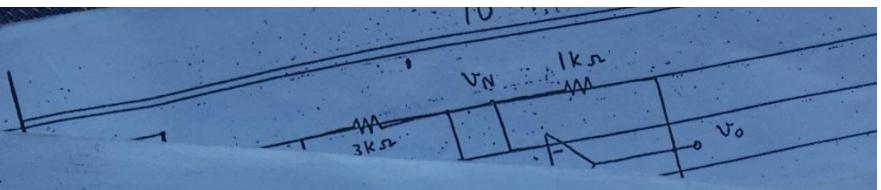when $R_{eq} = 1k\Omega$ then $k = 0$ but
in (1)



$$= \frac{1}{(R_1 + \infty)} R$$

R_2

6.19

$R_1 R$

R_2

$$R_2 = R_1 R$$

(2)

change

when $R_{\text{ref}} = -10k\Omega$ then $k=1$ put in

$$+10 = \frac{1}{(R_1 + 100)} R$$

R_2

$$10 R_2 = (R_1 + 100) R \quad (3)$$

from (2)

$$10 R_1 R = (R_1 + 100) R$$

$$9 R_1 = 100$$

$$R_1 = \frac{100}{9} = 11.11$$

$$R_1 = 11.11 k\Omega$$

(4)

$$R_2 = 11.11 R$$

(5)

put in (3) ~~(3)~~

$$\begin{aligned}
 & R_2 = 11 \cdot 11 R \\
 & 11 \cdot 11 R = 100 k \Omega \\
 & R_2 = 10 k \Omega
 \end{aligned}$$

$$R_2 = 11 \cdot 11 R \quad (5)$$

assume $R = 1 k \Omega$ then

$$R_2 = 11 \cdot 11 k \Omega$$

check :-

put in (1) :-

$$R_{eq} = - \left(\frac{11 \cdot 11 + 100k}{11 \cdot 11} \right) k \Omega$$

when $k = 0$

$$R_{eq} = -1 k \Omega$$

when $k = 1$

$$R_{eq} = -10 k \Omega$$

$$\begin{array}{l}
 R_2 \\
 \downarrow \\
 R_i
 \end{array}$$

$$\begin{array}{l}
 V \\
 \uparrow \\
 V_i
 \end{array}$$

$$\begin{array}{l}
 V_N - V_i \\
 R_i \\
 (V_N - V_i)
 \end{array}$$


$$\begin{array}{l}
 + R_i \\
 V
 \end{array}$$

$$\begin{array}{l}
 V - V_i \\
 R
 \end{array}$$

$$\begin{array}{l}
 3R_2(V \\
 \downarrow
 \end{array}$$

$$\begin{array}{l}
 3R_2V \\
 \downarrow
 \end{array}$$

6.20 (a) ~~REVIEW~~ given

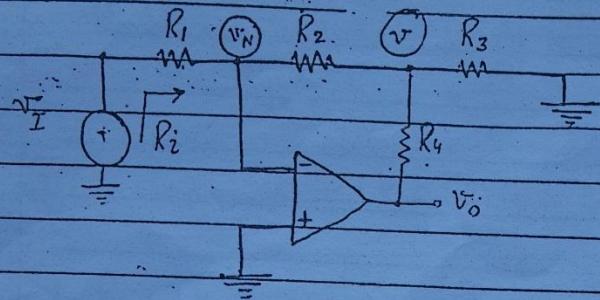

at ν_N

$$\frac{V_N - V_I}{R_1} + \frac{V_N - V}{R_2} = 0 \quad \rightarrow \textcircled{1}$$

at v:

$$\frac{V - V_N}{R_2} + \frac{V - V_0}{R_4} + \frac{V - 0}{R_3} = 0 \quad (2)$$

from (1)

$$R_2 v_N - R_2 v_I + R_1 v_N - R_1 v = 0$$

$$(R_1 + R_2) v_N - R_2 v_E - R_1 v = 0$$

$$V = \frac{(R_1 + R_2) V_N - R_2 V_I}{R_1}$$


from (2)

$$v = R_3 R_4 v = R_3 R_4 v_N + R_2 R_3 v - R_2 R_3 v_0 + R_2 R_4 v$$

$$R_3 R_4 v_N = (R_2 R_4 + R_2 R_3 + R_2 R_4) v = R_2 R_3 v_0$$

from (3)

from (3) put the value of V_0

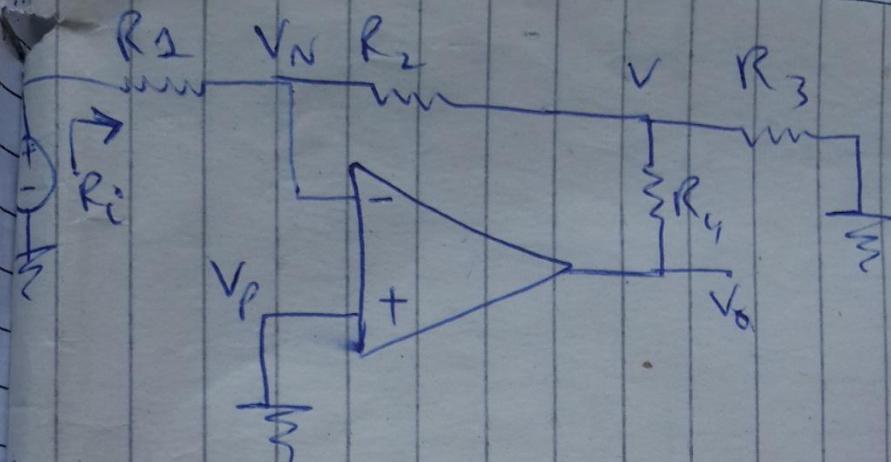

$$\frac{V_N - V_i}{R_1} + \frac{V_N - V}{R_2} = 0$$

$$(V_N - V_i) + R_1 (V_N - V) = 0$$

$$R_1 R_2$$

$$+ R_1) V_N - V_i R_2 - V R_1 = 0$$

$$V_N = \frac{V_i R_2 + V R_1}{R_1 + R_2}$$

①

$$\frac{V - V_o}{R_4} + \frac{V}{R_3} + \frac{V - V_N}{R_2} = 0$$

$$3R_2(V - V_o) + R_2 R_4 (V) + R_3 R_4 (V - V_N) = 0$$

$$R_4 R_3 R_2$$

$$3R_2 V - R_3 R_2 V_o + R_2 R_4 V + R_3 R_4 V - R_3 R_4 V_N = 0$$

V

①

②

$\frac{V_o}{V}$

$\frac{V_o}{V}$

②

$\frac{V_N}{V}$

I

$\frac{V}{R}$

$$V(R_2R_3 + R_2R_4 + R_3R_4) = R_3R_2V_0 + R_3R_4V_N \quad (2)$$

$$V_P = 0$$

$$V_N = V_P$$

$$(1) \Rightarrow \frac{V_i R_2 + V_i R_1}{R_1 + R_2} = 0$$

$$V = -\frac{V_i R_2}{R_1}$$

$$(2) \Rightarrow -\frac{V_i R_2}{R_1} (R_2R_3 + R_2R_4 + R_3R_4) = R_3R_2V_0$$

$$\begin{aligned} \frac{V_0}{V_i} &= -\frac{R_2}{R_1} (R_2R_3 + R_2R_4 + R_3R_4) \cdot \frac{1}{R_3R_2} \\ &= -\frac{R_2}{R_1} \left[\frac{R_2R_3}{R_2R_3} + \frac{R_2R_4}{R_2R_3} + \frac{R_3R_4}{R_2R_3} \right] \\ &= -\frac{R_2}{R_1} \left[1 + \frac{R_4}{R_3} + \frac{R_4}{R_2} \right] \end{aligned}$$

$$\boxed{\frac{V_0}{V_i} = -\frac{R_2}{R_1} (R)}$$

$$I = 0$$

$$A) \frac{V_i}{I} = \frac{V_i - V_N}{R_1}$$

$$V_N = 0$$

$$I = \frac{V_i}{R_1}$$

$$\therefore R_i = R_1$$

$$\boxed{R_i = \frac{V_i}{I}}$$

328

$$R_3 R_4 v_N = (R_3 R_4 + R_2 R_3 + R_2 R_4) \frac{(R_1 + R_2) v_N - R_2 v_I}{R_1}$$

 ~~$R_2 R_3 v_0$~~

~~$R_3 R_4 v_N = (R_3 R_4 + R_2 R_3 + R_2 R_4) \frac{(R_1 + R_2) v_N - R_2 v_I}{R_1}$~~

 ~~$R_2 R_3 v_0$~~

$$R_3 R_4 v_N = \frac{(R_3 R_4 + R_2 R_3 + R_2 R_4) (R_1 + R_2)}{R_1} v_N -$$

$$\frac{(R_3 R_4 + R_2 R_3 + R_2 R_4) R_2}{R_1} v_I - R_2 R_3 v_0$$

$$\frac{(R_3 R_4 + R_2 R_3 + R_2 R_4) R_2}{R_1} v_I + R_2 R_3 v_0 = \frac{(R_3 R_4 + R_2 R_3 + R_2 R_4) (R_1 + R_2)}{R_1} v_N$$


 ~~$R_3 R_4 v_N$~~

$$(R_3 R_4 + R_2 R_3 + R_2 R_4) R_2 v_I + R_1 R_2 R_3 v_0 = \frac{(R_3 R_4 + R_2 R_3 + R_2 R_4)}{(R_1 + R_2) - R_1 R_3 R_4} v_N$$

$$v_N = \frac{(R_3 R_4 + R_2 R_3 + R_2 R_4) R_2 v_I + R_1 R_2 R_3 v_0}{[(R_3 R_4 + R_2 R_3 + R_2 R_4) (R_1 + R_2) - R_1 R_3 R_4]} \quad (4)$$

at $v_I = v_0 = 0$ a) $v_I = -v_N = a$ put in (4) we get

$$0 =$$

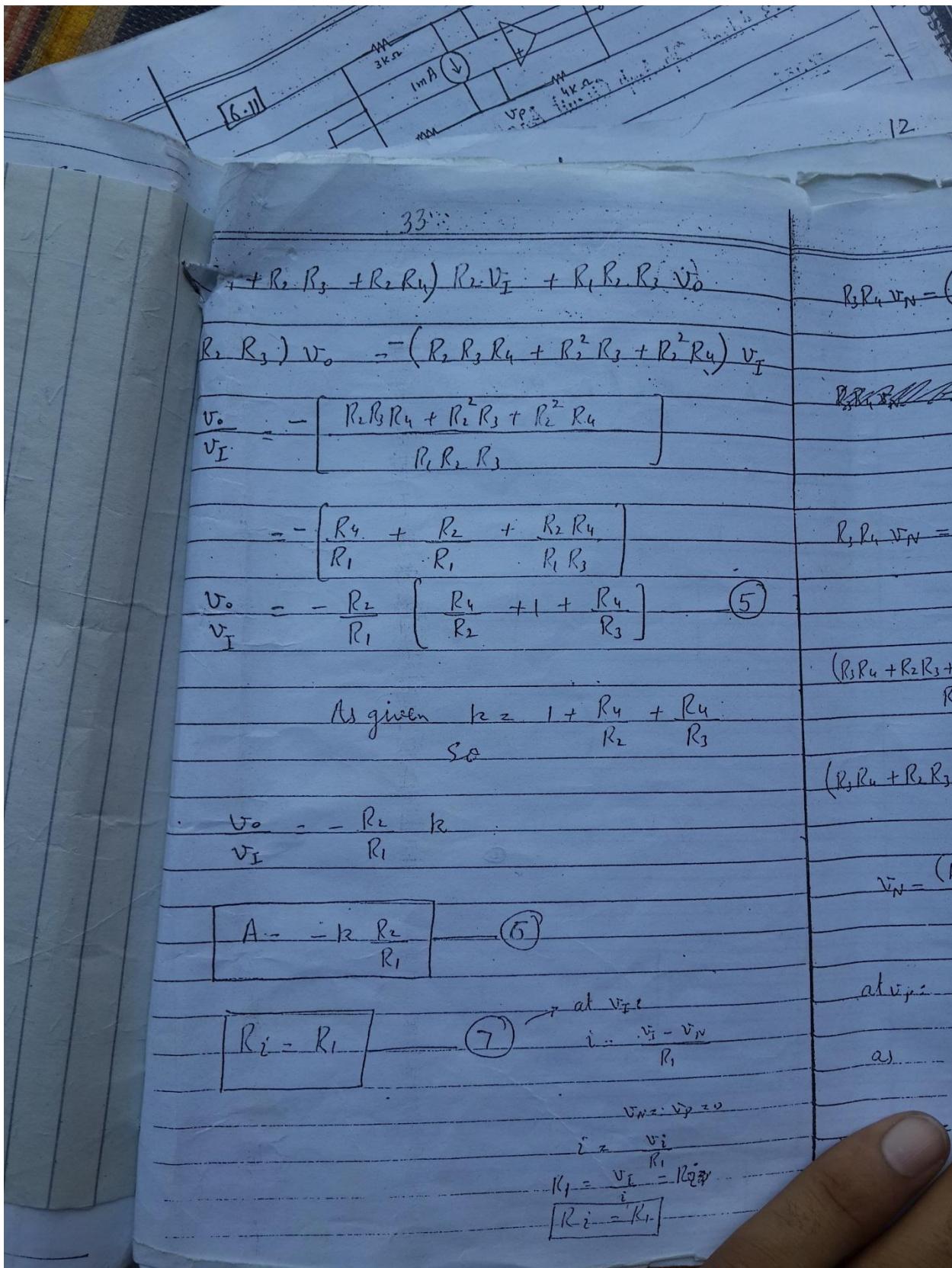

$$(b) R_i = 100 \text{ k}\Omega$$

$$A = -200$$

$$A = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right) \quad (5)$$

$$R_i = R_1 \quad (7)$$

$$R_1 = R_i = 100 \text{ k}\Omega$$

$$R_1 = 100 \text{ k}\Omega$$

put in (5) & $A = 200$

$$f_{200} = f R_2 \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

$$200 = \frac{R_2}{100 \text{ k}} + \frac{R_4}{100 \text{ k}} + \frac{R_2 R_4}{100 \text{ k} R_3}$$

$$20,000 \text{ k} = R_2 + R_4 + \frac{R_4 R_2}{R_3} \quad (8)$$


Assuming $R_2 = 10 \text{ k}\Omega$
 $R_4 = 20 \text{ k}\Omega$
 $R_3 = 0.01 \text{ k}\Omega$

we get $A \approx -200$

Check:-

$$A = -\frac{10 \text{ k}}{100 \text{ k}} \left(1 + \frac{20 \text{ k}}{10 \text{ k}} + \frac{20 \text{ k}}{0.01 \text{ k}} \right)$$

$$A = -200 \cdot 3 \frac{V}{V}$$

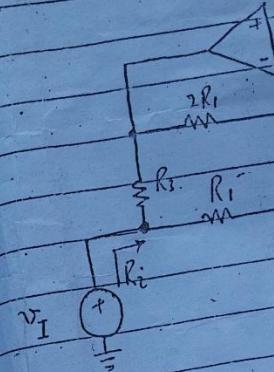

$$V_A = V_N$$

$$V_N = V_I + V_N =$$

$$R$$

$$V_P = V_N =$$

$$V_I = -V_C$$

$$V_2 - V_1 +$$

$$R$$

$$3V_2 - V$$

$$3(V_1) -$$

$$8V_1$$

$$-8(V_1)$$

$$\frac{V_0}{V}$$


Operational

(b)

$A = -$

$R_i =$

R_i

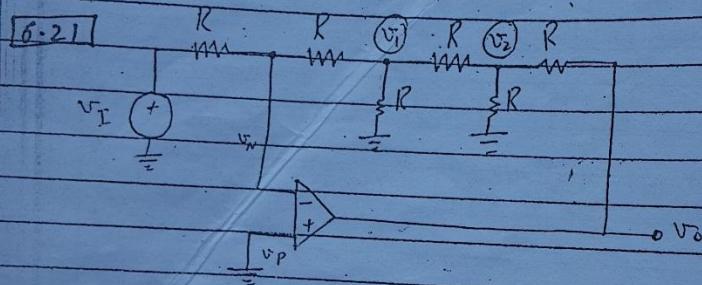

at V_N :

$$\frac{V_N - V_I}{R} + \frac{V_N - V_1}{R} = 0$$

$$V_N - V_I + 2V_N - V_I = 0$$

$$-V_I = V_I - 2V_N$$

①

$200 =$

$20,000 R$

at V_1 :

$$\frac{V_I - V_N}{R} + \frac{V_I - 0}{R} + \frac{V_I - V_2}{R} = 0$$

$$V_I - V_N + V_I + V_I - V_2 = 0$$

$$3V_I = V_N + V_2$$

②

Assuming

Check:-

$A =$

at V_2 :

$$\frac{V_2 - V_I}{R} + \frac{V_2 - 0}{R} + \frac{V_I - V_o}{R} = 0$$

$A =$

36

$$v_2 = v_1 + v_3 + v_4 - v_0 = 0$$

$$3v_2 = v_1 + v_0 \quad (3)$$

As $v_p = v_n = 0$ put in (1) & (2), then it becomes

$$-v_1 = v_1 \quad (1)$$

$$3v_1 = v_1 \quad (2)$$

$$3v_2 = v_1 + v_0 \quad (3)$$

put $v_2 = 3v_1$ in (3)

[15.2]

$$3(3v_1) = v_1 + v_0$$

$$8v_1 = v_1 + v_0$$

$$8v_1 = v_0 \quad (3)$$

put $v_1 = -v_2$ in (3)

KHALID PHOTO STUDIO
J.E.T

$$+\frac{v_1 - v_2}{R} = 0$$

$$-v_2 = 0$$


v_2

$$\frac{v_0}{v_1} = 8 \frac{v}{v}$$

$$A = -8 \frac{v}{v}$$

3.7

(5)

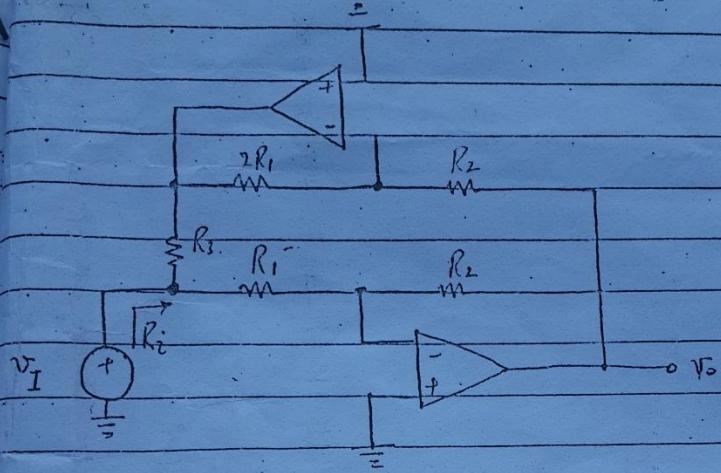A₁ = -200At V_N

$$\frac{V_1 - V_N}{R} + \frac{V_N - V_1}{R} = 0$$

$$\therefore V_P = V_N = 0$$

$$[V_1 = -V_2]$$

At V₁

$$\frac{V_1 - V_N}{R} + \frac{V_1 - V_2}{R} + \frac{V_1 - V_2}{R} = 0$$

$$V_1 + V_1 + V_1 - V_2 = 0$$

$$[V_2 = 3V_1]$$

(8)

$$\frac{V_2 - V_1}{R} + \frac{V_2}{R} + \frac{V_2 - V_0}{R} = 0$$

$$3V_2 - V_1 - V_0 = 0$$

$$3(3V_1) - V_1 - V_0 = 0$$

$$8V_1 - V_0 = 0$$

$$-8(V_1) = V_0$$

$$\boxed{\frac{V_0}{V_1} = -8}$$